



Homework #1

Problems 1.15, 1.23, 1.24, 1.28,
and 1.30



Problem 1.15a

Through repeated application of Thévenin's theorem, find the Thévenin equivalent of the circuit in Fig. P1.15 between node 4 and ground, and hence find the current that flows through a load resistance of $3\text{ k}\Omega$ connected between node 4 and ground.



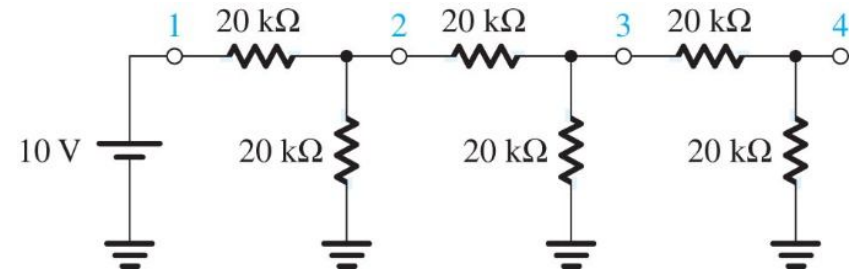


Figure P1.15

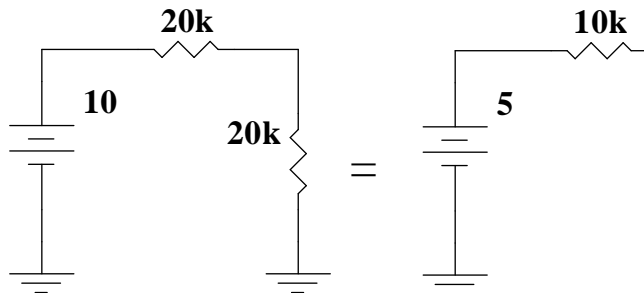

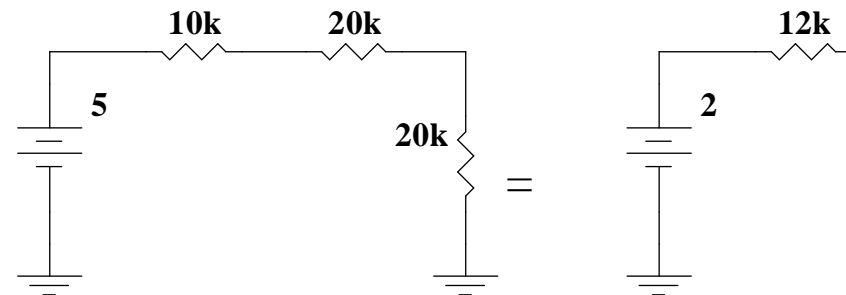At node 2 we have 5V with $10\text{ k}\Omega$ series resistance.



At node 3 we have 5V in with $30\text{ k}\Omega$ series and $20\text{ k}\Omega$ shunt resistance which yields 2V with $12\text{ k}\Omega$ series resistance



Problem 1.15b

Through repeated application of Thévenin's theorem, find the Thévenin equivalent of the circuit in Fig. P1.15 between node 4 and ground, and hence find the current that flows through a load resistance of $3\text{ k}\Omega$ connected between node 4 and ground.


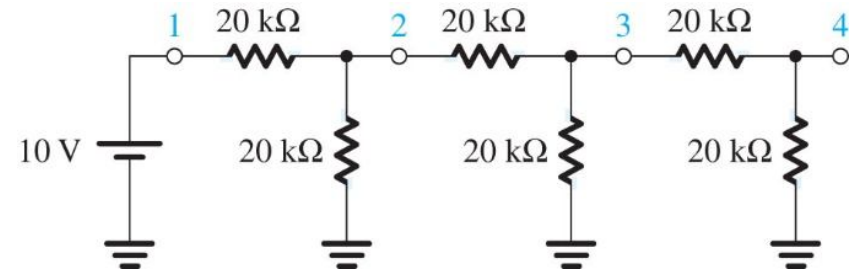
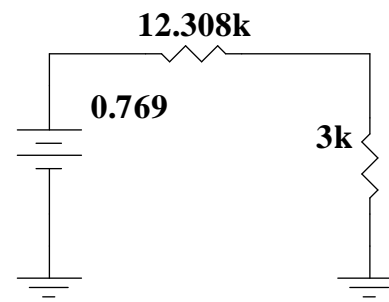


Figure P1.15

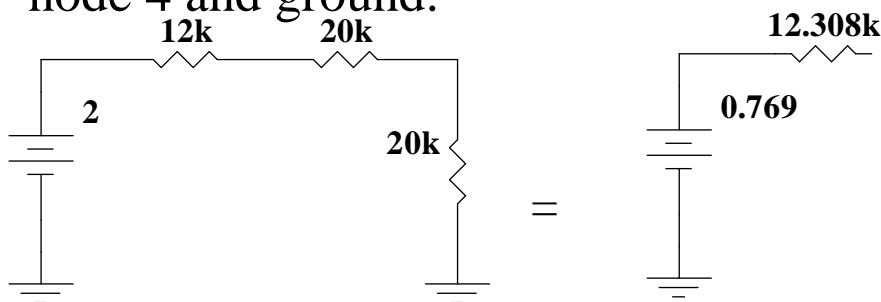

At node 4 we have 2V in with $32\text{ k}\Omega$ series and $20\text{ k}\Omega$ shunt resistance which yields 0.77V with $12.3\text{ k}\Omega$ series resistance



When a $3\text{ k}\Omega$ load resistance is added we get the following current

$$I = \frac{0.77\text{V}}{12.3\text{k}\Omega + 3\text{k}\Omega} = 0.050\text{mA}$$



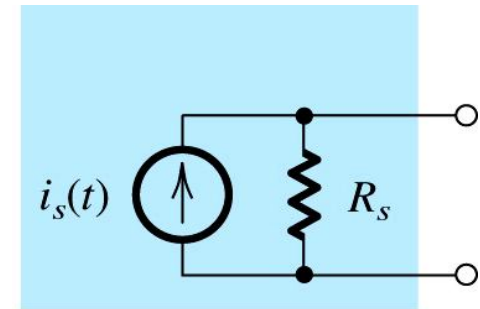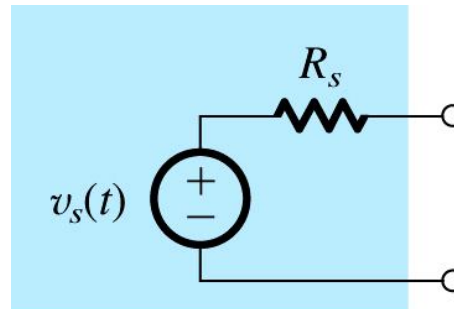Problem 1.23

Any given signal source provides an open-circuit voltage, v_{oc} , and a short-circuit current i_{sc} . For the following sources, calculate the internal resistance, R_s ; the Norton current, i_s ; and the Thevenin voltage, v_s .



(a) $v_{oc} = 1 \text{ V}$, $i_{sc} = 0.1 \text{ mA}$

$$v_s = v_{oc} = 1 \text{ V}; i_s = i_{sc} = 0.1 \text{ mA}, R_s = v_{oc}/i_{sc} = 10 \text{ k}\Omega$$


(b) $v_{oc} = 0.1 \text{ V}$, $i_{sc} = 1 \text{ }\mu\text{A}$

$$v_s = v_{oc} = 0.1 \text{ V}; i_s = i_{sc} = 1 \text{ }\mu\text{A}, R_s = v_{oc}/i_{sc} = 100 \text{ k}\Omega$$



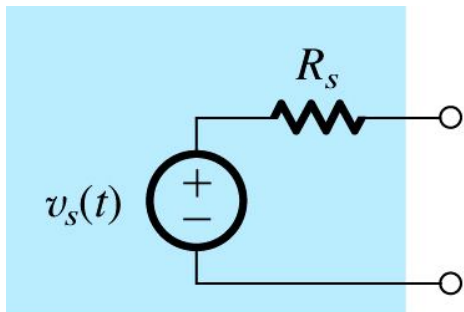Problem 1.24

A particular signal source produces an output of 40 mV when loaded by a 100-k Ω resistor and 10 mV when loaded by a 10-k Ω resistor. Calculate the Thevenin voltage, Norton current, and source resistance.



$$v_o = v_s \frac{R_L}{R_L + R_s} \Rightarrow v_s = v_o \frac{R_L + R_s}{R_L} = v_o \left(1 + \frac{R_s}{R_L} \right)$$

$$v_s = 40\text{mV} \left(1 + \frac{R_s}{100\text{k}\Omega} \right) = 10\text{mV} \left(1 + \frac{R_s}{10\text{k}\Omega} \right)$$

$$R_s = 50\text{k}\Omega$$

$$v_s = 40\text{mV} \left(1 + \frac{50\text{k}\Omega}{100\text{k}\Omega} \right) = 10\text{mV} \left(1 + \frac{50\text{k}\Omega}{10\text{k}\Omega} \right) = 60.0\text{mV}$$

$$i_s = \frac{v_s}{R_s} = \frac{60\text{mV}}{50\text{k}\Omega} = 1.2\mu\text{A}$$



Problem 1.28

To familiarize yourself with typical values of angular frequency ω , conventional frequency f , and period T , complete the entries in the following table:

case	ω (rad/s)	f (Hz)	T (s)
a		5×10^9	
b	2×10^9		
c			1×10^{-10}
c		60	
e	6.28×10^4		
f			1×10^{-5}

$$\omega = 2\pi f$$

$$f = \omega / 2\pi$$

$$T = 1/f = 2\pi/\omega$$



Problem 1.28


To familiarize yourself with typical values of angular frequency ω , conventional frequency f , and period T , complete the entries in the following table:

case	ω (rad/s)	f (Hz)	T (s)
a	3.14E+10	5.00E+09	2.00E-10
b	2.00E+09	3.18E+08	3.14E-09
c	6.28E+10	1.00E+10	1.00E-10
c	3.77E+02	60.00	1.67E-02
e	6.28E+04	9.99E+03	1.00E-04
f	6.28E+05	1.00E+05	1.00E-05

$$\omega = 2\pi f$$

$$f = \omega / 2\pi$$

$$T = 1/f = 2\pi/\omega$$

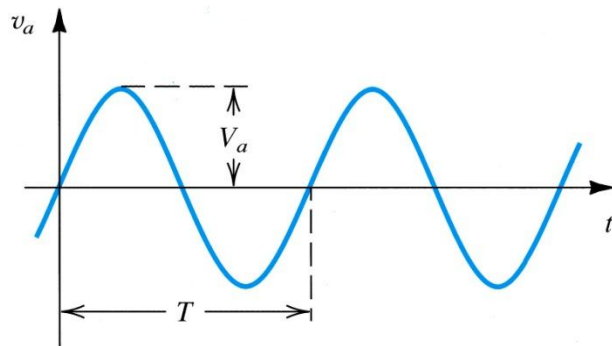

Problem 1.30

$$v_a(t) = V_a \sin(\omega t)$$

Give expressions for the sine-wave voltage signals having:

(a) 10-V peak amplitude and 1-kHz frequency

$$v_a(t) = 10 \sin(2\pi 1000t)$$

(b) 120-V_{rms}, and 60-Hz frequency

$$v_a(t) = 120\sqrt{2} \sin(2\pi 60t)$$

(c) 0.2-V peak-to-peak and 2000-rad/s frequency

$$v_a(t) = 0.1 \sin(2000t)$$

(d) 100-mV peak and 1 ms period

$$v_a(t) = 0.1 \sin(2\pi 1000t)$$