

Problem 1

Solution:

Known quantities:

The schematic of the circuit (see Figure P3.10).

Find:

The Thévenin equivalent resistance seen by resistor R_5 , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when R_5 is the load.

Analysis:

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = 25 \, \Omega \parallel (75 \, \Omega + 200 \, \Omega) = 22.92 \, \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

For node #1:

$$\frac{v_1}{200} + \frac{v_1 - v_2}{75} = 0.2$$

For node #2:

$$\frac{v_2 - v_1}{75} + \frac{v_2}{25} + \frac{v_2 - v_3}{50} + i_{10V} = 0$$

For node #3:

$$\frac{v_3 - v_2}{50} = i_{10V}$$

For the voltage source:

$$v_3 + 10 = v_2$$

Solving the system,

$$v_1 = 13.33 \, \text{V}, \, v_2 = 3.33 \, \text{V} \text{ and } v_3 = -6.67 \, \text{V}.$$

Therefore,

$$v_{OC} = v_3 = -6.67 \, \text{V}.$$

(3) Replace the load with a short circuit. Redraw the circuit.

For mesh (a):

$$i_a(50) = 10$$

For mesh (b):

$$i_b(300) - i_c(25) = 40$$

For mesh (c):




$$i_b(25) - i_c(25) = 10$$

Solving the system,

$$i_a = 200 \, \text{mA}, \, i_b = 109 \, \text{mA} \text{ and } i_c = -291 \, \text{mA}.$$

Therefore,

$$i_{SC} = i_c = -291 \, \text{mA}.$$

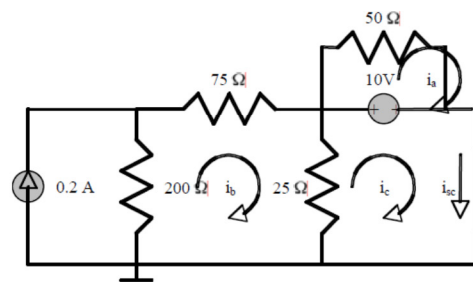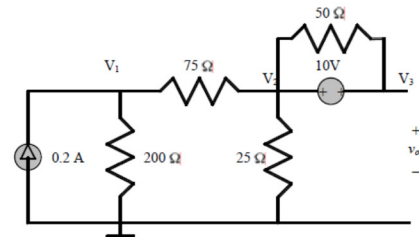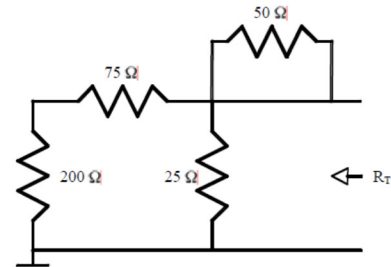

Problem 2

Solution:

Known quantities:

The schematic of the circuit (see Figure P3.23).

Find:

The Thévenin equivalent resistance seen by resistor R_5 , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when R_5 is the load.

Analysis:

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = 0.5 \, \Omega + 0.25 \, \Omega + (0.5 \, \Omega \parallel 0.5 \, \Omega) = 1 \, \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

For node #1:

$$\frac{v_1 - 3}{0.5} + \frac{v_1}{0.5} + \frac{v_1 - v_2}{0.25} = 0$$

For node #2:

$$\frac{v_2 - v_1}{0.25} + 0.5 = 0$$

Solving the system,

$$v_1 = 1.375 \, \text{V} \text{ and } v_2 = 1.25 \, \text{V}.$$

Therefore,

$$v_{OC} = v_2 = 1.25 \, \text{V}.$$

(3) Replace the load with a short circuit. Redraw the circuit.

For mesh (a):

$$i_a(0.5 + 0.5) - i_b(0.5) = 3$$

For meshes (b) and (c):

$$-i_a(0.5) + i_b(0.5 + 0.25) + i_c(0.5) = 0$$

For the current source:




$$i_b - i_c = 0.5$$

Solving the system,

$$i_a = 3.875 \, \text{A}, \quad i_b = 1.75 \, \text{A} \text{ and } i_c = 1.25 \, \text{A}.$$

Therefore,

$$i_{SC} = i_c = 1.25 \, \text{A}.$$

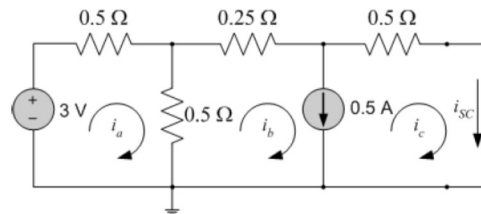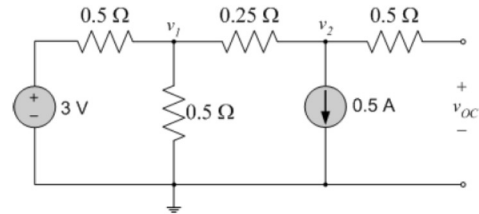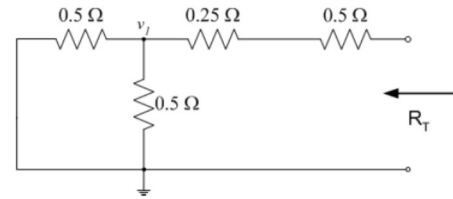

Problem 3

Solution:

Known quantities:

The schematic of the circuit (see Figure P3.25).

Find:

The Thévenin equivalent resistance seen by resistor R_4 , the Thévenin (open-circuit) voltage and the Norton (short-circuit) current when R_4 is the load.

Analysis:

(1) Remove the load, leaving the load terminals open circuited, and the voltage sources. Redraw the circuit.

$$R_T = R_2 \parallel (R_3 + (R_1 \parallel R_5)) = 20 \, \Omega \parallel (20 \, \Omega + (50 \, \Omega \parallel 15 \, \Omega)) = 12.24 \, \Omega$$

(2) Remove the load, leaving the load terminals open circuited. Redraw the circuit.

For node #1:

$$\frac{v_1 - 12}{50} + \frac{v_1 - v_2}{20} + i_{5V} = 0$$

For node #2:

$$\frac{v_2 - v_1}{20} + \frac{v_2}{20} = 0$$

For node #3:

$$\frac{v_3}{15} - i_{5V} = 0$$

For the 5-V voltage source:

$$v_1 - v_3 = 5$$

Solving the system,

$$v_1 = 5.14 \, \text{V}, \, v_2 = 2.57 \, \text{V}, \, v_3 = 0.13 \, \text{V} \text{ and } i_{5V} = 8.95 \, \text{mA}.$$

Therefore,

$$v_{OC} = v_2 - v_3 = 2.44 \, \text{V}.$$

(3) Replace the load with a short circuit. Redraw the circuit.

For mesh (a):

$$i_a(90) - i_b(20) - i_c(20) = 12$$

For mesh (b):

$$-i_a(20) + i_b(20) + 5 = 0$$

For mesh (c):

$$-i_a(20) + i_c(35) = 0$$

Solving the system,

$$i_a = 119.5 \, \text{mA}, \, i_b = -130.5 \, \text{mA} \text{ and } i_c = 68.3 \, \text{mA}.$$

Therefore,

$$i_{SC} = i_c - i_b = 198.8 \, \text{mA}.$$

