

CPEG 422/622 Spring 2020

Homework 3

Due March 16th at midnight (through Canvas)

Put your name in the comment part of the code you submitted!

1. Please implement a 24-bit universal shift register with VHDL programming, the register should have clear, parallel load, shift right, shift left, and store function. The entity view is shown below:

```
entity shift_register is
Port {
    clock: in STD_LOGIC;
    clear: in STD_LOGIC;
    control:      in STD_LOGIC_VECTOR(1 downto 0);
    serial_in:    in STD_LOGIC;
    parallel_in:  in STD_LOGIC_VECTOR(23 downto 0);
    serial_out:   out STD_LOGIC;
    parallel_out: out STD_LOGIC_VECTOR(23 downto 0)
};
end shift_register;
```

- a) Clear is synchronous reset (clock rising edge sensitive)
- b) Control signals (also synchronized by clock rising edge) defined as:
 - 00 STORE (hold Serial_out, Parallel_out and register values)
 - 01 RIGHT (shift right, Serial_in is loaded to the leftmost register, and rightmost bit is sent to Serial_out)
 - 10 LEFT (shift left, Serial_in is loaded to the rightmost register, and leftmost bit is sent to Serial_out)
 - 11 PARALLEL (load "Parallel_in" to the register in parallel.)

Please submit your design source file and testbench.

Grading policy:

No syntax error – 10

Assignment of Q (states) is correctly implemented with case or if statements – 5


Implementation is synchronous, inside a process, triggered by the rising edge of clock, and clock is in the sensitivity list – 5

The four modes are correct – 5 pts each, total 20

Testbench correctly tests the four modes – 10

 2. An FSM that controls booth multiplication is shown below, please write a VHDL code to implement this FSM. Submit your source files and testbench.

```
entity booth_control is
  Port (
    clock : in STD_LOGIC;
    reset : in STD_LOGIC;
    start : in STD_LOGIC;
    count_up : in STD_LOGIC;
    init : out STD_LOGIC;
    loadA : out STD_LOGIC;
    shift : out STD_LOGIC;
    done : out STD_LOGIC
  );
end booth_control;
```



- a) reset is synchronous (clock rising edge sensitive)
- b) Initial state is S_0 , and FSM has four states in total.
 - S_0 : Idle, circuit is ready.
 - S_1 : Init, initialize components.
 - S_2 : LoadA, selectively load result from adder/subtractor to product register.
 - S_3 : Shift, shift product register and multiplier register one bit to the right.
- c) State transitions caused by input (synchronized by clock rising edge) are:
 - S_0 : if $start=1$, $S_0 \rightarrow S_1$; otherwise remains in S_0 .
 - S_1 : S_1 always moves to S_2 regardless of the inputs.
 - S_2 : S_2 always moves to S_3 regardless of the inputs.
 - S_3 : if $count_up=1$, $S_3 \rightarrow S_0$; otherwise if $S_3 \rightarrow S_2$.
- d) Outputs at each state are:
 - S_0 : $done=1$; $init=0$; $loadA=0$; $shift=0$;
 - S_1 : $done=0$; $init=1$; $loadA=0$; $shift=0$;
 - S_2 : $done=0$; $init=0$; $loadA=1$; $shift=0$;
 - S_3 : $done=0$; $init=0$; $loadA=0$; $shift=1$;

Grading policy:

No syntax error – 10

Reset is synchronous – 5

Implementation is synchronous, inside a process, triggered by the rising edge of clock, and clock is in the sensitivity list – 5

Assignment of Q (next state logic) is correctly implemented with case or if statements – 10

Output logic are correctly implemented with case or if statements – 10

Testbench correctly tests FSM functions – 10