



Homework #7


Problems 4.2, 4.3, 4.9, 4.17, and
4.23



Problem 4.2


For the circuits shown in Fig. P4.2 using ideal diodes, find the values of the voltages and currents indicated.

Figure P4.2

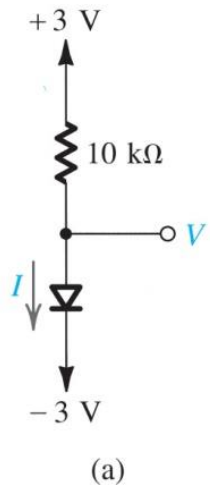


$$I = \frac{3\text{V} - (-3\text{V})}{10\text{k}\Omega} = 0.6\text{mA}$$

$$V = -3\text{V}$$

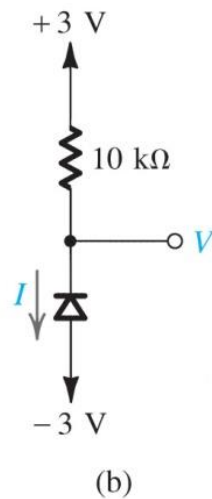


$$I = 0\text{mA}$$

$$V = +3\text{V}$$

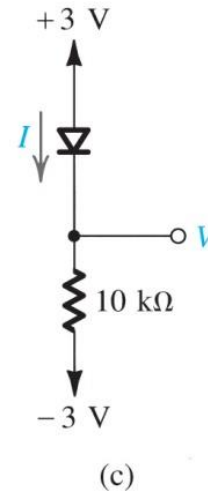

$$I = \frac{3\text{V} - (-3\text{V})}{10\text{k}\Omega} = 0.6\text{mA}$$

$$V = +3\text{V}$$

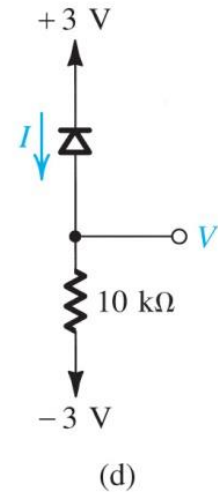

$$I = 0\text{mA}$$


$$V = -3\text{V}$$



Problem 4.3

For the circuits shown in Fig. P4.3 using ideal diodes, find the values of the voltages and currents indicated.


Figure P4.3

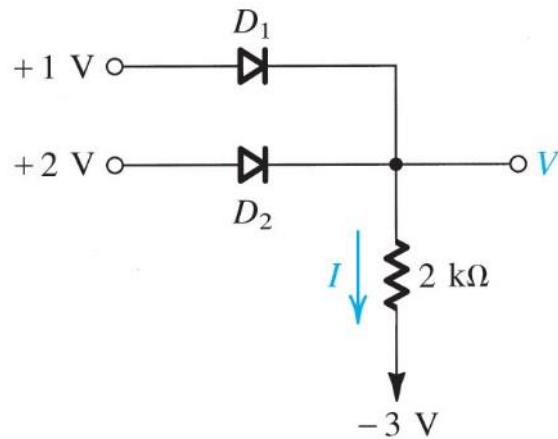

(a)

$$I = \frac{2\text{ V} - (-3\text{ V})}{2\text{ k}\Omega} = 2.5\text{ mA}$$

$$V = +2\text{ V}$$

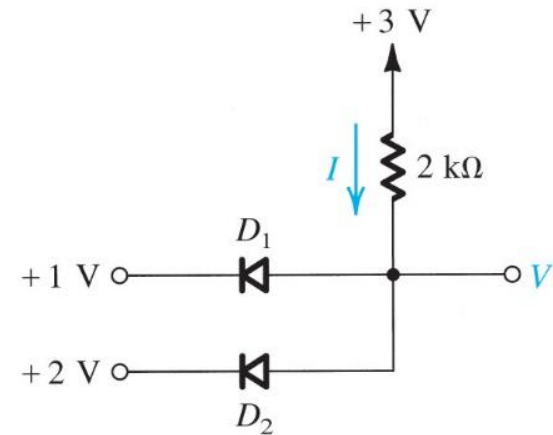

(b)

$$I = \frac{3\text{ V} - 1\text{ V}}{2\text{ k}\Omega} = 1\text{ mA}$$

$$V = +1\text{ V}$$



Problem 4.9

Assuming that the diodes in the circuits of Fig. P4.9 are ideal, find the values of the labeled voltages and currents.

Assume D_1 is conducting, then the voltage at the anode is 0 V and D_2 is also conducting and the output voltage, $V = 0$ V.

$$I = \frac{3V}{12k\Omega} - \frac{3V}{6k\Omega} = 0.25\text{mA} - 0.5\text{mA}$$


$$I = -0.25\text{mA}$$

Not possible!! so D_1 is off.

$$I = 0\text{mA}$$

$$V = -3V + 6V \frac{6k\Omega}{18k\Omega} = -1V$$

Which verifies that D_1 is off.

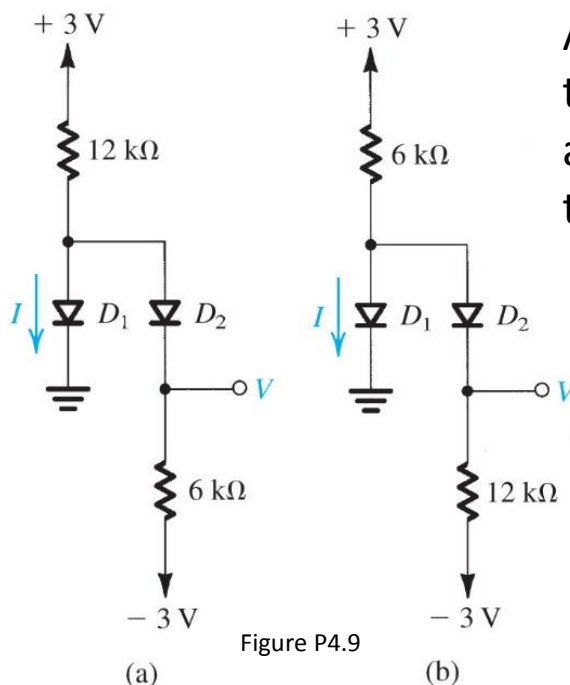

Assume D_1 is conducting, then the voltage at the anode is 0 V and D_2 is also conducting and the output voltage, $V = 0$ V.

$$I = \frac{3V}{6k\Omega} - \frac{3V}{12k\Omega} = 0.5\text{mA} - 0.25\text{mA}$$

$$I = 0.25\text{mA}$$

$$V = 0V$$



Problem 4.17

Calculate the value of the thermal voltage, V_T , at -55°C , 0°C , $+40^\circ\text{C}$, and $+125^\circ\text{C}$.
At what temperature is V_T exactly 25 mV?

$$V_T = 0.0862T \text{ mV}$$

Problem 4.17		
Temp (C)	Temp (K)	V_T (mV)
-55	218	18.79
0	273	23.53
40	313	26.98
125	398	34.31

$$T = \frac{V_T}{0.0862}$$

$$T = \frac{25\text{mV}}{0.0862} = 290.0232019\text{K}$$

Problem 4.23

The circuit in Fig. P4.23 utilizes three identical diodes having $I_S = 10^{-14}$ A. Find the value of the current I required to obtain an output voltage $V_O = 2.0$ V. If a current of 1 mA is drawn away from the output terminal by a load, what is the change in output voltage?

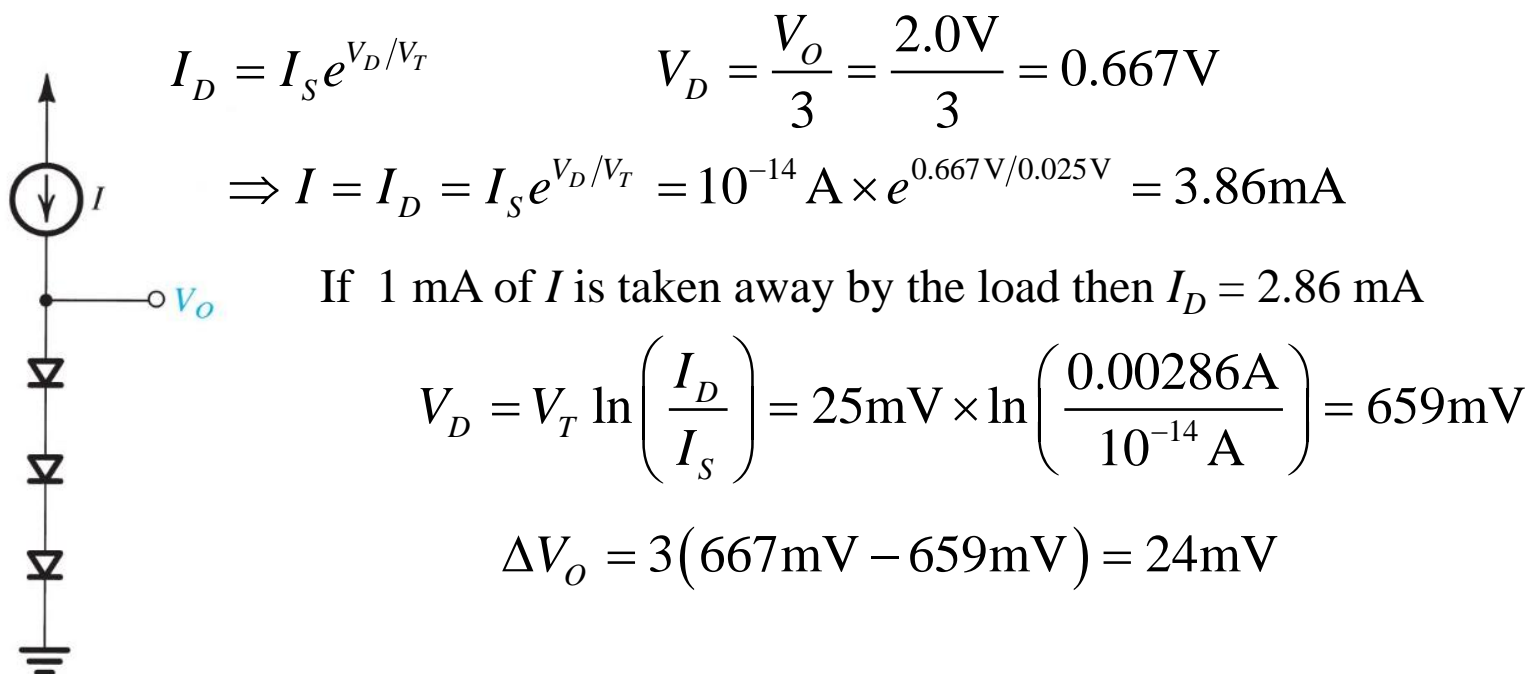


Figure P4.23