

Problem 1

A capacitor consists of two circular plates of radius 5 cm and separation 1.2 mm. (a) Estimate the capacitance. (b) If the field toward the middle of the capacitor is 25 V/m, estimate the charge on the capacitor plates.

Problem 2

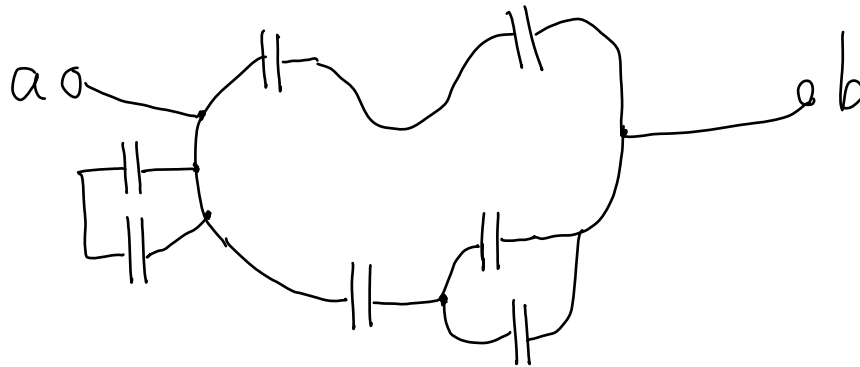
A parallel-plate air capacitor of capacitance 400 pF has a charge ± 500 nC. The plates are 2 mm apart. Find (a) the potential difference, (b) the plate areas, (c) the electric field between the plates, and (d) the surface charge density of the plates.

Problem 3


(a) For capacitors $C_1 = 8\mu\text{F}$ and $C_2 = 6\mu\text{F}$, find their capacitance in series and in parallel. (b) Find the charge and voltage difference on each capacitor when they are connected in series with a 12 V battery. (c) Find the charge and voltage difference on each capacitor when they are connected in parallel with a 12 V battery.

Problem 4

The figure below gives a circuit containing a number of capacitors, each of capacitance $C = 6\mu\text{F}$. Find the capacitance between the terminals a and b.

**Problem 5**

What are the charge on and potential difference across each capacitor in the figure below.

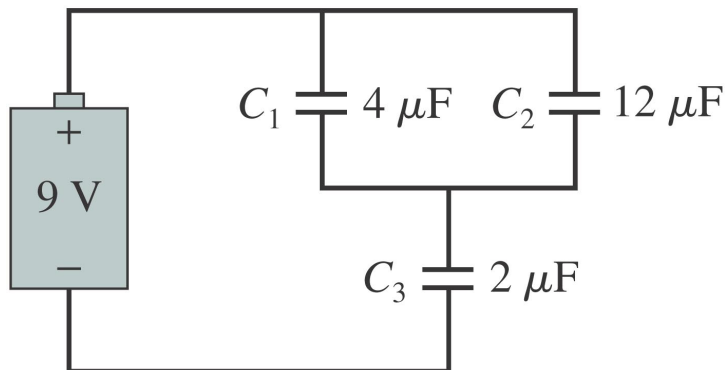

Problem 6

Ch 24 # 23

Problem 7

Ch 24 # 87

Problem 8

Ch 24 #89

Problem 9

The voltage across a $100\text{ }\mu\text{F}$ capacitor takes the following values. Calculate the expression for the current through the capacitor in each case.

a. $v_C(t) = 40 \cos(20t - \pi/2) \text{ V}$

b. $v_C(t) = 20 \sin 100t \text{ V}$

c. $v_C(t) = -60 \sin(80t + \pi/6) \text{ V}$

d. $v_C(t) = 30 \cos(100t + \pi/4) \text{ V}$

Problem 10

The current through a 250-mH inductor takes the following values. Calculate the expression for the voltage across the inductor in each case.

a. $i_L(t) = 5 \sin 25t \text{ A}$

b. $i_L(t) = -10 \cos 50t \text{ A}$

c. $i_L(t) = 25 \cos(100t + \pi/3) \text{ A}$

d. $i_L(t) = 20 \sin(10t - \pi/12) \text{ A}$