


**Problem 1**

Ch. 26, #56


**Problem 2**

The circuit below is used to measure the internal resistance of a battery. The battery being tested is a NiMH battery cell.

- A fresh battery is being tested, and it is found that the voltage  $V_{out}$  is 2.28 V with the switch open and 2.27 V with the switch closed. Find the internal resistance of the battery.
- The same battery is tested one year later, and  $V_{out}$  is found to be 2.2 V with the switch open but 0.31 V with the switch closed. Find the internal resistance of the battery.

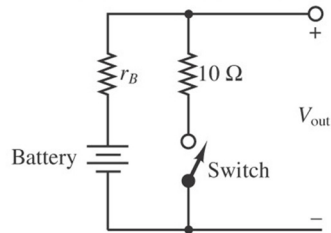
**Problem 3**

For the circuit below, find the current through and voltage across each resistor. Place your results in a table for ease of reading.

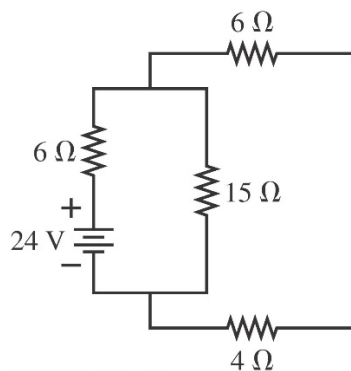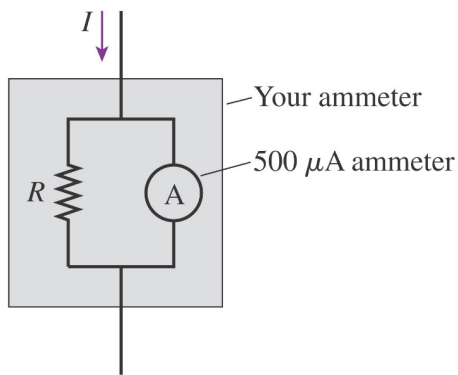**Problem 4**

A circuit you are building needs an ammeter that goes from 0 mA to a full-scale reading of 50 mA. Unfortunately, the only ammeter in the storeroom goes from 0  $\mu$ A to a full-scale reading of only 500  $\mu$ A. Fortunately, you have just finished a physics class, and you realized that you can make this ammeter work by putting a resistor in parallel with it, as shown in the Figure below. You have measured that the resistance of the ammeter is 50.0  $\Omega$ , not the 0  $\Omega$  of an ideal ammeter.

- What value of  $R$  must you use so that the meter will go to full scale when the current  $I$  is 50 mA?
- What is the effective resistance of your ammeter?



### Problem 5

Use KCL/KVL method to solve Ch 26 # 32

### Problem 6

Use KCL/KVL method to solve Ch 26 #33

### Problem 7

Use KCL/KVL method to solve Ch 26 #34

### Problem 8

Ch 26 #36

### Problem 9

Let  $\mathcal{E}_1 = 6\text{V}$ ,  $\mathcal{E}_2 = 10\text{V}$ ,  $r_1 = 0.01\ \Omega$ ,  $r_2 = 0.02\ \Omega$ , and  $R = 0.01\ \Omega$ .

(a) Use junction and loop rules to solve for currents in each branch.

(b) What is the voltage across  $R$ ?

(c) Calculate the heating power on each resistor. For each battery, determine if it is discharging or charging. Calculate the rate of charging or discharging.

