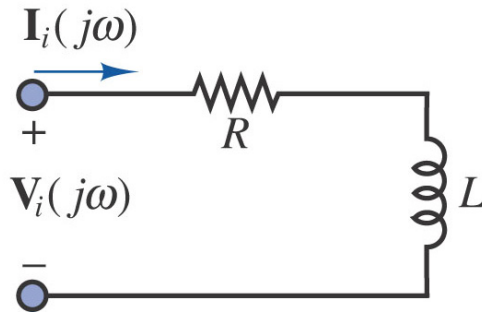


### Problem 1

In the circuit below, where  $L = 2 \text{ mH}$  and  $R = 2 \text{ k}\Omega$ ,


- Determine how the input impedance  $Z(j\omega) = \frac{V_i(j\omega)}{I_i(j\omega)}$  behaves at extremely high and low frequencies.
- Find an expression for the impedance.
- Show that this expression can be manipulated into the form  $Z(j\omega) = R \left[ 1 + j \frac{\omega L}{R} \right]$ .
- Determine the frequency  $\omega = \omega_c$  for which the imaginary part of the expression in part c is equal to 1.
- Estimate the magnitude and phase angle of  $Z(j\omega)$  at  $\omega = 10^5 \text{ rad/s}$ ,  $10^6 \text{ rad/s}$ , and  $10^7 \text{ rad/s}$ .


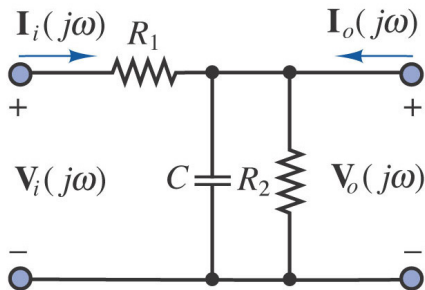
### Problem 2


In the circuit below:  $R_1 = 1.3 \text{ k}\Omega$ ,  $R_2 = 1.9 \text{ k}\Omega$ , and  $C = 0.5182 \text{ }\mu\text{F}$ .

- Determine how the voltage transfer function  $H_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$  behaves at extremes of high and low frequencies.
- Obtain an expression for the voltage transfer function and show that it can be manipulated into the form  $H_v(j\omega) = \frac{H_0}{1 + jf(\omega)}$  where  $H_0 = \frac{R_2}{R_1 + R_2}$  and  $f(\omega) = \frac{\omega R_1 R_2 C}{R_1 + R_2}$ .
- Determine the frequency at which  $f(\omega) = 1$  and the value of  $H_0$ .



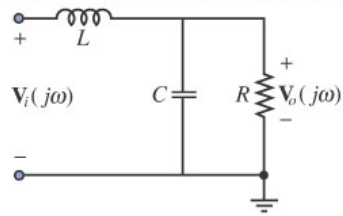
### Problem 3


Are the filters shown below low-pass, high-pass, band-pass, or band-stop (notch) filters?



(a)

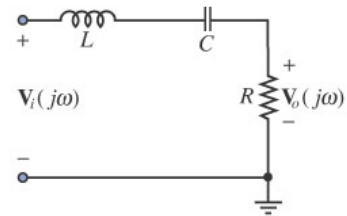


(b)

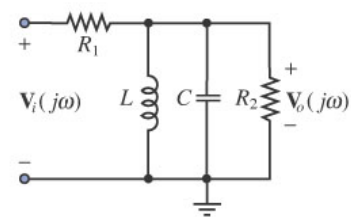


(c)
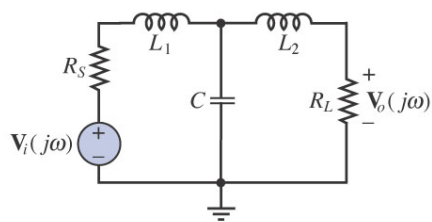
### Problem 4


Determine if each of the circuits shown below is a low-pass, high-pass, band-pass, or band-stop (notch) filter.




(a)

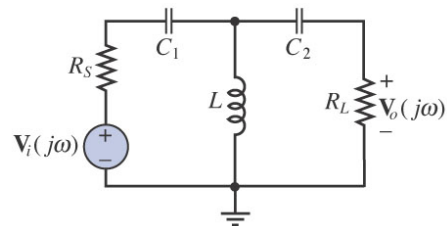

(c)

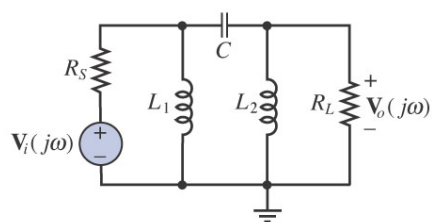

(b)

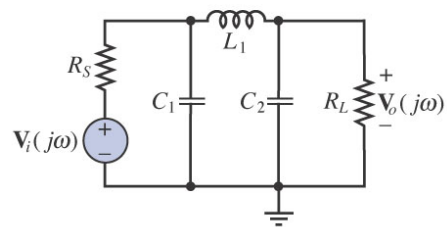

(d)