

Chapter 1 Direct Current Circuits

* Ohm's law (ch. 25)


Basic Concepts

Electric charge Q : fundamental quantity of electricity

Smallest charge, electron, -1.6×10^{-19} Coulomb (C)

Electric current: $I = \frac{\Delta Q}{\Delta t}$, unit: Ampere (A)
Coulomb/sec.

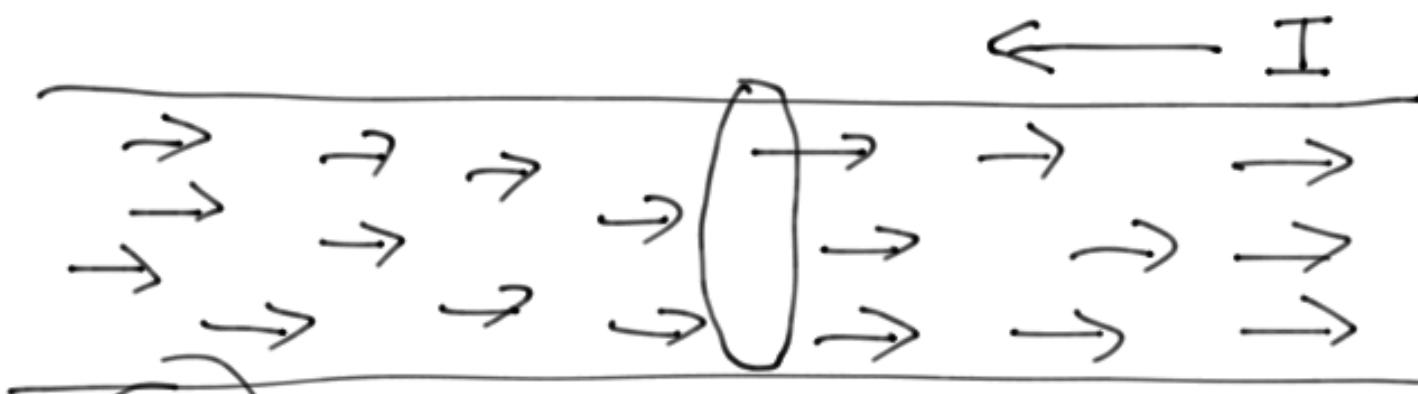Continuous flow of charges gives rise to electric current. Electric current (I) is the rate at which charges cross a given cross-section in a circuit.



(-e)

electrons moving to the right

Electric current flows to the left.

Direction of current is opposite to direction of motion of electrons.

During time period Δt , amount of charge ΔQ passes through cross-section.

$$I = \frac{\Delta Q}{\Delta t}$$

Next question : what drives electric current ?

Electric field $\xleftarrow{\text{in analogy}}$ gravitational field.

Electric potential
(voltage) \longleftrightarrow gravitational potential energy

electric charge \longleftrightarrow object.

Voltage : electric potential difference .

Total work per unit charge done by electric field associated with the motion of charge between two points.

Unit : volt , [$V = 1 \text{ Joule/Coulomb}$ potential energy difference per unit charge .]

qV: electric potential energy

mgh: gravitational potential energy

V is in analogy to gh.

see voltage as a "driving force" for
electric currents.

Just like water currents flow from a higher
point to a lower point, electric current
flows from a higher potential to a
lower potential.


Ohm's law

$$R = \frac{\Delta V}{I} \rightarrow \begin{matrix} \text{voltage difference} \\ \text{electric current} \end{matrix}$$

Electric current is proportional to the voltage difference between two ends of a conductor.

The proportionality constant is defined as resistance R .


$$V_1 > V_2$$

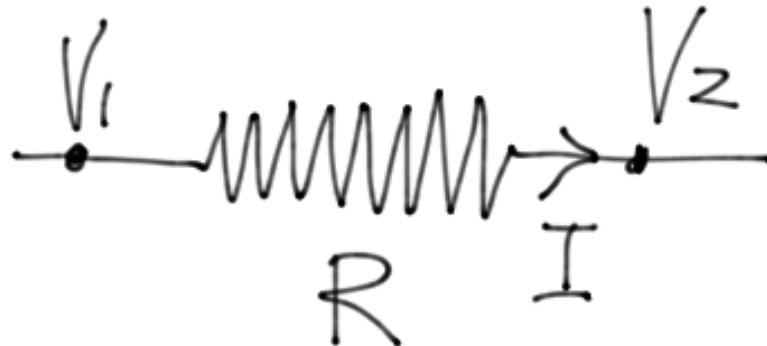

$$\Delta V = V_1 - V_2$$

$$I = \frac{\Delta V}{R}$$

slope of curve: $\frac{1}{R}$

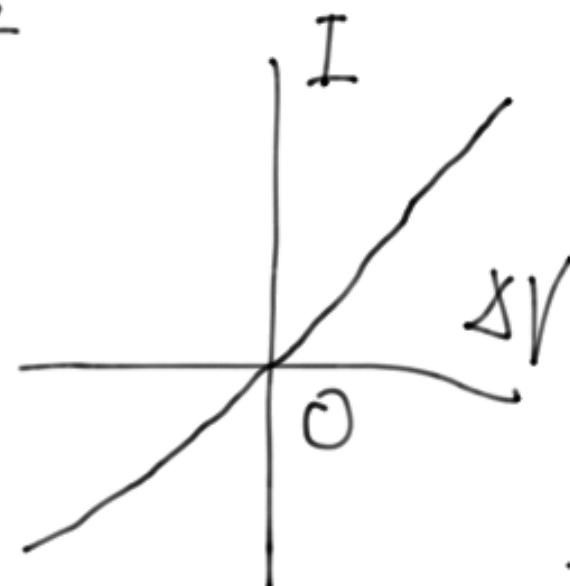

Recap:


- * Current flows from higher voltage to lower voltage.
- * R is independent of ΔV or I for conductors.
- * Voltage difference causes current in conductors.

Also note, ΔV can be simplified to V

So, $R = \frac{V}{I}$

Ohm's law is not universal.
Some materials (semiconductors or polymers)
do not obey Ohm's law.

semiconductor diode :

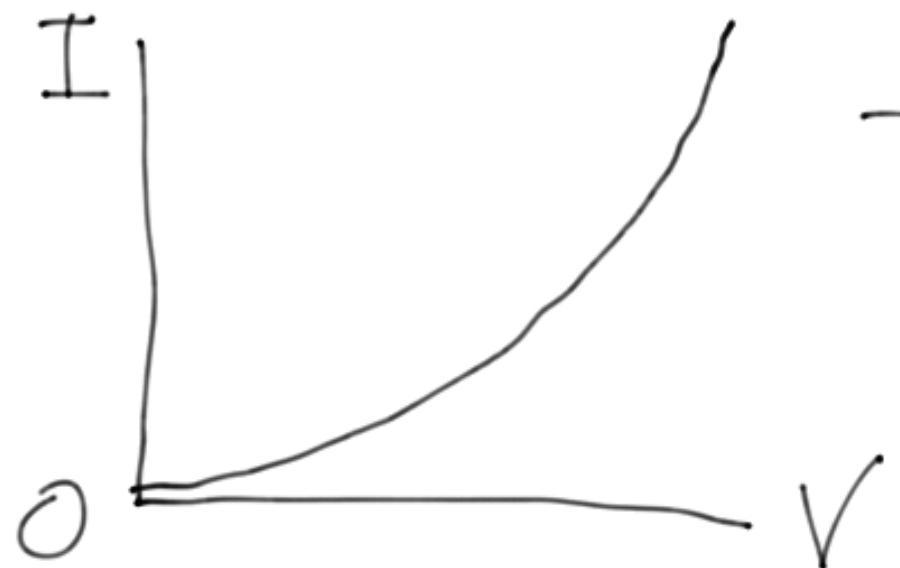

→ not "linear"
non-ohmic .

Resistivity :

Consider a conducting wire with uniform cross section.

$$R = \rho \frac{L}{A}$$

L : length

A : (cross-sectional) area.

ρ : resistivity

Resistance (R) depends on both materials and geometries.

Resistivity (ρ) only depends on materials.

Joule heating power.

Electric power

electric field moving charge \rightarrow doing work.

$$\text{Power } (P) = \frac{\text{Work}}{\text{time}} = \frac{\text{Work}}{\text{charge}} \cdot \frac{\text{charge}}{\text{time}}$$
$$= V \cdot I$$

↓ ↓
V I

unit of P: Joule/time = Watt

$$P = I V \quad I = \frac{V}{R}$$

$$P = \left(\frac{V}{R}\right) V = \frac{V^2}{R}$$

$$P = I (IR) = I^2 R$$

} only for conductors
that obey ohm's
law.

Example

1000 W hair dryer, $V=120V$.

$$I=? \quad R=?$$

$$P=IV, \quad I=\frac{P}{V}=\frac{1000W}{120V}=8.33(A)$$


$$P=\frac{V^2}{R} \quad R=\frac{V^2}{P}=\frac{(120)^2}{1000}=14.4(\Omega)$$

what happens if you use it in 220V lines.

$$P=\frac{V^2}{R}=\frac{(220)^2}{14.4}=366(W)>1000W$$


way above rated power. may damage
the filament (resistor inside).

emf: electro-motive force.

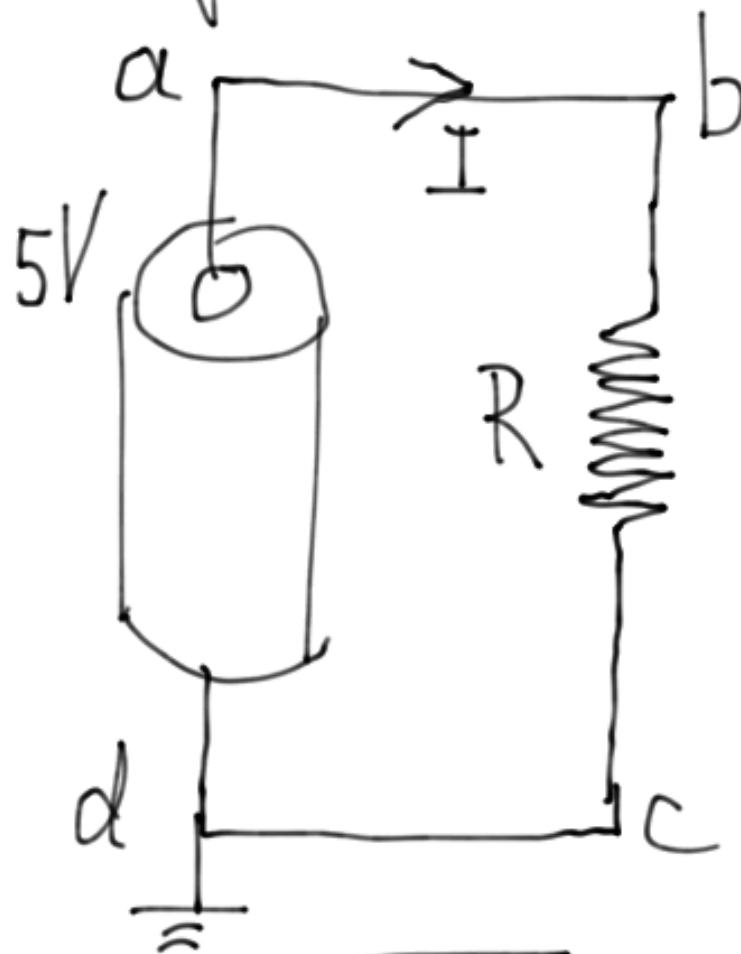

battery:
charge pump

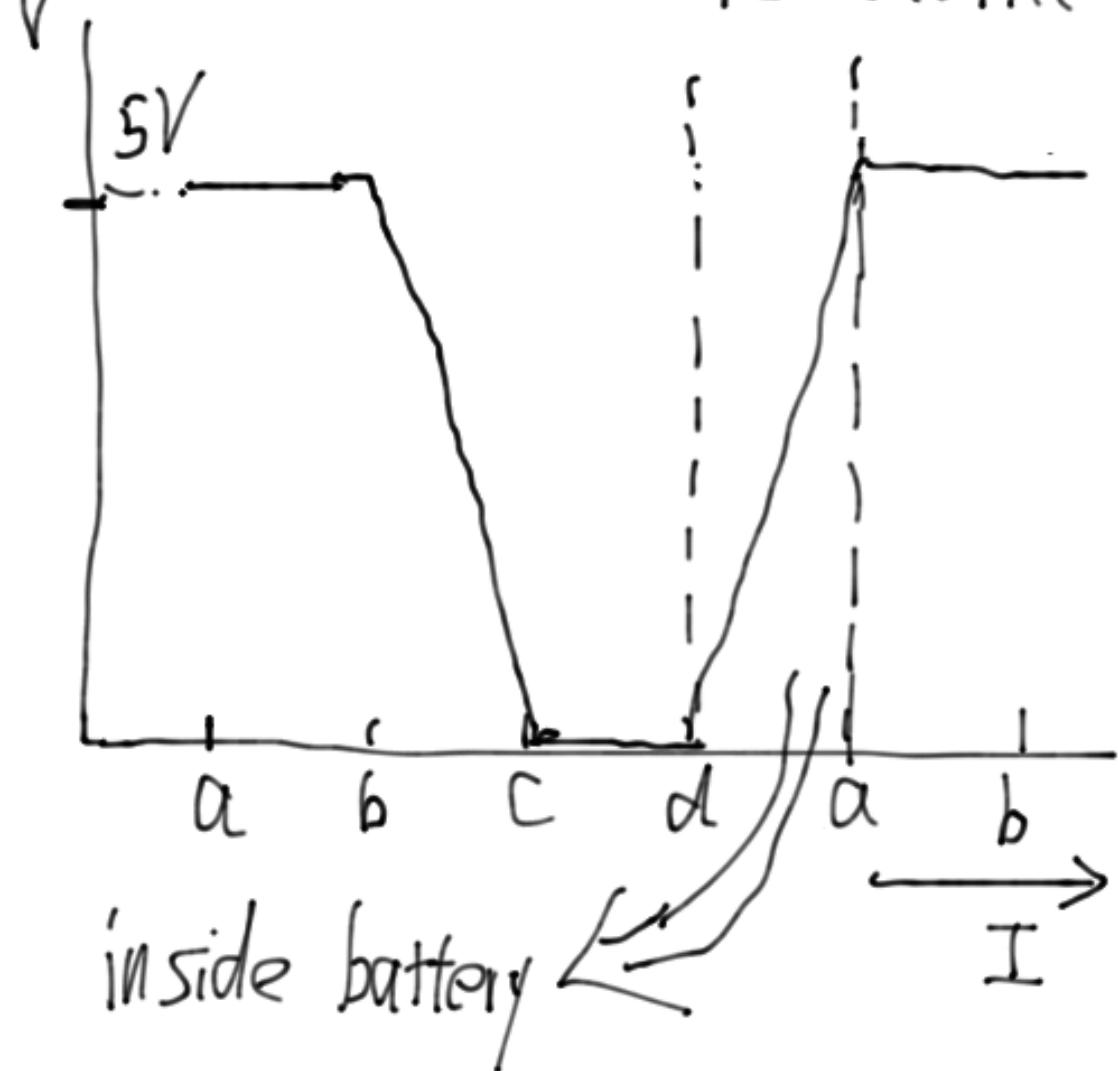[ideal] wires : zero resistance
[ideal] battery : no internal resistance



emf: the current -causing energy sources are called electromotive forces (emf).


batteries and generators are emfs.

emf (ϵ) is in unit of volt (v)


Work per unit charge done by energy sources other than electricity for some specific path.

Question


Is there a current in each case?

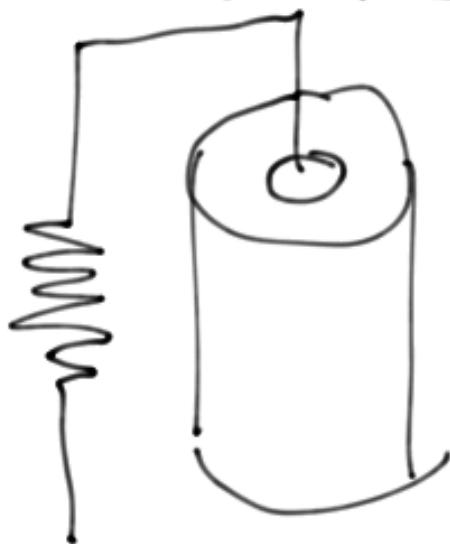

(a)

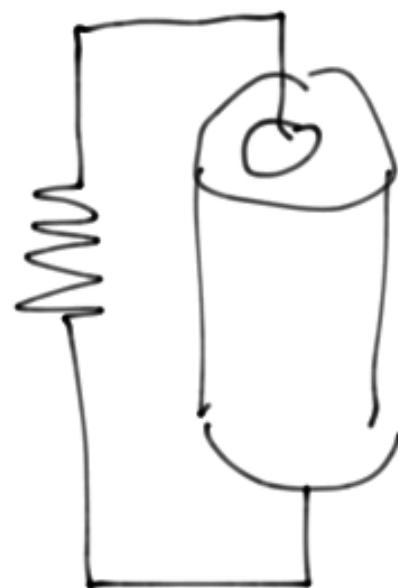


(b)

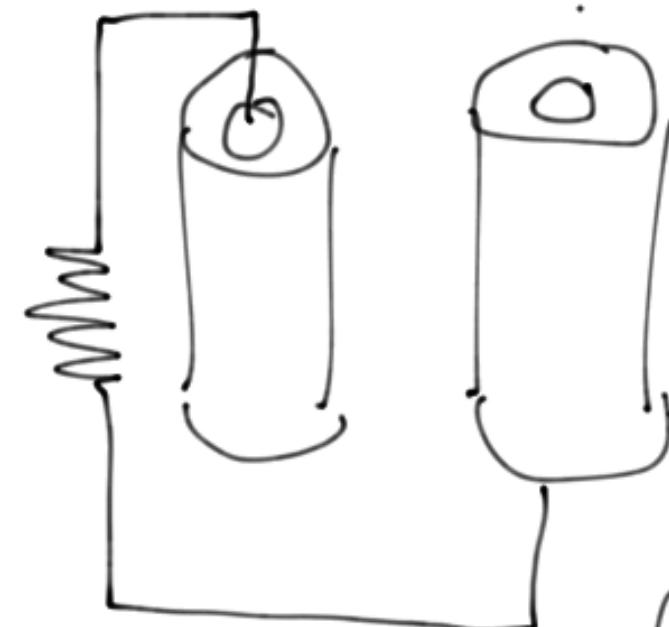

(c)

Have close circuits for current flow.

Also avoid a short circuit:

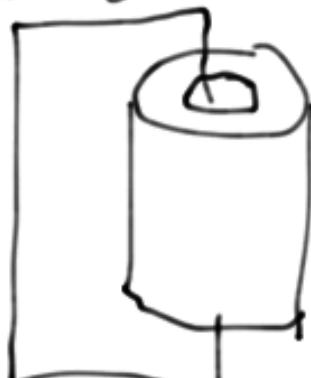


$$I = \frac{V}{R} = \frac{E}{R=0} = \infty$$


$$P = \frac{V^2}{R=0} \rightarrow \infty$$

* Resistors in series and in parallel

Resistors in series

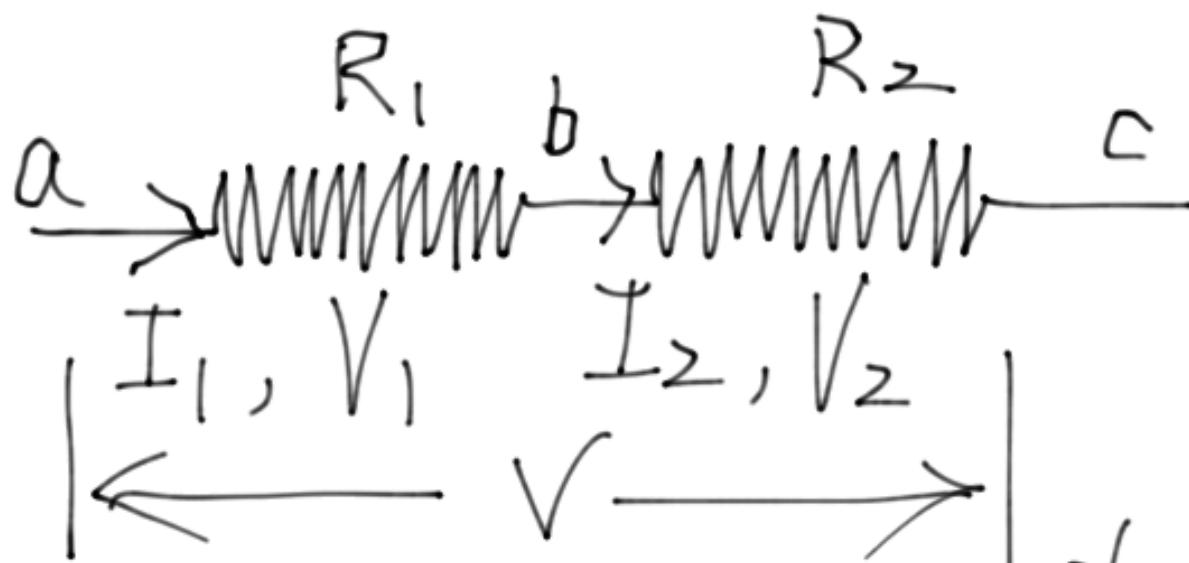

charge conservation

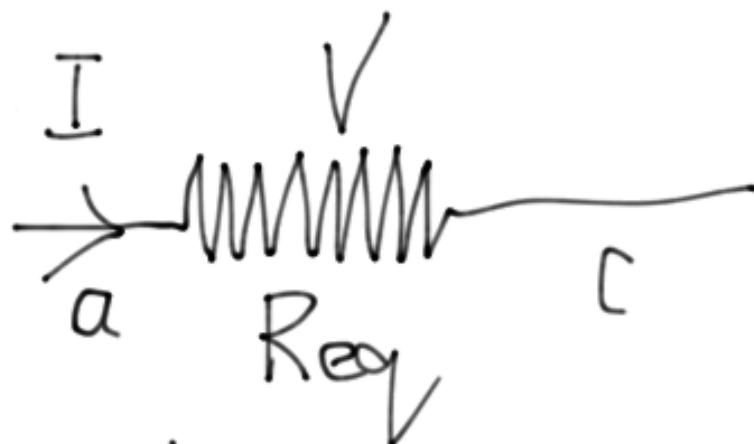

equivalent resistor

$$V_1 = V_a - V_b$$

$$V_2 = V_b - V_c$$

$$\begin{aligned} V_1 + V_2 &= (V_a - V_b) + (V_b - V_c) \\ &= V_a - V_c = V \end{aligned}$$

$$V_1 = I_1 R_1 = IR_1 \quad V_2 = I_2 R_2 = IR_2$$

$$V = IR_{\text{eq}}$$

$$V = V_1 + V_2, \quad IR_{\text{eq}} = IR_1 + IR_2$$

$$R_{\text{eq}} = R_1 + R_2$$

Voltage divider rule.

$$V_1 = IR_1 = \frac{V}{R_{\text{eq}}} \cdot R_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = IR_2 = \frac{V}{R_{\text{eq}}} R_2 = \frac{R_2}{R_1 + R_2} V$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}, \quad \frac{V_1}{V} = \frac{R_1}{R_1 + R_2}, \quad \frac{V_2}{V} = \frac{R_2}{R_1 + R_2}$$


Extend to N resistors in series

$$V_1 : V_2 : V_3 : \dots : V_N = R_1 : R_2 : R_3 : \dots : R_N$$

$$R_{\text{eq}} = R_1 + R_2 + \dots + R_N$$

$$R_{\text{eq}} > \max(R_1, R_2, \dots, R_N)$$

Resistors in parallel

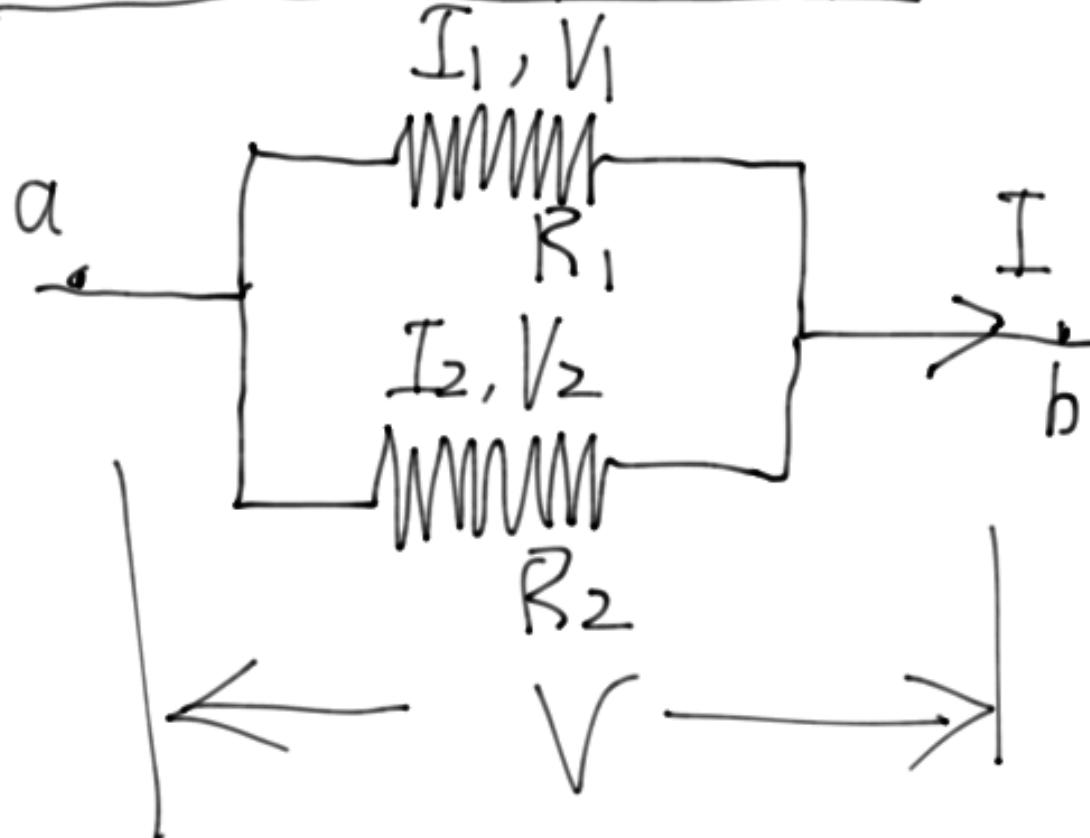

$$I = I_1 + I_2$$

charge conservation


$$V = V_1 = V_2 = V_a - V_b$$

$$I = \frac{V}{R_{eq}}, \quad I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
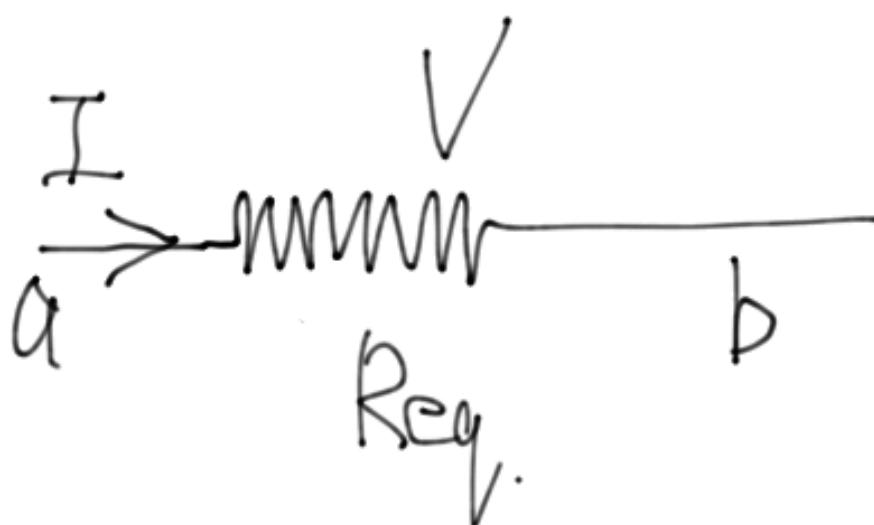
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Define $\frac{1}{R} = G$ conductance

$$G_{eq} = G_1 + G_2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \left| \begin{array}{l} \frac{R_1}{R_1 + R_2} \\ \left(\frac{R_1}{R_1 + R_2} + 1 \right) \end{array} \right\} R_1$$

$$= \frac{R_2}{\left(1 + \frac{R_2}{R_1} \right) R_1} \wedge R_2$$

$$R_{eq} \leq \min(R_1, R_2)$$

Current divider rule


$$I_1 = \frac{V}{R_1} = \frac{I R_{\text{req}}}{R_1} = I \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right) \frac{1}{R_1}$$
$$= I \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = I \frac{G_1}{G_1 + G_2}$$

Similarly $I_2 = I \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = I \frac{G_2}{G_1 + G_2}$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1} = \frac{G_1}{G_2}$$

branch current inversely proportional to branch resistance.

Generalize to N resistors

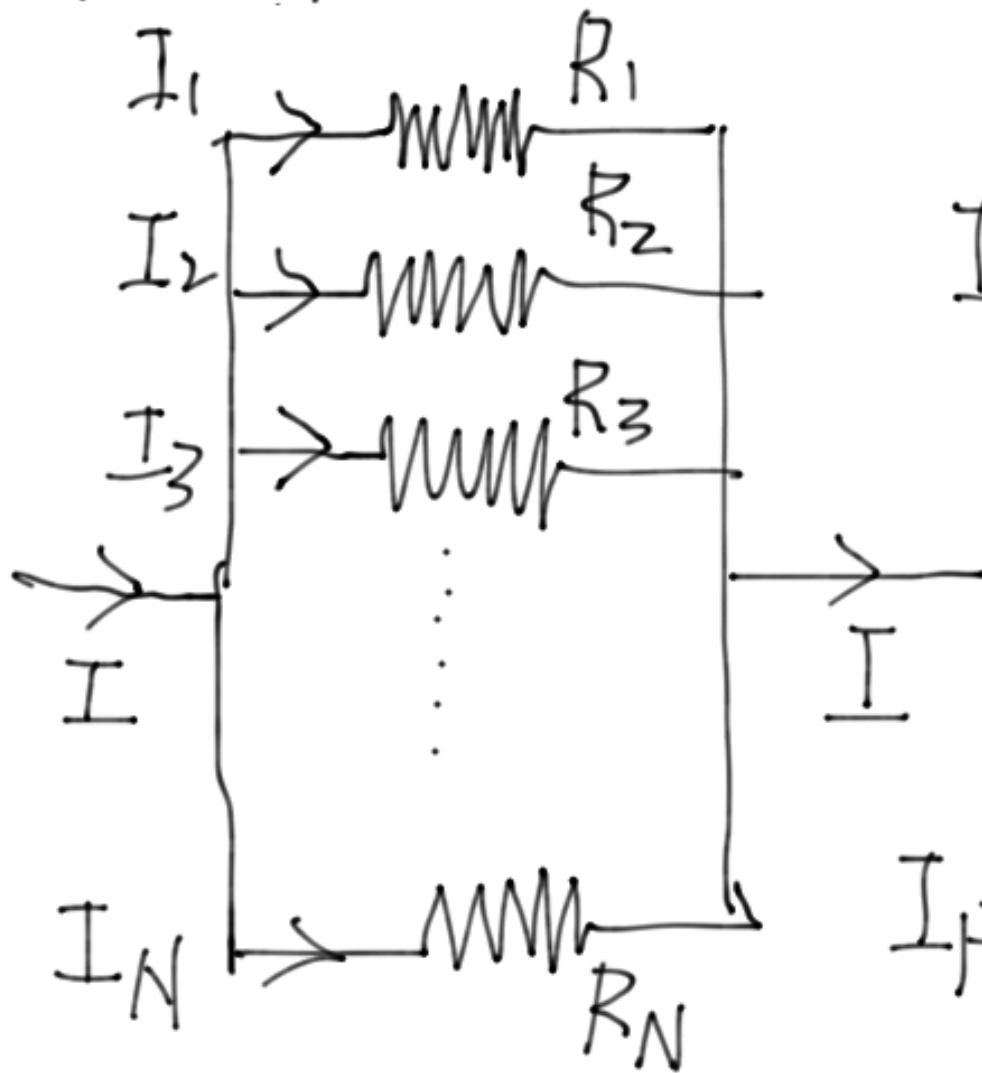

same \sqrt{V} for each R

$$I = I_1 + I_2 + \dots + I_N$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

$$G_{eq} = G_1 + G_2 + \dots + G_N$$

$$I_F = I \cdot \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \dots + \frac{1}{R_N}}$$

$$I_n = I \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \dots + \frac{1}{R_N}}$$

Example

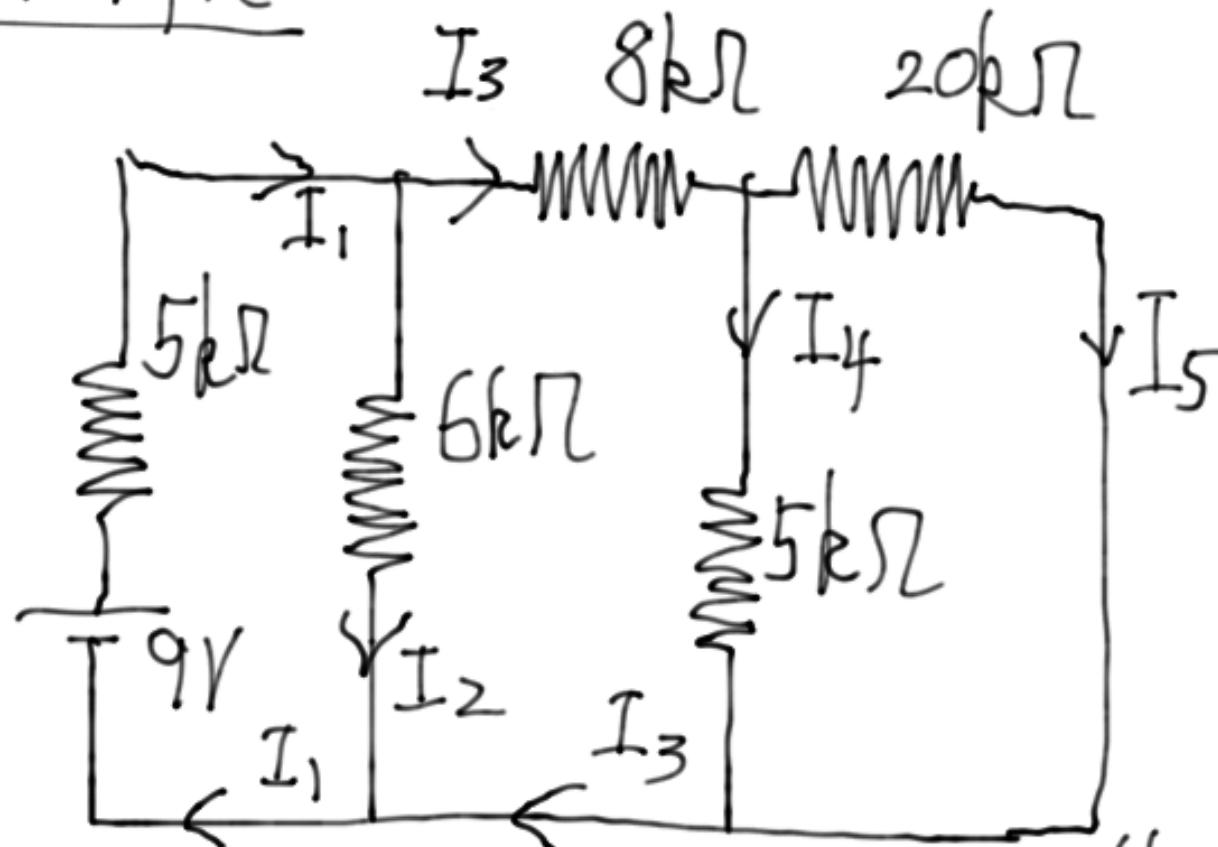


(a) What is the current through battery?

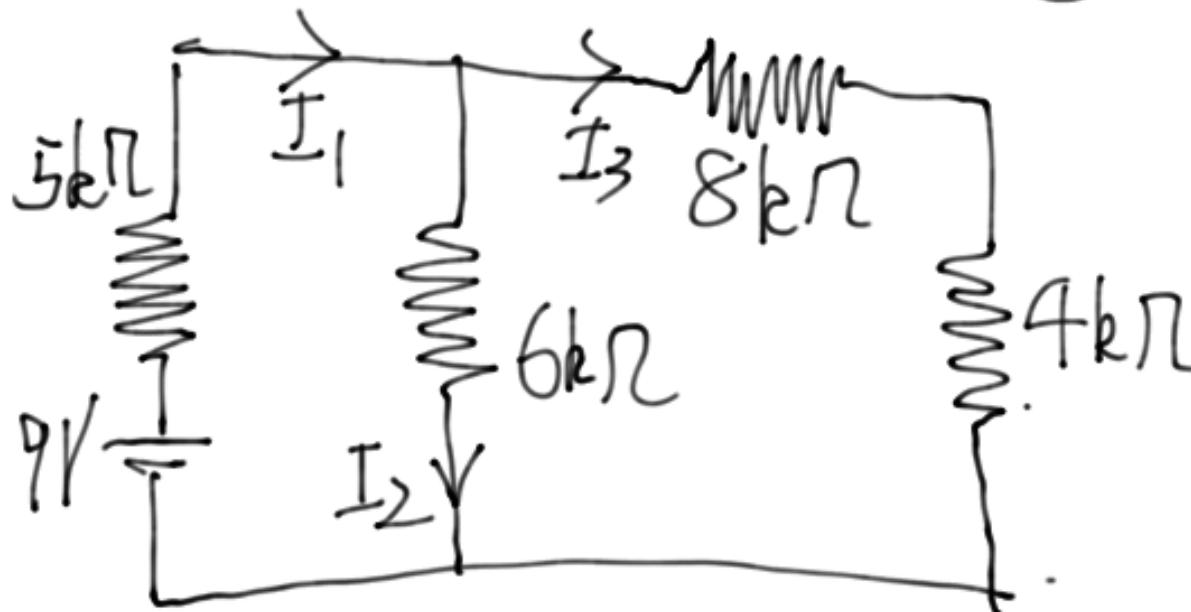
(b) What is the current through each resistor?

First reduce circuit by finding R_{eq} .
Then restore circuit step by step.

$$5k\Omega \parallel 20k\Omega \quad R_{eq} = \frac{5 \times 20}{5+20} = 4k\Omega$$




$$R_{eq} = 8 + 4 = 12k\Omega$$

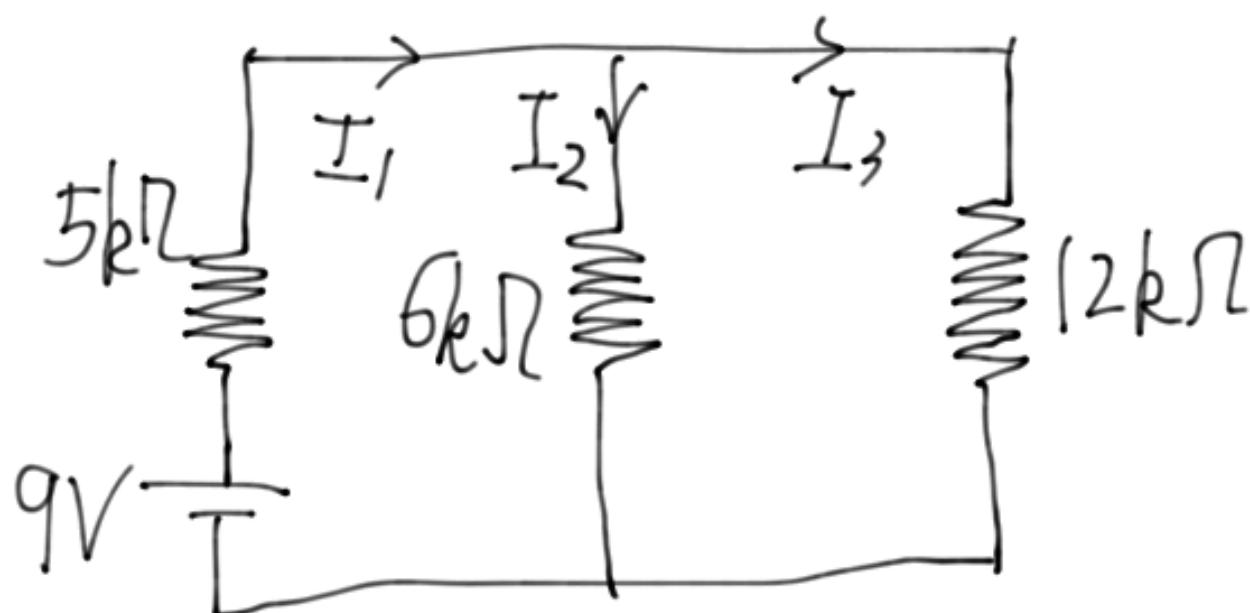


$$6k\Omega \parallel 12k\Omega$$

$$\frac{12 \times 5}{12 + 6}$$

$$= 4k\Omega$$

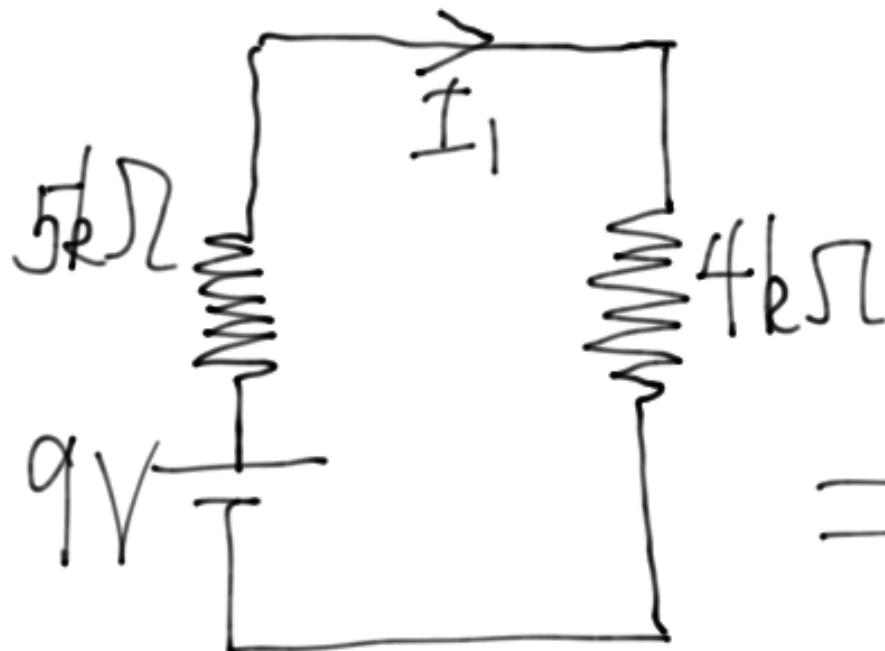


$$5+4=9k\Omega.$$

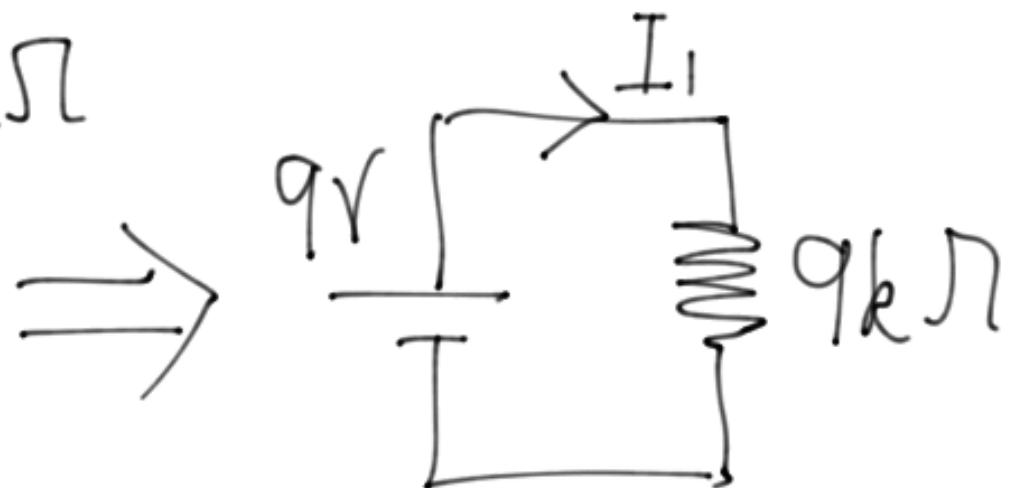

$$I_1 = \frac{9V}{9k\Omega} = 1mA$$


Current through battery

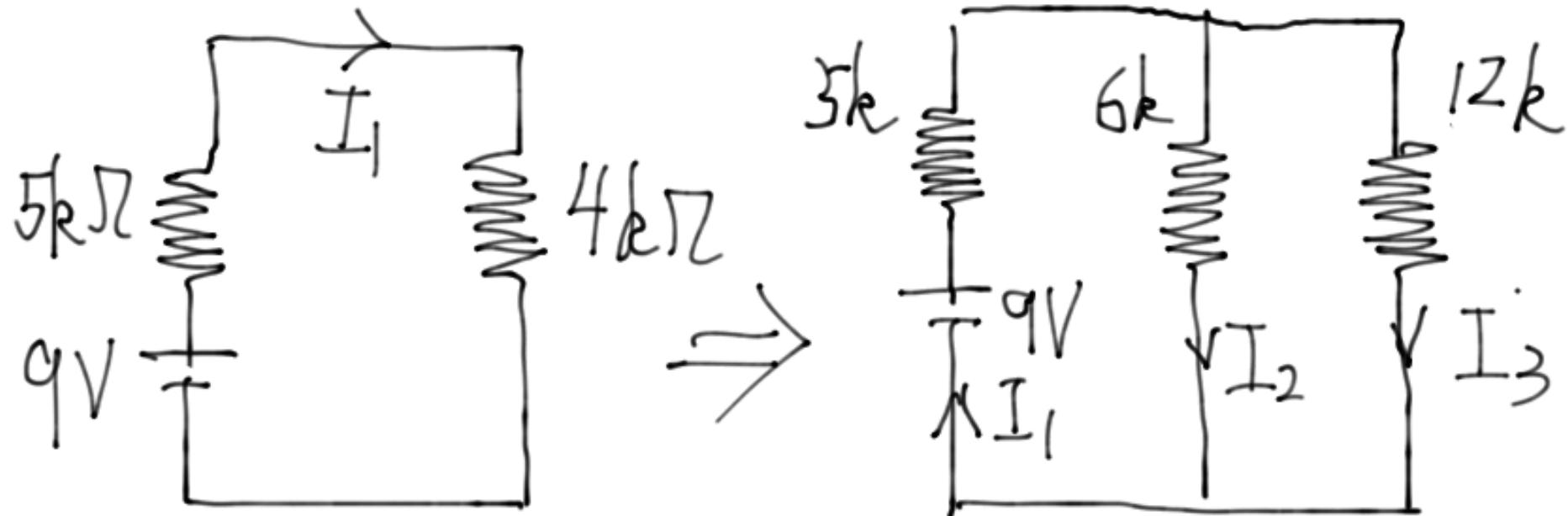Now restore circuit to find current in each resistor.




$$I_2 = I_1 \cdot \frac{1/6}{1/6 + 1/12} = 0.67 \text{ mA}$$
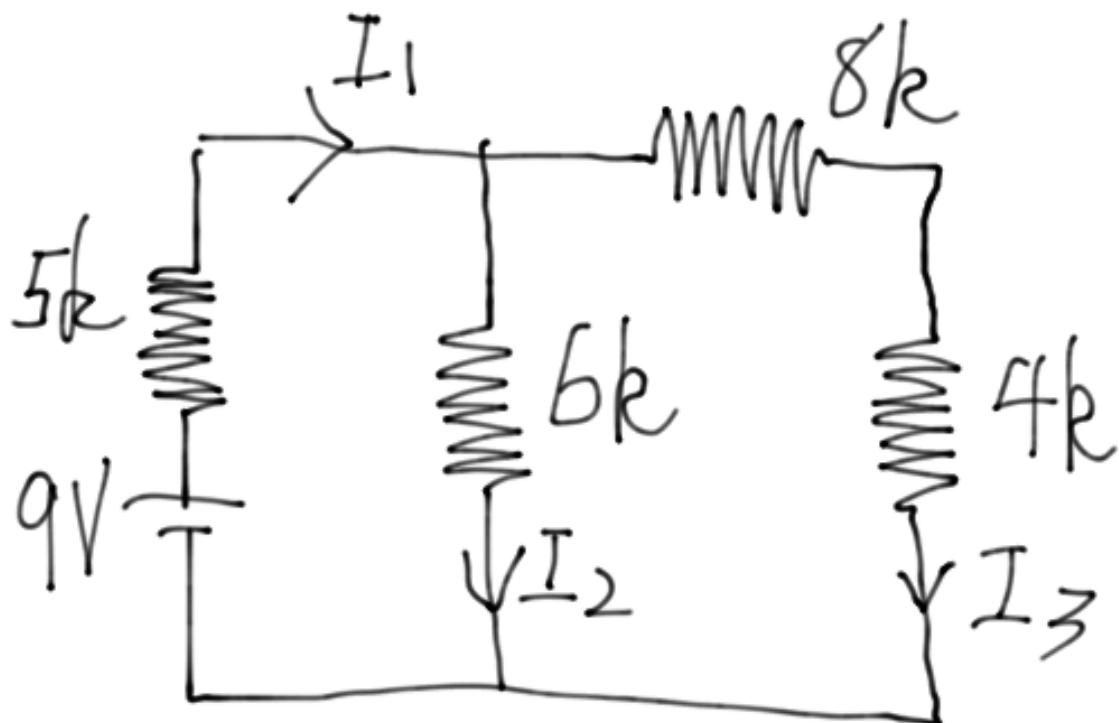
$$I_3 = I_1 \cdot \frac{1/12}{1/6 + 1/12} = 0.33 \text{ mA}$$



$$I_4 = I_3 \cdot \frac{1/5}{1/5 + 1/20}$$

$$= 0.26 \text{ mA}$$

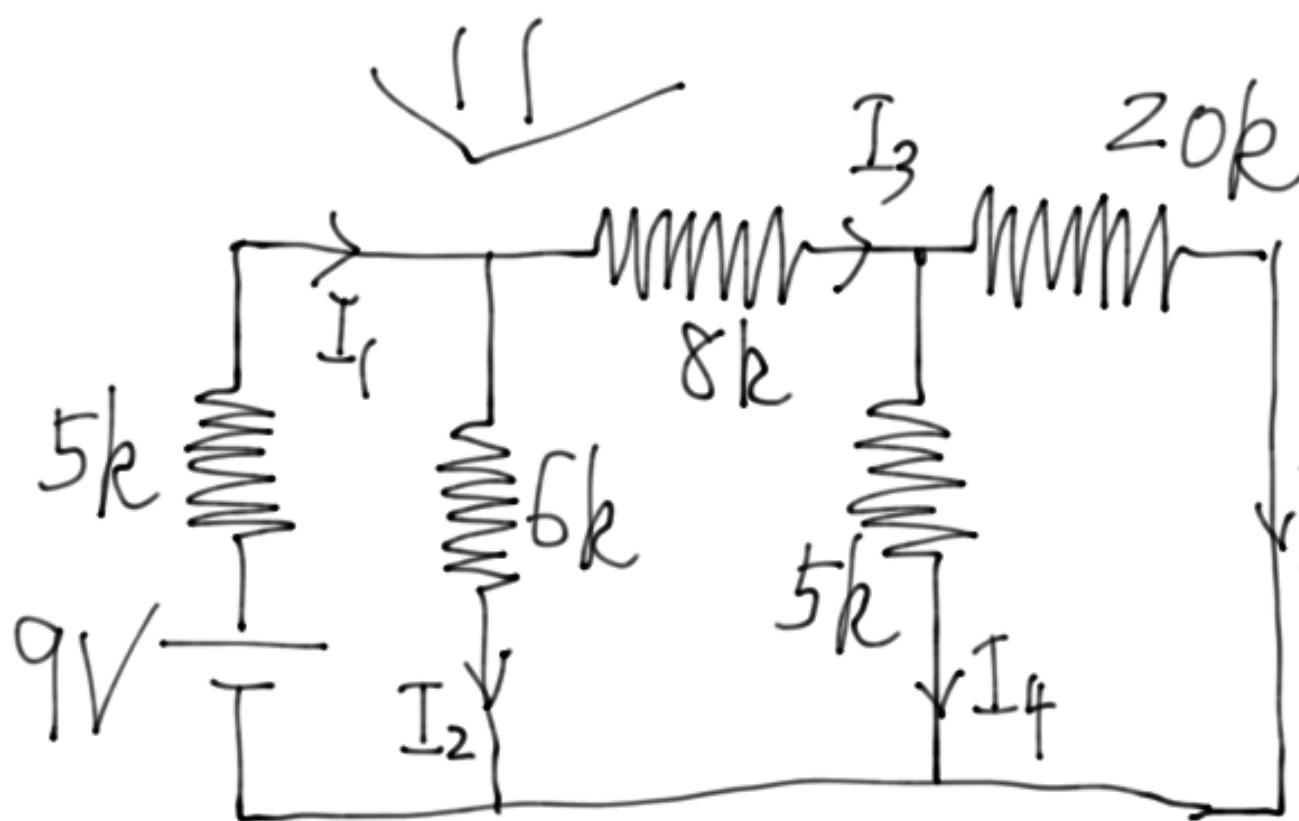


$$I_5 = I_3 - I_4$$

$$\approx 0.33 - 0.26$$

$$I_5 = 0.07 \text{ (mA)}$$

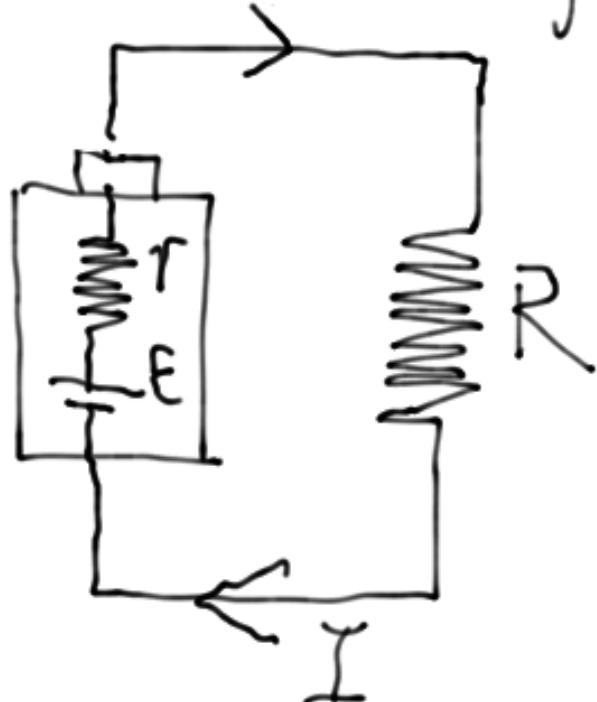* Practical emf, ammeters, and voltmeters



ideal battery : $r=0$
and $I=\frac{\epsilon}{r}$

practical battery:

$r > 0$ internal resistance

Load resistor R and internal resistor r are in series. $I = \frac{\epsilon}{R+r}$

voltage on load resistor (terminal voltage):

$$\Delta V_R = I \cdot R = \left(\frac{\epsilon}{R+r} \right) R$$

$$= \epsilon \cdot \frac{R}{R+r} < \epsilon$$

Load voltage < emf because of r.

Same result can be obtained by voltage divider rule:


$$\Delta V_R = \epsilon \cdot \frac{R}{R+r}$$

Or $\Delta V_R = \epsilon - I_r$

$$= \epsilon - \left(\frac{\epsilon}{R+r} \right) r = \epsilon \cdot \frac{R}{R+r}$$

When $r \ll R$, $\Delta V_R \rightarrow \epsilon$.

Example :

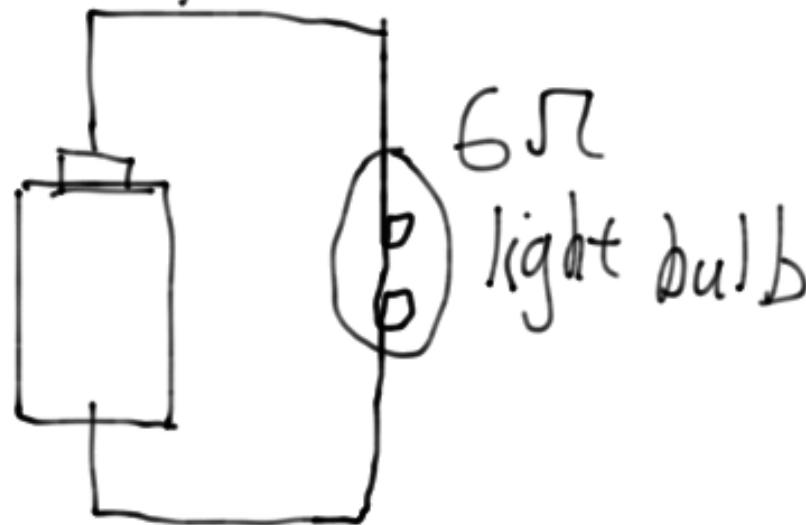

P=? on light bulb?

$\Delta V = ?$

$$\Delta V = \mathcal{E} \cdot \frac{R}{R+r} = 3 \cdot \frac{6}{1+6} = 2.57 \text{ (V)}$$

battery: $\mathcal{E}=3 \text{ V}$


$r=1 \Omega$

$$P = \frac{(\Delta V)^2}{R} = \frac{(2.57)^2}{6} = 1.10 \text{ (W)}$$

Alternative method:

$$I = \frac{\mathcal{E}}{R+r} = \frac{3}{1+6} = 0.428 \text{ (A)}$$
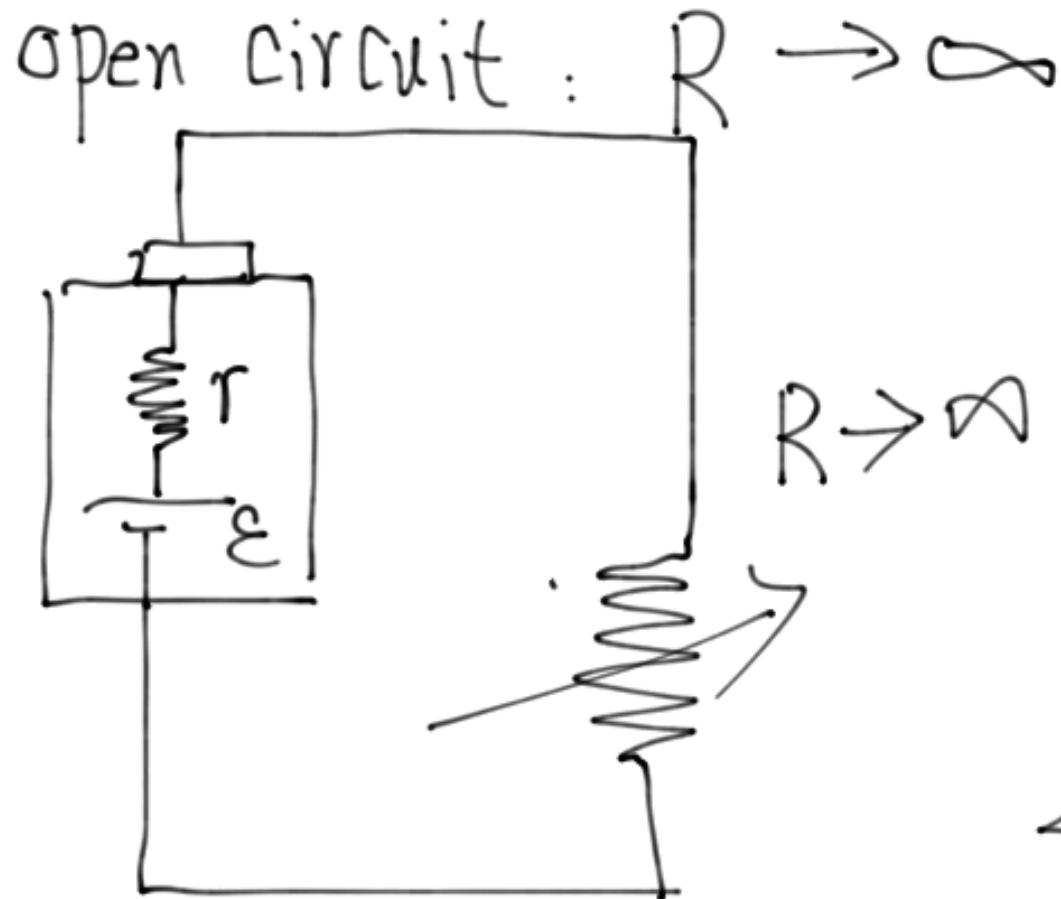
$$\Delta V = IR = 2.57 \text{ (V)} \quad P = I^2 R = 1.10 \text{ (W)}$$




$$\Delta V_R = \epsilon \cdot \frac{R}{R+r} = \epsilon \cdot \frac{1}{1 + \frac{r}{R}}$$

$$\Delta V_R \rightarrow \epsilon$$

For open circuit : $\Delta V_R = \epsilon$

Short circuit :

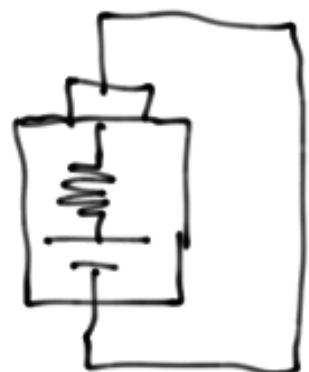

$$\Delta V_R = \epsilon \cdot \frac{1}{1 + \frac{r}{R}} \rightarrow 0$$

all voltage drops on internal resistor.

r is usually small.

For short circuit, current $I = \frac{\epsilon}{r}$ is large.
Power $P = \frac{\epsilon^2}{r}$ is also large.

Consider a short circuited car battery:-

$$\epsilon = 12 \text{ V}, \quad r = 0.02 \Omega$$


$$I = \frac{\epsilon}{r} = \frac{12}{0.02} = 600 \text{ A}$$

$$P = \frac{\epsilon^2}{r} = 7200 \text{ W}$$

Chemical energy rapidly converts to heat.

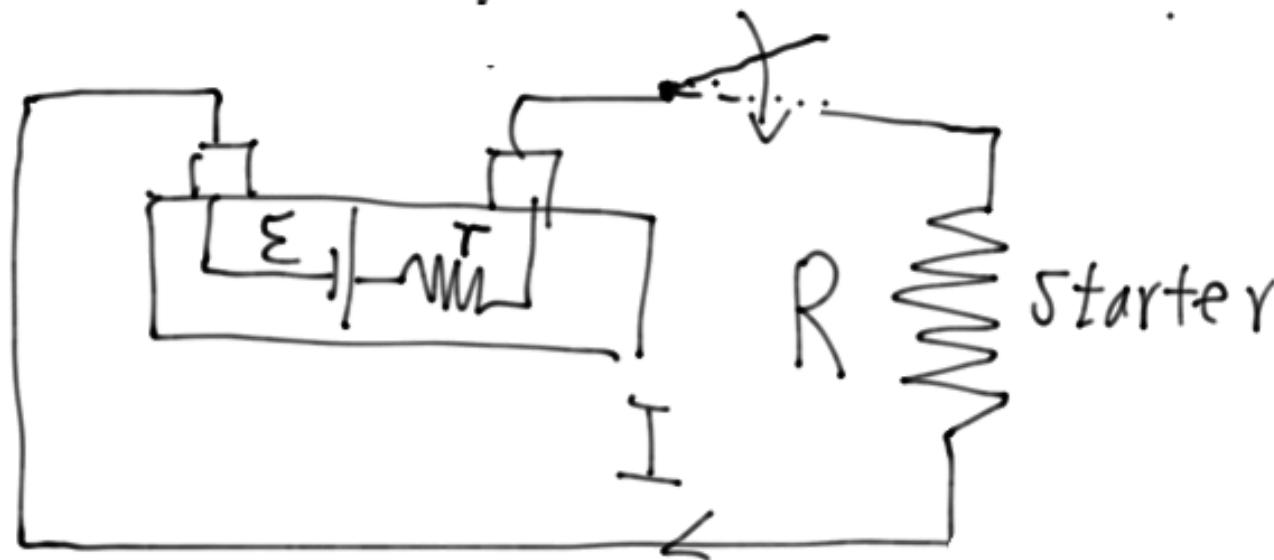Example:

$\epsilon = 12 \text{ V}$ car battery. Starter draws 95 A and terminal voltage drops to 8.4 V . $R = ?$ $r = ?$




$$V_R = \epsilon - Ir, r = \frac{\epsilon - V_R}{I} = \frac{12 - 8.4}{95} = 0.038 \Omega$$

$$R = \frac{V_R}{I} = \frac{8.4}{95} = 0.088 \Omega$$

Is it possible to have terminal Voltage $> \epsilon$?

battery 1

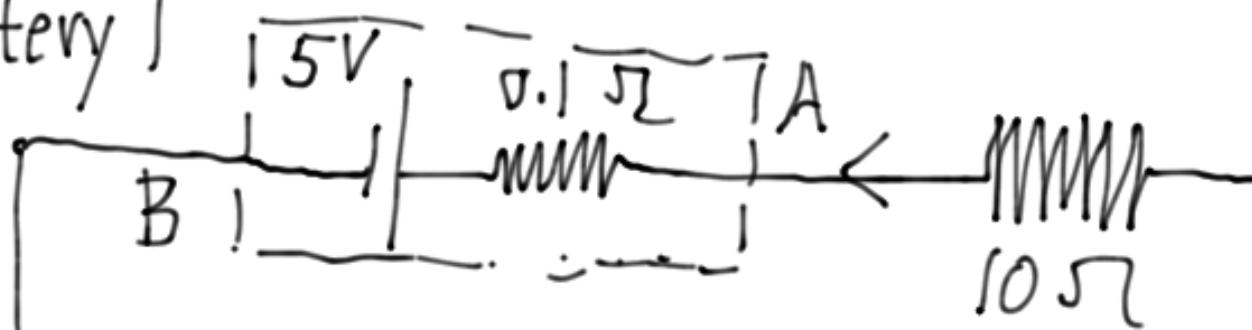


$$I = \frac{10 - 5}{(10 + 0.1 + 0.1)} = 0.5 \text{ A}$$

terminal voltages $\Delta V_1 = V_A - V_B = 5 + 0.5 \times 0.1 = 5.05 \text{ V}$

$$\Delta V_2 = V_C - V_D = 10 - 0.5 \times 0.1 = 9.95 \text{ V} > 10 \text{ V}$$

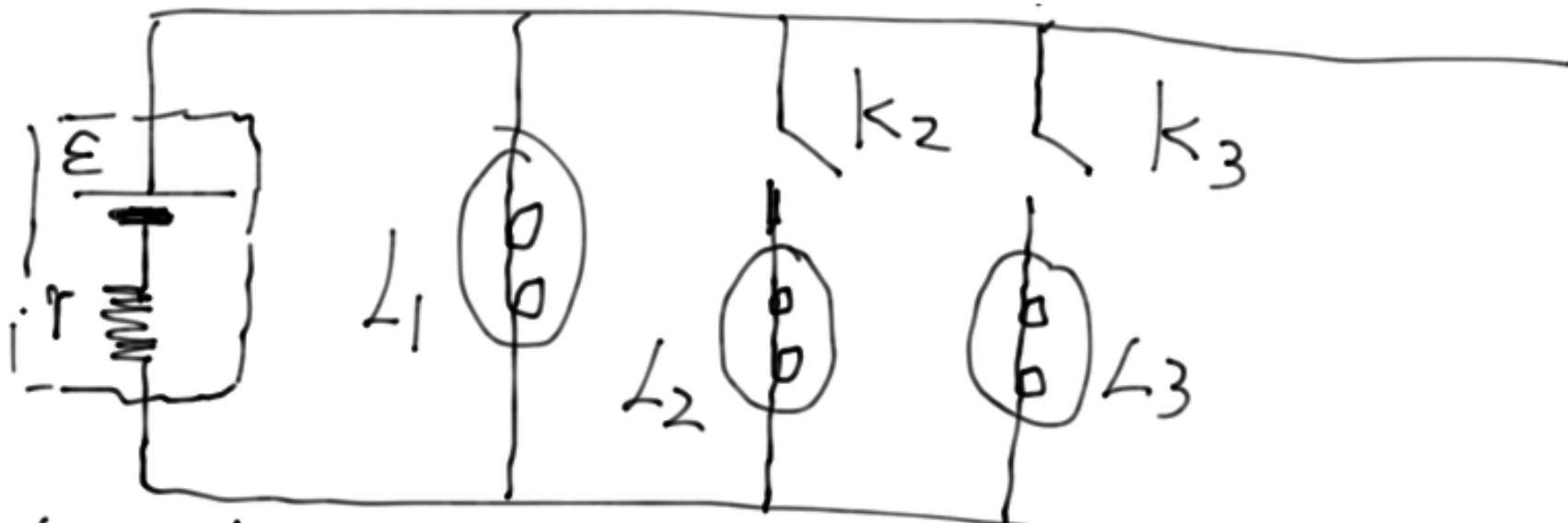Question L_1, L_2, L_3 , identical light bulbs
with resistance R




How does brightness of L_1 changes when k_2 (and then k_3) is closed?

Load voltage $V_L = E \cdot \frac{R_L}{R_L + r} = E \cdot \frac{1}{1 + r/R_L}$
When k_2 closed, $R_L \downarrow V_L \uparrow$, brightness \uparrow
Similar with k_3 .


Ammeter

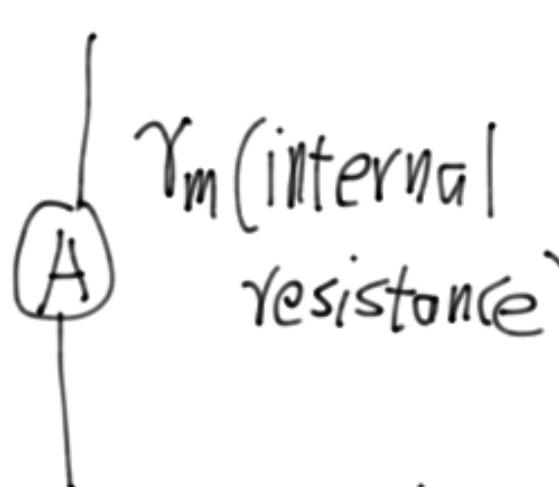- measure current
- put in series
- low internal resistance (compared to load)




r_m (internal
resistance)

A circuit to be measured

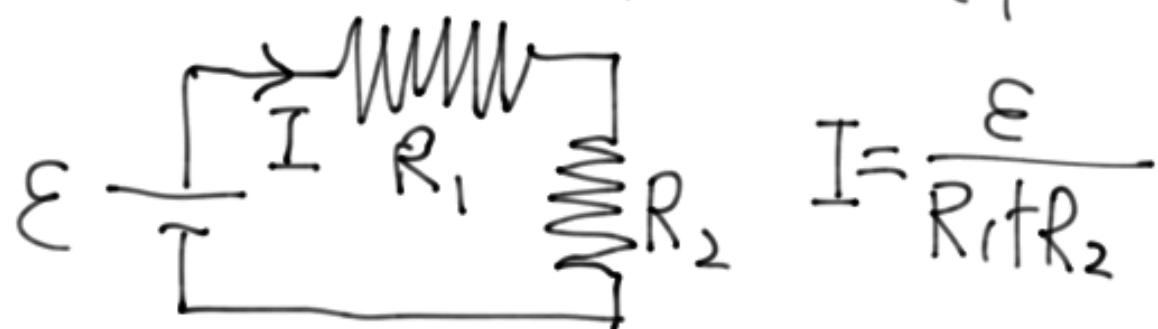

symbol
for
ammeter

insert Ammeter in Series

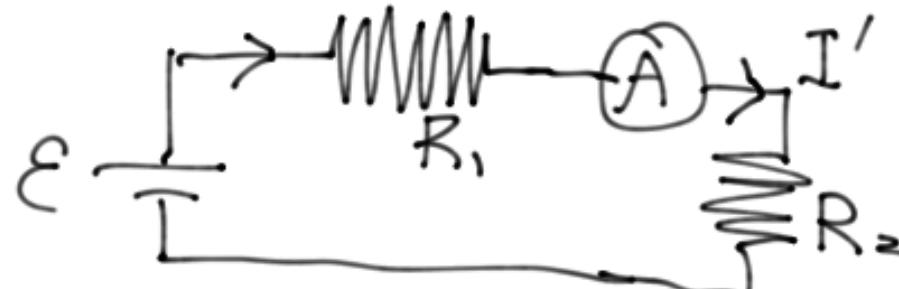

when $r_m \ll R_1, R_2$, $I' \approx I$

$$I' = \frac{\epsilon}{R_1 + R_2 + r_m}$$

Ideal ammeter ✓
 $r_m = 0$

Voltmeter

— Measure voltage

— put in parallel


— Large internal resistance (compared to load)




r_m : internal resistance.

symbol
for
voltmeter

A circuit to be measured

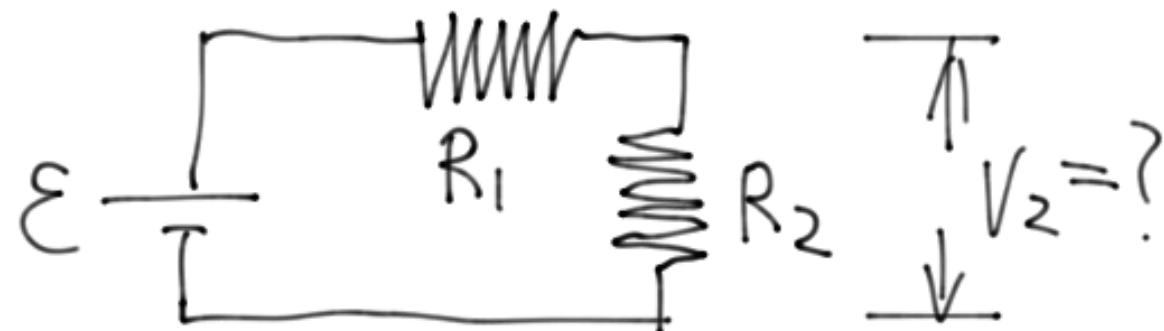

put \textcircled{v} in parallel with R_2

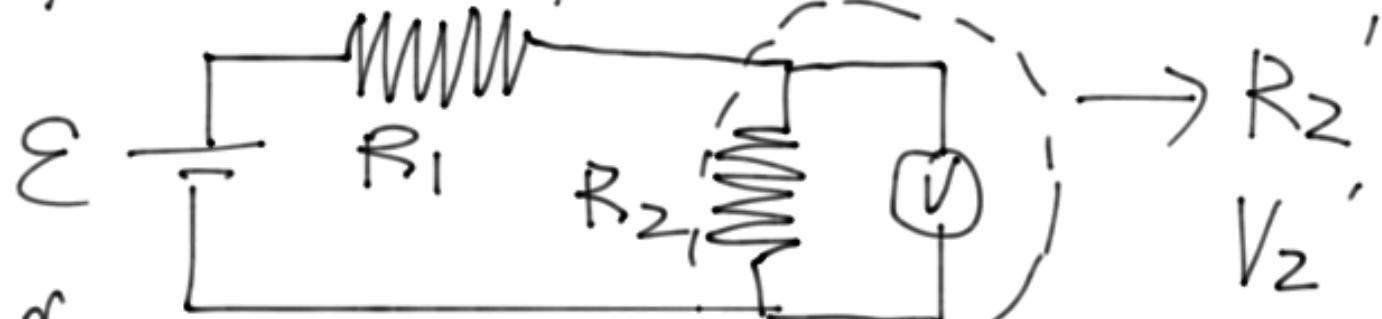

$$R_2' = \frac{R_2 r_m}{R_2 + r_m} = \frac{R_2}{(1 + R_2/r_m)}$$

When $r_m \gg R_2$, $R_2' \approx R_2$, $V_2' \approx V_2$

Expand range of ammeter and voltmeter:

An ammeter has full range of 30mA .

$r_m = 1\text{k}\Omega$. Can you expand range to 10mA ?

Question: Is $1\text{k}\Omega$ too large for ammeter?


Well, compare it to load resistance.

typical load for a circuit with 30mA ,
driven by 3V emf:

$$\frac{3\text{V}}{30\text{mA}} = \frac{3\text{V}}{3 \times 10^{-5}\text{A}} = 10^5\Omega = 100\text{k}\Omega.$$

r_m is much smaller than load: $\gg 1\text{k}\Omega$.

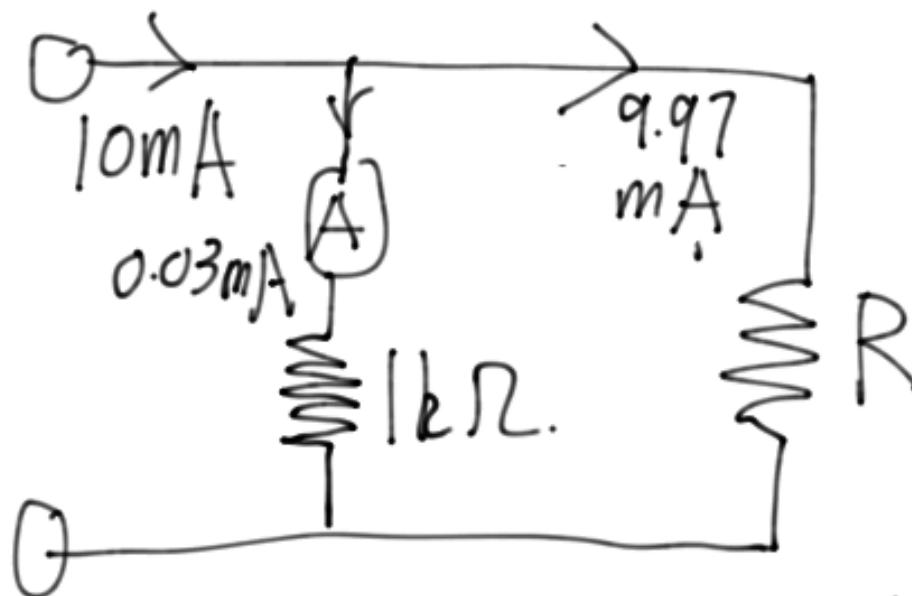How to expand range to 10mA?
use a shunt resistor.



Method. #1

$$(1000\Omega)(0.03mA) = (10mA) \frac{1000R}{100+R}$$
$$I_1 = \frac{1000R}{1000+R}$$
$$R = 3.0\Omega$$

Method 2:

$$10mA \cdot \frac{\frac{1}{1000}}{\frac{1}{1000} + \frac{1}{R}} = 0.03mA$$


Method 3:

$$(9.97mA) R = (0.03mA) 1000\Omega$$

Result: put a 3.0Ω resistor in parallel.

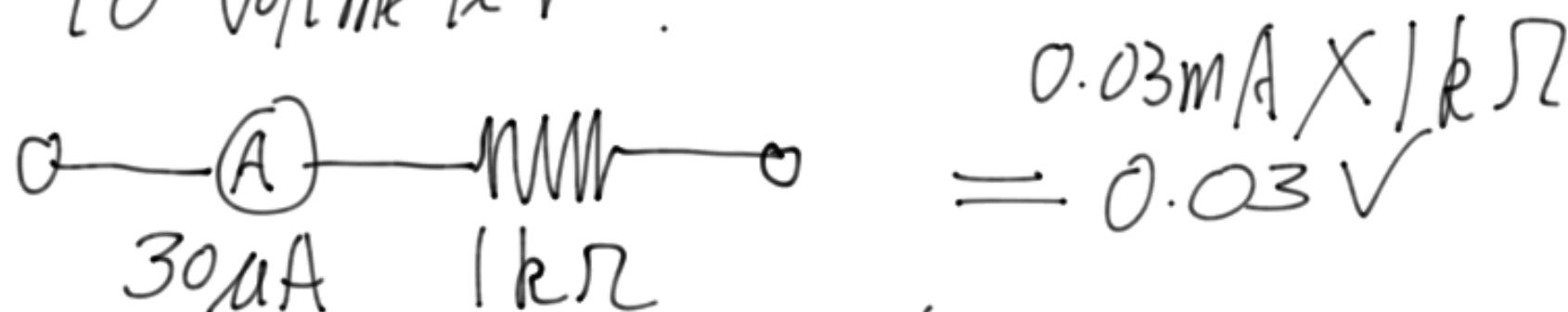Exercise : How to expand range to 100mA?


→ How to convert a ammeter (galvanometer) to Voltmeter ?



original meter can only measure 0.03V.

How to expand range to measure 30V?

put a large resistor in series :

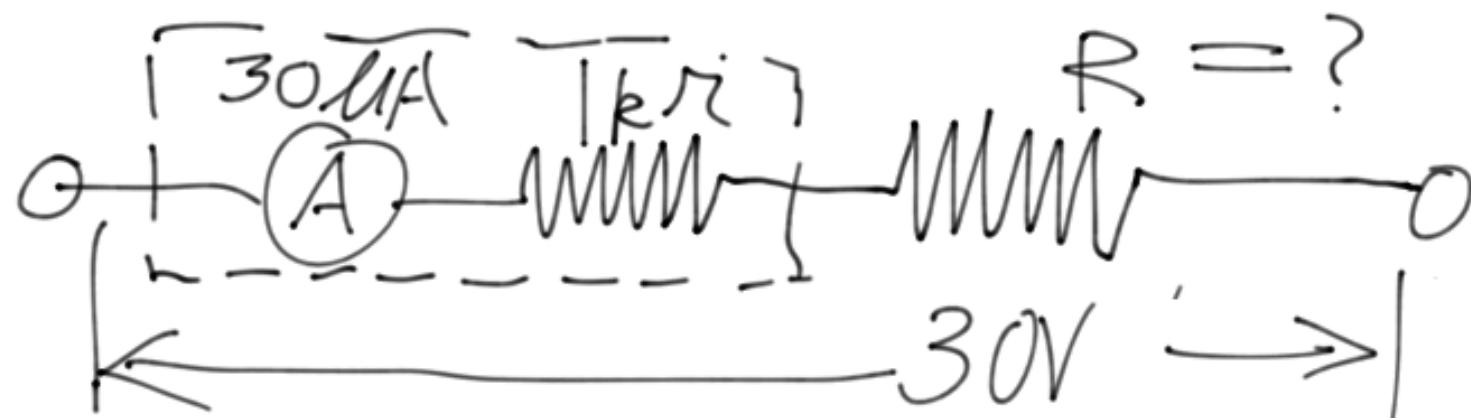

Method #1

$$\frac{30V}{R+1000} = 30\mu A = 3 \times 10^{-5} A$$

$$R = 10^6 \Omega = 1 M\Omega$$


Method. #2

$$30V \cdot \frac{1000}{R+1000} = 0.03V$$

$$R = 1 M\Omega.$$

$$r_m' = r_m + R = 1000 + 10^6 = 10^6 \Omega.$$

* Current sources

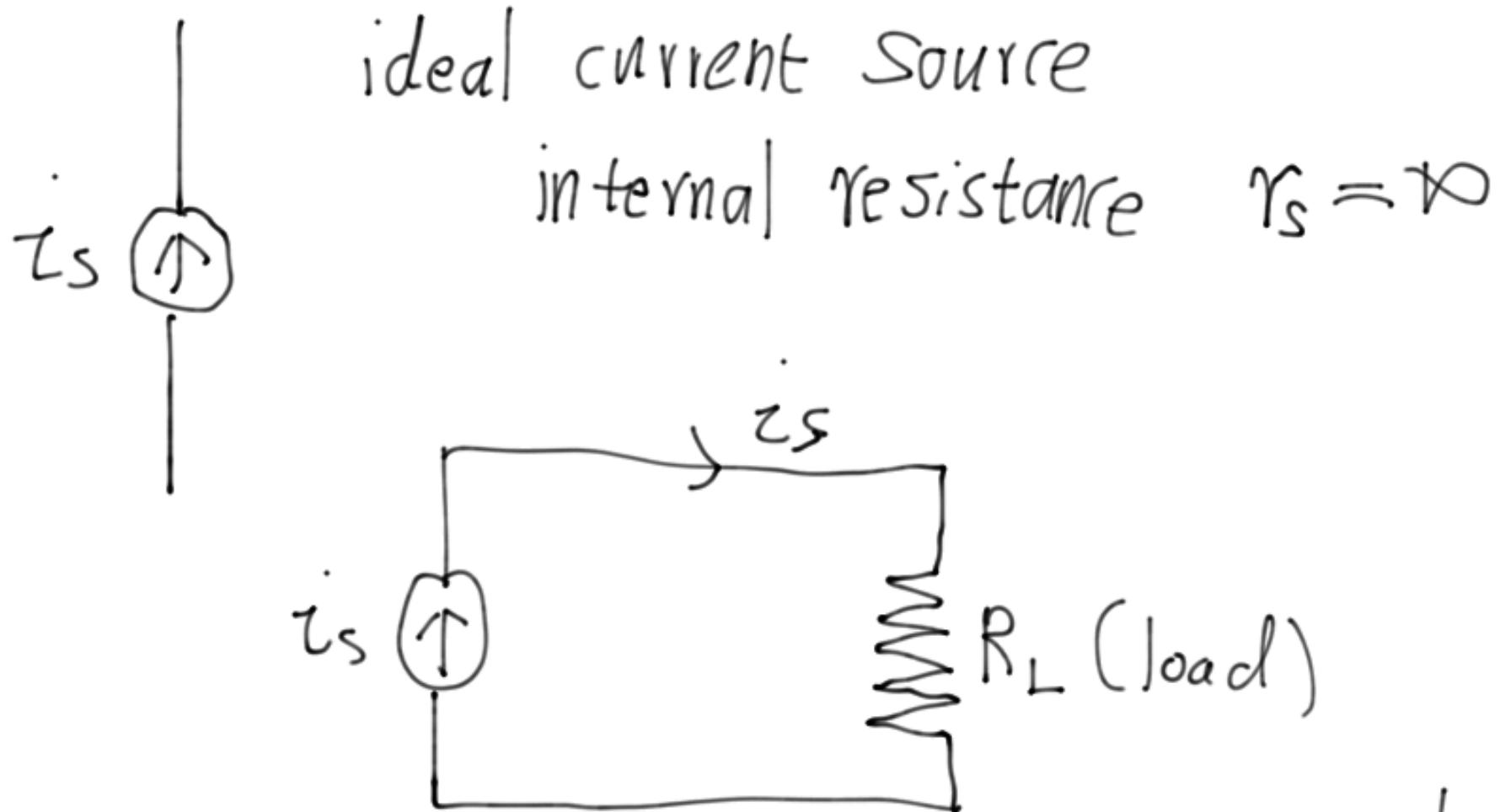

The output current supplied by ideal current source does not depend on load.


Practical current source:

ideal current source in parallel with finite r_s .



$$r_s < \infty$$

When connecting to a load resistor,

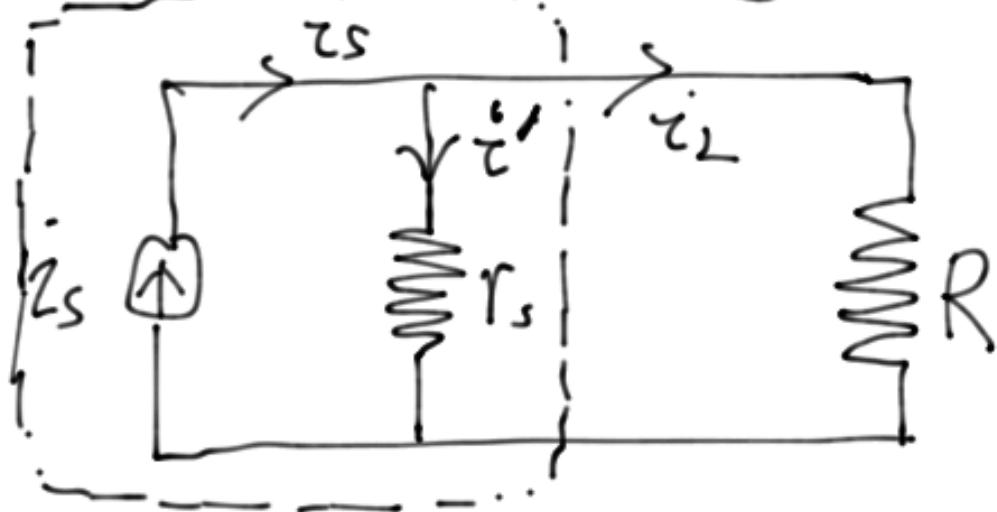

$$r_s // R$$

output current:

$$i_L = z_s \frac{1/R}{1/r_s + 1/R}$$


$$z_L = z_s \cdot \frac{r_s}{R+r_s} = z_s \frac{1}{\left(\frac{R}{r_s} + 1\right)}$$

z_L depends on R_L

When $R \ll r_s$, $z_L \approx z_s$

So a good current source typically has a large internal resistance (compared to load resistance).

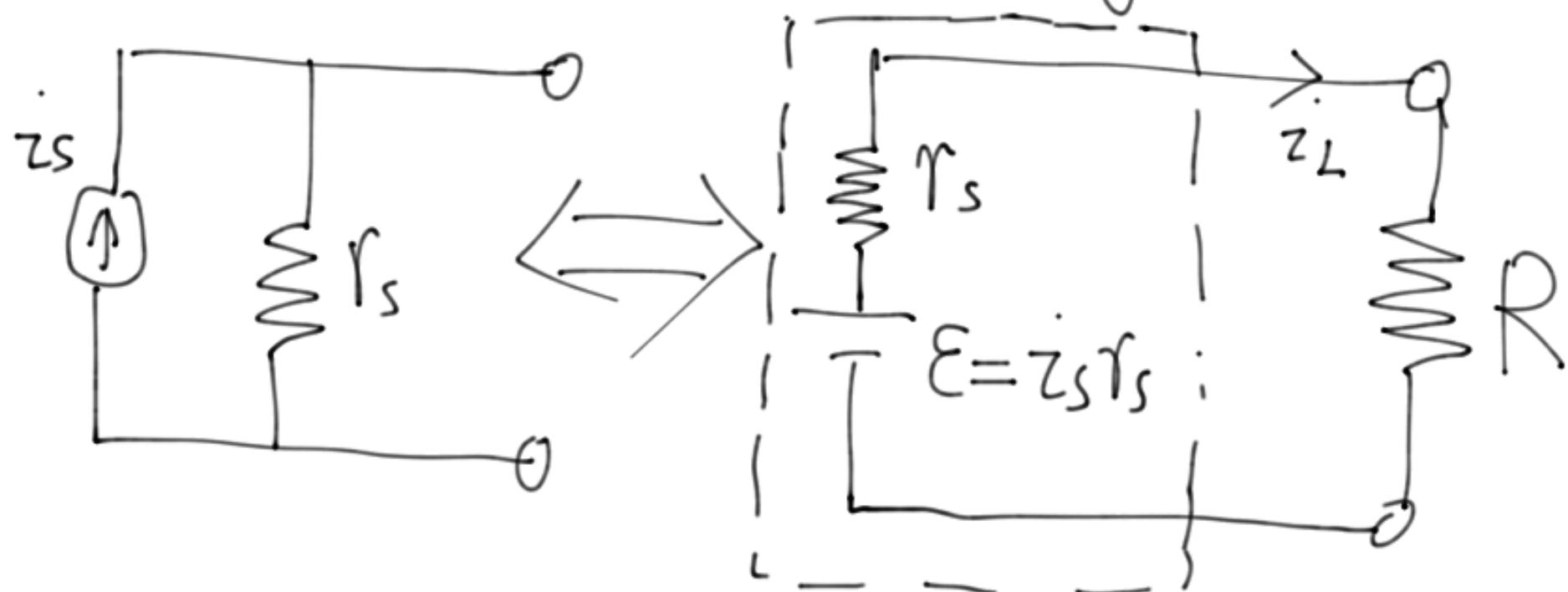Current Source is equivalent to a voltage source in series with a large resistor.




$$i_L = \frac{\epsilon}{r_s + R} = \frac{i_s r_s}{r_s + R} = i_s \cdot \frac{1}{1 + R/r_s}$$

when $r_s \gg R$, $i_L \approx i_s$

Same as i_L for current source.

Recap on sources

ideal voltage source

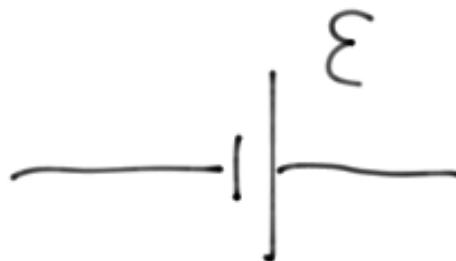


$$r_s = 0$$

ideal Current Source



$$r_s = \infty$$


practical
voltage source

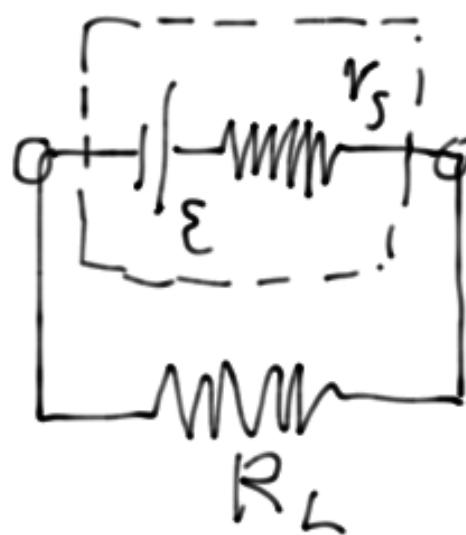

$$r_s > 0$$

$$V_L = \epsilon \cdot \frac{R_L}{r_s + R_L}$$

practical
Current Source:

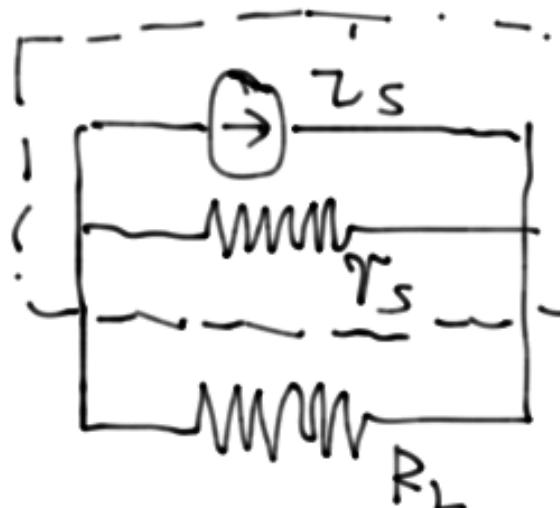

$$r_s < \infty$$


$$i_L = z_s \cdot \frac{r_s}{R_L + r_s}$$

They are equivalent when $\epsilon = z_s \cdot r_s$

* Kirchhoff's laws

Some circuits are too complicated for combination rules.

Two emfs in two branches

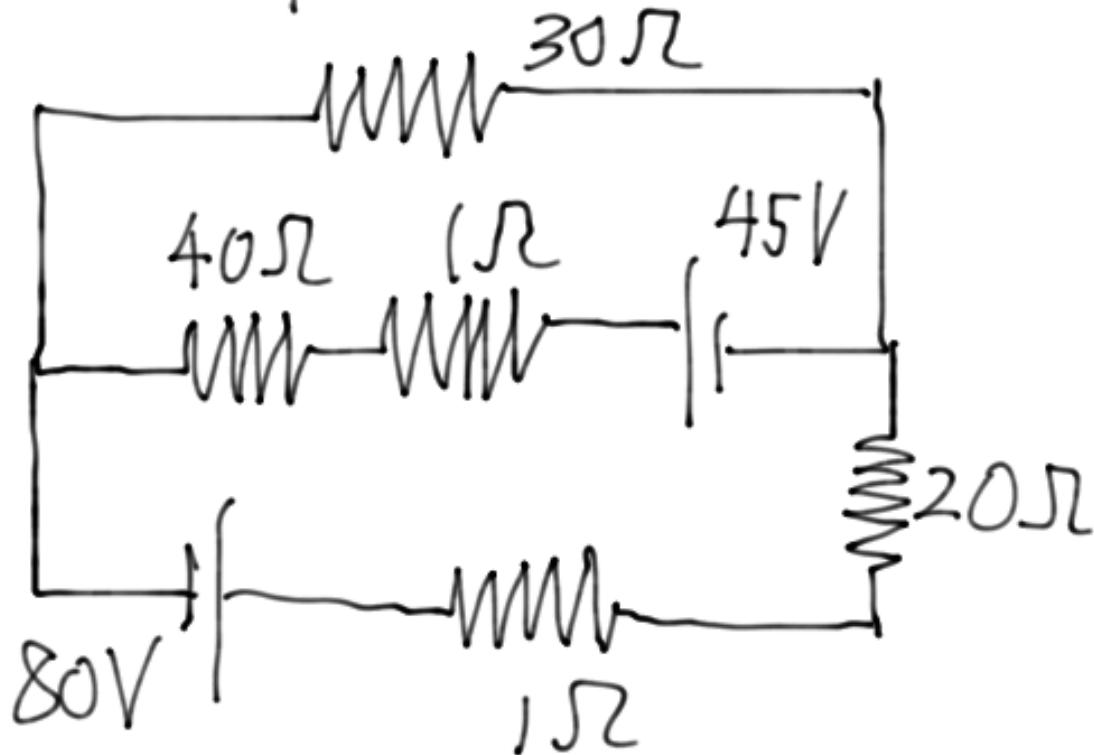

Instead, we use Kirchhoff's laws.

Kirchhoff's current law (KCL)
(junction rule.)

At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving the junction.

Kirchhoff's voltage law (KVL)
(loop rule)

The sum of the changes in potential around any closed loop of a circuit must be zero

KCL is based on charge conservation.

KVL is based on energy conservation.

Approach and solution


1. Label the currents and directions in each branch

Direction: arbitrary.

2. Identify the unknowns: I_1 ,

I_2 , I_3

So need three equations.

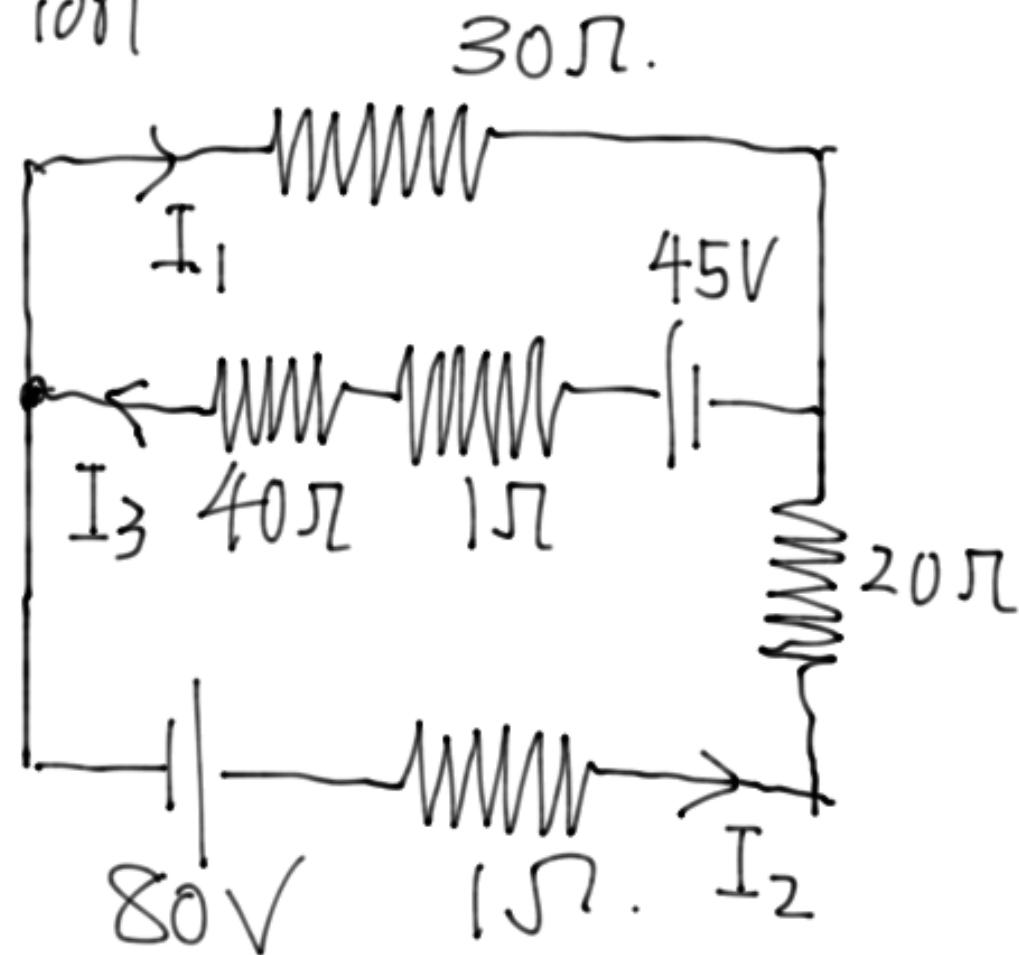

3. KCL

$$I_3 = I_1 + I_2 \quad (1)$$

4. KVL

upper loop cw $\sum \Delta V = 0$

$$-30I_1 + 45 - I_1 I_3 - 40I_3 = 0$$

$$-30I_1 + 45 - 41I_3 = 0 \quad (2)$$

lower loop cw

$$+40I_3 + I_3 - 45 + 20I_2 + I_2 - 80 = 0$$

$$21I_2 + 41I_3 - 125 = 0 \quad (3)$$

Substitute (1) into (2) and (3)

$$71I_1 + 41I_2 = 45 \quad \leftarrow$$

$$41I_1 + 62I_2 = 125 \Rightarrow I_2 = 2.02 - 0.66I_1$$

$$I_1 = -0.86 \text{ (A)}$$

↳ negative sign, I_1 is opposite to assumed direction.

$$I_2 = 2.59 \text{ (A)} \quad I_3 = 1.73 \text{ (A)}$$

Note :

you can choose the outer loop instead.
of the lower loop for Eq. (3)


outer loop, (cw)

$$-30I_1 + 20I_2 + I_2 - 80 = 0$$

$$-30I_1 + 21I_2 - 80 = 0 \quad (3')$$

Solve (1), (2), (3') for I_1, I_2, I_3 .

Example

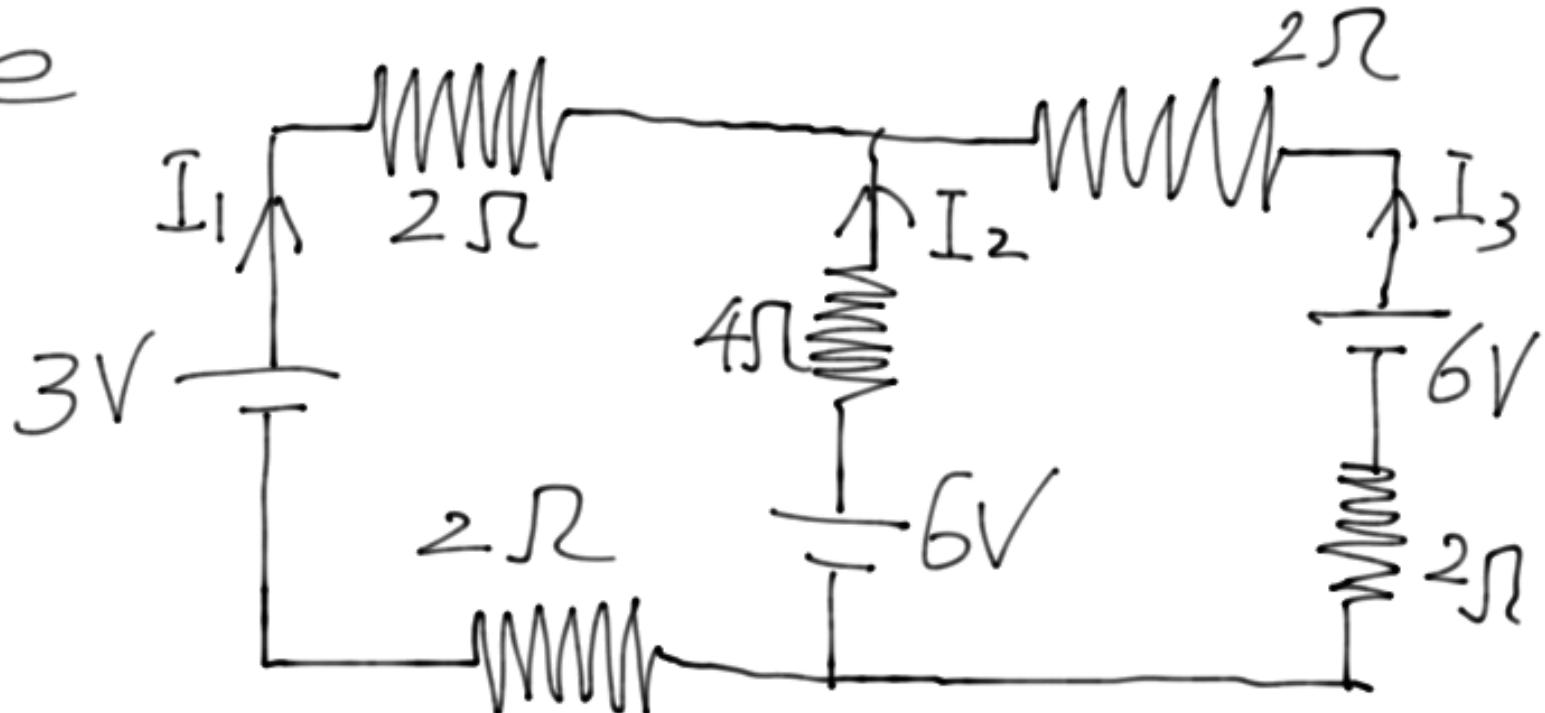

$$I_1 + I_2 + I_3 = 0 \quad (1)$$

left loop CW $3 - 2I_1 + 4I_2 - 6 - 2I_1 = 0$

$$4I_1 - 4I_2 + 3 = 0 \quad (2)$$

right loop CW $6 - 4I_2 + 2I_3 - 6 + 2I_3 = 0$

$$I_1 = -0.5 \text{ A} \quad I_2 = I_3 = 0.25 \text{ A} \quad (3)$$

* Mesh analysis

In Kirchhoff's laws,
we use branch currents
as variables.

3 variables.

3 equations.



$$I_1 + I_2 + I_3 = 0$$

Define mesh currents
 i_1 and i_2

$$I_1 = i_1$$

$$I_3 = -i_2$$

$$I_2 = i_2 - i_1$$

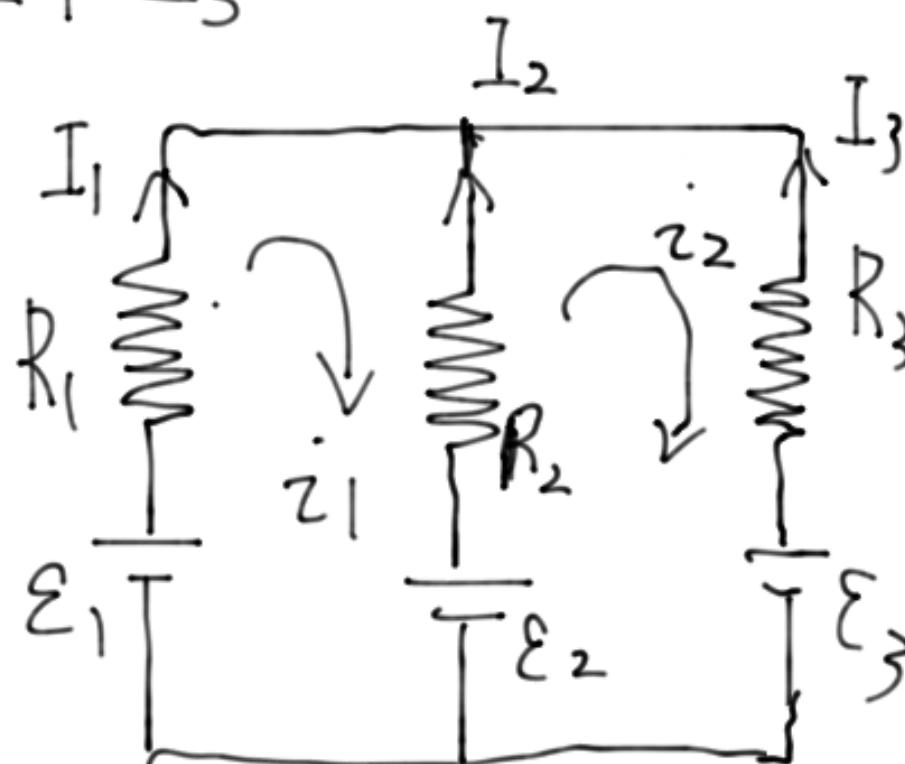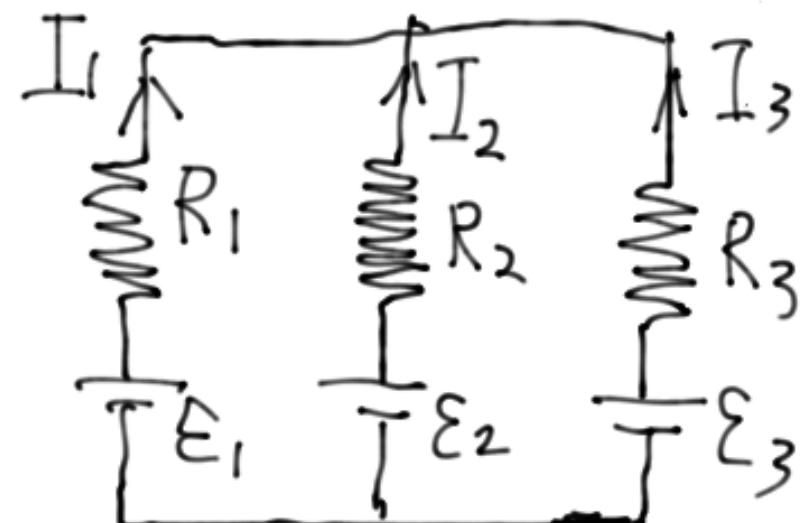

$$I_1 + I_2 + I_3 = z_1 + (-z_2) + (z_2 - z_1) = 0$$

By defining mesh currents z_1' and z_2 , KCL is automatically satisfied.

Loop equations (KVL)

left mesh: $\mathcal{E}_1 - I_1 R_1 + I_2 R_2 - \mathcal{E}_2 = 0$

$$\mathcal{E}_1 - z_1' R_1 + (z_2 - z_1') R_2 - \mathcal{E}_2 = 0$$

$$z_1'(R_1 + R_2) - z_2 R_2 = \mathcal{E}_1 - \mathcal{E}_2 \quad (1)$$

Right mesh: $-R_2 z_1 + (R_2 + R_3) z_2 = \mathcal{E}_2 - \mathcal{E}_3 \quad (2)$

Similarly 2 equations, 2 variables