

## FET EQUATION SHEET

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2 = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2 \text{ (nMOS)}, \quad I_D = \frac{1}{2} k'_p \frac{W}{L} (v_{GS1} - V_t)^2 = \frac{1}{2} k'_p \frac{W}{L} V_{OV}^2 \text{ (pMOS)}$$

$$g_m = \frac{I_D}{V_{OV}/2} = \frac{2I_D}{V_{OV}}; \quad r_o = \frac{|V_A|}{I_D}$$

### The NMOS differential pair

$$v_{id} = v_{G1} - v_{G2}$$


$$i_{D1} = \frac{I}{2} + \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right) \sqrt{1 - \left( \frac{v_{id}/2}{V_{OV}} \right)^2} \approx \frac{I}{2} + \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right)$$

$$i_{D2} = \frac{I}{2} - \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right) \sqrt{1 - \left( \frac{v_{id}/2}{V_{OV}} \right)^2} \approx \frac{I}{2} - \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right)$$

$$V_{CM \max} = V_t + V_D = V_t + V_{DD} - \frac{I}{2} R_D$$

$$V_{CM \min} = -V_{SS} + V_{CS} + V_{GS}$$
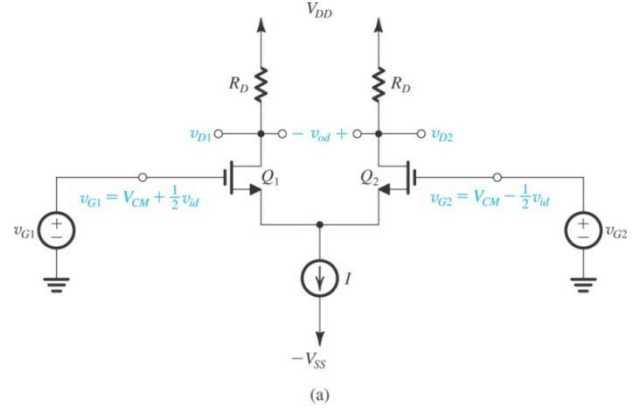
$$A_d \equiv \frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = g_m (R_D \parallel r_o)$$



$$\text{Input offset voltage due to differences in load resistances: } V_{OS} = \frac{V_O}{A_d} = \left( \frac{V_{OV}}{2} \right) \left( \frac{\Delta R_D}{R_D} \right)$$

$$\text{Input offset voltage due to differences in device dimensions: } V_{OS} = \left( \frac{V_{OV}}{2} \right) \left( \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\text{Input offset voltage due to differences in threshold voltage: } V_{OS} = \Delta V_t$$

$$\text{RMS, or typical, total input offset voltage: } V_{OS} = \sqrt{\left( \frac{V_{OV}}{2} \frac{\Delta R_D}{R_D} \right)^2 + \left( \frac{V_{OV}}{2} \frac{\Delta(W/L)}{(W/L)} \right)^2 + (\Delta V_t)^2}$$

### The active loaded NMOS differential pair


$$G_m \equiv \frac{i_o}{v_{id}} = g_{m1,2}$$

$$R_o \equiv \frac{v_x}{i_x} = r_{o2} \parallel r_{o4}$$

$$A_d \equiv \frac{v_{od}}{v_{id}} = G_m R_o = g_m (r_{o2} \parallel r_{o4})$$

$$A_{cm} \equiv \frac{v_{od}}{v_{icm}} \approx -\frac{1}{2g_{m3}R_{SS}}$$

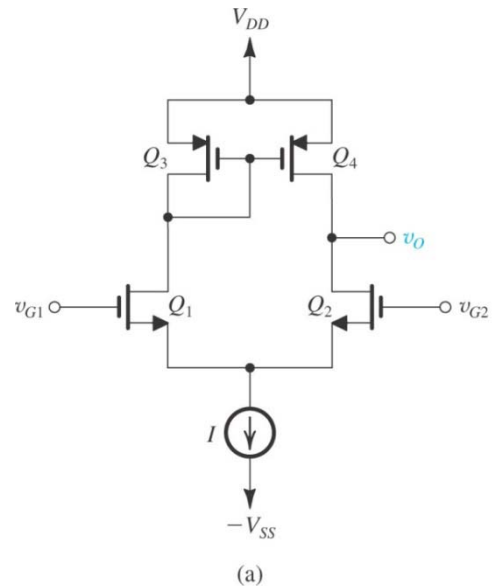where  $R_{SS}$  is the output resistance of the current source



## BJT EQUATION SHEET

$$I_C = I_S e^{v_{BE}/V_T} ; \alpha = \beta/(\beta+1) ; \quad I_C = \alpha I_E ; \quad v_{BE2} = v_{BE1} + V_T \ln \left( \frac{i_{C2}}{i_{C1}} \right)$$

$$g_m = \frac{I_C}{V_T} ; \quad r_\pi = \frac{\beta}{g_m} ; \quad r_e = \frac{V_T}{I_E} ; \quad r_o = \frac{V_A}{I_C}$$

### The basic BJT differential-pair configuration

$$v_{id} = v_{B1} - v_{B2}$$


$$i_{E1} = \frac{I}{1 + e^{-v_{id}/V_T}}$$

$$i_{E2} = \frac{I}{1 + e^{v_{id}/V_T}}$$

$$V_{CMmax} \approx V_C + 0.4 = V_{CC} - \alpha \frac{I}{2} R_C + 0.4$$

$$V_{CMmin} = -V_{EE} + V_{CS} + V_{BE}$$
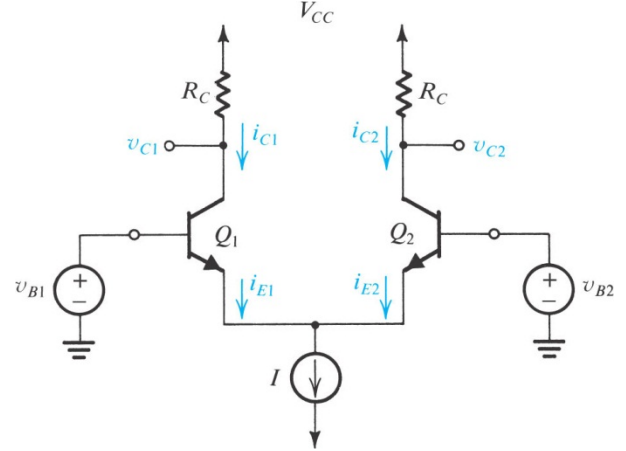
$$A_d \equiv \frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = g_m (R_C \parallel r_o)$$



Input offset voltage due to differences in load resistances:  $V_{OS} = \frac{V_O}{A_d} = V_T \left( \frac{\Delta R_D}{R_D} \right)$

Input offset voltage due to differences in device dimensions:  $V_{OS} = V_T \left( \frac{\Delta I_S}{I_S} \right)$

RMS, or typical, total input offset voltage:  $V_{OS} = V_T \sqrt{\left( \frac{\Delta R_C}{R_C} \right)^2 + \left( \frac{\Delta I_S}{I_S} \right)^2}$

Input offset current:  $I_{OS} = \frac{I}{2(\beta+1)} \left( \frac{\Delta \beta}{\beta} \right) = I_B \left( \frac{\Delta \beta}{\beta} \right)$

### The active loaded PNP differential pair

$$G_m \equiv \frac{i_o}{v_{id}} = g_m$$

$$R_o \equiv \frac{v_x}{i_x} = r_{o2} \parallel r_{o4}$$

$$A_d \equiv \frac{v_{od}}{v_{id}} = G_m R_o = g_m (r_{o2} \parallel r_{o4})$$

$$A_{cm} \equiv \frac{v_{od}}{v_{icm}} \simeq -\frac{r_{o4}}{\beta_3 R_{EE}}$$

where  $R_{EE}$  is the output resistance of the current source

