



Homework #3

Problems 2.2, 2.8, 2.10, 2.44, and
2.49

Problem 2.2

The circuit of Fig. P2.2 uses an op amp that is ideal except for having a finite gain A . Measurements indicate $v_o = 4.0$ V when $v_I = 1.0$ V. What is the op-amp gain A ?

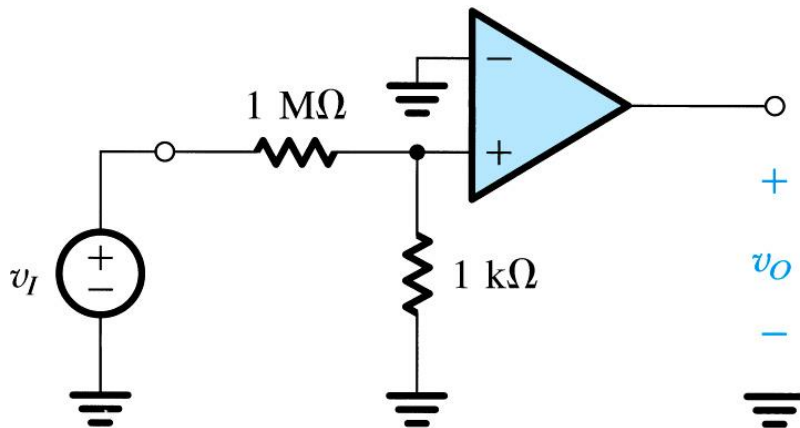


Figure P2.2

$$v_o = Av_+$$

$$v_+ = v_I \frac{1k}{1k + 1M} = \frac{v_I}{1001}$$


$$\frac{v_o}{v_I} = \frac{4V}{1V} = \frac{A}{1001}$$

$$A = 4004V/V$$




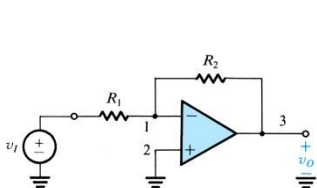Problem 2.8


Assuming ideal op amps, find the voltage gain v_o/v_I and input resistance R_{in} of each of the circuits in Fig. P2.8.




$$\frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

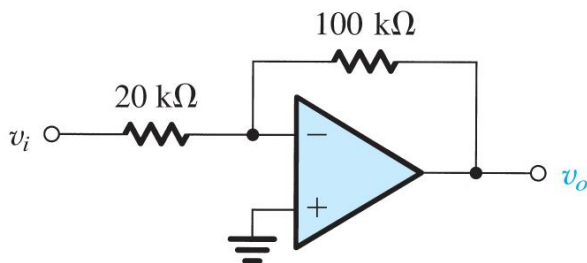

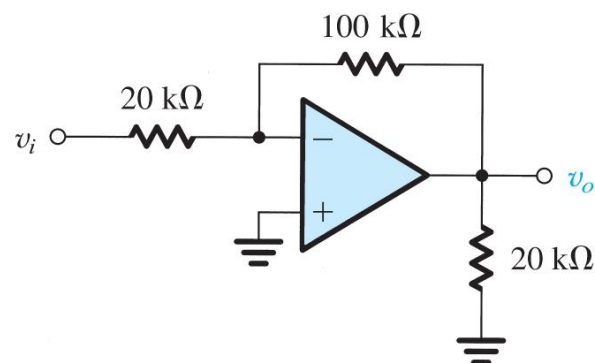
$$\frac{v_o}{v_I} = -\frac{100k}{20k} = -5V/V, R_{in} = 20k\Omega \quad \text{(a)}$$


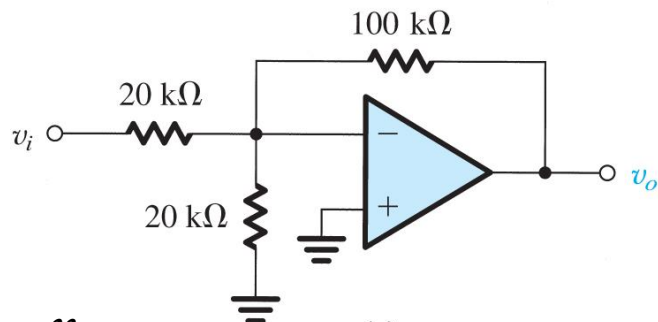
$$\frac{v_o}{v_I} = -5V/V, R_{in} = 20k\Omega \quad \text{(b)}$$


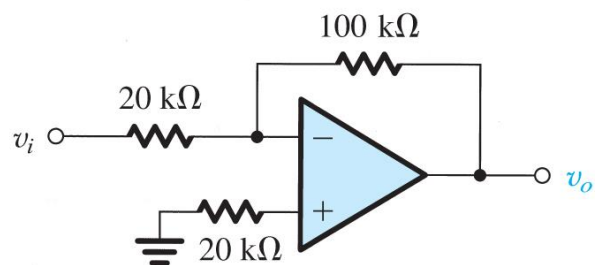
$$\frac{v_o}{v_I} = -5V/V, R_{in} = 20k\Omega \quad \text{(c)}$$




$$\frac{v_o}{v_I} = -5V/V, R_{in} = 20k\Omega \quad \text{(d)}$$

Figure P2.8

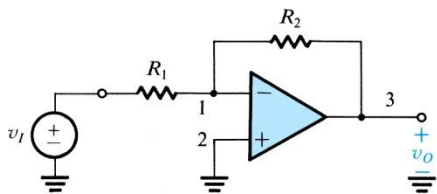Problem 2.10

You are provided with an ideal op amp and three 10-k Ω resistors. Using series and parallel resistor combinations, how many different inverting-amplifier circuit topologies are possible? What is the largest (noninfinite) available voltage gain? What is the smallest (nonzero) available gain? What are the input resistances in these two cases?




$$\frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

R_1	R_2	v_o/v_i	R_{in}
10k Ω	20k Ω	-2 V/V	10k Ω
10k Ω	5k Ω	-0.5 V/V	10k Ω
20k Ω	10k Ω	-0.5 V/V	20k Ω
5k Ω	10k Ω	-2 V/V	5k Ω

Problem 2.44

Given an ideal op amp to implement designs for the following closed-loop gains, what values of resistors (R_1, R_2) should be used? Where possible, use at least one 10-k Ω resistor as the smallest resistor in your design.

- | | |
|--------------|-------------------------------------------------------------------------------|
| (a) +1 V/V | $R_2 = 0 \text{ k}\Omega, R_1 = 10 \text{ k}\Omega \text{ or } \infty \Omega$ |
| (b) +2 V/V | $R_2 = 10 \text{ k}\Omega, R_1 = 10 \text{ k}\Omega$ |
| (c) +21 V/V | $R_2 = 200 \text{ k}\Omega, R_1 = 10 \text{ k}\Omega$ |
| (d) +100 V/V | $R_2 = 990 \text{ k}\Omega, R_1 = 10 \text{ k}\Omega$ |

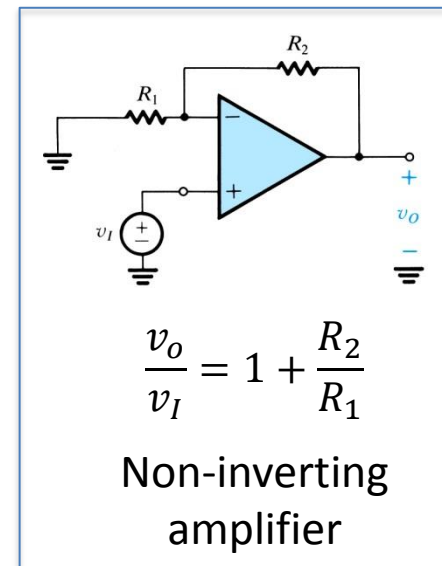

Problem 2.49

Derive an expression for the voltage gain, v_o/v_I , of the circuit in Fig. P2.49.

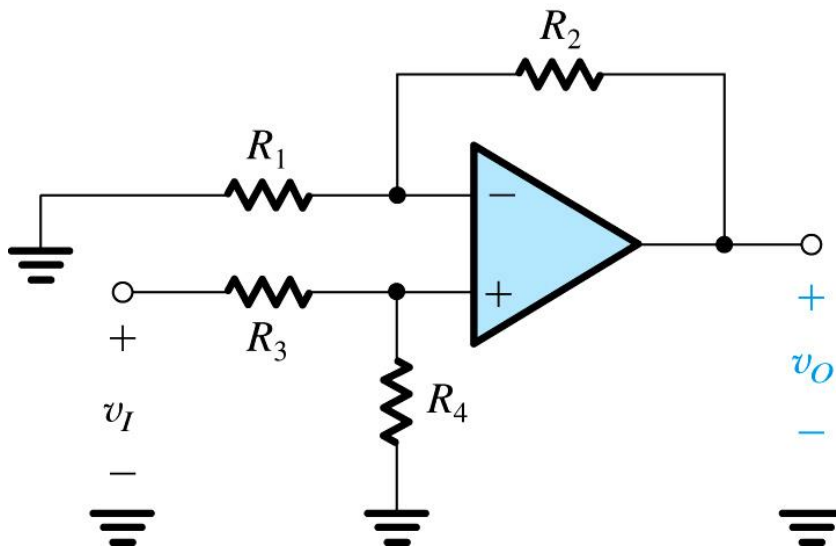


Figure P2.49

$$v_+ = v_I \frac{R_4}{R_4 + R_3} = v$$

$$v_- = v_o \frac{R_1}{R_1 + R_2} = v$$

$$v_I \frac{R_4}{R_4 + R_3} = v_o \frac{R_1}{R_1 + R_2}$$

$$\frac{v_o}{v_I} = \left(\frac{R_1 + R_2}{R_1} \right) \frac{R_4}{R_4 + R_3}$$

$$\frac{v_o}{v_I} = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$