

# CPEG660-VLSI-Project2-Proposal

8\_Inputs\_Responder, to find which input is fastest.

Wangqing Shen

Qianzi Yan

Xiwei Zhang

## 1. Total description:


We want to design a circuit to respond which one of the eight input signal comes in first. In the first part, we use D-Flip Flop and 8-input NAND gate to lock other inputs when the fastest one comes in. In the middle part, we need to change the 8 outputs of the D-Flip flop to 4 inputs. In the last part, the fastest one is shown by how many LCD lights are lighted when attached to output circuit. (LCD lights are not included in our circuit).

## 2. Table of all input and output pins

I/O	Input								Output							
Name	A0	A1	A2	A3	A4	A5	A6	A7	a	b	c	d	e	f	g	h
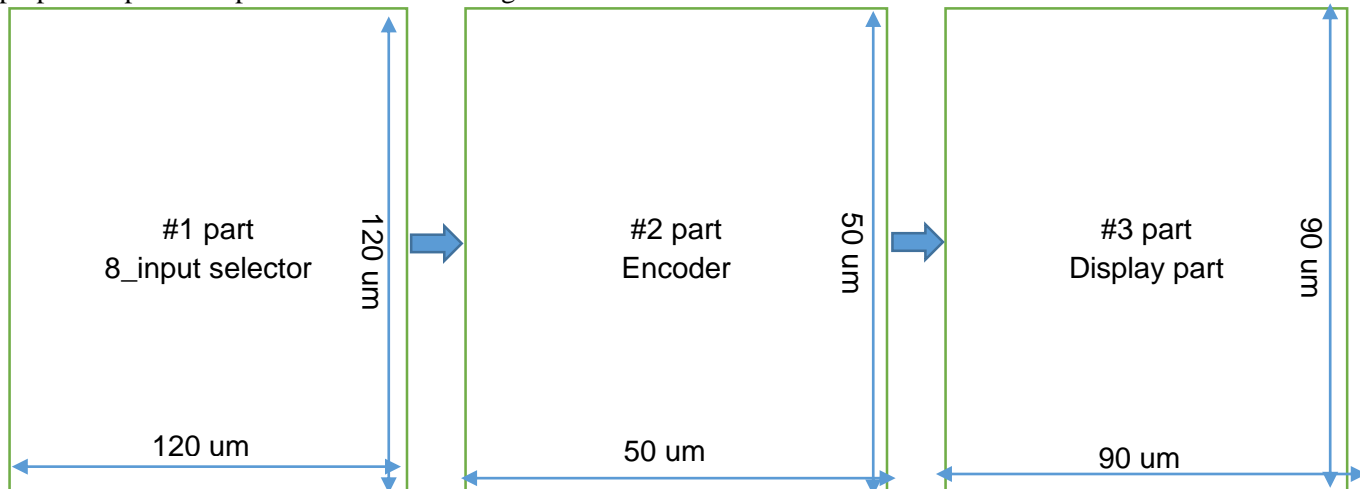
## 3. Floorplan

We prepare to put three parts from left to the right.




## 4. Introduction of each part

### (i) 8\_Input selector

This part is to recognize the one which catch the command more quickly after start. It mainly used D flip flop to deliver signal.

Part #1 Schematic

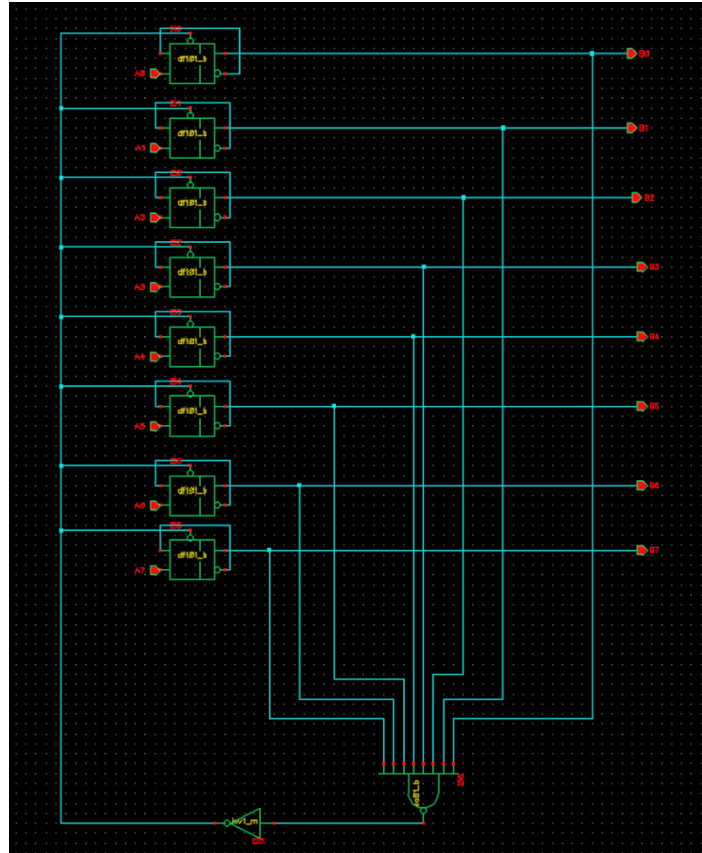

## (ii) Encoder

This part is designed to transform the eight inputs to 4 binary bits (1 represents for high voltage and 0 represents for low voltage) to represent which one is the fastest.

Part #2 Truth Table

Input								Output			
B0	B1	B2	B3	B4	B5	B6	B7	C3	C3	C1	C0
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	1	1
0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	1	0	1
0	0	0	0	0	1	0	0	0	1	1	0
0	0	0	0	0	0	1	0	0	1	1	1
0	0	0	0	0	0	0	1	1	0	0	0

The principle of output:

$$C0 = B0 + B2 + B4 + B6$$

$$C1 = B1 + B2 + B5 + B6$$

$$C2 = B3 + B4 + B5 + B6$$

$$C3 = B7$$

## (iii) Logical part to show which one is the fastest

The output will connect to 7 LCD lights and the numbers of LCD lights which are turned on represents the number of the voter. So when lights turn on, it means someone is the fastest.

Part #3 Truth Table

Input				Output							
C3	C2	C1	C0	a	b	c	d	e	f	g	h
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	1	1
0	0	1	1	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	1	1	1	1
0	1	0	1	0	0	0	1	1	1	1	1
0	1	1	0	0	0	1	1	1	1	1	1
0	1	1	1	0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1	1	1	1	1