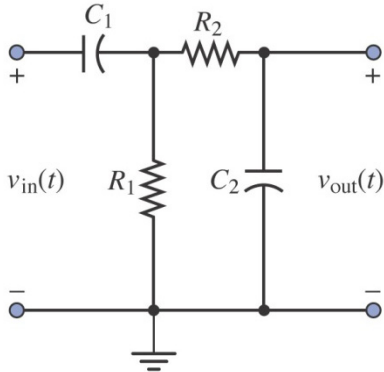
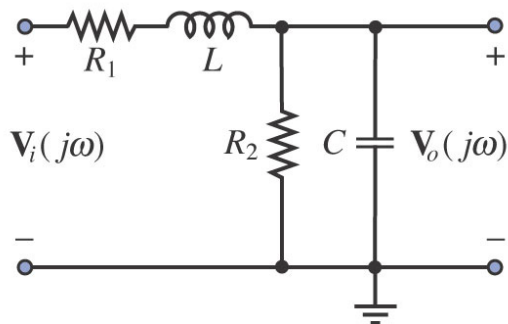


Problem 1

Determine the transfer function of the filter circuit below. Plot the magnitude and the phase of the transfer function versus frequency. $R_1 = 20 \text{ k}\Omega$; $R_2 = 100 \text{ k}\Omega$; $C_1 = 100 \text{ }\mu\text{F}$; $C_2 = 5 \text{ }\mu\text{F}$.

**Problem 2**

Determine the filter type and calculate and plot the transfer function. $L = 11 \text{ mH}$; $C = 0.47 \text{ nF}$; $R_1 = 2.2 \text{ k}\Omega$; $R_2 = 3.8 \text{ k}\Omega$.

**Problem 3**

In the filter circuit below, $R_s = 500 \text{ }\Omega$; $R_L = 5 \text{ k}\Omega$; $R_c = 4 \text{ k}\Omega$; $L = 1 \text{ mH}$; $C = 5 \text{ pF}$. Computer and plot the transfer function. What type of filter is this?

