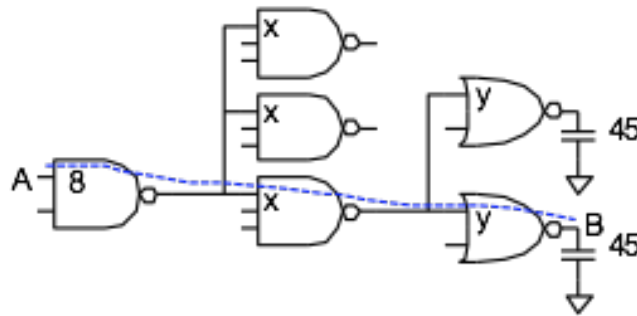


Homework 1

1. Select gate sizes X and Y for least delay (D) from A to B. Calculate D.



2. Calculate delay for the buffers below. Which one is fastest?

