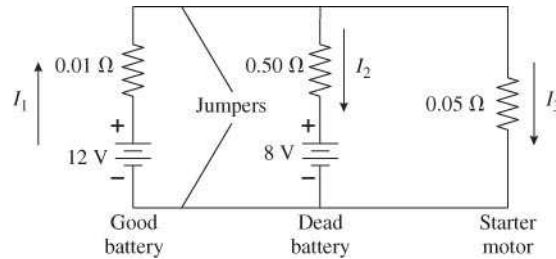


## Problem 1

**Model:** The wires are ideal, but the batteries are not.

**Visualize:**



**Solve:** (a) The good battery alone can drive a current through the starter motor

$$I = \frac{12 \text{ V}}{(0.01 \Omega + 0.05 \Omega)} = 200 \text{ A}$$

(b) Alone, the dead battery drives a current

$$I = \frac{8.0 \text{ V}}{(0.50 \Omega + 0.05 \Omega)} = 14.5 \text{ A}$$

(c) Let  $I_1$ ,  $I_2$ ,  $I_3$  be defined as shown in the figure above. Kirchhoff's laws applied to the good battery and dead battery loop, good battery and starter motor loop, and the top middle junction yield three equations in the three unknown currents:

$$12 \text{ V} - I_1(0.01 \Omega) - I_3(0.05 \Omega) = 0$$

$$12 \text{ V} - I_1(0.01 \Omega) - I_2(0.50 \Omega) - 8.0 \text{ V} = 0$$

$$I_1 = I_2 + I_3$$

Substituting for  $I_1$  from the third equation into the first and second equations gives

$$12 \text{ V} - I_2(0.01 \Omega) - I_3(0.06 \Omega) = 0$$

$$4 \text{ V} - I_2(0.51 \Omega) - I_3(0.01 \Omega) = 0$$

Solving for  $I_2$  from the first equation,

$$I_2 = \frac{12 \text{ V} - I_3(0.06 \Omega)}{(0.01 \Omega)}$$

Substituting into the second equation and solving for  $I_3$  yields the current through the starter motor is 199 A.

(d) Substituting the value for  $I_3$  into the expression for  $I_2$  yields the current through the dead battery is 3.9 A.

**Assess:** The good battery is charging the dead battery as well as running the started motor. A total of 203 A flows through the good battery.

## Problem 2

### ***Solution:***

Circuit shown in Figure P3.14.

### **Find:**

Current  $i_1$  and  $i_2$ .

### **Analysis:**

For mesh #1:

$$i_1(1 + 3) + i_2(-3) = 1$$


For mesh #2:

$$i_1(-3) + i_2(3 + 2) = -2$$

Solving,

$$i_1 = -0.091\text{A}$$

$$i_2 = -0.455\text{A}$$

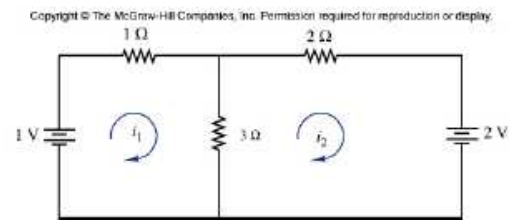

### Problem 3

#### **Solution:**

#### **Known quantities:**

The values of the resistors and of the voltage sources (see Figure P3.25).

#### **Find:**

The voltage across the  $10\ \Omega$  resistor in the circuit of Figure P3.25 using mesh current analysis.

#### **Analysis:**

For mesh (a):

$$i_a(50 + 20 + 20) - i_b(20) - i_c(20) = 12$$

For mesh (b):

$$-i_a(20) + i_b(20 + 10) - i_c(10) + 5 = 0$$

For mesh (c):

$$-i_a(20) - i_b(10) + i_c(20 + 10 + 15) = 0$$


Solving,

$$i_a = 127.5\ \text{mA}$$


$$i_b = -67.8\ \text{mA}$$

$$i_c = 41.6\ \text{mA}$$

$$\text{and } v_{R_4} = 10(i_b - i_c) = 10(-0.109) = -1.09\ \text{V}.$$

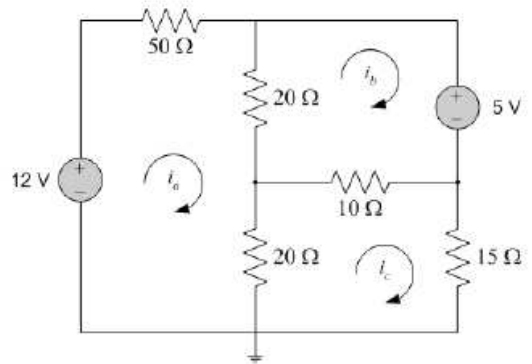

Problem 4

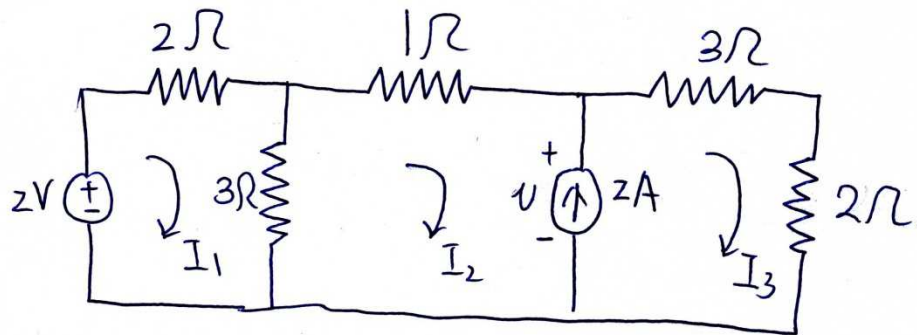

$$(2+3)I_1 - 3I_2 = 2 \quad (1)$$

$$(3+1)I_2 - 3I_1 = -v \quad (2)$$

$$(3+2)I_3 = v \quad (3)$$

$$I_3 - I_2 = 2 \quad (4)$$

From ~~(4)~~ (4) we have  $I_3 = I_2 + 2 \quad (5)$

From (1) we have  $5I_1 = 3I_2 + 2$   
 $\therefore I_1 = 0.6I_2 + 0.4 \quad (6)$

(2)+(3) yields  $4I_2 - 3I_1 + 5I_3 = 0 \quad (7)$

Substitute (5) (6) into (7)  
 we have  $I_2 = -1.22(A)$

then  $I_3 = 0.78(A)$   
 $I_1 = -0.33(A)$

## Problem 5

### Solution:

#### Known quantities:

Circuit shown in Figure P3.51.

#### Find:

Thevenin equivalent circuit

#### Analysis:

$$R_{TH} = 1\Omega + 4\Omega \parallel 5\Omega = 3.22\Omega$$

$$R_{TH} = 1 + \frac{1}{\frac{1}{5} + \frac{1}{4}} = 1 + \frac{20}{9} = \frac{29}{9}\Omega = 3.222\Omega$$


Voltage divider gives

$$V = \left( \frac{4}{4+5} \right) 36 = 16\text{ V}$$

KVL:

$$v_{oc} = -0(1) + v = v = 16\text{ V}$$

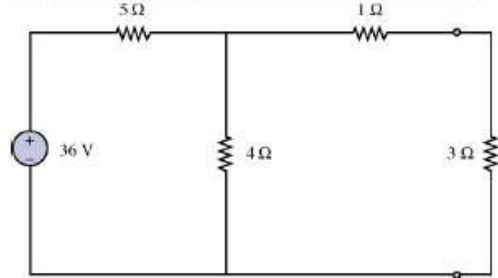Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



## Problem 6

### Solution:

#### Known quantities:

Circuit shown in Figure P3.53.

#### Find:

Norton equivalent circuit

#### Analysis:

$$R_N = 3\Omega + 1\Omega + (3\Omega \parallel 1\Omega) = 4.75\Omega$$

Using the mesh analysis approach

$$4i_1 - 3i_2 = 2$$

$$-3i_1 + 4i_2 + 3i_{SC} = 0$$

$$i_2 - i_{SC} = 2$$

$$\text{Solving, } i_{SC} = -0.42\text{ A} \Rightarrow i_N = -0.42\text{ A}$$

It means the magnitude of  $i_{SC}$  is 0.42A and the direction of  $i_{SC}$  is count-clockwise.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

