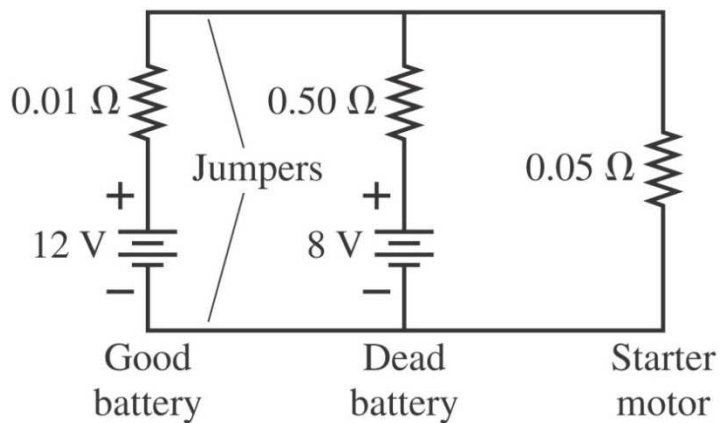


### Problem 1


A 12 V car battery dies not so much because its voltage drops but because chemical reactions increase its internal resistance. A good battery connected with jumpers cables can both start the engine and recharge the dead battery. Consider the automotive circuit below.

- How much current could the good battery alone drive through the starter motor?
- How much current is the dead battery alone able to drive through the starter cable?
- With the jumper cables attached, how much current passes through the starter motor?
- With the jumper cables attached, how much current passes through the dead battery, and in which direction?



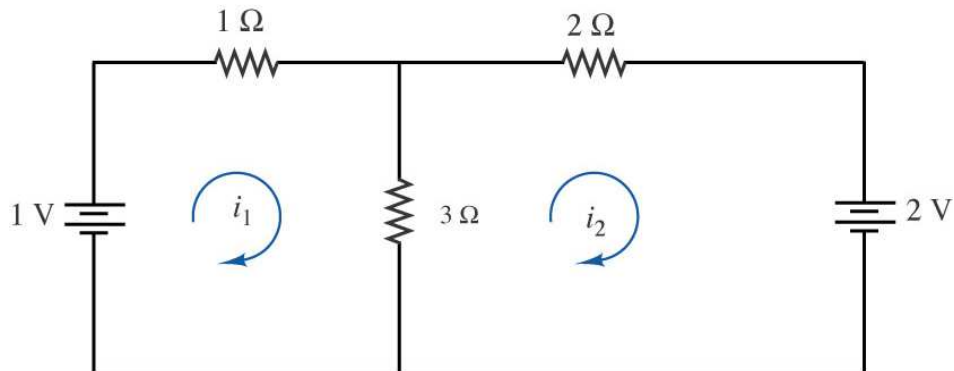
### Problem 2

Use mesh analysis, find the mesh currents  $i_1$  and  $i_2$  for the circuit below.



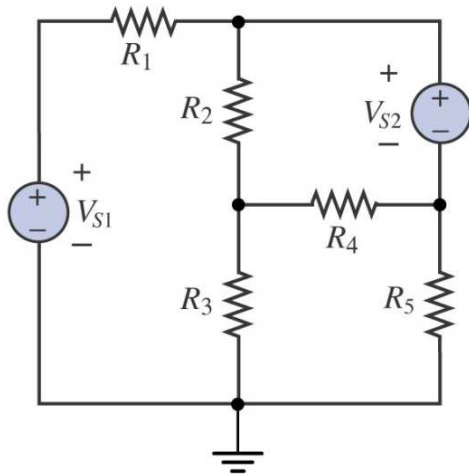
### Problem 3

Use mesh current analysis, find the voltage  $v$  across  $R_4$  in the circuit below. Let  $V_{S1}=12\text{V}$ ;  $V_{S2}=5\text{V}$ ;  $R_1=50\ \Omega$ ;  $R_2=R_3=20\ \Omega$ ;  $R_4=10\ \Omega$ ;  $R_5=15\ \Omega$ .



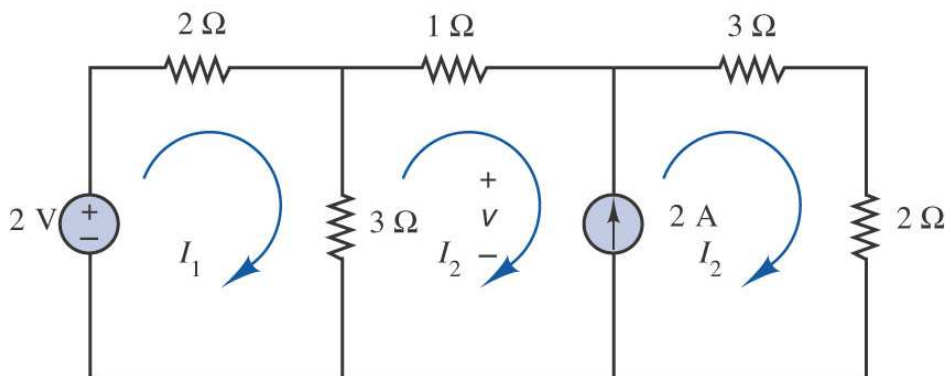
#### Problem 4

Use mesh current analysis, find the currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit below. Assume polarity according to  $I_2$ .



#### Problem 5

Find the Thevenin equivalent circuit as seen by the  $3\ \Omega$  resistor for the circuit in the Figure below.

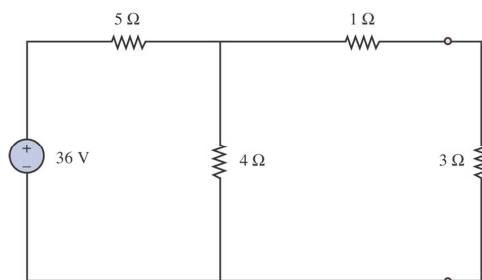

**Problem 6**

Find the Norton equivalent of the circuit to the left of the  $2\ \Omega$  resistor in the figure below.

