


Problem 1

Determine $i_3(t)$ in the circuit below if

$$i_1(t) = 141.4 \cos(\omega t + 2.356) \text{ mA}$$

$$i_2(t) = 50 \sin(\omega t - 0.927) \text{ mA}$$


$$\omega = 377 \text{ rad/s}$$

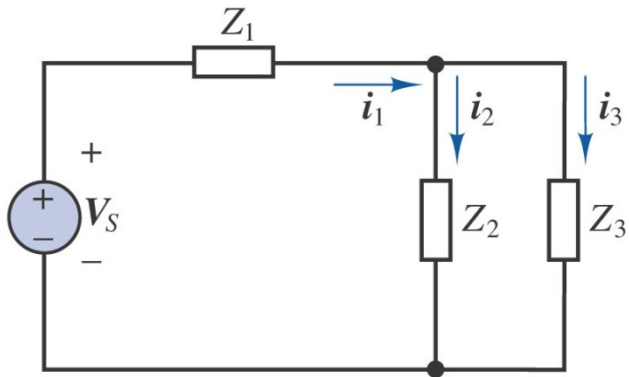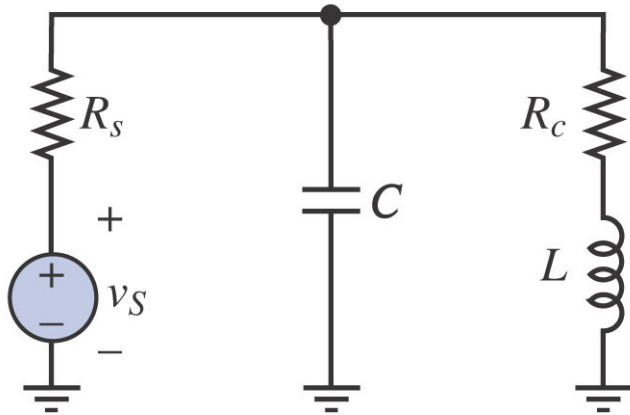**Problem 2**

Determine the current supplied by the source in the circuit below if


$$v_s(t) = 10 \cos(\omega t + 0) \text{ V}$$
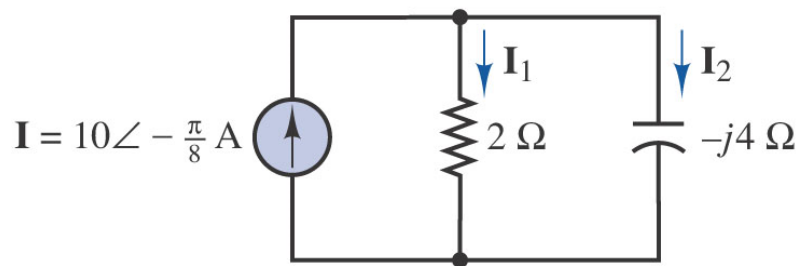
$$\omega = 6 \text{ Mrad/s}, R_s = 50 \, \Omega, R_c = 40 \, \Omega, L = 20 \, \mu\text{H}, \text{ and } C = 1.25 \text{ nF}.$$

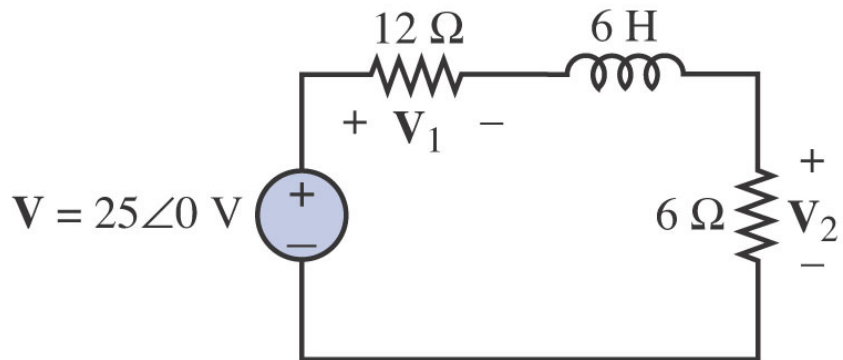


Problem 3


Solve for \mathbf{I}_1 in the circuit below.

**Problem 4**

Solve for \mathbf{V}_2 in the circuit below. Assume $\omega = 2 \text{ rad/s}$.

**Problem 5**

In the circuit below, find the impedance Z , given $\omega = 4 \text{ rad/s}$.

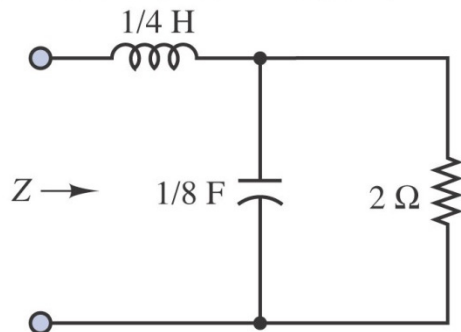

Problem 6

Solve for $i_L(t)$ in the circuit below using phasor techniques, if $v_s(t) = 2 \cos 2t$ V, and $R_1 = 4 \Omega$, $R_2 = 4 \Omega$, $L = 2$ H, and $C = 0.25$ F.

