

Problem 1

In phasor form:

a) $V(j\omega) = 155\angle -25^\circ \text{ V}$

b) $V(j\omega) = 5\angle -130^\circ \text{ V}$

c) $I(j\omega) = 10\angle 63^\circ + 15\angle -42^\circ = (4.54 + j8.91) + (11.15 - j10.04) = 15.69 - j1.13 = 15.73\angle -4.12^\circ \text{ A}$

d) $I(j\omega) = 460\angle -25^\circ - 220\angle 75^\circ = (416.90 - j194.40) - (56.94 - j212.50) = 359.96 + j18.10 = 360.4\angle 2.88^\circ \text{ A}$

Problem 2

a) $4 + j4 = 4\sqrt{2}\angle 45^\circ = 5.66\angle 45^\circ$

b) $-3 + j4 = 5\angle 126.9^\circ$

c) $j + 2 - j4 - 3 = -1 - j3 = 3.16\angle -108.4^\circ$

Problem 3

a) $(50 + j10)(4 + j8) = (50.99\angle 11.30^\circ)(8.94\angle 63.43^\circ) = 456.1\angle 74.7^\circ$

$(50 + j10)(4 + j8) = 200 + j400 + j40 + j^2 80 = 120 + j440 = 456.1\angle 74.7^\circ$

b) $(j2 - 2)(4 + j5)(2 + j7) = (2.82\angle 135^\circ)(6.40\angle 51.34^\circ)(7.28\angle 74.05^\circ) = 131.8\angle 260.4^\circ = 131.8\angle -99.6^\circ$

$(j2 - 2)(4 + j5)(2 + j7) = -36 - j126 - j4 - j^2 14 = -22 - j130 = 131.8\angle -99.6^\circ$


Problem 4

Solution:

Known quantities:

The values of the impedance, $R_1 = 2.3 \text{ k}\Omega$, $R_2 = 1.1 \text{ k}\Omega$, $L = 190 \text{ mH}$, $C = 55 \text{ nF}$ and the voltage applied to the circuit shown in Figure P4.47, $v_s(t) = 7 \cos(3000t + 30^\circ) \text{ V}$.

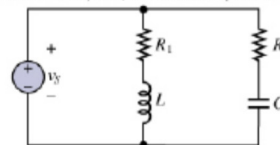Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Find:

The equivalent impedance of the circuit.

Analysis:

$$X_L = \omega L = \left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(190 \text{ mH}) = 0.57 \text{ k}\Omega \Rightarrow Z_L = +j \cdot X_L = +j \cdot 0.57 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{\left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(55 \text{ nF})} = 6.061 \text{ k}\Omega \Rightarrow Z_C = -j \cdot X_C = -j \cdot 6.061 \text{ k}\Omega$$

$$Z_{eq1} = Z_{R1} + Z_L = R_1 + jX_L = 2.3 + j \cdot 0.57 \text{ k}\Omega = 2.37\angle 13.92^\circ \text{ k}\Omega$$

$$Z_{eq2} = Z_{R2} + Z_C = R_2 - jX_C = 1.1 - j \cdot 6.061 \text{ k}\Omega = 6.16\angle -79.71^\circ \text{ k}\Omega$$

$$\begin{aligned} Z_{eq} &= \frac{Z_{eq1} \cdot Z_{eq2}}{Z_{eq1} + Z_{eq2}} = \frac{(2.37\angle 13.92^\circ \text{ k}\Omega)(6.16\angle -79.71^\circ \text{ k}\Omega)}{(2.3 + j \cdot 0.57 \text{ k}\Omega) + (1.1 - j \cdot 6.061 \text{ k}\Omega)} = \\ &= \frac{14.60\angle -65.79^\circ \text{ k}\Omega^2}{3.4 - j \cdot 5.491 \text{ k}\Omega} = \frac{14.60\angle -65.79^\circ \text{ k}\Omega^2}{6.458\angle -58.23^\circ \text{ k}\Omega} = 2.261\angle -7.56^\circ \text{ k}\Omega \end{aligned}$$

Problem 5

$$V_{s1}(j\omega) = V_{s2}(j\omega) = 170 \angle 0^\circ \text{ V}$$

$$V_s(j\omega) = V_{s1}(j\omega) + V_{s2}(j\omega) = 340 \angle 0^\circ$$

$$I_{Z_3}(j\omega) = \frac{V_s(j\omega)}{Z_3}$$

$$Z_3 = 17 \angle 0.192 = 17 \angle 11^\circ \Omega$$

$$I_{Z_3}(j\omega) = \frac{340 \angle 0^\circ}{17 \angle 11^\circ}$$

$$= 20 \angle -11^\circ$$

$$i_{Z_3}(t) = 20 \cos(377t - 11^\circ)$$

Problem 6

To have $I_i(j\omega)$ and $V_o(j\omega)$ in phase.

$Z_{CRL} = \frac{V_o(j\omega)}{I_i(j\omega)}$ has to be a real number.

$$Z_{CRL} = Z_C // (Z_R + Z_L)$$

$$= \frac{Z_C (Z_R + Z_L)}{Z_C + Z_R + Z_L}$$

$$Z_C = -\frac{j}{\omega C} = -\frac{j}{\omega \times (220 \times 10^{-12})} = -\frac{4.54 \times 10^9}{\omega} j \Omega$$

$$Z_L = j\omega L = j\omega (19 \times 10^{-3}) = 0.019 j\omega \Omega$$

$$Z_R = 120 \Omega$$

$$Z_{CRL} = \frac{-\frac{4.54}{\omega} \times 10^9 j (120 + 0.019 j\omega)}{120 + 0.019 \omega j - \frac{4.54}{\omega} \times 10^9 j}$$

$$= \frac{8.63 \times 10^7 - \frac{5.45}{\omega} \times 10^{11} j}{120 + j(0.019\omega - \frac{4.54 \times 10^9}{\omega})}$$

For Z_{CRL} to be real, the phasor angles of denominator and numerator has to be the same.

$$\therefore \frac{-\frac{5.45}{\omega} \times 10^{11}}{8.63 \times 10^7} = \frac{0.019\omega - \frac{4.54}{\omega} \times 10^9}{120}$$

$$-\frac{6.32 \times 10^3}{\omega} = \frac{0.019\omega - \frac{4.54}{\omega} \times 10^9}{120}$$

$$4.54 \times 10^8 = \frac{4.54 \times 10^9}{0.019} \times 10^8$$

$$\omega = \sqrt{\frac{4.54 \times 10^9}{0.019}} \times 10^4 \text{ rad/s}$$

$$\omega = 4.89 \times 10^5 \text{ rad/s}$$

Problem 7

Solution:

Known quantities:

The values of the impedance and the voltage applied to the circuit shown in Figure P4.54.

Find:

The current in the circuit.

Analysis:


Assume clockwise currents:

$$\omega = 3 \frac{\text{rad}}{\text{s}}, V_S = 12 \angle 0^\circ \text{ V}$$

$$Z_C = \frac{1}{j\omega C} = -j \Omega, Z_L = j\omega L = j9 \Omega \Rightarrow Z_{\text{total}} = 3 + j9 - j = 3 + j8 \Omega$$

$$I = \frac{12}{3 + j8} = 0.4932 - j1.3151 \text{ A} = 1.4045 \angle -69.44^\circ \text{ A}, i(t) = 1.4 \cos(\omega t - 69.4^\circ) \text{ A}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

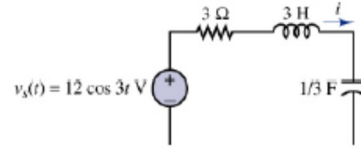

Problem 8

Solution:

Known quantities:

Circuit shown in Figure P4.68, the values of the resistance, $R = 9 \Omega$, capacitance, $C = 1/18 \text{ F}$, inductance,

$L_1 = 3 \text{ H}$, $L_2 = 3 \text{ H}$, $L_3 = 3 \text{ H}$, and the voltage source $v_s(t) = 36 \cos\left(3t - \frac{\pi}{3}\right) \text{ V}$.

Find:

The voltage across the capacitance v using phasor techniques.

Analysis:

$$\omega = 3 \frac{\text{rad}}{\text{s}}, V_s = 36 \angle -60^\circ \text{ V}$$

$$Z_{L_2} = j\omega L_2 = j3 \cdot 3 = j9 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j3 \cdot (1/18)} = -j6 \Omega$$

$$Z_{L_3} = j\omega L_3 = j3 \cdot 3 = j9 \Omega$$

$$Z_{eq} = \frac{1}{Z_{L_3} \parallel (Z_{L_2} + Z_C)} = \frac{1}{\frac{1}{Z_{L_3}} + \frac{1}{Z_{L_2} + Z_C}} = \frac{1}{\frac{1}{j9} + \frac{1}{j9 - j6}} = \frac{j9}{4} = 2.25 \angle 90^\circ \Omega$$


$$Z_T = Z_R + Z_{L_1} + Z_{eq} = 9 + j3 \cdot 3 + j2.25 = 9 + j11.25 = 14.407 \angle 51.34^\circ \Omega$$

$$I = \frac{V_s}{Z_T} = \frac{36 \angle -60^\circ \text{ V}}{14.407 \angle 51.34^\circ \Omega} = 2.499 \angle -111.34^\circ \text{ A}$$

$$V_{eq} = I Z_{eq} = (2.499 \angle -111.34^\circ)(2.25 \angle 90^\circ) = 5.623 \angle -21.34^\circ \text{ V}$$

$$V = \frac{Z_C}{(Z_{L_2} + Z_C)} V_{eq} = \frac{-j6}{j9 - j6} 5.623 \angle -21.34^\circ = 11.25 \angle 158.66^\circ \text{ V}$$

$$v = 11.25 \cos(3t - 158.66^\circ) \text{ V}$$

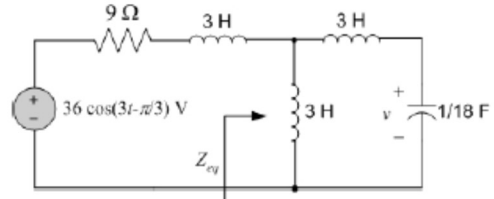

Problem 9

Solution:

Known quantities:

Circuit shown in Figure P4.69, the values of the resistance, $R = 5 \Omega$, capacitance, $C = 1/2 \text{ F}$, inductance, $L_1 = 0.5 \text{ H}$, $L_2 = 1 \text{ H}$, $L_3 = 10 \text{ H}$, and the current source $i_s(t) = 6 \cos(2t) \text{ A}$.

Find:

The current through the inductance i_{L_2} .

Analysis:

$$\omega = 2 \frac{\text{rad}}{\text{s}}, \quad Z_{L_2} = j\omega L_2 = j2 \Omega, \quad Z_C = \frac{1}{j\omega C} = -j \Omega, \quad Z_{L_1} = j\omega L_1 = j20 \Omega$$

$$I = \frac{Z_{L_3} + Z_C}{(Z_{L_3} + Z_C) + (R + Z_{L_2})} I_s = \frac{j20 - j}{(j20 - j) + (5 + j2)} 6 \angle 0^\circ = \frac{j19}{5 + j21} 6 \angle 0^\circ = 5.28 \angle 13.4^\circ \text{ A}$$

$$i = 5.28 \cos(2t + 13.4^\circ) \text{ A}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

