


* Mesh analysis

In kirchhoff's laws, we use branch currents as variable.

3 variables

3 equations

$$I_1 + I_2 + I_3 = 0$$

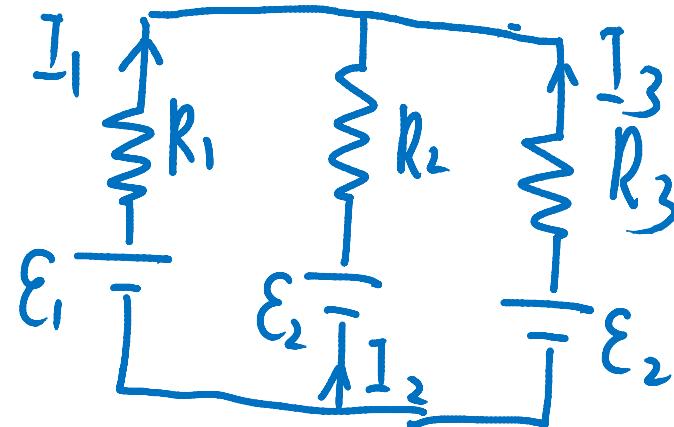


Define mesh currents i_1 and i_2

$$I_1 = i_1$$

$$I_3 = -i_2$$

$$I_2 = i_2 - i_1$$

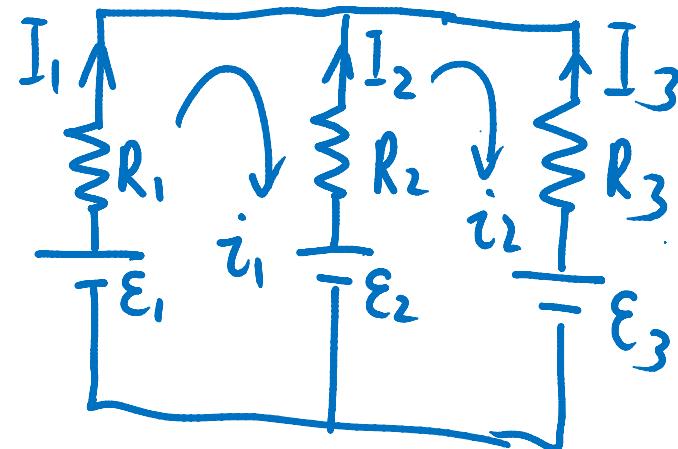

$$I_1 + I_2 + I_3 = i_1 + (-i_2) + (i_2 - i_1) = 0$$


By defining mesh current i_1 and i_2 , KCL is automatically satisfied.

loop equations (kVL)

$$I_1 = i_1$$

$$I_2 = i_2 - i_1$$

$$I_3 = -i_2$$

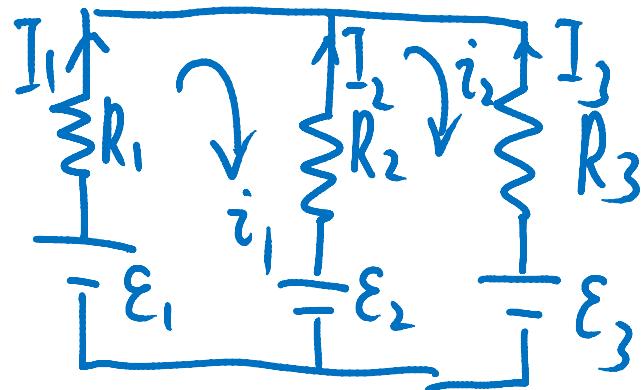

left mesh $\varepsilon_1 - I_1 R_1 + I_2 R_2 - \varepsilon_2 = 0$

$$\varepsilon_1 - i_1 R_1 + (i_2 - i_1) R_2 - \varepsilon_2 = 0$$

$$i_1(R_1 + R_2) - i_2 R_2 = \varepsilon_1 - \varepsilon_2 \quad (1)$$

similarly right mesh $-R_2 i_1 + (R_2 + R_3) i_2 = \varepsilon_2 - \varepsilon_3 \quad (2)$

only two equations.


Mesh analysis

Step 1: assignment of mesh currents
(ccw)

mesh is a loop that does not contain other loops.

Step 2. Apply KVL to each mesh

- The so-called self-resistance is the effective resistance of the resistors in series within a mesh. The mutual resistance is the resistance that the mesh has in common with a neighboring mesh.
- To write down the mesh equation, evaluate the self-resistance, then multiply by the mesh current. This have units of voltage
- From that, subtract the product of mutual resistance and current from the neighboring mesh for each such neighbor.
- Equate the result above to the driving voltage, taken to be positive if its polarity tends to push current in the same direction as the

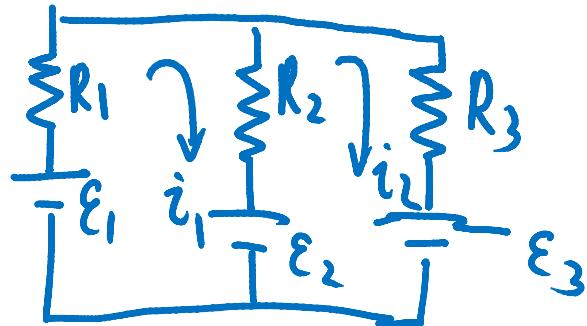


assigned mesh current.

mesh 1. $(R_1 + R_2) i_1 - R_2 i_2 = \epsilon_1 - \epsilon_2$

mesh 2. $-R_2 i_1 + (R_2 + R_3) i_2 = \epsilon_2 - \epsilon_3$

Example

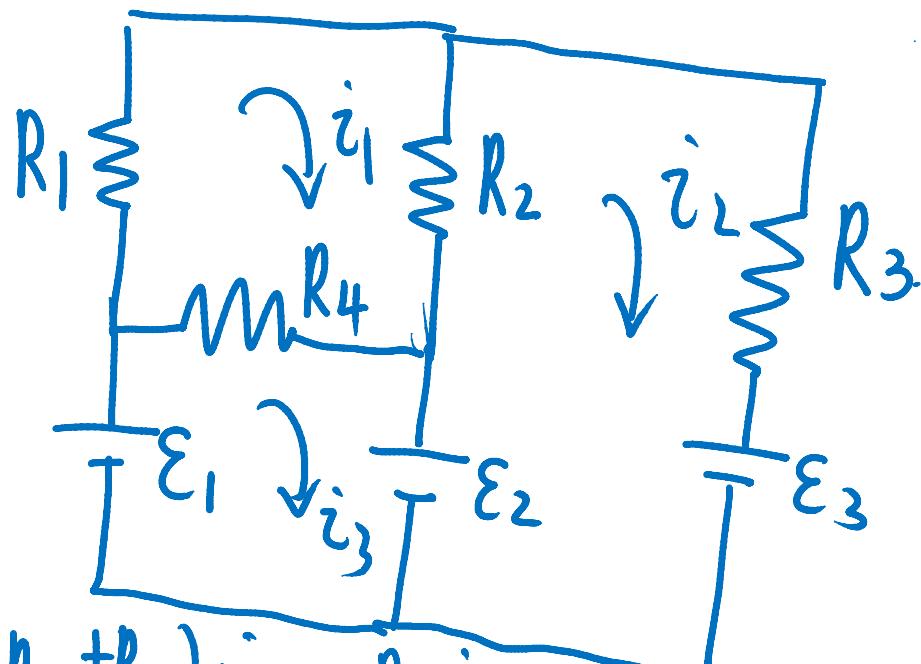


mesh 1. $(R_1 + R_2 + R_4) i_1 - R_2 i_2 - R_4 i_3 = 0$

mesh 2. $-R_2 i_1 + (R_2 + R_3) i_2 + 0 = \epsilon_2 - \epsilon_3$

mesh 3.

$$\text{mesh 3. } -R_4 i_1 + R_4 i_3 = \varepsilon_1 - \varepsilon_2$$

Example

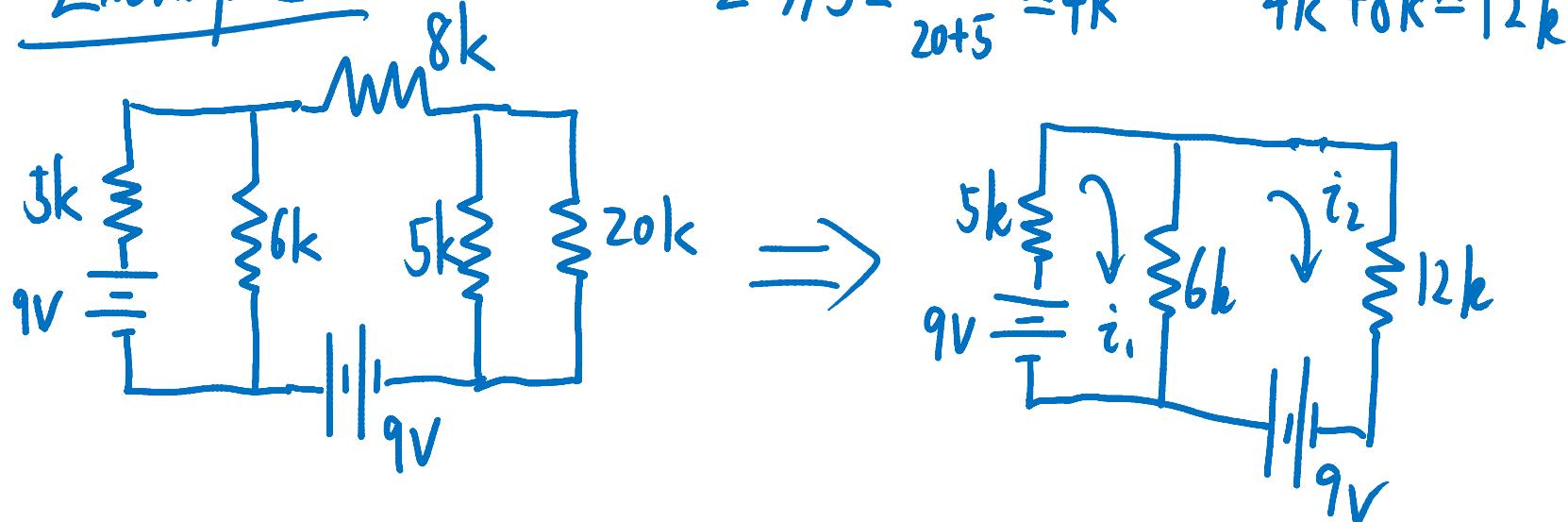

$$20//5 = \frac{20 \times 5}{20+5} = 4\text{k} \quad 4\text{k} + 8\text{k} = 12\text{k}$$

$$\text{left mesh: } 11i_1 - 6i_2 = 9$$

$$\text{right mesh: } 18i_2 - 6i_1 = 9$$

$$i_1 = 1.33 \text{ (mA)}$$

$$i_2 = 0.94 \text{ (mA)}$$


A Comparison between kVL/kCL method and mesh analysis

| | kVL/kCL | mesh analysis |
|----------------------------------|---|---|
| independent variables | branch currents | mesh currents |
| number of equations | number of branches | number of meshes |
| underlying principles | kCL and kVL | kVL explicit kCL implicit |
| sign conventions | evaluate voltage change around loop | Self resistance, mutual resistance source directions |
| How to deal with current sources | current in branch is the preset value of current source | |

Application jump start a car

good car battery:
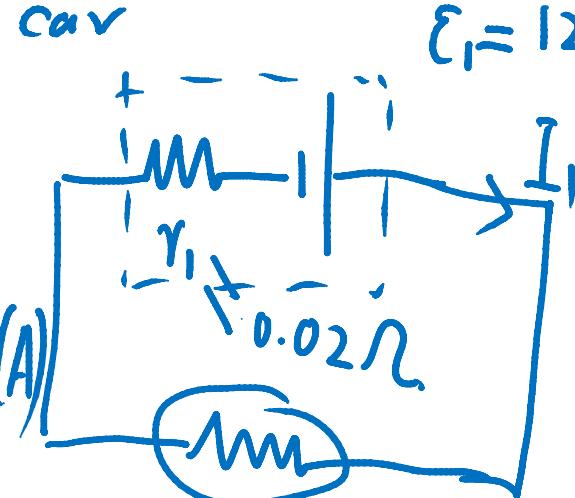
$$I_1 = \frac{\varepsilon_1}{r_1 + R} = \frac{12.5}{0.02 + 0.15} = 73.5 \text{ (A)}$$





Weak car battery

$$I_2 = \frac{\varepsilon_2}{r_2 + R} = \frac{10.1 \text{ V}}{(0.1 + 0.15) \Omega}$$

$$= 40.4 \text{ (A)} < I_1$$

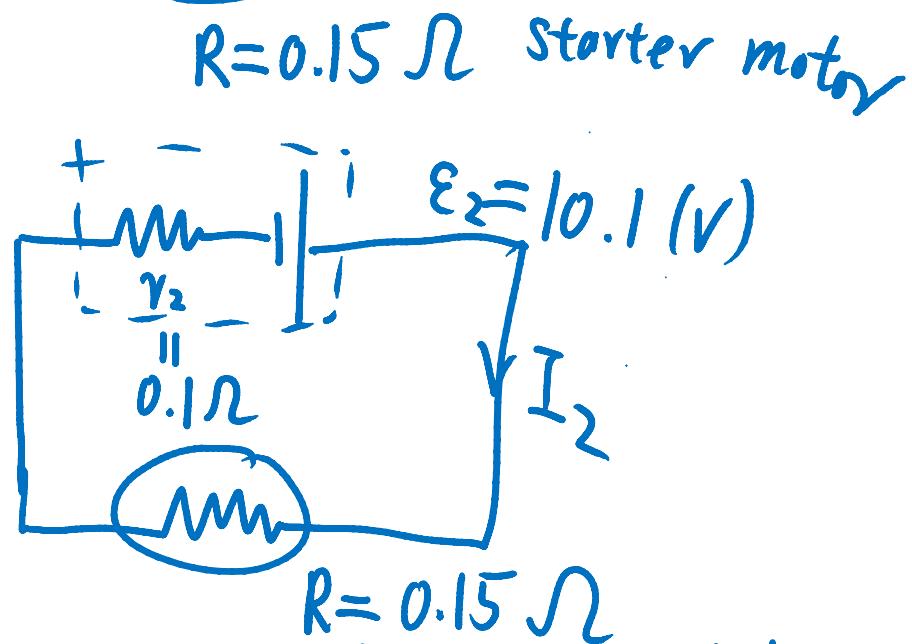Jump start: good battery starts motor and recharge weak battery.



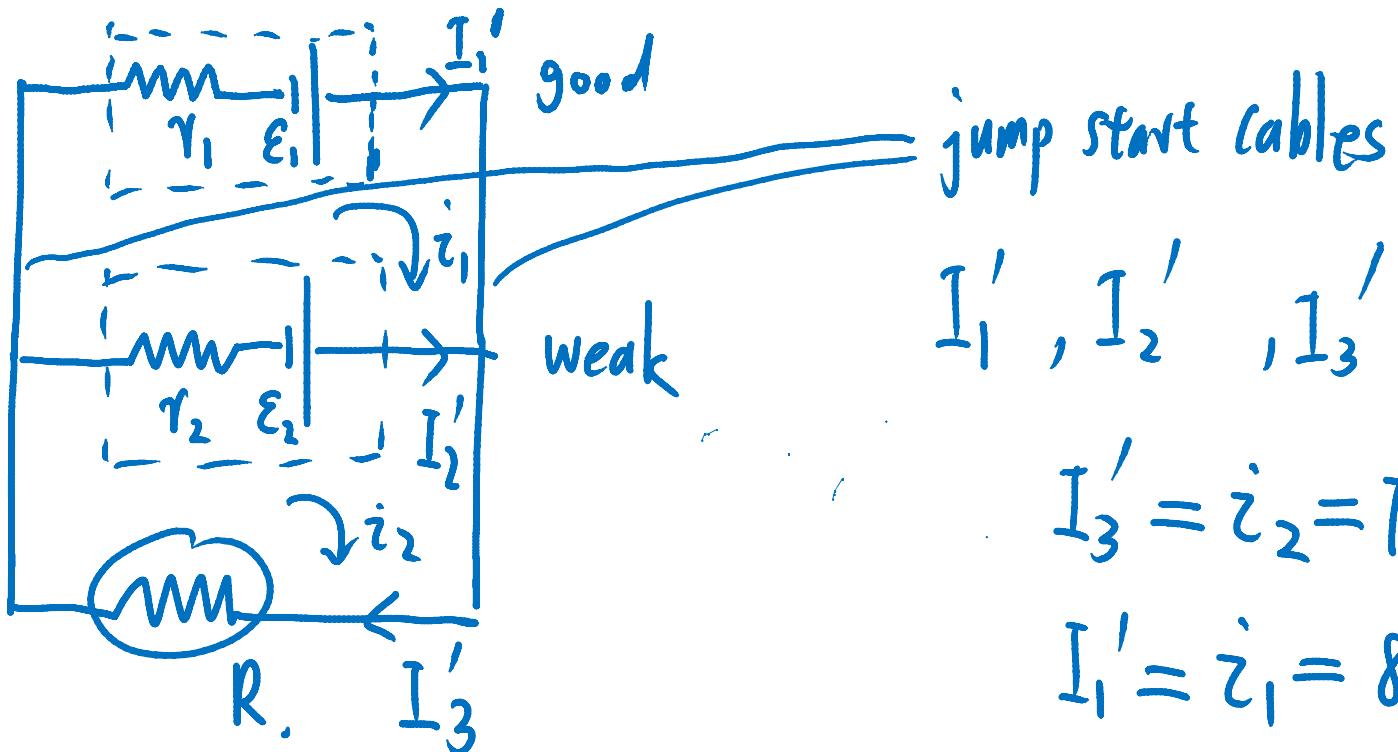

$$(\gamma_1 + \gamma_2) i_1 - \gamma_2 i_2 = E_1 - E_2$$

$$(\gamma_2 + R) i_2 - \gamma_2 i_1 = E_2$$

$$\left\{ \begin{array}{l} 0.12 i_1 - 0.1 i_2 = 2.4 \\ -0.1 i_1 + 0.25 i_2 = 10.1 \end{array} \right. \quad (1)$$

$$\left\{ \begin{array}{l} 0.12 i_1 - 0.1 i_2 = 2.4 \\ -0.1 i_1 + 0.25 i_2 = 10.1 \end{array} \right. \quad (2)$$


$$I_1' = i_1 = 80.5 \text{ (A)}$$

$$I_3' = i_2 = 72.6 \text{ (A)} \approx I_1$$

$$I_2' = i_2 - i_1 = -7.9 \text{ (A)}$$


opposite to defined direction
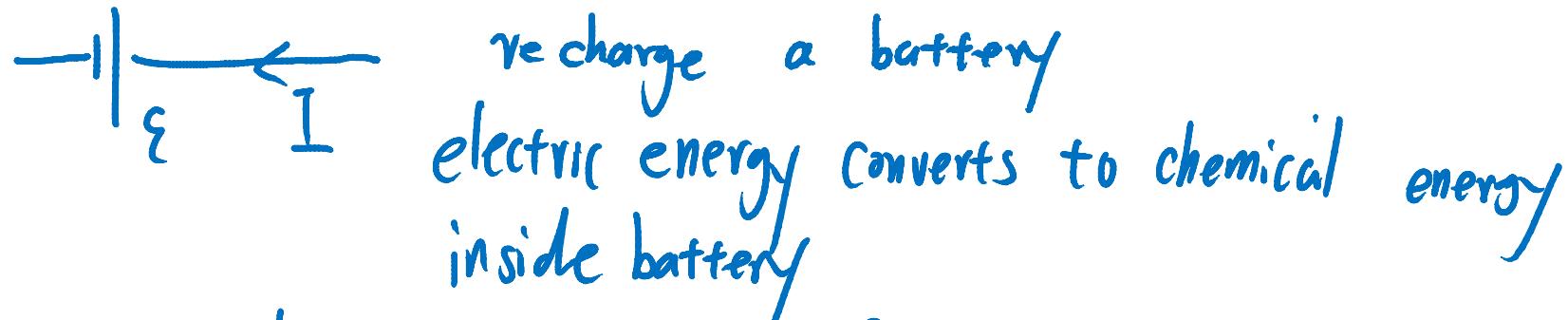
$$\Rightarrow \left\{ \begin{array}{l} i_1 = 80.5 \text{ (A)} \\ i_2 = 72.6 \text{ (A)} \end{array} \right.$$



rate of energy conversion (power): $P = I \varepsilon$

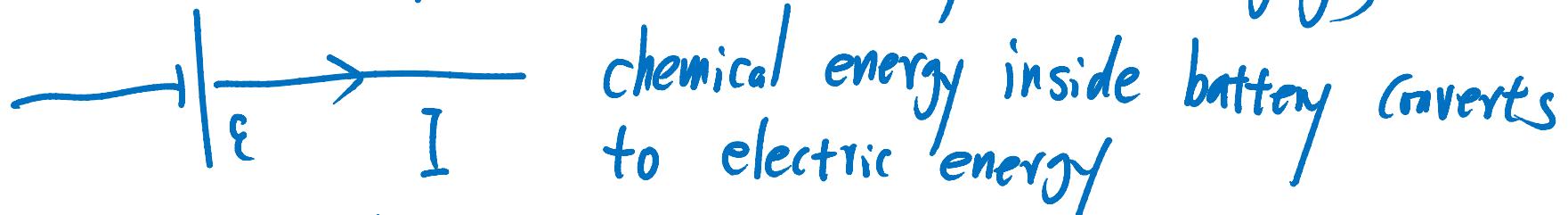Normal operation of a battery (discharging)




rate of energy conversion (power): $P = I \varepsilon$

Discharging power of ε ,

$$= \text{charging power of } \varepsilon_1 + \text{heating on resistors } (r_1, r_2, R)$$

Mesh analysis with current sources


Example

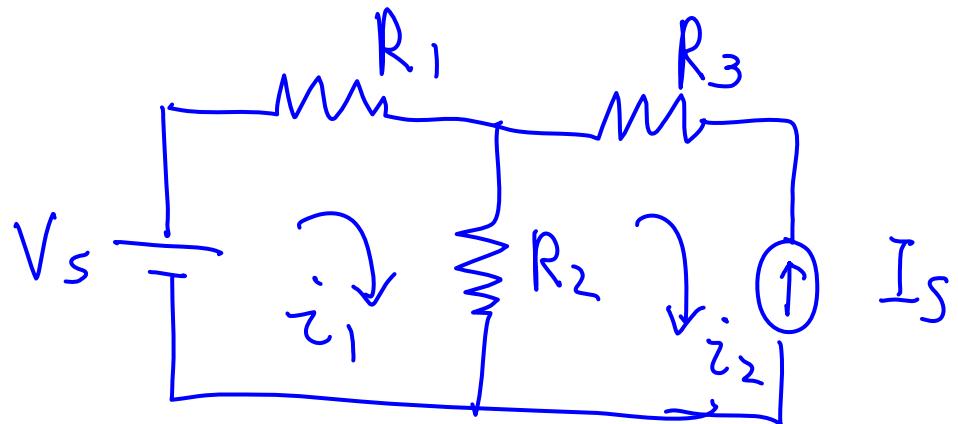

mesh

$$\begin{cases} (R_1 + R_2) \dot{z}_1 - R_2 \dot{z}_2 = V_s \\ \dot{z}_2 = -I_s \end{cases}$$

Example,

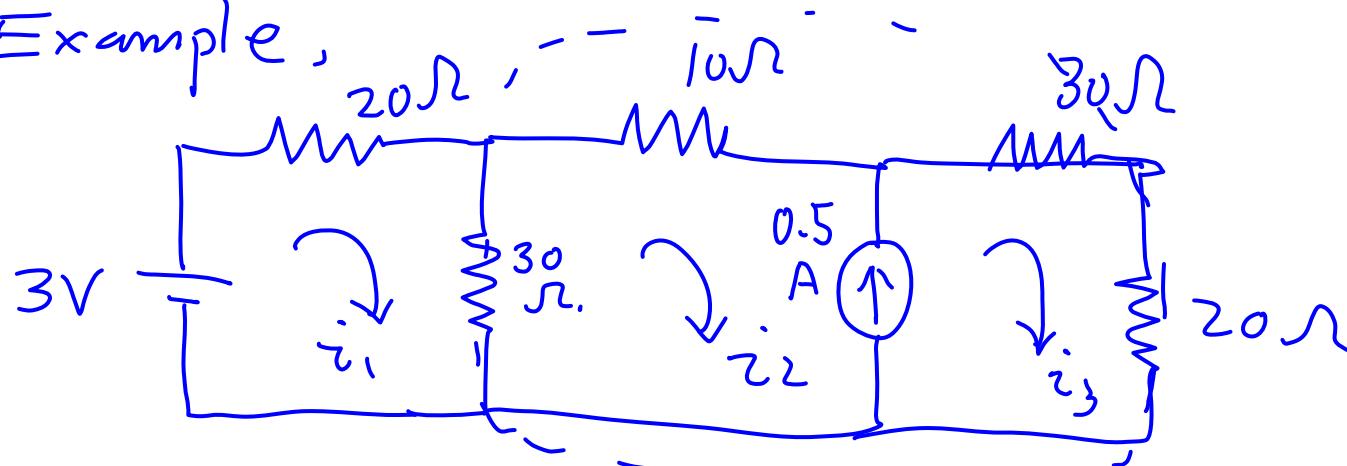




$$(20 + 30)\bar{i}_1 - 30\bar{i}_2 = 3 \quad (1)$$

$$\bar{i}_3 - \bar{i}_2 = 0.5 \quad (2)$$

$$30(\bar{i}_1 - \bar{i}_2) - 10\bar{i}_2 - (30 + 20)\bar{i}_3 = 0 \quad (3)$$

* Thevenin and Norton equivalent circuits

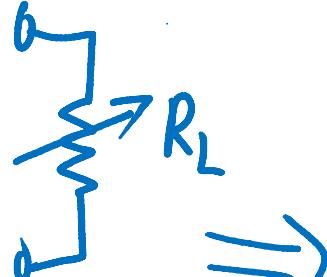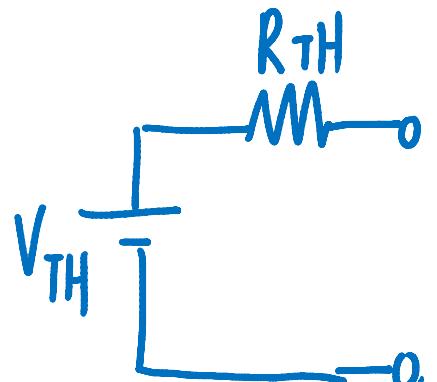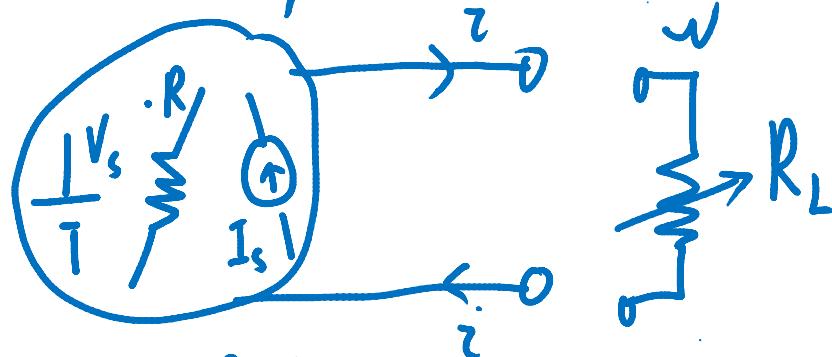
Arbitrary Network Consisting of sources and resistors



$$V_{TH} = V_m \text{ (open circuit voltage)}$$


$$\frac{V_{TH}}{R_{TH}} = i_m \text{ (short circuit current)}$$
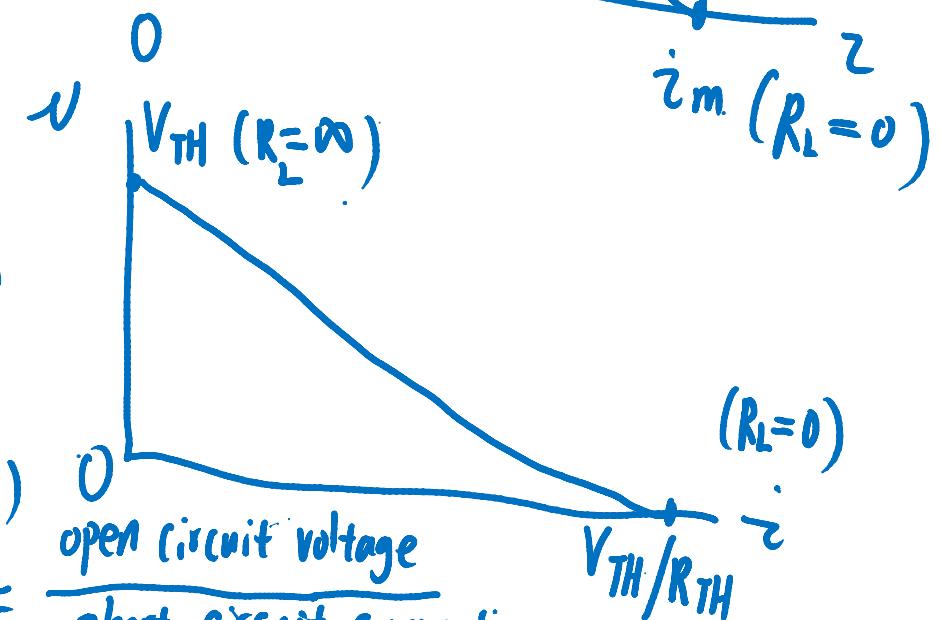
$$R_{TH} = \frac{V_{TH}}{i_m} = \frac{V_m}{i_m} = \frac{\text{open circuit voltage}}{\text{short circuit current}}$$







R_{TH} is also the resistance of network seen from the two terminals.

Thevenin's Theorem

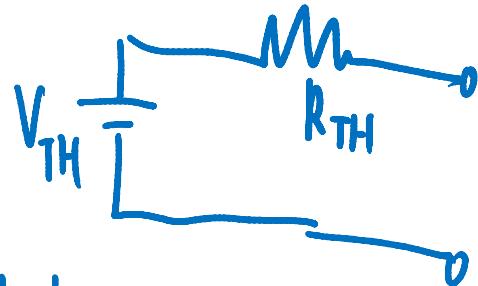

- Any two terminal linear circuit can be replaced with a voltage source in series with a resistance which will produce the same effects at the terminals.
- V_{TH} is the open circuit voltage V_{oc} between the two terminals of the circuit that the Thevenin equivalent circuit is replacing.
- R_{TH} is the ratio of V_{oc} to the short circuit current I_{sc} .
In linear circuits, this is equivalent to "killing" the sources and evaluating the resistance between the terminals. Voltage sources are killed by replacing it with a wire ; Current sources are killed by disconnecting them.

Norton Equivalent Circuit.

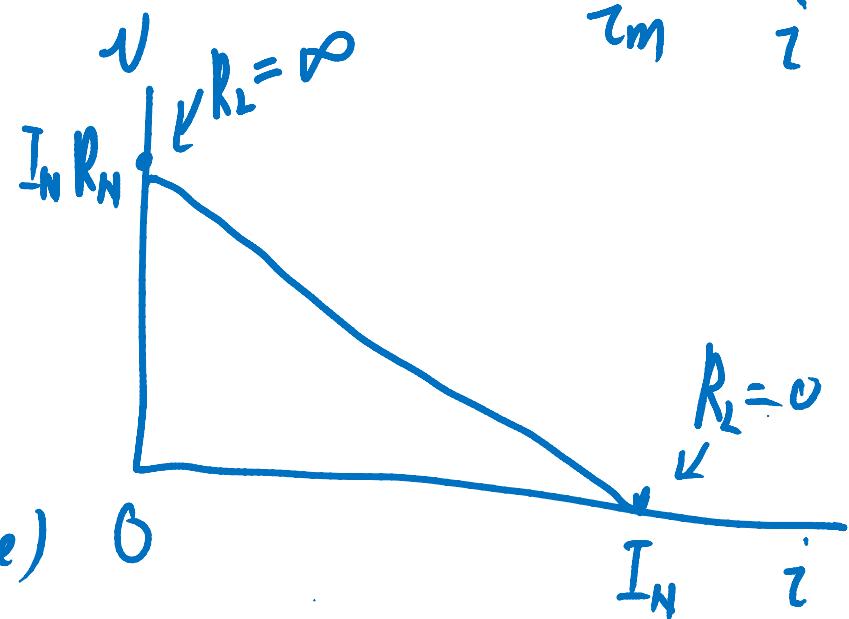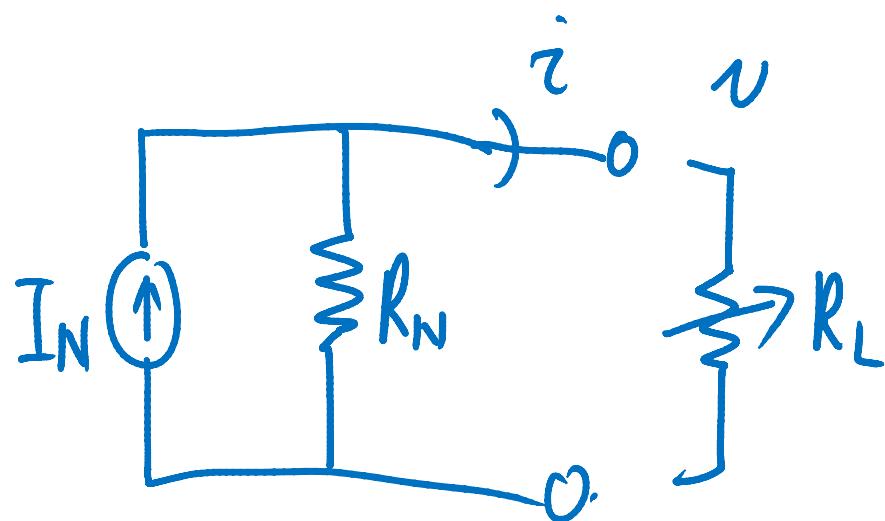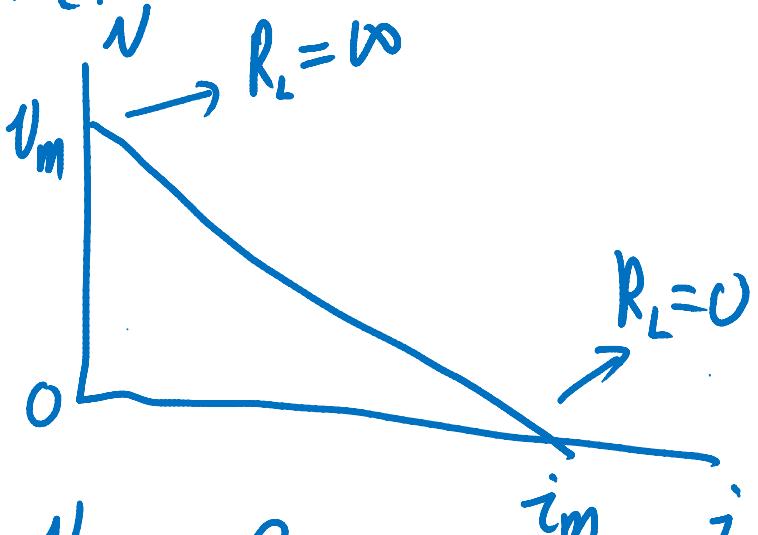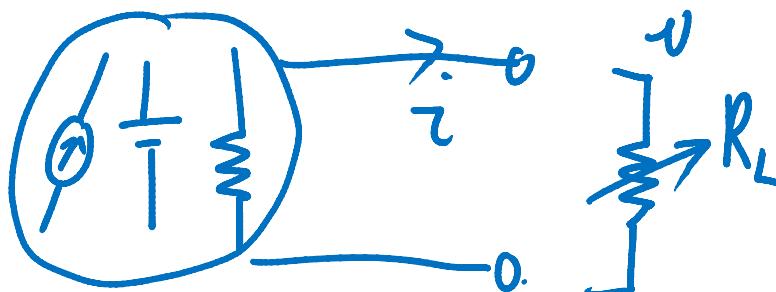

$$I_N R_N = V_m \text{ (open circuit voltage)}$$

$$I_N = i_m \text{ (short circuit current)}$$

$$R_N = \frac{V_m}{I_N} = \frac{V_m}{i_m} = \frac{\text{open circuit voltage}}{\text{short circuit current}} = R_{TH}$$


$$R_N = R_{TH}$$

$$V_{TH} = I_N R_N = V_{oc}$$

$$I_N = \frac{V_{TH}}{R_N} = \frac{V_{TH}}{R_{TH}}$$

$$R_N = R_{TH} = \frac{V_{oc}}{I_{sc}}$$

Norton Theory

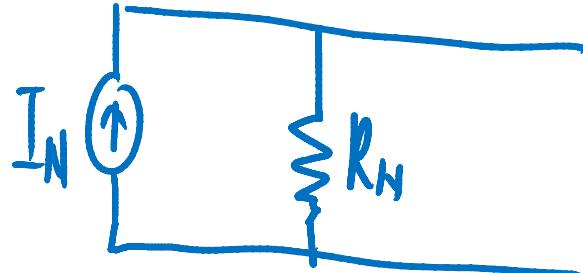


- Any two terminal linear circuit can be replaced with a current source in parallel with a resistance which will produce the same effects at the terminals.
- I_N is short circuit current I_{sc} of the circuit that the Norton equivalent circuit is replacing.
- R_N is the ratio of V_{oc} to the short circuit current I_{sc} .
Or calculating the equivalent resistance after killing the sources.

Calculation of R_{TH} and R_N


$$R_N = R_{TH}$$

~~see~~ Set all sources to zero ("killing" the source)



Voltage source : replace with a wire

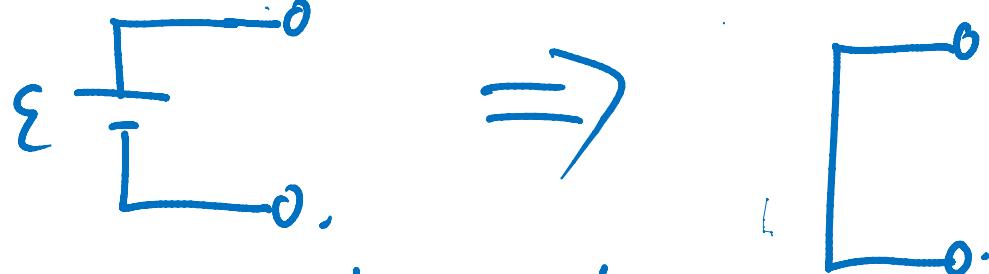

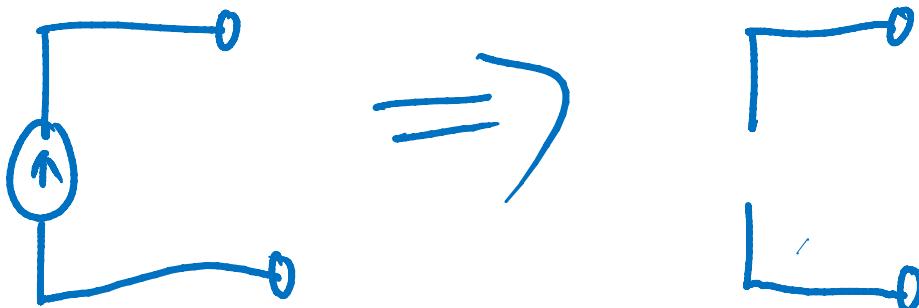Current Source : replace with open circuit




Example:

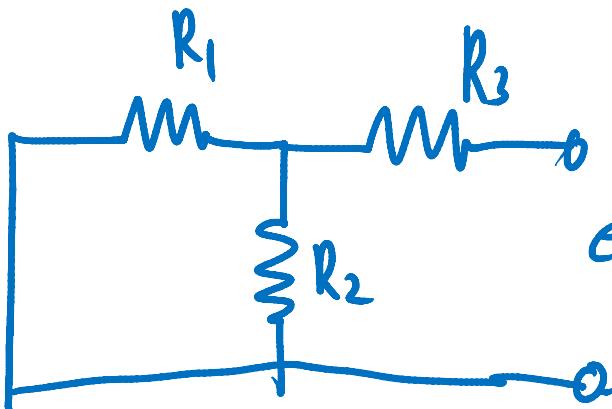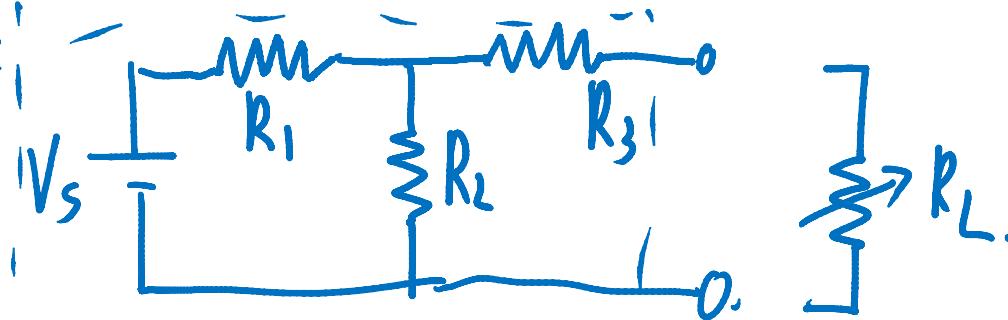


$$R_N = R_{TH} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

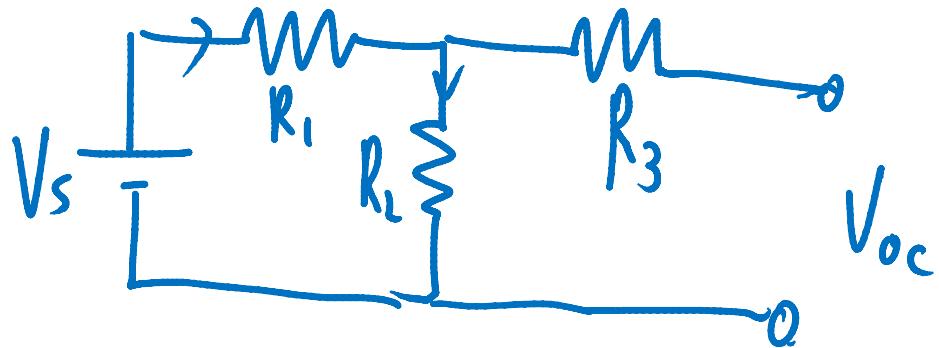Calculate $V_{TH} = V_{oc}$ open circuit voltage.



$$V_{oc} = V_{R_2} = V_s \cdot \frac{R_2}{R_1 + R_2} = V_{TH}$$


Thevenin equivalent:

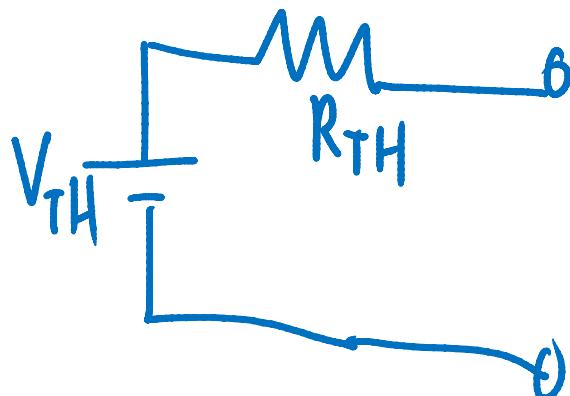

$$V_{TH} = V_s \cdot \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

Same network Do Norton equivalent.

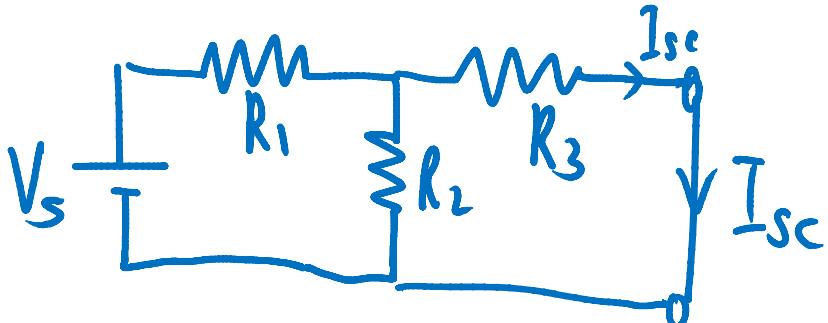


Calculate I_N (I_{sc})

$$I_{sc} = \left(\frac{V_s}{R_1 + R_2 // R_3} \right) \cdot \left(\frac{1/R_3}{1/R_2 + 1/R_3} \right)$$

$$= \frac{V_s}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \cdot \frac{R_2}{R_2 + R_3}$$


$$= \frac{V_s R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} = I_N$$
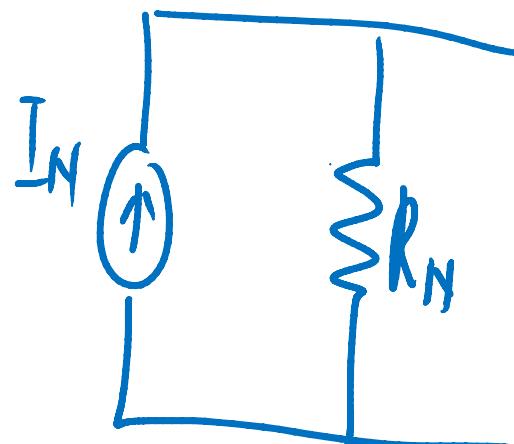
$$R_N = R_{TH} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$




$$\text{Verify } V_{TH} = I_N R_N$$

Example.

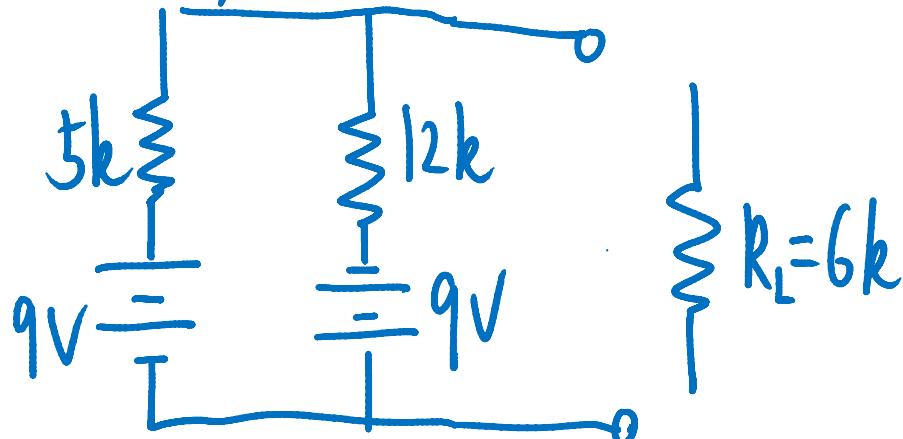


$$R_{TH} = R_N = R_{eq}$$

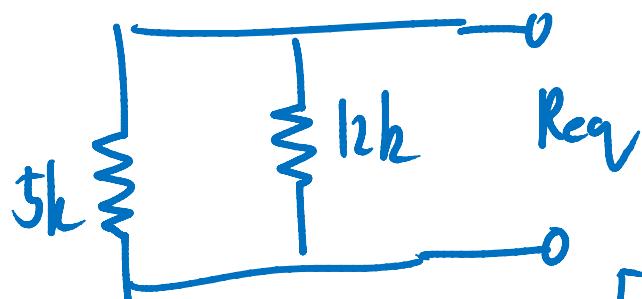

$$R_N = R_{TH} = 5k \parallel 12k = \frac{5 \times 12}{5 + 12} = 3.53 \text{ k}\Omega$$

$$\therefore I_N = \frac{V_{TH}}{R_{TH}} = \frac{3.71}{3.53} = 1.05 \text{ mA}$$

$V_{oc} = ?$ open circuit voltage

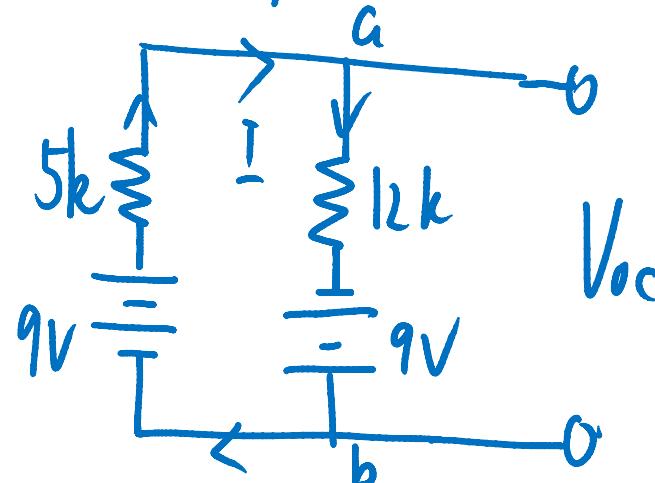

$$I = \frac{9+12}{5+12} = 1.06 \text{ mA}$$


$$V_{oc} = V_a - V_b \\ = \Delta V_{b-a}$$

$$= -9 + 12 \times (1.06)$$


$$= 3.71 \text{ V}$$

$$V_{TH} = 3.71 \text{ V}$$


Thevenin equivalent

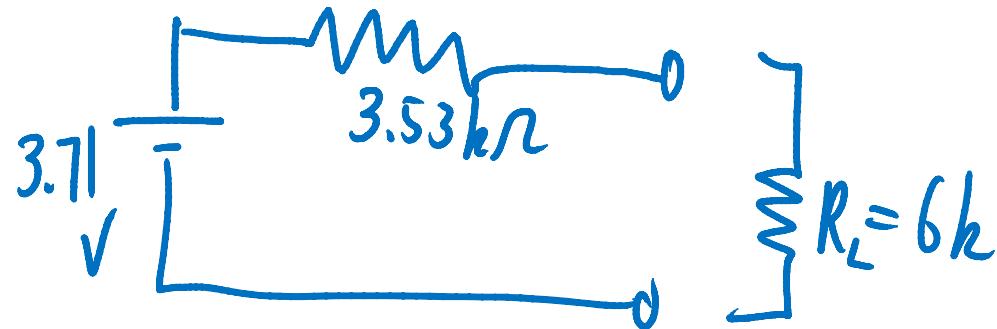

Norton equivalent

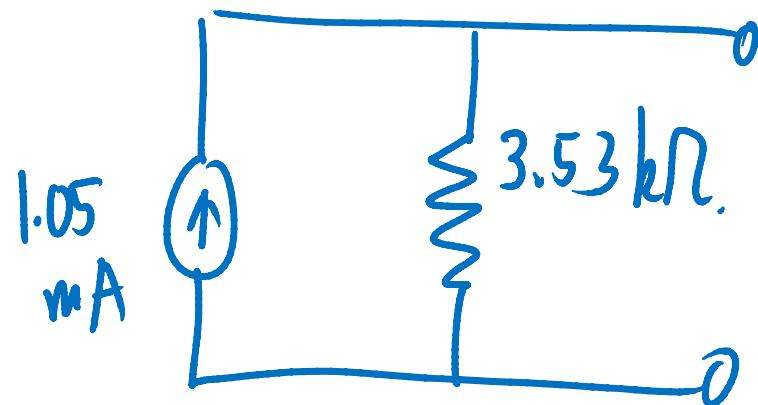

$I_{sc} = ?$ short circuit current

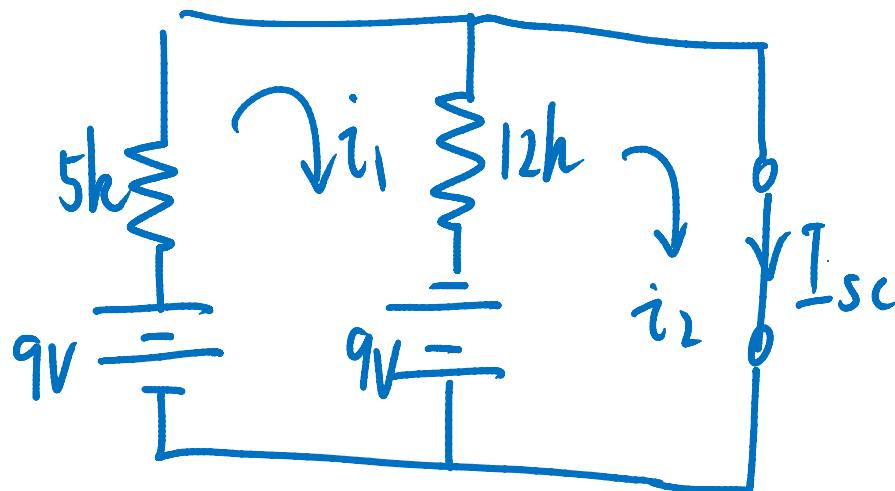

$$I_{sc} = i_2$$

$$17i_1 - 12i_2 = 18$$

$$12i_2 - 12i_1 = -9$$

$$I_N = I_{sc} = i_2 = 1.05 \text{ mA}$$