 



# Basic Language Concepts

# Describing Design Entities



- Primary programming abstraction is a *design entity*
  - Register, logic block, chip, board, or system
- What aspects of a digital system do we want to describe?
  - Interface: how do we connect to it
  - Function: what does it do?
 
# Describing the Interface: The Entity Construct




- The interface is a collection of *ports*
  - Ports are a new programming object: *signal*
  - Ports have a type, e.g., bit
  - Ports have a mode: in, out, inout (bidirectional)

# The Signal Object Type

- VHDL supports four basic objects: variables, constants, signals and file types (1993)
- Variable and constant types
  - Follow traditional concepts
- The signal object type is motivated by digital system modeling
  - Distinct from variable types in the association of time with values
  - Implementation of a signal is a sequence of time-value pairs!
    - Referred to as the driver for the signal

# Example Entity Descriptions

 


**entity** ALU32 **is**

```
port(      A, B: in bit_vector (31 downto 0);  
          C : out bit_vector (31 downto 0);  
          Op: in bit_vector (5 downto 0);  
          N, Z: out bit);
```

**end entity** ALU32;

MSB

LSB

 


**entity** D\_ff **is**

```
port(      D, Q, Clk, R, S: in bit;  
          Q, Qbar : out bit);
```

**end entity** D\_ff;
 
# Describing Behavior: The Architecture Construct




```
entity half_adder is  
port (a, b : in bit;  
       sum, carry : out bit);  
end entity half_adder;
```


```
architecture behavioral of half_adder is  
begin  
  sum <= (a xor b) after 5 ns;  
  carry <= (a and b) after 5 ns;  
end architecture behavior;
```

- Description of events on output signals in terms of events on input signals: the *signal assignment* statement
- Specification of propagation delays
- Type **bit** is not powerful enough for realistic simulation: use the IEEE 1164 value system


# Example Entity Descriptions: IEEE 1164

 
 
```
entity ALU32 is
port(      A, B: in std_ulogic_vector (31 downto 0);
          C : out std_ulogic_vector (31 downto 0);
          Op: in std_ulogic_vector (5  downto 0);
          N, Z: out std_logic);
end entity ALU32;
```


 
```
entity D_ff is
port(      D, Q, Clk, R, S: in std_ulogic;
          Q, Qbar : out std_ulogic);
end entity D_ff;
```



```
library IEEE;  
use IEEE.std_logic_1164.all;
```

} Declarations for a  
design entity


```
entity half_adder is  
port (a, b : in std_ulogic;  
       sum, carry : out std_ulogic);  
end entity half_adder;
```


```
architecture behavioral of half_adder is  
begin  
    sum <= (a xor b) after 5 ns;  
    carry <= (a and b) after 5 ns;  
end architecture behavioral;
```

- Use of the IEEE 1164 value system requires inclusion of the library and package declaration statements



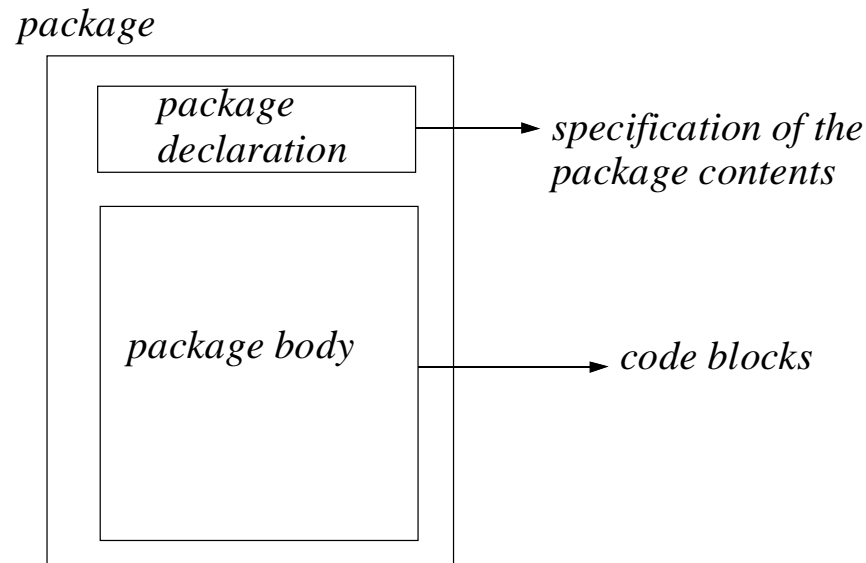- Libraries are logical units that are mapped to physical directories
- Packages are repositories for type definitions, procedures, and functions



 

- Separate the specification of the interface from that of the implementation
  - An entity may have multiple architectures
- Configurations associate an entity with an architecture
  - Binding rules: default and explicit
- Use configurations (more later!)

- *Primary* design units
  - Entity
  - Configuration
  - Package Declaration
  - These are not dependent on other design units
- *Secondary* design units
  - Package body
  - Architecture
- Design units are created in design files
- Now you know the layout of a VHDL program!

# A VHDL Model Template

```
library library-name-1, library-name-2;  
use library-name-1.package-name.all;  
use library-name-2.package-name.all;
```

} Declare external libraries and visible components

```
entity entity_name is  
port(      input signals : in type;  
         output signals : out type);  
end entity entity_name;
```

} Define the interface

```
architecture arch_name of entity_name is
```

```
-- declare internal signals
```

```
-- you may have multiple signals of different types
```

```
signal internal-signal-1 : type := initialization;
```

```
signal internal-signal-2 : type := initialization;
```

} Declare signals used to connect components

```
begin
```

```
-- specify value of each signal as a function of other signals
```

```
internal-signal-1 <= simple, conditional, or selected CSA;
```

```
internal-signal-2 <= simple, conditional, or selected CSA;
```

} Definition of how & when *internal* signal values are computed

```
output-signal-1  <= simple, conditional, or selected CSA;
```

```
output-signal-2  <= simple, conditional, or selected CSA;
```

} Definition of how & when *external* signal values are computed

```
end architecture arch_name;
```

```

library IEEE;
use IEEE.std_logic_1164.all;
entity full_adder is
  port (in1, in2, c_in: in std_logic;
        sum, c_out: out std_logic);
end entity full_adder;


```

```



architecture dataflow of full_adder is
  signal s1, s2, s3 : std_logic;
  constant gate_delay: Time:= 5 ns;
begin
  L1: s1 <= (In1 xor In2) after gate_delay;
  L2: s2 <= (c_in and s1) after gate_delay;
  L3: s3 <= (In1 and In2) after gate_delay;
  L4: sum <= (s1 xor c_in) after gate_delay;
  L5: c_out <= (s2 or s3) after gate_delay;
end architecture dataflow;

```


} Declarations

 

- The *constant* programming object
  - Values cannot be changed
- Use of *signals* in the architecture
  - Internal signals connect components
- A statement is executed when an event takes place on a signal in the RHS of an expression
  - 1-1 correspondence between signal assignment statements and signals in the circuit
  - Order of statement execution follows propagation of events in the circuit
  - Textual order **does not** imply execution order

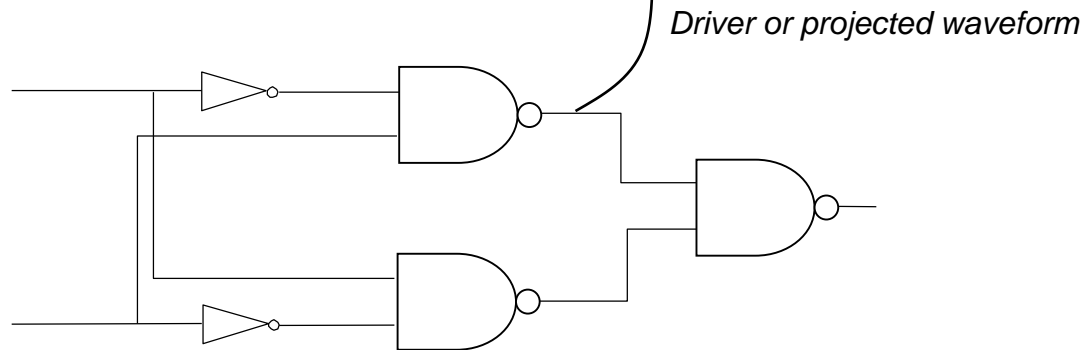 

 **$s \leq (\text{In1 nand In2}) \text{ after gate\_delay}$**



In the absence of initialization, default values are determined by signal type

Waveform elements describe time-value pairs


*Transactions* are internal representations of signal value assignments

- Events correspond to new signal values

- A transaction may lead to the same signal value




# Implementation of Signals (cont.)

 


- *Driver* is set of future signal values: current signal value is provided by the transaction at the head of the list
- We can specify multiple waveform elements in a single assignment statement
  - Specifying multiple future values for a signal
- Rules for maintaining the driver
  - Conflicting transactions

# Example: Waveform Generation

 

`signal <= '0','1' after 10 ns,'0' after 20 ns,'1' after 40 ns;`

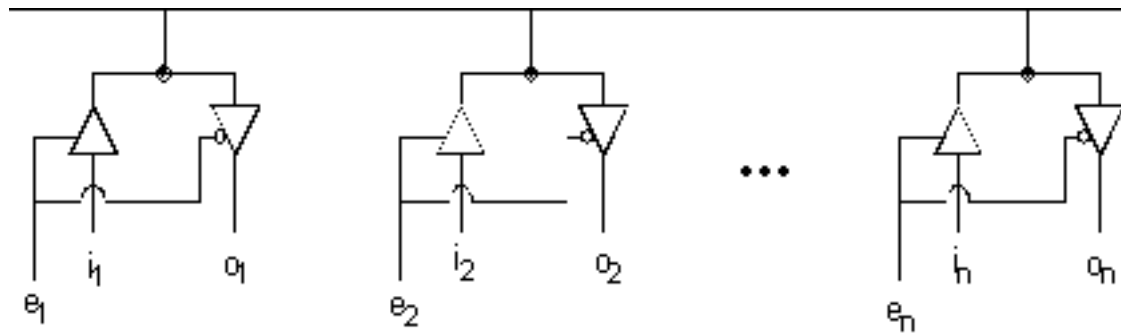- Multiple waveform elements can be specified in a single signal assignment statement
- Describe the signal transitions at future point in time
  - Each transition is specified as a waveform element



- At any point in time what is the value of the bus signal?
- We need to “resolve” the value
  - Take the value at the head of all drivers
  - Select one of the values according to a resolution function
- Predefined IEEE 1164 resolved types are `std_logic` and `std_logic_vector`

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
Sel: in std_logic_vector(1 downto 0);
Z : out std_logic_vector (7 downto 0));
end entity mux4;
architecture behavioral of mux4 is
begin
Z <= In0 after 5 ns when Sel = "00" else
In1 after 5 ns when Sel = "01" else
In2 after 5 ns when Sel = "10" else
In3 after 5 ns when Sel = "11" else
"00000000" after 5 ns;
end architecture behavioral;
```

*note type*

Evaluation Order is important!

- First true conditional expression determines the output value

```

library IEEE;
use IEEE.std_logic_1164.all;
entity pr_encoder is
port (S0, S1,S2,S3: in std_logic;
Z : out std_logic_vector (1 downto 0));
end entity pr_encoder;
architecture behavioral of pr_encoder is
begin
Z <=      “00” after 5 ns when S0 = ‘1’ else
          “01” after 5 ns when S1 = ‘1’ else
          unaffected when S2 = ‘1’ else
          “11” after 5 ns when S3 = ‘1’ else
          “00” after 5 ns;
end architecture behavioral;

```

- “unaffected”: Value of the signal is not changed.

```

library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
Sel: in std_logic_vector(1 downto 0);
Z : out std_logic_vector (7 downto 0));
end entity mux4;
architecture behavioral-2 of mux4 is
begin
with Sel select
Z <= (In0 after 5 ns) when "00",
(In1 after 5 ns) when "01",
(In2 after 5 ns) when "10",
(In3 after 5 ns) when "11"
(In3 after 5 ns) when others;
end architecture behavioral;

```

← All options must be covered and only one must be true!


- The “when others” clause can be used to ensure that all options are covered
- The “unaffected” clause may also be used here

- Inertial delay
  - Default delay model
  - Suitable for modeling delays through devices such as gates
- Transport Delay
  - Model delays through devices with very small inertia, e.g., wires
  - All input events are propagated to output signals
- Delta delay
  - What about models where no propagation delays are specified?
  - Infinitesimally small delay is automatically inserted by the simulator to preserve correct ordering of events
 
# VHDL simulation cycle

- The current time  $T_c$  is set to  $T_n$ ;
- Each active signal is updated; as result of signal updates events are generated.
- Each process that was suspended waiting on signal events that occurred in this simulation cycle resumes; processes also resume which were waiting for a certain, completed, time to elapse;
- Each resumed process executes until it suspends;
- The time  $T_n$  of the next simulation cycle is determined as the earliest of the following three time values:
  - 1. TIME'HIGH;
  - 2. The next time at which a driver becomes active
  - 3. The next time at which a process resumes;






- *signal* <= **reject** *time-expression inertial value-expression* **after** *time-expression*;
- Most general form of a waveform element

```

architecture transport_delay of half_adder is
signal s1, s2: std_logic:= '0';
begin
  s1 <= (a xor b) after 2 ns;
  s2 <= (a and b) after 2 ns;
  sum <= transport s1 after 4 ns;
  carry <= transport s2 after 4 ns;
end architecture transport_delay;

```

 

```


library IEEE;
use IEEE.std_logic_1164.all;
entity combinational is
  port (In1, In2: in std_logic;
        z : out std_logic);
end entity combinational;

```


```

architecture behavior of combinational
  signal s1, s2, s3, s4: std_logic:= '0';
begin
  s1 <= not In1;
  s2 <= not In2;
  s3 <= not (s1 and In2);
  s4 <= not (s2 and In1);
  z <= not (s3 and s4);
end architecture behavior;

```

 

# Delta Delays: Behavior

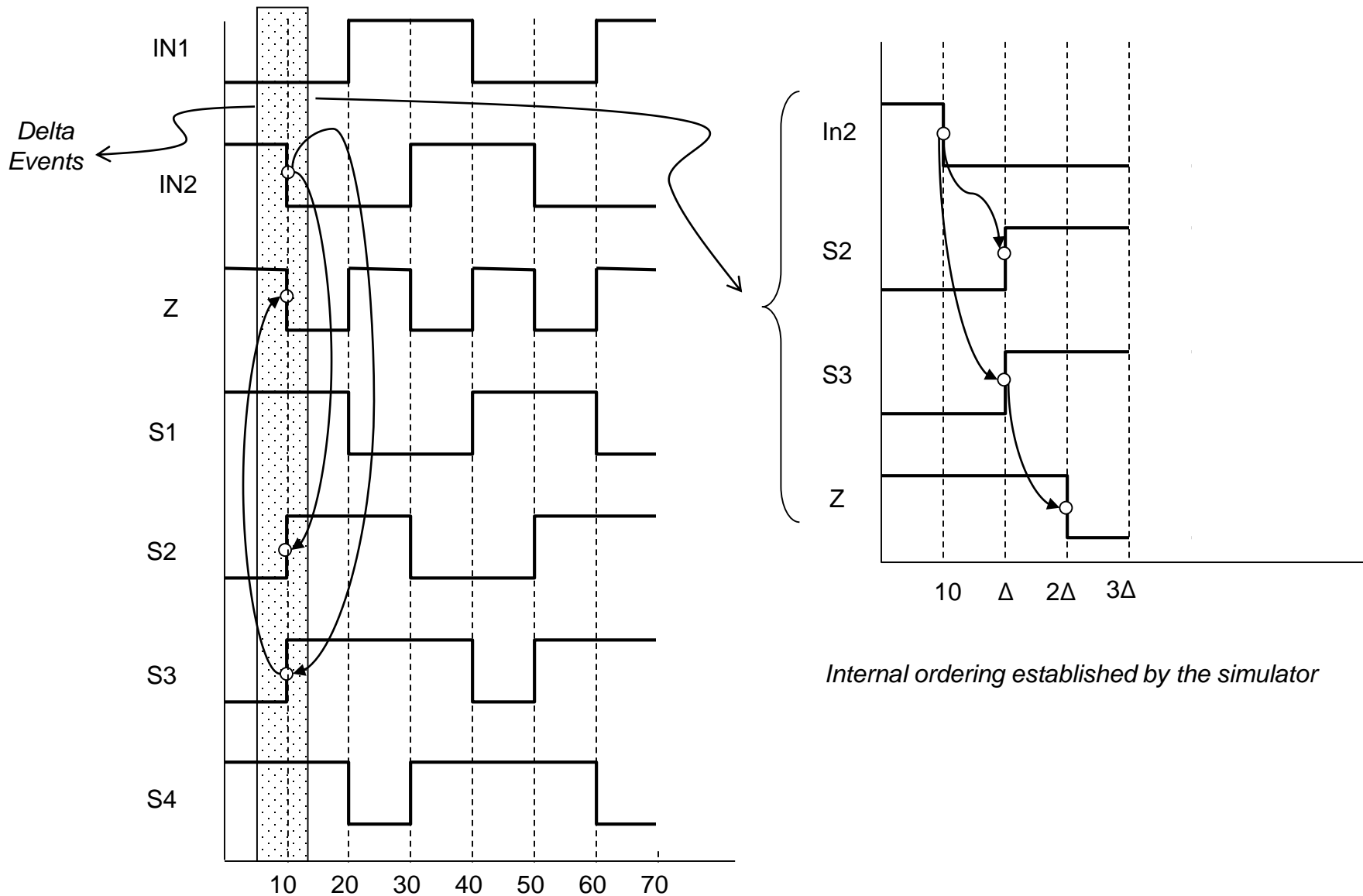

- Delay models
  - Inertial
    - For devices with inertia such as gates
    - VHDL 1993 supports pulse rejection widths
  - Transport
    - Ensures propagation of all events
    - Typically used to model elements such as wires
  - Delta
    - Automatically inserted to ensure functional correctness of code blocks that do not specify timing
    - Enforces the data dependencies specified in the code

- Primary unit of abstraction is a design entity
- Design units include
  - Primary design units
    - entity, configuration, package declaration
  - Secondary design units
    - architecture, package body
- Concurrent signal assignment statements
  - Simple, selected, conditional
  - Can be coalesced to form models of combinational circuits