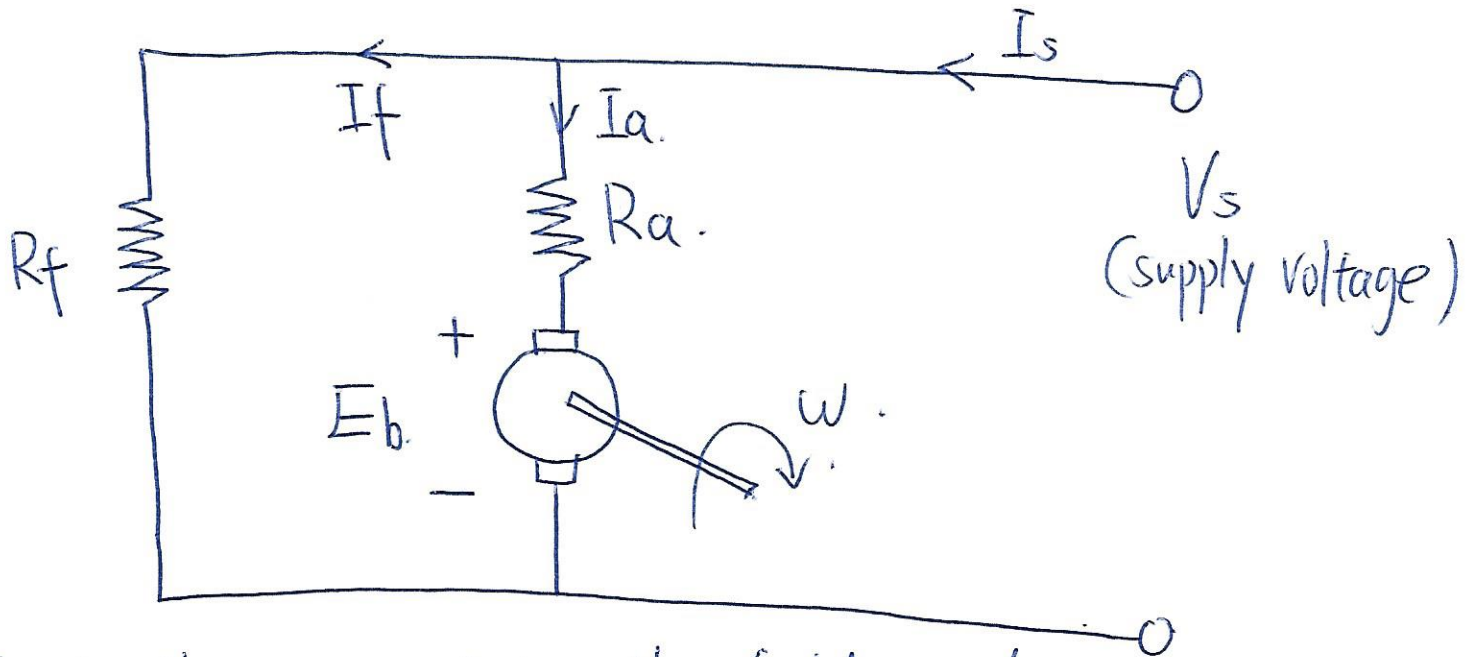


D.C. motors.

More specifically D.C. shunt motors



I_f is the current into the field windings on stator,
 R_f is the field winding resistance.

I_a is the current into the armature windings,
 R_a is the armature winding resistance.

V_s is the supply voltage; I_s is supply current,
 E_b is the back emf. caused by armature
~~rotation~~ inside magnetic flux.
rotation.

Basic equations

$$E_b = k_a \phi \omega. \quad (1)$$

torque $T = k_a \phi I_a. \quad (2).$ developed torque.

$$V_s = E_b + I_a R_a. \quad (3).$$

$$I_s = I_f + I_a. \quad (4).$$

k_a is armature constant. (determined by the geometry and configuration of armature windings)

ϕ is the magnetic flux $\phi \propto I_f$

Eq. (1) comes from $\mathcal{E} = B l v$. motional emf.

Eq. (2) comes from $F = B i l$. Ampere force.

Additional formulas

$$P = T \omega. \quad (5) \text{ mechanical power delivered.}$$

in analogy to $P = F \cdot v$ for linear motion.

$$P = E_b I_a. \quad (6). \text{ electrical power into the } \text{motor} \text{ armature.}$$

$$T \omega = E_b I_a. \quad \text{energy conserved.}$$

Units. for variables

T : N-m

ω : Standard unit: rad/s

Conventional unit: rpm

$$1 \text{ rpm} = \frac{2\pi}{60} \text{ rad/s}$$

ϕ : Weber. (Wb).

k_a : dimensionless

P : Standard unit: W.

Conventional unit: hp.

$$1 \text{ hp} = 746 \text{ W.}$$

From Eq (3),
$$I_a = \frac{V_s - E_b}{R_a}$$

Using ~~From~~ Eq (1),
$$I_a = \frac{V_s - k_a \phi \omega}{R_a}$$


From Eq. (2),
$$I_a = \frac{T}{k_a \phi}$$

$$\therefore \frac{T}{k_a \phi} = \frac{V_s - k_a \phi \omega}{R_a}$$

$$T = \frac{V_s k_a \phi}{R_a} - \frac{k_a^2 \phi^2}{R_a} \omega$$


$$T = \frac{k_a \phi}{R_a} (V_s - k_a \phi \omega)$$

torque - speed.
relation.

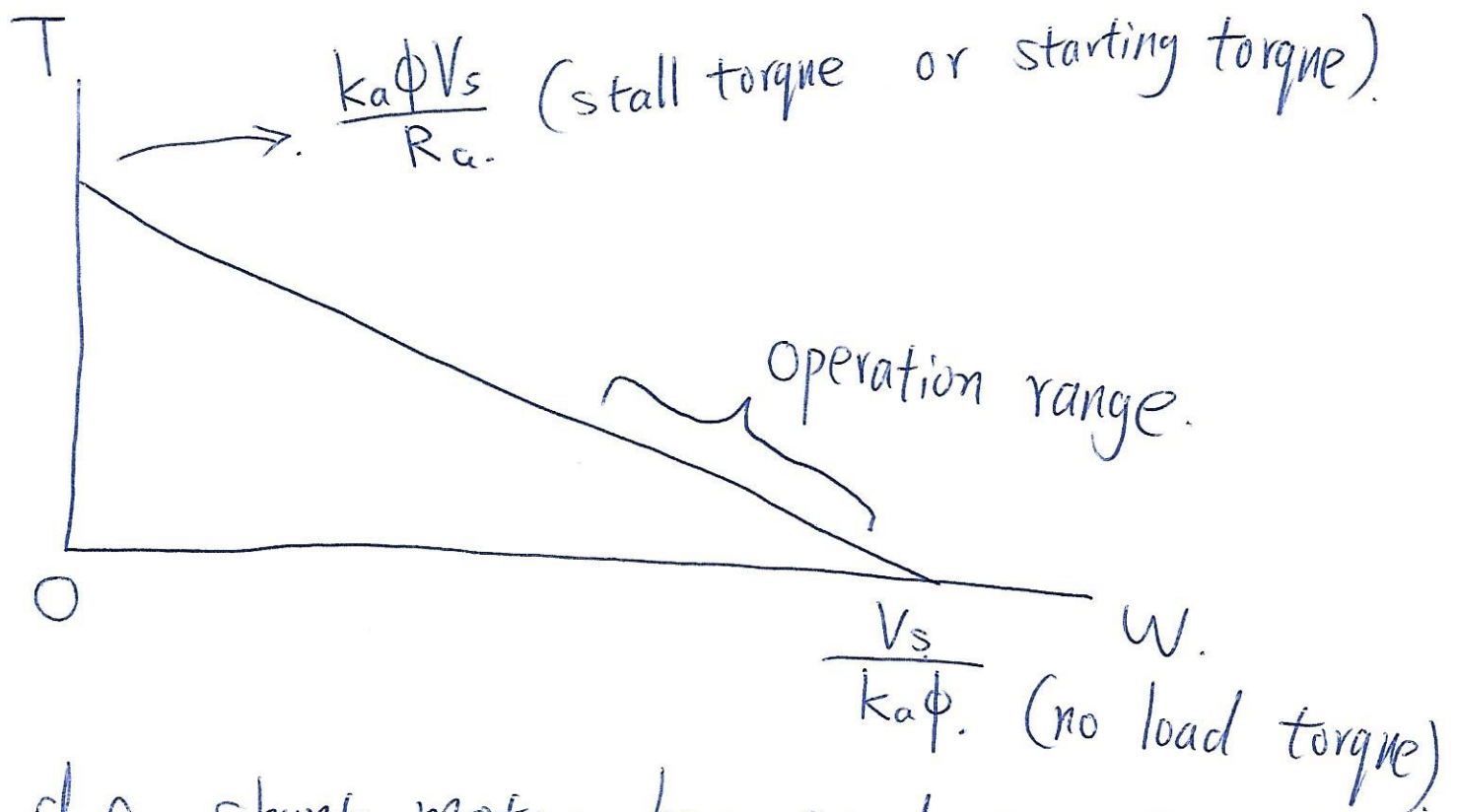


d.c. shunt motor has good speed regulation.
 Offers nearly constant speed.

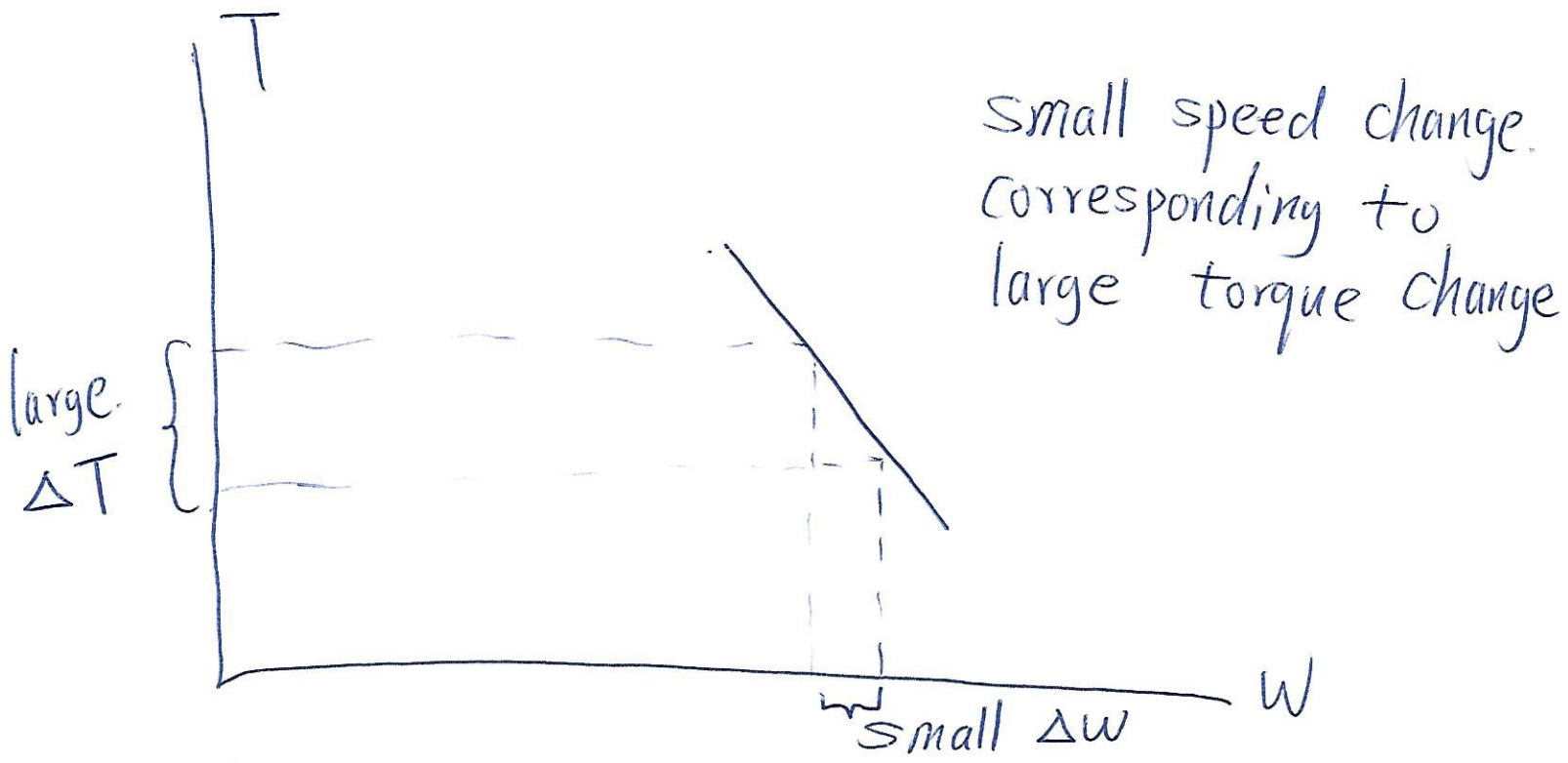R_a is usually very small. Therefore the slope of $T-\omega$ curve is large.




- dc shunt motor is good for applications that require a constant speed.
- Increase of load torque \rightarrow decrease of ω
 \rightarrow decrease of $E_b (= k_a \phi \omega)$ \rightarrow increase of I_a ,
 \rightarrow increase of torque.
 It is self-regulating
- Small R_a . So. $E_b = V_s - I_a R_a$ is nearly constant unless I_a is very large.

* Match d.c. shunt motor to a load.

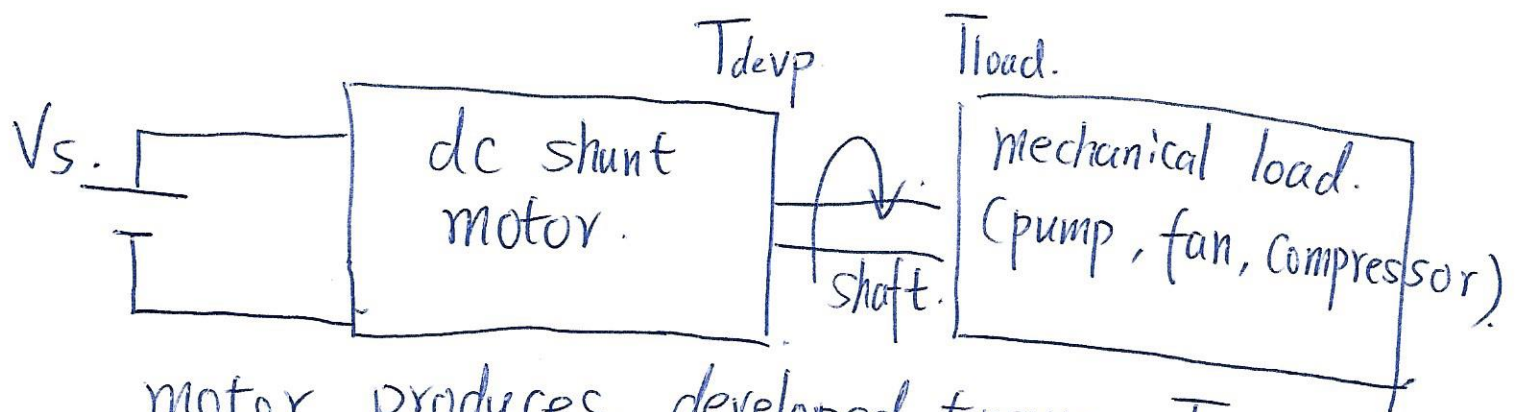


motor produces developed torque: T_{dev} .
 load requires speed-dependent torque: T_{load} .

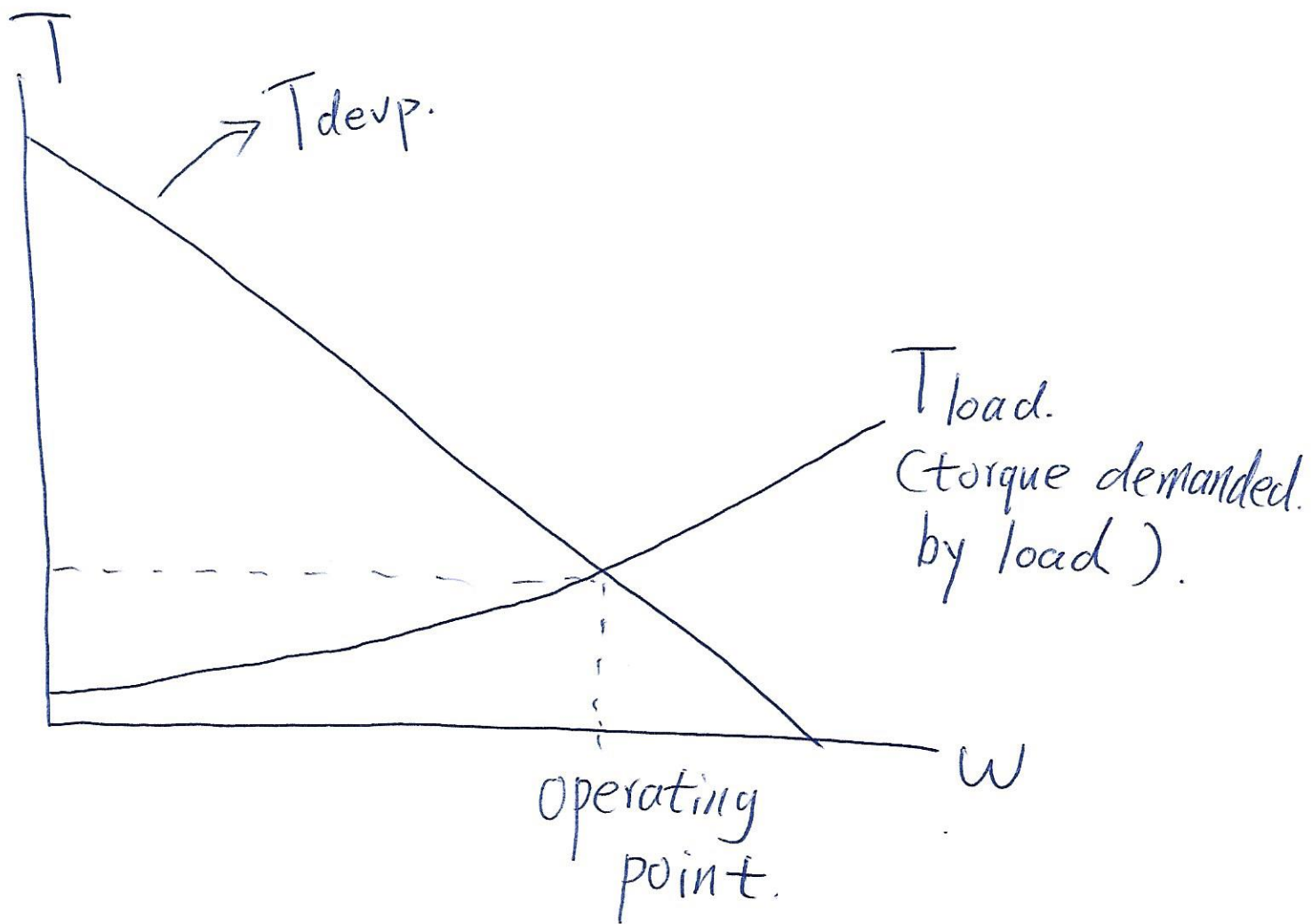$T_{dev} - \omega$ curve.
 $T_{load} - \omega$ curve. are different.



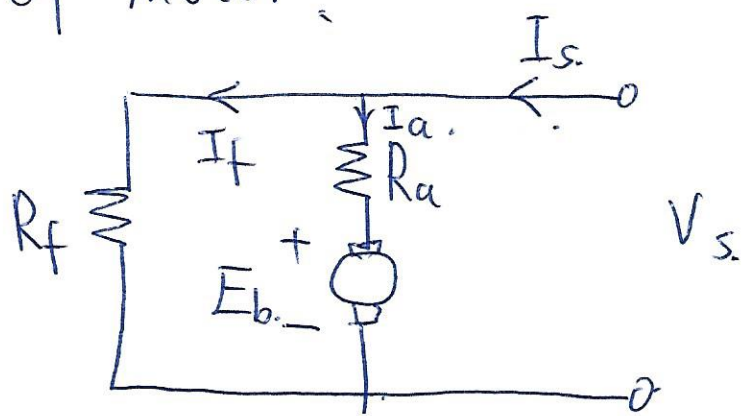Example.

D.C. Shunt motor is driven by $V_s = 240V$.
The source current is $I_s = 30A$, and the
field current $I_f = 1.4A$. Armature resistance
is $R_a = 0.6 \Omega$. Flux is $\phi = 0.020 Wb$.
Machine Constant is $k_a = 159.15$.
Find the speed (ω) and torque (T)
of motor.



$$I_a = I_s - I_f = 30 - 1.4 \\ = 28.6 A$$

$$E_b = V_s - I_a R_a$$

$$= 240 - 28.6 \times 0.6$$

$$= 222.8 (V)$$

$$E_b = k_a \phi \omega$$

$$\omega = \frac{E_b}{k_a \phi} = \frac{222.8}{159.15 \times 0.02}$$

$$= 70 \text{ rad/s.}$$


$$= 70 \times \frac{60}{2\pi} \text{ rpm.} = 669 \text{ rpm.}$$

$$T = k_a \phi I_a = 159.15 \times 0.02 \times 28.6 = 91 \text{ N.m.}$$

Example. A 200-V dc shunt motor draws 10A at 1800 rpm. The armature resistance is $R_a = 0.15\Omega$. Field winding resistance is $R_f = 350\Omega$. What is the torque and power developed by the motor?

$$V_s = 200\text{ V} \quad I_s = 10\text{ A} \quad R_a = 0.15\Omega$$

$$R_f = 350\Omega$$

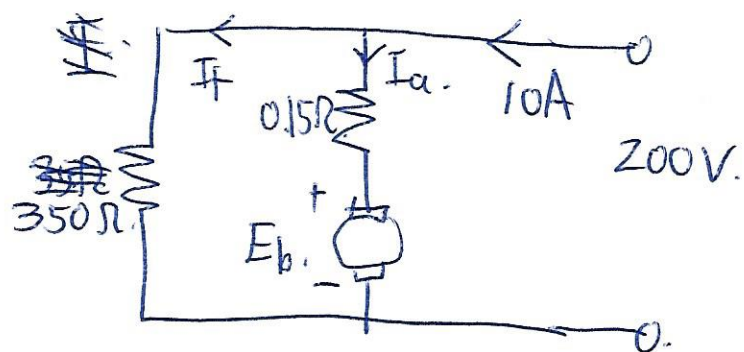

$$I_f = \frac{200\text{ V}}{350\Omega} = 0.571\text{ A}$$

$$I_a = 10 - 0.571 = 9.43\text{ A}$$

$$E_b = 200 - 9.43 \times 0.15 = 198.58\text{ V}$$

$$P = I_a E_b = T \omega \quad \omega = 1800 \times \frac{2\pi}{60} = 188.5 \frac{\text{rad}}{\text{s}}$$

$$T = \frac{I_a \cdot E_b}{\omega} = \frac{9.43 \times 198.58}{188.5} = 9.93\text{ (N}\cdot\text{m)}$$

$$P = I_a E_b = T \omega = 1872\text{ (W)} = 2.51\text{ hp}$$

You could also use $E_b = k_a \phi \omega$ to calculate $k_a \phi$ first.
Then use $T = k_a \phi I_a$ to calculate T .

Example. dc shunt motor

$$V_s = 7.2V \quad R_f = 12\Omega \quad R_a = 0.2\Omega$$

Motor draws a total current of 8.6 A when speed is 120 rpm.

- (1) Calculate torque ^{and power.} at 120 rpm.
(2) Calculate no-load speed.

$$I_f = \frac{7.2}{12} = 0.6 A$$

$$I_a = 8.6 - 0.6 = 8.0 A$$

$$E_b = 7.2 - 8.0 \times 0.2 = 5.6 (V)$$

$$E_b = k_a \phi \omega \quad \omega = 120 \times \frac{2\pi}{60} = 12.57 \left(\frac{\text{rad}}{s}\right)$$

$$k_a \phi = \frac{E_b}{\omega} = \frac{5.6}{12.57} = 0.445 (Wb)$$

$$T = k_a \phi I_a = 0.445 \times 8.0 = 3.56 (N.m)$$

Here you can ~~also~~ also calculate power at 120 rpm

$$P = I_a E_b = T \omega = 44.7 (W) = 0.06 hp$$

"No-load" means $T' = 0$

$$\text{So } I_a' = 0 \quad \therefore E_b' = V_s = 7.2V$$

$$E_b' = k_a \phi \omega'$$

$$\omega' = \frac{E_b'}{k_a \phi} = \frac{7.2}{0.445} = 16.18 \frac{\text{rad}}{s} = 154 \text{ rpm}$$