

Problem 1

Find the phasor form of the following functions:

- a. $v(t) = 155 \cos(377t - 25^\circ) \text{ V}$
- b. $v(t) = 5 \sin(1000t - 40^\circ) \text{ V}$
- c. $i(t) = 10 \cos(10t + 63^\circ) + 15 \cos(10t - 42^\circ) \text{ A}$
- d. $i(t) = 460 \cos(500\pi t - 25^\circ) - 220 \sin(500\pi t + 15^\circ) \text{ A}$

Problem 2

Convert the following complex numbers to polar form:

- a. $4 + j4$
- b. $-3 + j4$
- c. $j + 2 - j4 - 3$

Problem 3

Convert the following to polar form and compute the product. Compare the result with that obtained using rectangular form.


- a. $(50 + j10)(4 + j8)$
- b. $(j2 - 2)(4 + j5)(2 + j7)$

Problem 4

Determine the equivalent impedance in the circuit shown below.

$$v_s(t) = 7 \cos\left(3,000t + \frac{\pi}{6}\right) \text{ V}$$

$R_1 = 2.3 \text{ k}\Omega$, $R_2 = 1.1 \text{ k}\Omega$, $L = 190 \text{ mH}$, and $C = 55 \text{ nF}$.

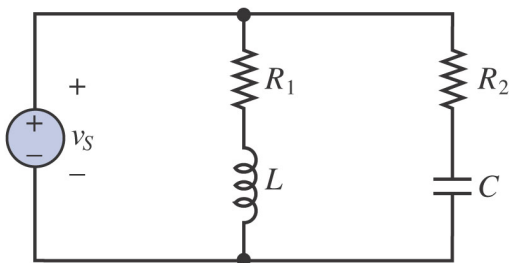

Problem 5


Determine the current through Z_3 in the circuit below.

$$v_{s1} = v_{s2} = 170 \cos(377t) \text{ V}$$

$$Z_1 = 5.9 \angle 0.122 \text{ } \Omega$$

$$Z_2 = 2.3 \angle 0 \text{ } \Omega$$


$$Z_3 = 17 \angle 0.192 \text{ } \Omega$$

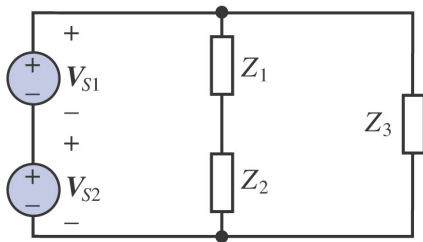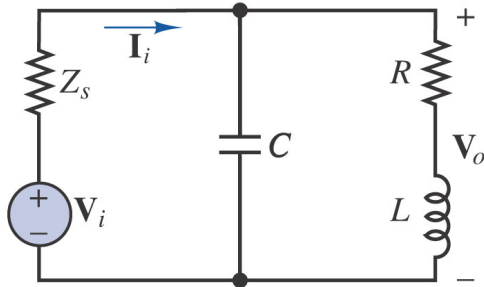**Problem 6**


Determine the frequency so that the current I_i and voltage V_o in the circuit below are in phase.

$$Z_s = 13,000 + j\omega 3 \text{ } \Omega$$

$$R = 120 \text{ } \Omega, L = 19 \text{ mH, and } C = 220 \text{ pF}$$


**Problem 7**

Use phasor techniques, solve for the current in the circuit below.

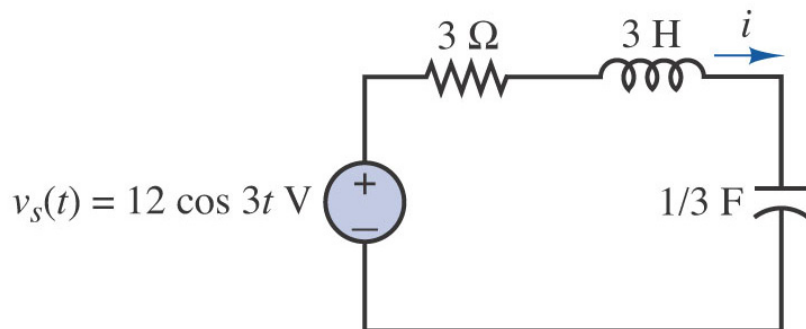

Problem 8

Use phasor techniques, solve for v in the circuit below

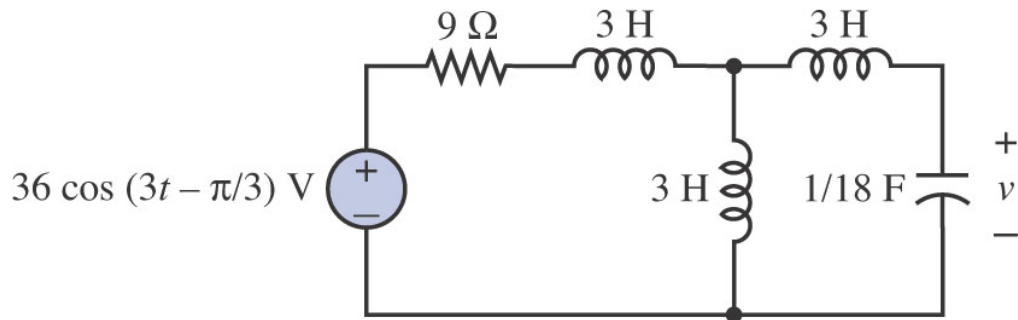**Problem 9**

Use the phasor techniques, solve for i in the circuit below.

