 


Study guide for the second exam

1. Analyze the sequential circuit shown below. Assume the registers are edge triggered with $t_{clk-q, \max} = 4ns$, $t_{clk-q, \min} = 2ns$, $t_{setup} = 1ns$, and $t_{hold} = 1ns$:



- What is the maximum operating frequency of this system if there is no skew and jitter?
- What is the maximum random clock skew that this system can tolerate?

Solution:

$$(1) \quad T > t_{clk-q, \max} + t_{logic, \max} + t_{setup}$$

$$T > 4ns + 25ns + 1ns = 30ns$$

$$T > 4ns + 20ns + 1ns = 25ns$$

$$\Rightarrow F_{clk, \max} = 33.3MHz$$

$$(2) \quad t_{skew} + t_{hold} < t_{clk-q, \min} + t_{logic, \min}$$

$$t_{skew} < 2ns + 5ns - 1ns = 6ns$$

$$t_{skew} < 2ns + 8ns - 1ns = 9ns$$








$$\Rightarrow t_{skew, \max} = 6ns$$

$$F = \frac{1}{T}$$

2. Consider a 5 mm-long, 1-micron wide metal2 wire in a 0.6 m process. The sheet resistance is 0.08 ohms/square, and the capacitance is 0.2 fF / m. Construct a 3-segment PI-model for the wire.

$$R = R_0 \frac{L}{W} = 0.08 \cdot \frac{5 \times 10^{-3}}{1 \times 10^{-6}} = 0.08 \times 5000 = 400 \Omega$$

       3. A 10x unit-sized inverter drives a 2x inverter at the end of the 5 mm wire from Exercise 2. Assume 1X inverter has input capacitance of 6fF and output resistance of 10KOhm. Estimate the propagation delay using the Elmore delay model; neglect diffusion capacitance.



$$0.1\mu F \quad 0.1\mu F \quad T \rightarrow$$

$$D = RC$$

$$R_1 \cdot C_1 + (R_1 + R_2) \cdot C_2 + (R_1 + R_2 + \dots + R_n) C_n$$

$$1k \cdot 0.1\mu F + (1.4k) 0.1\mu F + 6.4k \cdot 0.12\mu F$$

Example

- Compute the sheet resistance of a 0.22 μm thick Cu wire in a 65 nm process. The resistivity of thin film Cu is $2.2 \times 10^{-8} \Omega \cdot \text{m}$. Ignore dishing.

$$R_w = \frac{\rho}{t} = \frac{2.2 \times 10^{-8} \Omega \cdot \text{m}}{0.22 \times 10^{-6} \text{m}} = 0.1 \frac{\Omega}{\square}$$

- Find the total resistance if the wire is 0.125 μm wide and 1 mm long. Ignore the barrier layer.

$$R = R_w \cdot \frac{L}{W} = 0.1 \frac{1}{0.125 \times 10^{-3}} = 800 \Omega$$


15: Wires

CMOS VLSI Design 4th Ed.

13

Wire RC Delay

 - Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 1 mm wire. Assume wire capacitance is 0.2 fF/ μm and that a unit-sized inverter has $R = 10 \text{ K}\Omega$ and $C = 0.1 \text{ fF}$.



15: Wires


CMOS VLSI Design 4th Ed.

19

$$D = 100 \text{ fF} (1000 \Omega) + 100 \text{ fF} (1800 \Omega) + 0.6 \text{ fF} (1800 \Omega) =$$




RC

 


Study guide for the second exam

 4. A four-bit carry ripple adder (CRA) built from four full-bit adders is shown below. [10]





 A four-bit carry-save adder (CSA) built from four full-bit adders is shown below.



Suppose we want to add four 4-bit words (e.g. $0001 + 0111 + 1101 + 0010 = 10111$). The left-side schematic shows how to do this using three CPA adders. The right-side schematic shows how to do this using two CSA adders and one CRA adder. How many full-bit adders does each circuit use? Assume that a full-adder has the longest propagation delay from any input to any output of T_0 , what is the propagation delay for each circuit?

1 full adder $p_d = t_0$

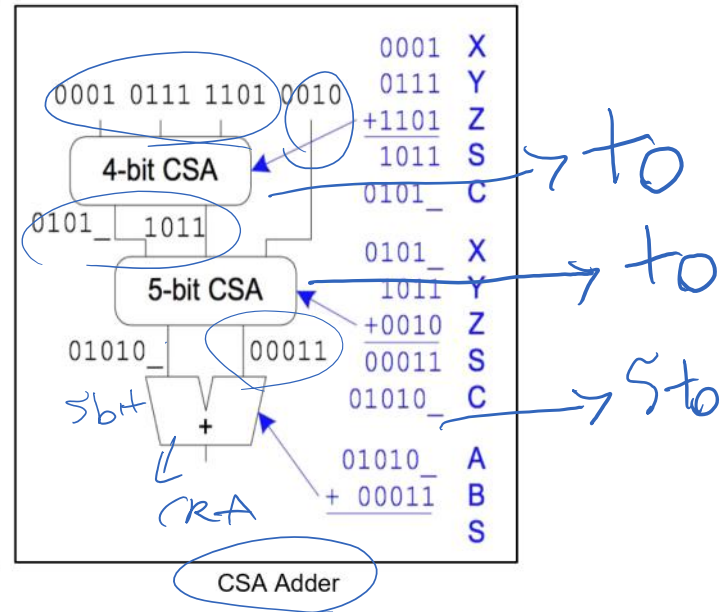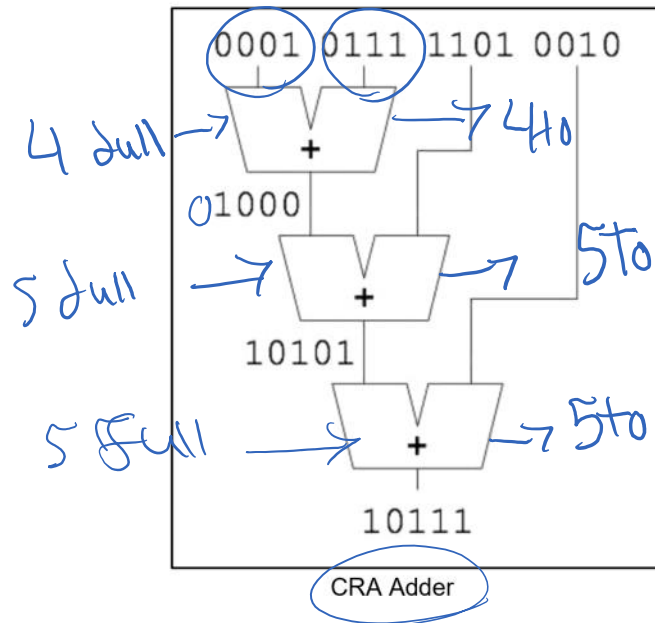

Full adders in CRA adder = 14

Full adders in CSA adder = 14

Propagation delay for CRA adder = 14 t_0


Propagation delay for CSA adder = 7 t_0

Study guide for the second exam

5. Suppose you want to multiply two 4-bit numbers. The circuit to realize this is shown below. How many full-bit adders does this circuit use? Assume that a full-adder has propagation delay from any input to any output of T_0 , and "and" gate delay of T_1 , what is the propagation delay for the highlighted critical path? [5]

1100	:	12_{10}	multiplicand
0100	:	5_{10}	
1100			partial products
0000			
1100			
0000			product
00111100	:	60_{10}	

full adder
 $Pd = T_0$
 and $Pd = T_1$

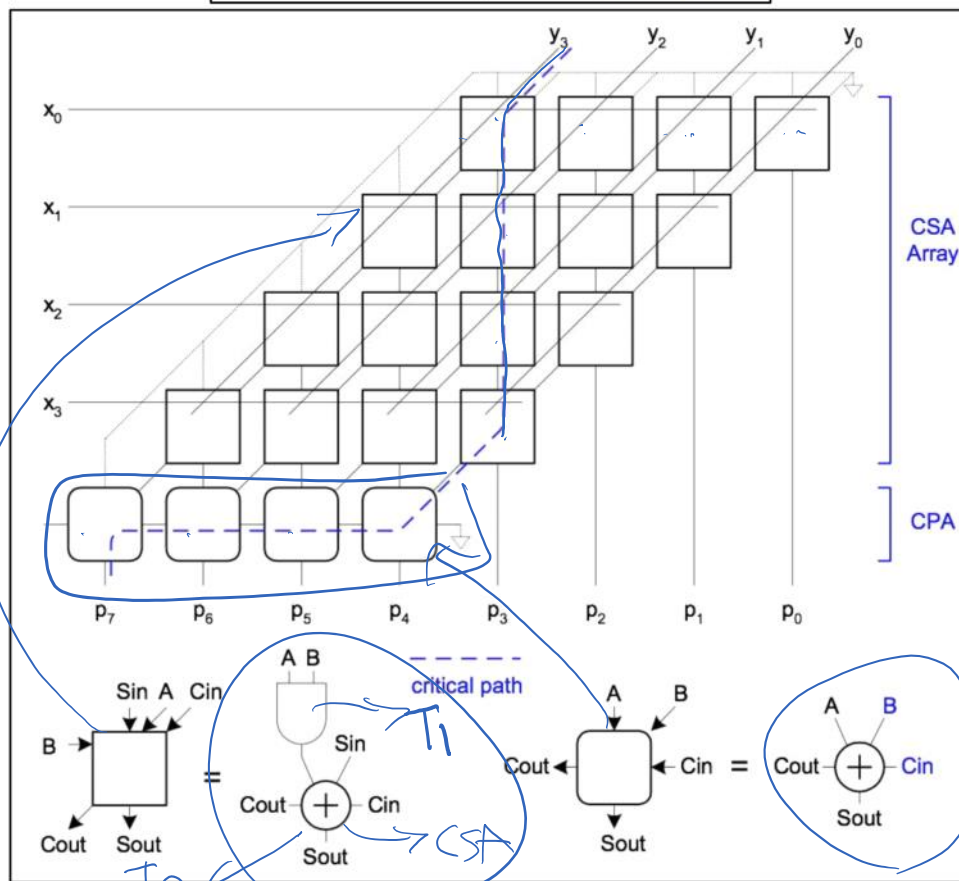

Full adders in four-bit multiplier = 20

Propagation delay for four-bit multiplier = _____

$$4 \cdot T_1 + 4T_0 + 4T_0 = 8T_0 + 4T_1$$

$$4(T_1 + T_0)$$

Timing Diagrams

Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time


Combinational Logic


D Flip-Flop

D Latch

14: Sequential Circuits CMOS VLSI Design 4th Ed. 19

t_{pd}	Logic Propagation Delay	Longest delay from input A to output Y in logic block
t_{cd}	Logic Contamination Delay	Shortest
t_{pcq}	Latch/Flop Clk->Q Prop. Delay	Longest delay from CLK to Q
t_{ccq}	Latch/Flop Clk->Q Cont. Delay	Shortest
t_{pdq}	Latch D->Q Prop. Delay	Longest delay from D to Q
t_{cdq}	Latch D->Q Cont. Delay	Shortest
t_{setup}	Latch/Flop Setup Time	how long data must be stable before edge of clk
t_{hold}	Latch/Flop Hold Time	how long data stable AFTER CLK edge

 

 

Multiplication

□ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ \underline{0101} : 5_{10} \\ 1100 \\ 00000 \\ 11000 \\ 000000 \\ \hline 0111100 \end{array}$$

multiplier
partial products
product

□ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product