

Problem 1

Solution:

Known quantities:

Schematic of the circuit shown in Figure P2.74; for part b: value of R_p and current displayed on the ammeter.

Find:

The current i ; the internal resistance of the meter.

Assumptions:

$$r_a \ll 50 \text{ k}\Omega$$

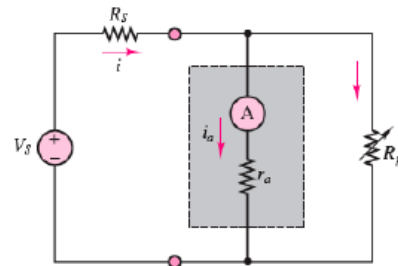


Figure P2.74

Analysis:

a) Assuming that $r_a \ll 50 \text{ k}\Omega$

$$i \approx \frac{V_s}{R_s} = \frac{12}{50000} = 240 \text{ }\mu\text{A}$$

b) With the same assumption as in part a)

$$i_{\text{meter}} = 150 \cdot (10)^{-6} = \frac{R_p}{r_a + R_p} i$$

or:


$$150 \cdot (10)^{-6} = \frac{15}{r_a + 15} 240 \cdot 10^{-6}$$

Therefore, $r_a = 9 \text{ }\Omega$.

Problem 2

Model: The wires and batteries are ideal.

Visualize:

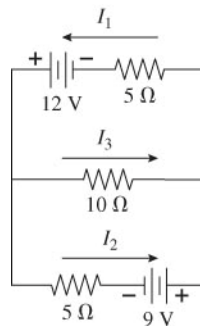

Solve: Assign currents I_1 , I_2 , and I_3 as shown in the figure. If I_3 turns out to be negative, we'll know it really flows right to left.

Apply Kirchhoff's loop rule counterclockwise to the top loop from the top right corner:

$$-I_1 (5 \text{ }\Omega) + 12 \text{ V} - I_3 (10 \text{ }\Omega) = 0.$$

Apply the loop rule counterclockwise to the bottom loop starting at the lower left corner:

$$-I_2 (5 \text{ }\Omega) + 9 \text{ V} + I_3 (10 \text{ }\Omega) = 0.$$

Note that since we went against the current direction through the (10 Ω) resistor the potential increased. Apply the junction rule to the right middle:


$$I_1 = I_2 + I_3.$$

These three equations can be solved for the current I_3 by subtracting the second equation from the first then making the substitution $I_2 - I_1 = -I_3$ which was derived from the third equation. The result is $I_3 = \frac{3}{25}$ A = 0.12 A, left to right.

Problem 3

Model: The wires and batteries are ideal.

Visualize:

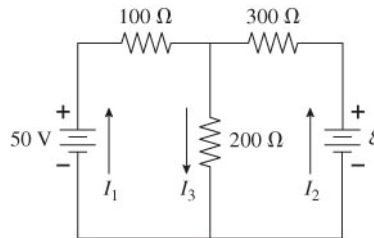

Solve: If no power is dissipated in the 200 Ω resistor, the current through it must be zero. To see if this is possible, set up Kirchhoff's rules for the circuit, then assume the current through the 200 Ω resistor is zero and see if there is a solution.

Assume the unknown battery is oriented with its positive terminal at the top and currents I_1 , I_2 , I_3 defined as shown in the figure above. Apply Kirchhoff's loop rule clockwise to the left loop:

$$50 \text{ V} - I_1 (100 \Omega) - I_3 (200 \Omega) = 0$$

Again, counterclockwise to the right hand loop:

$$\mathcal{E} - I_2 (300 \Omega) - I_3 (200 \Omega) = 0$$

The junction rule yields

$$I_1 + I_2 = I_3.$$

Now assume $I_3 = 0$ and solve for \mathcal{E} . In that case, the first equation gives

$$I_1 = \frac{50 \text{ V}}{100 \Omega} = \frac{1}{2} \text{ A}.$$

From the third equation, $I_2 = -I_1$, so the second equation gives us

$$\mathcal{E} = I_2 (300 \Omega) = \left(-\frac{1}{2} \text{ A} \right) (300 \Omega) = -150 \text{ V}$$

Thus $\mathcal{E} = 150 \text{ V}$ and it is oriented with negative terminal on top, opposite to our guess.