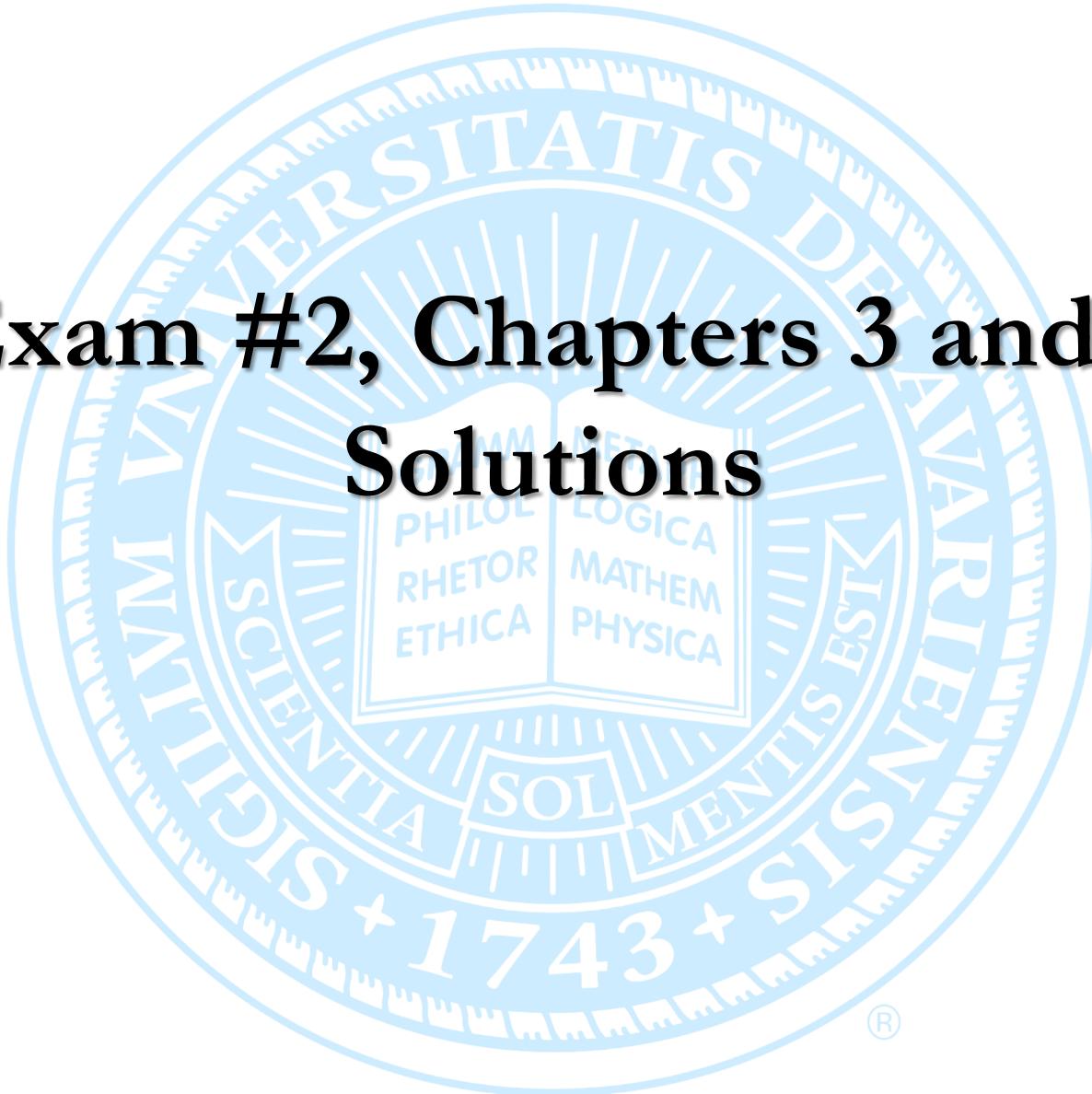




# Exam #2, Chapters 3 and 4 Solutions





# I. Vocabulary/Symbols

A. Anode	H. Dopant	O. Rectification	V.
B. Bipolar	I. Drift	P. Scale or Saturation	W.
C. Boron	J. Intrinsic	Q. Thermal Voltage	X.
D. Carbon	K. Mobility	R. Transfer Characteristic	Y.
E. Cathode	L. Phosphorus	S. Transfer Function	Z.
F. Depletion Region	M. Platinum	T. Tunnel Diode	
G. Diffusion	N. Quiescent	U.	

Definitions:

**J** Term for an undoped semiconductor.

**G** Type of current flow in a semiconductor due to variations in carrier concentration.

**I** Type of current flow in a semiconductor due to electric field.



# I. Vocabulary/Symbols

A. Anode	H. Dopant	O. Rectification	V.
B. Bipolar	I. Drift	P. Scale or Saturation	W.
C. Boron	J. Intrinsic	Q. Thermal Voltage	X.
D. Carbon	K. Mobility	R. Transfer Characteristic	Y.
E. Cathode	L. Phosphorus	S. Transfer Function	Z.
F. Depletion Region	M. Platinum	T. Tunnel Diode	
G. Diffusion	N. Quiescent	U.	

Definitions:

C Most common type of p-type dopant in silicon.

L Most common type of n-type dopant in silicon.

F Name of the region that is generated at the interface of a pn junction.



# I. Vocabulary/Symbols

A. Anode	H. Dopant	O. Rectification	V.
B. Bipolar	I. Drift	P. Scale or Saturation	W.
C. Boron	J. Intrinsic	Q. Thermal Voltage	X.
D. Carbon	K. Mobility	R. Transfer Characteristic	Y.
E. Cathode	L. Phosphorus	S. Transfer Function	Z.
F. Depletion Region	M. Platinum	T. Tunnel Diode	
G. Diffusion	N. Quiescent	U.	

Definitions:

**O** Process of converting an AC signal into a DC signal.

**N** Steady state, or DC, operating point.

**R** The output voltage as a function of input voltage.



# I. Vocabulary/Symbols

A. Anode	H. Dopant	O. Rectification	V.
B. Bipolar	I. Drift	P. Scale or Saturation	W.
C. Boron	J. Intrinsic	Q. Thermal Voltage	X.
D. Carbon	K. Mobility	R. Transfer Characteristic	Y.
E. Cathode	L. Phosphorus	S. Transfer Function	Z.
F. Depletion Region	M. Platinum	T. Tunnel Diode	
G. Diffusion	N. Quiescent	U.	

Definitions:

W Symbol for a Zener diode.

U Symbol for a light emitting diode.

V Symbol for a photodiode.



## II. Determining the change in forward bias voltage

A diode is forward biased such that the forward current is much greater than the saturation current. Find the change in voltage,  $\Delta V$ , across the diode when the current changes by a factor of 20. Use 25 mV for  $V_T$ .

$$I_D = I_S(e^{V_D/V_T} - 1)$$

For case where  $i \gg I_S$  the curve can be approximated by  $I_D \simeq I_S e^{V_D/V_T}$

$$V_D = V_T \ln \frac{I_D}{I_S}$$

At diode voltage  $V_1$      $I_1 = I_S e^{V_1/V_T}$

$$\frac{I_2}{I_1} = e^{(V_2-V_1)/V_T}$$

At diode voltage  $V_2$      $I_2 = I_S e^{V_2/V_T}$

$$\Delta V = V_2 - V_1 = V_T \ln \frac{I_2}{I_1} = 25\text{mV} \times \ln(20) = 74.89\text{mV}$$

$$\text{or } \Delta V = V_2 - V_1 = 2.3V_T \log \frac{I_2}{I_1} = 57.5\text{mV} \times \log(20) = 74.81\text{mV}$$



### III. Short Answer

- |   |   |
|---|---|
| 1. Number of free carriers per cm <sup>3</sup> ( $n_i$ ) at room temperature. | 1. <u>1.5 x10<sup>10</sup></u>            |
| 2. Number of free carriers per cm <sup>3</sup> ( $n_i$ ) at 0 K.              | 2. <u>0</u>                               |
| 3. Room Temperature in Kelvin.  | 3. <u>300 K</u>                           |
| 4. Thermal voltage at room temperature.                                       | 4. <u><math>\sim 25</math> mV/25.9 mV</u> |



## IV. Doped Silicon (a)

Consider doped silicon with  $N_D = 10^{18}/\text{cm}^3$ . Find the electron and hole concentrations at  $T = 300$  K. Calculate the resistivity and conductivity of this material. Use  $\mu_n = 1110 \text{ cm}^2/\text{V}\cdot\text{s}$  and  $\mu_p = 400 \text{ cm}^2/\text{V}\cdot\text{s}$  for the doped silicon.

$$n_n \simeq N_D = 10^{18} \text{ cm}^{-3}$$

$$p_n \simeq \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10} \text{ cm}^{-3})^2}{10^{18} \text{ cm}^{-3}} = 225 \text{ cm}^{-3}$$

Majority carrier is electrons

$$\rho = \frac{1}{\sigma} = \frac{1}{q(p\mu_p + n\mu_n)}$$

Minority carrier is holes

$$= \frac{1}{1.6 \times 10^{-19} \text{ C} \left( \frac{225}{\text{cm}^3} \left( 400 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \right) + \frac{10^{18}}{\text{cm}^3} \left( 1100 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \right) \right)}$$

$$= \frac{1}{177.6 \frac{\text{C}}{\text{V}\cdot\text{s}\cdot\text{cm}}} = 0.00563 \Omega\cdot\text{cm}$$

$$\sigma = \frac{1}{\rho} = 177.6 \frac{\text{S}}{\text{cm}}$$



### III. Doped Silicon (b)

If the temperature increases to 394.36 K, the intrinsic carrier concentration increases to  $4.0 \times 10^{11} \text{ cm}^{-3}$ . What are the new carrier concentrations and the new resistivity at the higher temperature assuming the mobilities stay the same?

$$n_i = BT^{3/2} e^{-E_g/2kT} = 4.0 \times 10^{11} \text{ cm}^{-3} \text{ at } 349.36 \text{ K}$$

$$n_n \simeq N_D = 10^{18} \text{ cm}^{-3} \quad p_n \simeq \frac{n_i^2}{N_D} = \frac{(4.0 \times 10^{11} \text{ cm}^{-3})^2}{10^{18} \text{ cm}^{-3}} = 1.6 \times 10^5 \text{ cm}^{-3}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{q(p\mu_p + n\mu_n)}$$


$$= \frac{1}{1.6 \times 10^{-19} \text{ C} \left( \frac{1.6 \times 10^5}{\text{cm}^3} \left( 400 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \right) + \frac{10^{18}}{\text{cm}^3} \left( 1100 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \right) \right)}$$

$$= \frac{1}{177.6 \frac{\text{C}}{\text{V} \cdot \text{s} \cdot \text{cm}}} = 0.00563 \Omega \cdot \text{cm}$$


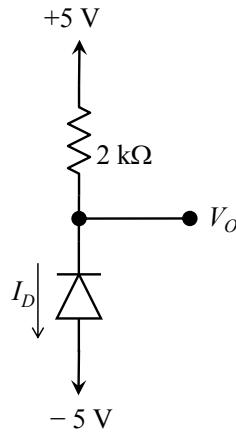
# V. Ideal and Constant Voltage Diodes

For the circuits shown below, find the values of the voltages and currents indicated using the ideal diode model and the constant voltage (0.7 V) model. **Make sure you include units.**




Ideal diode

$$V_O: +5 \text{ V}$$

constant  
voltage model

$$V_O: +5 \text{ V}$$

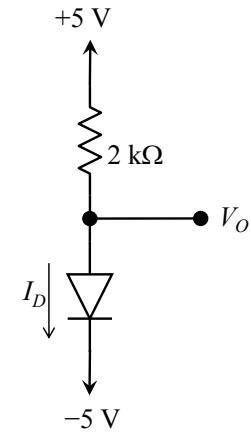


Ideal diode

$$V_O: -5 \text{ V}$$

constant  
voltage model

$$V_O: -4.3 \text{ V}$$

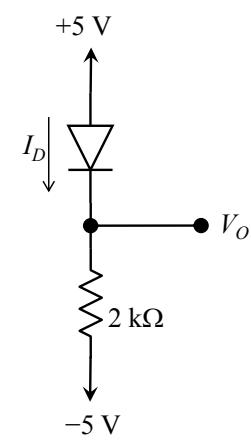

Ideal diode

$$V_O: 5 \text{ V}$$

constant  
voltage model

$$V_O: 4.3 \text{ V}$$

$$I_D: 0 \text{ mA}$$

$$I_D: 0 \text{ mA}$$

$$I_D: 5 \text{ mA}$$

$$I_D: 4.65 \text{ mA}$$


$$I_D: 5 \text{ mA}$$

$$I_D: 4.65 \text{ mA}$$


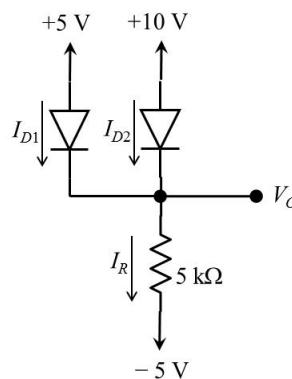
# VI. Ideal Diodes

For the circuits shown below, find the values of the voltages and currents indicated using the ideal diode model. **Make sure you include units.**




$$V_O: \underline{\hspace{2cm}}$$

$$I_{D1}: \underline{\hspace{2cm}}$$

$$I_{D2}: \underline{\hspace{2cm}}$$

$$I_R: \underline{\hspace{2cm}}$$

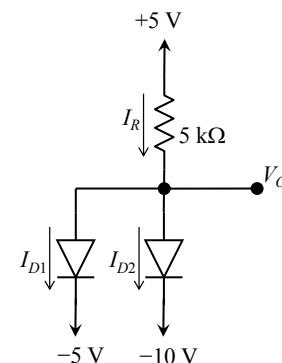


$$V_O: \underline{\hspace{2cm}}$$

$$I_{D1}: \underline{\hspace{2cm}}$$

$$I_{D2}: \underline{\hspace{2cm}}$$

$$I_R: \underline{\hspace{2cm}}$$

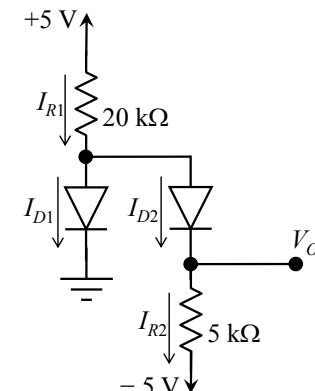

$$V_O: \underline{\hspace{2cm}}$$

$$I_{D1}: \underline{\hspace{2cm}}$$

$$I_{D2}: \underline{\hspace{2cm}}$$



$$I_{R1}: \underline{\hspace{2cm}}$$

$$I_{R2}: \underline{\hspace{2cm}}$$


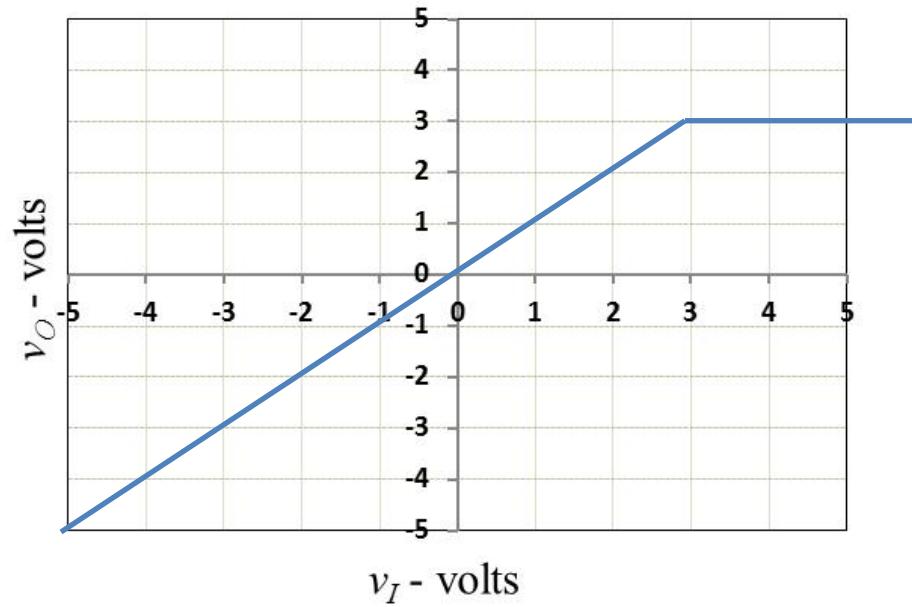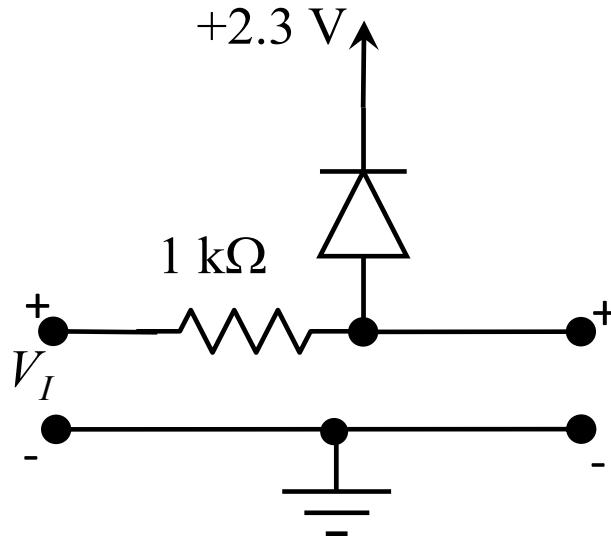
## VII. Limiting and Clamping Circuits



Sketch the transfer characteristic  $v_O$  versus  $v_I$ , for the limiter circuit shown below. All diodes begin conducting at a forward voltage drop of 0.5 V and have voltage drops of 0.7 V when conducting a current  $i_D \geq 1$  mA.




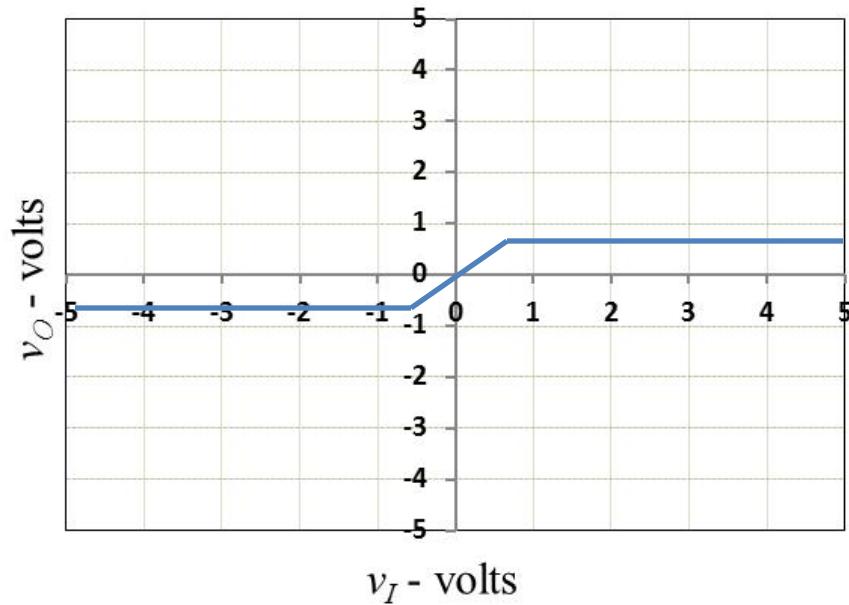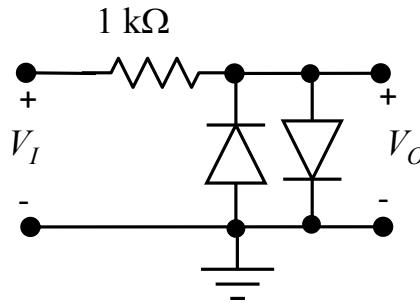
# VII. Limiting and Clamping Circuits


Sketch the transfer characteristic  $v_O$  versus  $v_I$ , for the limiter circuit shown below. All diodes begin conducting at a forward voltage drop of 0.5 V and have voltage drops of 0.7 V when conducting a current  $i_D \geq 1$  mA.




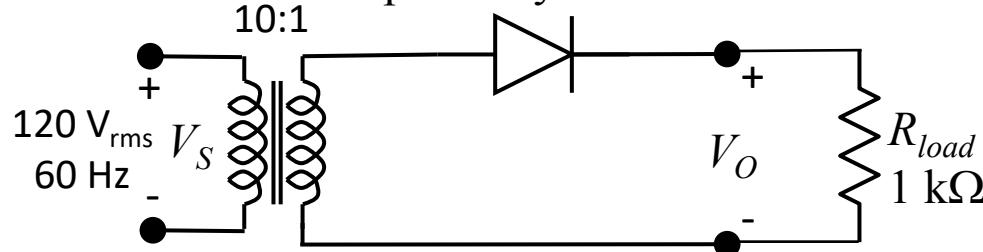
## VIII. Rectification

A half-wave rectifier circuit with a  $10\text{-k}\Omega$  load operates from a 120-V (rms) 60-Hz household supply through a 10-to-1 step-down transformer. It uses a silicon diode that can be modeled to have a 0.7-V drop for any current. Answer the following:



$V_{rms}$  out of transformer  $12V_{rms}$

$V_{opeak}$ :  $16.27V$

Fraction of a period diode is conducting 48.68% %

$I_{Lpeak}$ :  $16.27 \text{ mA}$

Max reverse bias voltage  $16.97 \text{ V}$

*Exam #2 Solutions*

$$V_{rms} = \frac{120V_{rms}}{10} = 12V_{rms}$$

$$V_{opeak} = \sqrt{2}(12V_{rms}) - V_D$$

$$V_{opeak} = 16.97 - 0.7 = 16.27V$$

$$V_s = 16.97V \times \sin \theta$$

$$V_s \geq 0.7V \text{ when}$$

$$\theta = \sin^{-1} \left( \frac{0.7}{16.97} \right) = 2.364^\circ \text{ or } 0.0412 \text{ rad}$$

$$\frac{\pi - 2\theta}{2\pi} = 48.68\%$$

$$I_{Lpeak} = \frac{V_{opeak}}{1k\Omega} = 16.27 \text{ mA}$$



# IX. Solving for the Q operating point

Assuming the availability of diodes for which  $V_D = 0.75$  V at  $I_D = 1.069$  mA, design a circuit that utilizes two identical diodes connected in series with a resistor  $R$  connected to a 24 V power supply. The voltage out,  $V_O$ , is to be 1.7 V. Use the exponential model to find  $I_D$  and  $R$ . Use 25 mV for  $V_T$ .

$$V_D = \frac{1.7V}{2} = 0.85V \quad I_D = I_S e^{V_D/V_T} \Rightarrow I_S = I_D e^{-V_D/V_T}$$

$$I_S = 1.069\text{mA} e^{-750\text{mV}/25\text{mV}} = 1 \times 10^{-16} \text{ A} = 0.1\text{fA}$$


$$V_D: \underline{850 \text{ mV}}$$

$$I_S: \underline{0.1 \text{ fA}}$$

$$I_D: \underline{58.365 \text{ mA}}$$

$$R: \underline{382 \Omega}$$
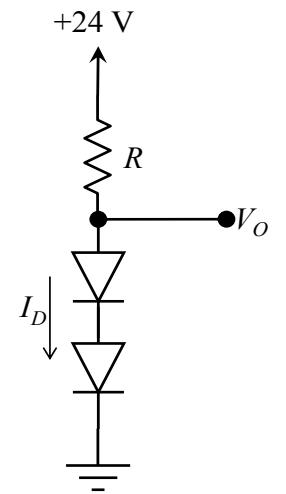
$$R = \frac{V_{DD} - V_O}{I_D} = \frac{24\text{V} - 1.7\text{V}}{58.365\text{mA}} = 382\Omega$$





# IX. Solving for the Q operating point


Assuming the availability of diodes for which  $V_D = 0.75$  V at  $I_D = 1.069$  mA, design a circuit that utilizes two identical diodes connected in series with a resistor  $R$  connected to a 24 V power supply. The voltage out,  $V_O$ , is to be 1.7 V. Use the exponential model to find  $I_D$  and  $R$ . Use 25 mV for  $V_T$ .

$$i_D = I_S e^{V_D/V_T} = (1 \times 10^{-16} \text{ A}) e^{800\text{mV}/25\text{mV}} = 7.9 \text{ mA}$$

$$R_d \text{ (per diode)}: \frac{0.428 \Omega}{r_d} = \frac{V_T}{I_D} = \frac{25\text{mV}}{53.86\text{mA}} = 0.428 \Omega$$


$$V_{op-p}: \underline{2.237\text{mV}}$$
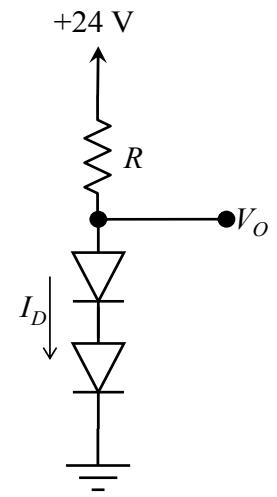
$$\begin{aligned} v_{op-p} &= v_{p-p} \frac{r_{dtotal}}{r_{dtotal} + R} = 1V_{pp} \frac{2 \times 0.428\Omega}{2 \times 0.428\Omega + 382\Omega} \\ &= 1V_{pp} \frac{0.856\Omega}{382.856\Omega} = 2.237\text{mV} \end{aligned}$$




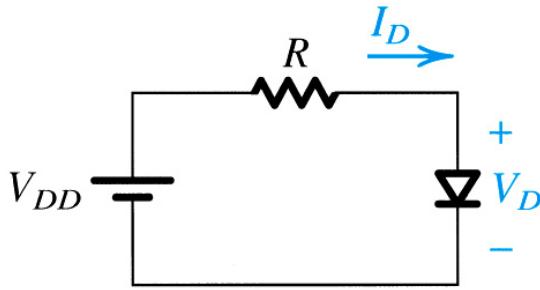
## X. Solve using the iterative technique



Assume that the diode in the circuit to the right has a current of 10 mA at a voltage of 0.75 V. Find the following with  $V_{DD} = 15$  V and  $R = 1$  k $\Omega$  using the iterative technique. Use 25 mV for  $V_T$ . Stop when there is no change  $> 1$  mV for  $V_D$ .


$$I_S = I_D e^{-V_D/V_T}$$

$$I_S = (10 \times 10^{-3} \text{ A}) e^{-750 \text{ mV} / 25 \text{ mV}}$$

$$= 9.36 \times 10^{-16} \text{ A}$$


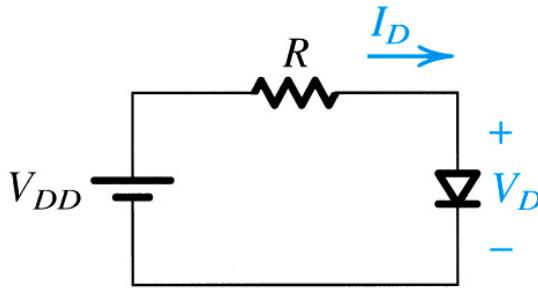
## X. Solve using the iterative technique



Assume that the diode in the circuit to the right has a current of 10 mA at a voltage of 0.75 V. Find the following with  $V_{DD} = 15$  V and  $R = 1$  k $\Omega$  using the iterative technique. Use 25 mV for  $V_T$ . Stop when there is no change > 1 mV for  $V_D$ .

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{15V - 0.75V}{1k\Omega} = 14.25mA$$

But 14.25 mA is more than the 10 mA specification current

$$V_2 - V_1 = V_T \ln \frac{I_2}{I_1}$$

$$V_2 = V_1 + V_T \ln \frac{I_2}{I_1}$$



$$V_2 = 750 \text{ mV} + (25 \text{ mV}) \ln \left( \frac{14.25 \text{ mA}}{10 \text{ mA}} \right) = 758.9 \text{ mV}$$

$$I_D = \frac{15V - 0.7589V}{1k\Omega} = 14.241mA$$

$$V_3 = 758.9 \text{ mV} + (25 \text{ mV}) \ln \left( \frac{14.241 \text{ mA}}{14.25 \text{ mA}} \right) = 758.9 \text{ mV}$$




# Iterative Solving

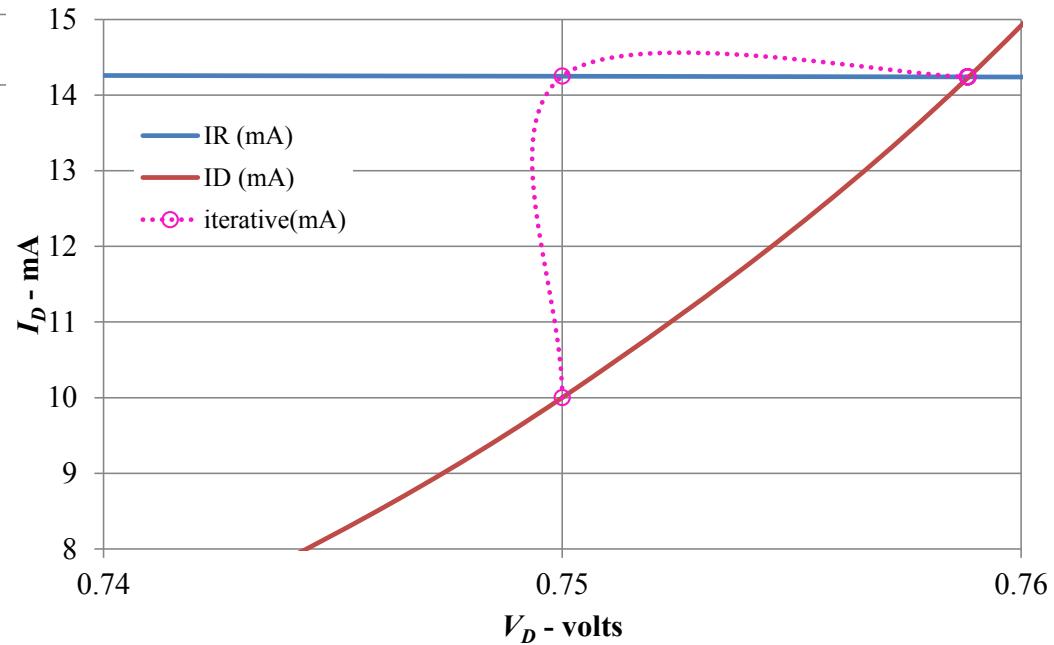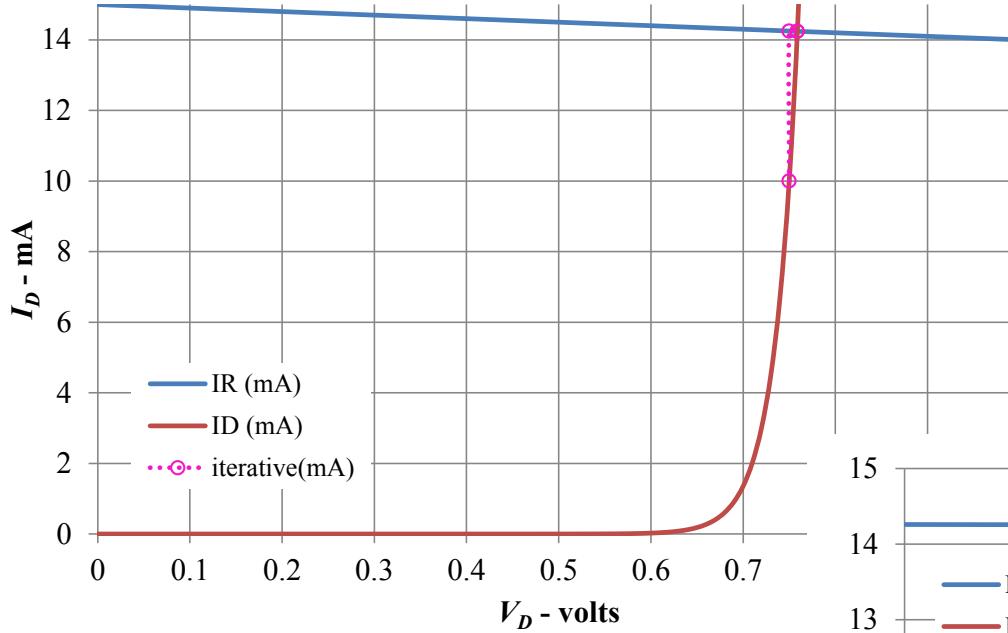



# Results


# Tests	92
Average	77.1 %
High	100% (3)
Low	26.5%

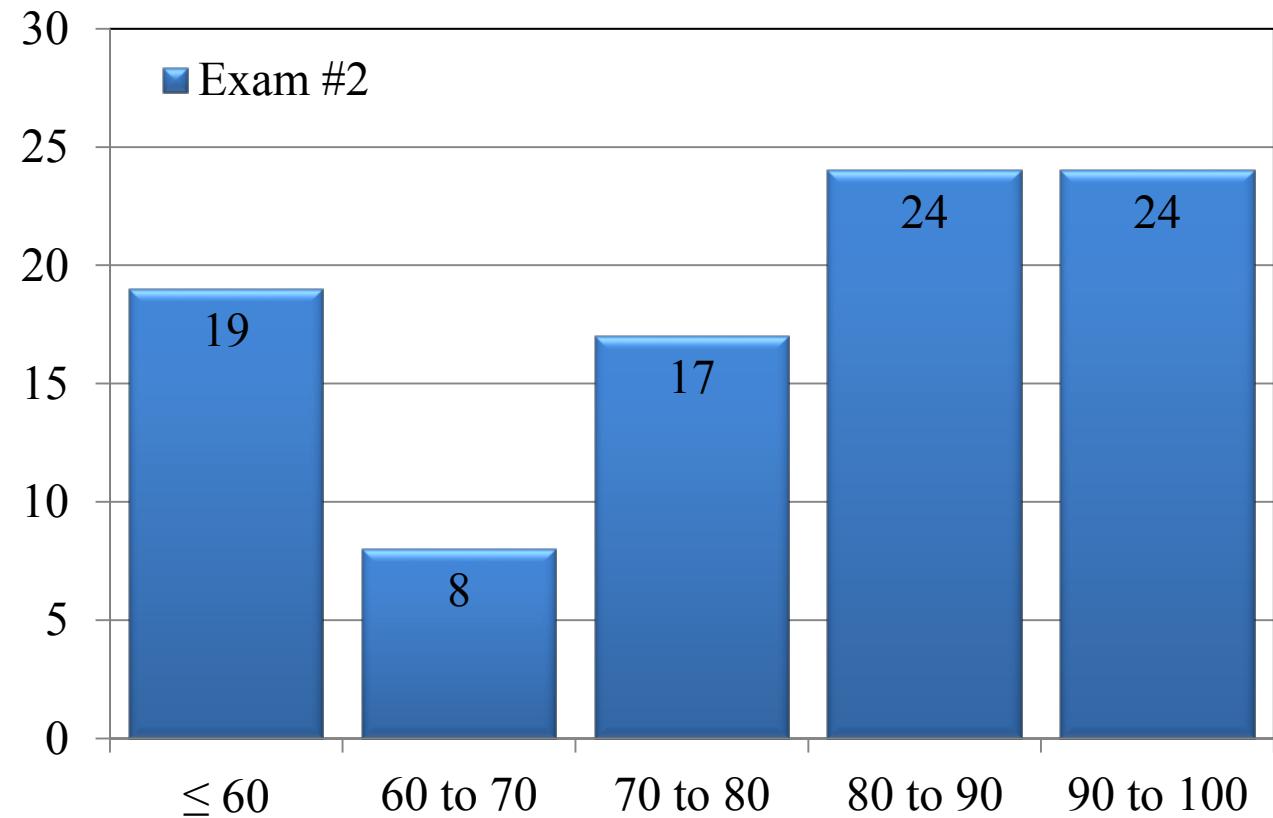



# Midterm Grade Distribution

Midterm Grades	Frequency	Grade
< 60	3	F
60 - 62	0	D-
62 - 64	1	D
64 - 66	0	D
66 - 68	0	D
68 - 70	1	D+
70 - 72	1	C-
72 - 74	2	C
74 - 76	3	C
76 - 78	1	C
78 - 80	3	C+
80 - 82	5	B-
82 - 84	4	B
84 - 86	4	B
86 - 88	5	B
88 - 90	9	B+
90 - 92	8	A-
92 - 94	10	A
94 - 96	9	A
96 - 98	14	A
98 -100+	12	A

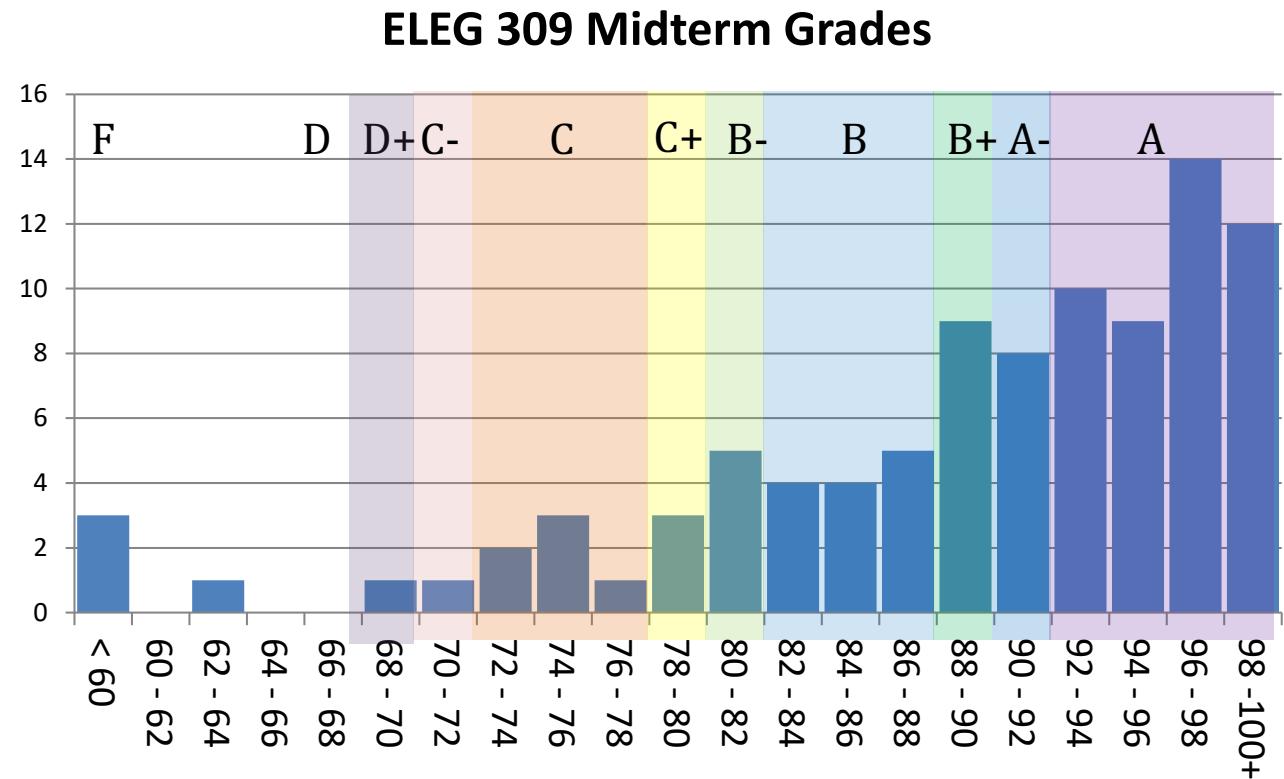

Average      87.86 %  
High            102.2%  
Low            28.24%