

Problem 1

Solution:

Known quantities:

Circuit shown in Figure P3.54.

Find:

Norton equivalent circuit

Analysis:

$$R_N = 5\Omega \parallel (3\Omega + 2\Omega \parallel 1\Omega) = 2.12\Omega$$




Using mesh analysis,

$$8 - 1(i_1 - i_2) - 2(i_1 - i_{SC}) = 0$$

$$-1(i_2 - i_1) - 5i_2 - 3(i_2 - i_{SC}) = 0$$


$$-2(i_{SC} - i_1) - 3(i_{SC} - i_2) = 0$$

$$\text{Solving, } i_{SC} = 3.05\text{A} \Rightarrow I_N = 3.05\text{A}.$$

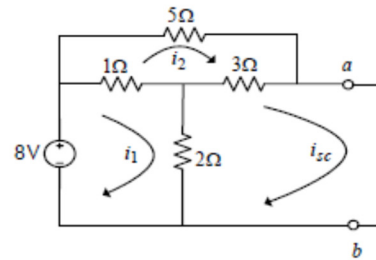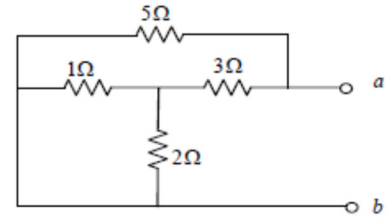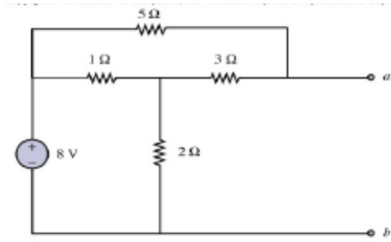

Problem 2

Calculate open circuit voltage.

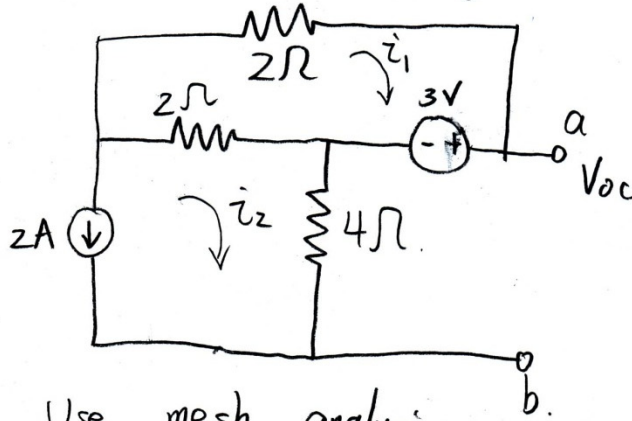

Use mesh analysis.

$$\begin{cases} 4i_1 - 2i_2 = -3 \\ i_2 = -2 \end{cases}$$


$$i_1 = -1.75(\text{A})$$

$$i_2 = -2(\text{A})$$

$$V_{oc} = V_a - V_b = -2 \times 4 + 3 = -5 \text{ V}$$


$$V_{TH} = V_{oc} = -5 \text{ V}$$

Calculate R_{TH} by killing the source.

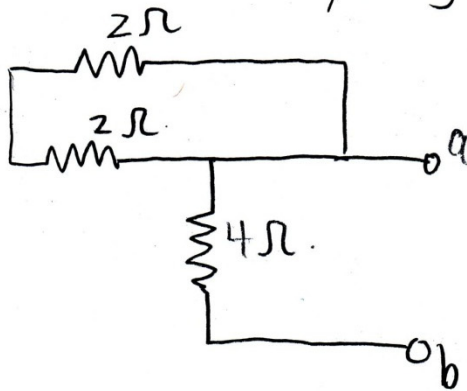

$$R_{TH} = R_{ab} = 4 \Omega$$

Thevenin equivalent circuit.

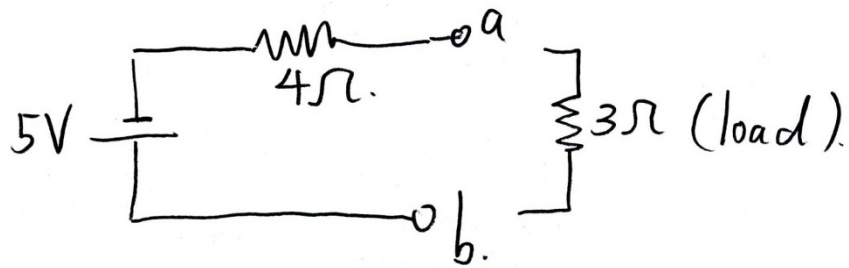


Voltage on 3Ω resistor.

$$\begin{aligned} V &= (-5) \cdot \frac{3\Omega}{4\Omega + 3\Omega} \\ &= -2.14 \text{ (V)} \end{aligned}$$

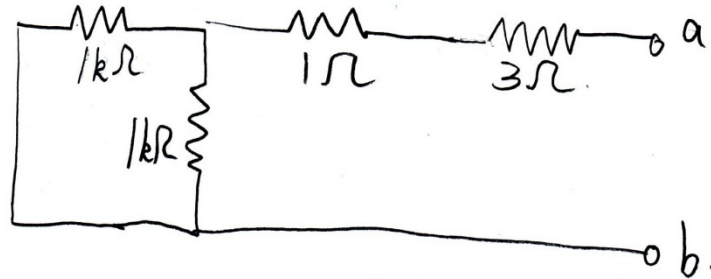Problem 3


Calculate R_{TH} (or R_N) by killing the source.



$$R_{TH} = R_N = R_{ab} = 1k\Omega // 1k\Omega + 1 + 3$$

$$R_{TH} = R_N = 504 \Omega$$

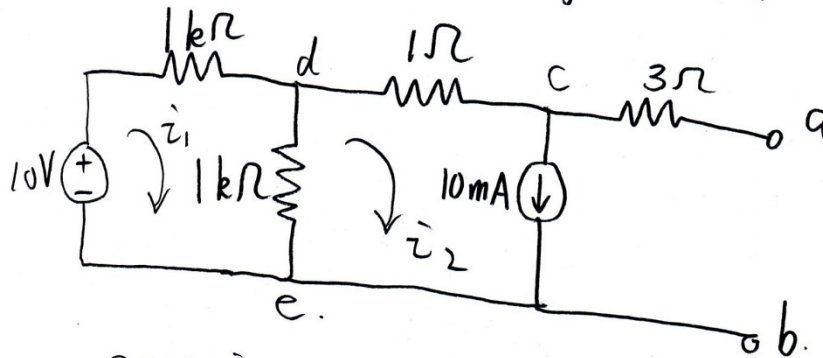Calculate open circuit voltage for V_{TH}




$$\begin{cases} 2000i_1 - 1000i_2 = 10 \\ i_2 = 0.01 \end{cases}$$

$$\therefore \begin{cases} i_1 = 0.01 \text{ (A)} \\ i_2 = 0.01 \text{ (A)} \end{cases}$$

$$V_{oc} = V_a - V_b = V_c - V_e = \Delta V_{e \rightarrow d \rightarrow c}$$

$$= (i_1 - i_2) \times 1000 - i_2 \times 1 = -0.01 \text{ (V)}$$

$$V_{TH} = V_{OC} = -0.01 \text{ (V)}$$

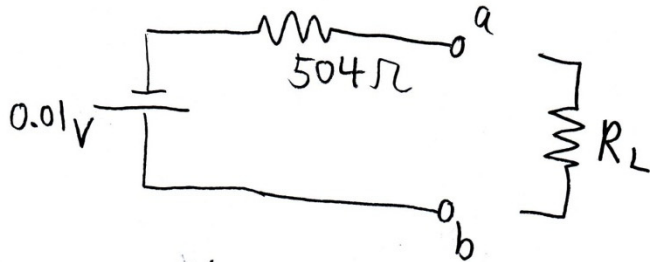


negative V_{TH} means that terminal a is the negative terminal.

Calculate I_N


$$I_N = \frac{V_{TH}}{R_N} = \frac{V_{TH}}{R_{TH}} = \frac{-0.01}{504} = -2.0 \times 10^{-5} \text{ (A)}$$

$$I_N = -0.02 \text{ (mA)}$$

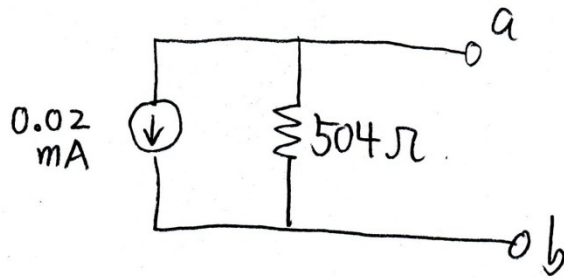

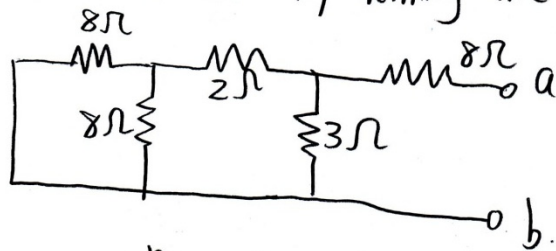Problem 4

Calculate $R_{TH} = R_N$ by killing the sources



$$R_{TH} = R_N = R_{ab}$$

$$8 \parallel 8 = 4\Omega$$


$$4\Omega + 2\Omega = 6\Omega$$

$$6\Omega \parallel 3\Omega = \frac{6 \times 3}{3 + 6} = 2\Omega$$

$$2\Omega + 8\Omega = 10\Omega$$

$$\therefore R_{TH} = R_N = 10\Omega$$

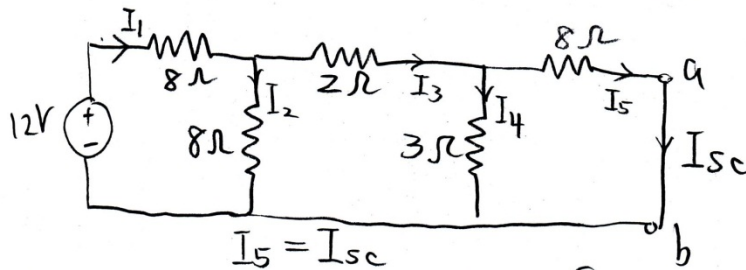Calculate the short circuit current I_{sc} for I_N



Req seen by 12V emf: $(8 \parallel 3 + 2) \parallel 8 + 8$


$$R_{eq} = 10.746\Omega$$

$$I_1 = \frac{12}{10.746} = 1.117 \text{ (A)}$$

$$I_3 = I_1 \cdot \frac{\frac{1}{4.182}}{\frac{1}{8} + \frac{1}{4.182}} = 1.117 \cdot \frac{8}{8 + 4.182} = 0.734 \text{ (A)}$$


$$I_{sc} = I_5 = I_3 \cdot \frac{\frac{1}{8}}{\frac{1}{3} + \frac{1}{8}} = 0.734 \cdot \frac{3}{3 + 8} = 0.200 \text{ (A)}$$

Norton equivalent circuit

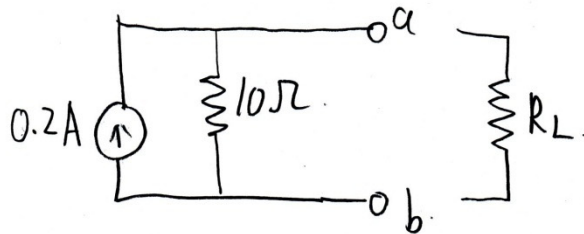


$$V_{TH} = I_N R_N = 0.2 \times 10 = 2 \text{ V}$$

Thevenin equivalent circuit

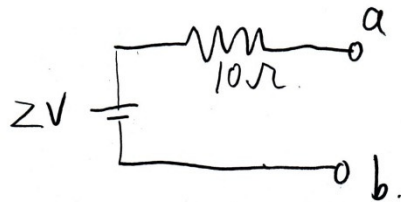


Problem 5

Kill the sources

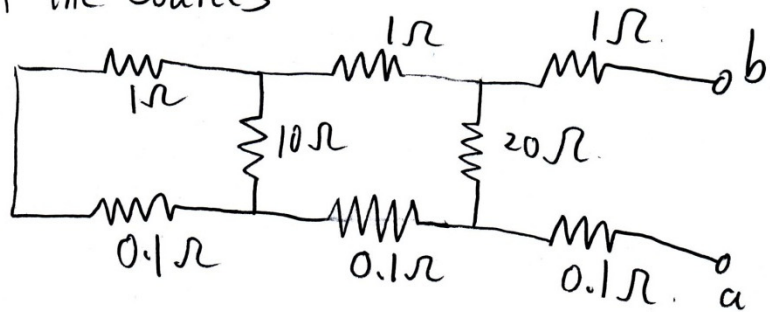


$$R_{TH} = R_N = R_{ab} = [(1+0.1)/10 + 1+0.1]/20 + 1+0.1 = 2.993 \Omega$$

Calculate V_{oc} for V_{TH} .

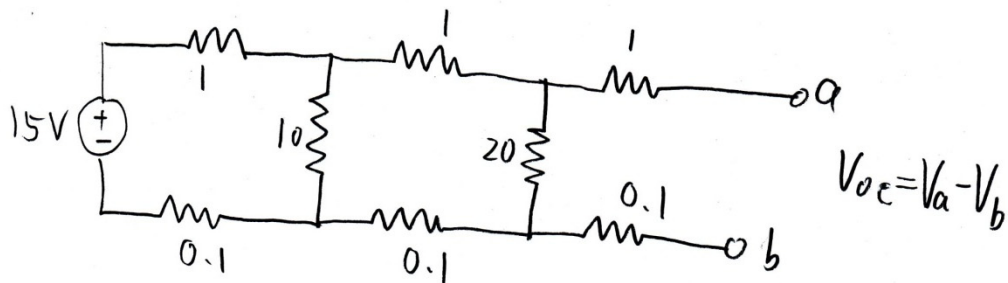

Reduce to

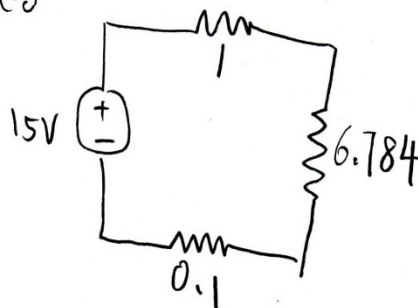


$$V_{6.784} = 15 \cdot \frac{6.784}{1+0.1+6.784} = 12.91 V$$

$$V_{ab} = 12.91 \times \frac{20}{1+0.1+20} = 12.24 (V)$$


$$V_{TH} = V_{oc} = V_{ab} = 12.24 (V)$$

Thevenin equivalent.

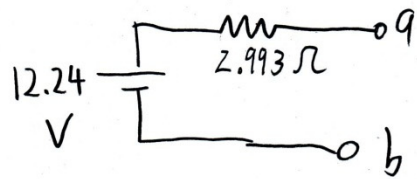


$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{12.24}{2.993} = 4.09 \text{ (A)}$$



Norton equivalent

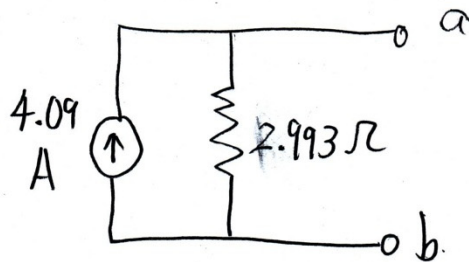

Problem 6

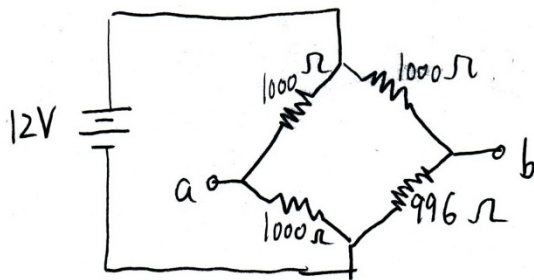


kill the source to calculate R_{TH}

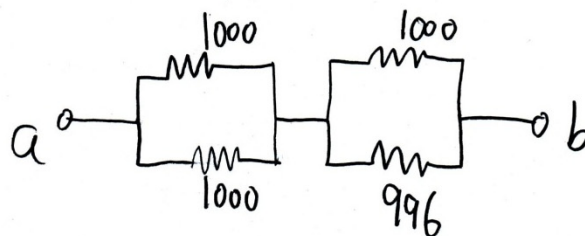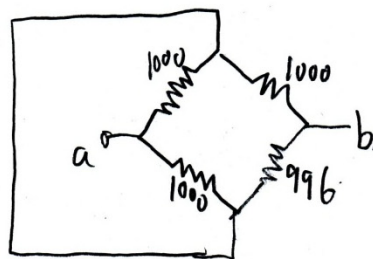

$$\begin{aligned} R_{TH} = R_{ab} &= 1000 // 1000 + 1000 // 996 \\ &= 500 + 499 \\ &= 999 (\Omega) \end{aligned}$$

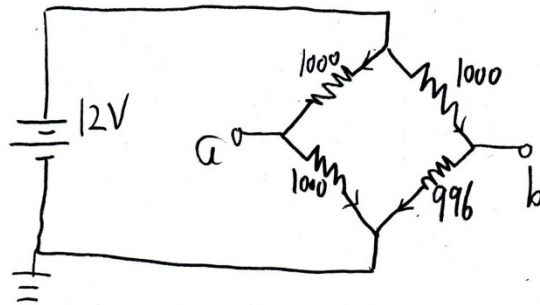Calculate open circuit voltage between a and b



→ suppose this point has zero potential

$$V_a = \frac{12V}{2000\Omega} \times 1000\Omega$$

$$= 6V$$

$$V_b = \frac{12V}{1996\Omega} \times 996\Omega = 5.988(V)$$

$$V_{TH} = V_{oc} = V_{ab} = 6 - 5.988 = 0.012(V)$$

$$= 12(mV)$$

Thevenin equivalent

