



Homework #12

Problems 6.35, 6.51, 6.58, and
6.61

Problem 6.35

For each of the circuits shown in Fig. P6.35, find the emitter base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8$ V independent of current level.


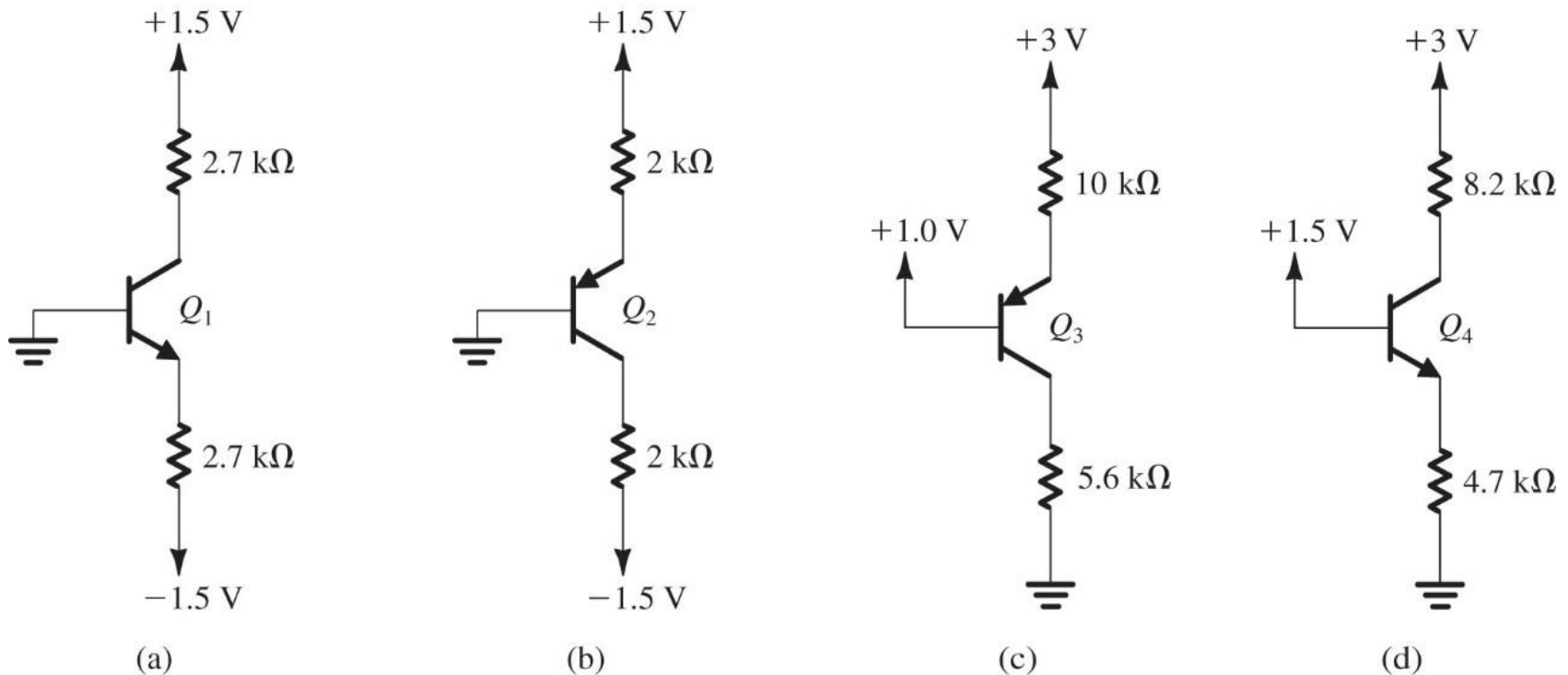


Figure P6.35

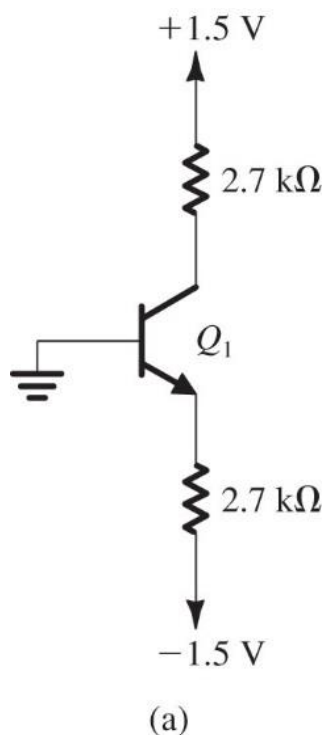

Problem 6.35a

For each of the circuits shown in Fig. P6.35, find the emitter base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8 \text{ V}$ independent of current level.



$$\beta := 50 \quad V_{BE} := 0.8 \text{ V}$$

$$I_E := \frac{-V_{BE} - -1.5 \text{ V}}{2.7 \text{ k}\Omega} = 259.259 \mu\text{A}$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 254.176 \mu\text{A}$$

$$V_B = 0 \text{ V}$$

$$I_B := I_E - I_C = 5.084 \mu\text{A}$$

$$V_E = -0.8 \text{ V}$$


$$I_B := \frac{I_C}{\beta} = 5.084 \mu\text{A}$$

$$V_C := 1.5 \text{ V} - I_C \cdot 2.7 \text{ k}\Omega = 0.814 \text{ V}$$



Problem 6.35b

For each of the circuits shown in Fig. P6.35, find the emitter base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8$ V independent of current level.

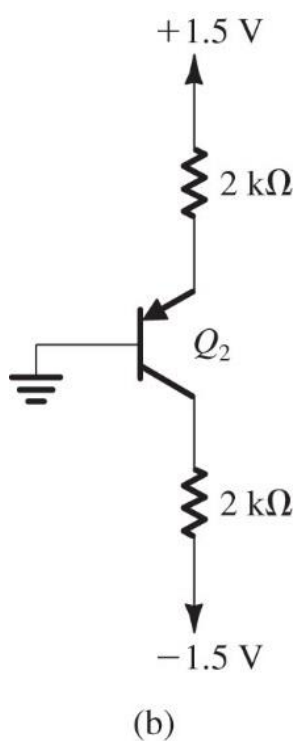

$$I_E := \frac{1.5V - V_{BE}}{2k\Omega} = 350\mu A$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 343.137 \mu A$$

$$I_B := I_E - I_C = 6.863 \mu A$$

$$I_B := \frac{I_C}{\beta} = 6.863\mu A$$

$$V_B = 0 \text{ V}$$


$$V_E = 0.8 \text{ V}$$

$$V_C := -1.5 \text{ V} + I_C \cdot 2k\Omega = -0.814 \text{ V}$$



Problem 6.35c

For each of the circuits shown in Fig. P6.35, find the emitter base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8$ V independent of current level.

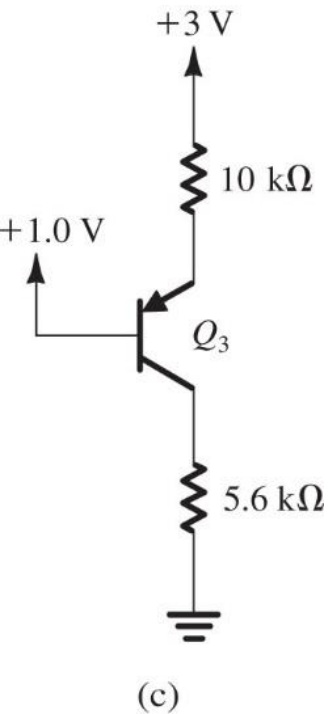

$$I_E := \frac{3V - (1V + V_{BE})}{10k\Omega} = 120\mu A$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 117.647 \mu A$$

$$V_B = 1 V$$

$$I_B := I_E - I_C = 2.353 \mu A$$

$$V_E = 1.8 V$$


$$I_B := \frac{I_C}{\beta} = 2.353\mu A$$

$$V_C := I_C \cdot 5.6k\Omega = 0.659 V$$



Problem 6.35d

For each of the circuits shown in Fig. P6.35, find the emitter base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8$ V independent of current level.

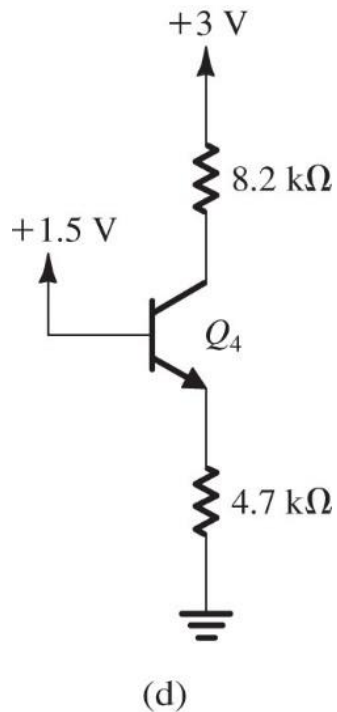

$$I_E := \frac{1.5V - V_{BE}}{4.7k\Omega} = 148.936\mu A$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 146.016 \mu A$$

$$I_B := I_E - I_C = 2.92 \mu A$$

$$I_B := \frac{I_C}{\beta} = 2.92\mu A$$

$$V_B = 1.5 \text{ V}$$

$$V_E = 0.7 \text{ V}$$

$$V_C := 3V - I_C \cdot 8.2k\Omega = 1.803 \text{ V}$$

Problem 6.51

The transistor in the circuit of Fig. P6.51 has a very high β . Find V_E and V_C for V_B (a) +2.0 V, (b) +1.7 V, and (c) 0 V.

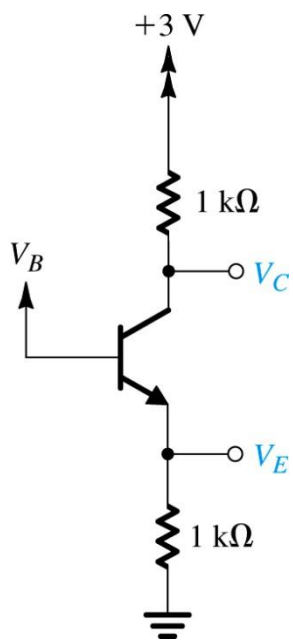


Figure P6.51

$$V_B \text{ (a) } +2 \text{ V}$$

$$V_B = 2 \text{ V}$$

$$V_E = 1.3 \text{ V}$$

$$I_E \approx I_C = \frac{1.3 \text{ V}}{1 \text{ k}\Omega} = 1.3 \text{ mA}$$

$$V_C = 3 \text{ V} - 1 \text{ k}\Omega \times 1.3 \text{ mA}$$

$$V_C = 1.7 \text{ V}$$

$$V_B \text{ (b) } +1.7 \text{ V}$$

$$V_B = 1.7 \text{ V}$$

$$V_E = 1.0 \text{ V}$$

$$I_E \approx I_C = \frac{1.0 \text{ V}}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$V_C = 3 \text{ V} - 1 \text{ k}\Omega \times 1 \text{ mA}$$

$$V_C = 2.0 \text{ V}$$

$$V_B \text{ (c) } 0 \text{ V}$$

$$V_B = 0 \text{ V}$$

$$V_E = 0 \text{ V}$$

$$I_E = I_C = 0 \text{ mA}$$

$$V_C = 3 \text{ V}$$



Problem 6.58a

In the circuit shown in Fig. P6.58, the transistor has $\beta = 40$. Find the values of V_B , V_E and V_C . If R_B is raised to $100\text{ k}\Omega$, what voltages result? With $R_B = 100\text{ k}\Omega$, what value of β would return the voltages to the values first calculated?

$$R_B = 20\text{ k}\Omega$$

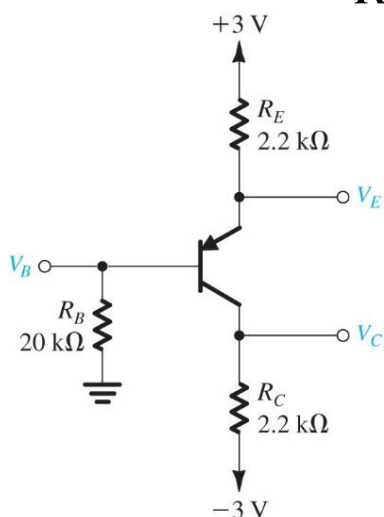


Figure P6.58

$$\beta = \frac{I_C}{I_B} = \frac{I_E - I_B}{I_B}$$

$$\beta I_B = I_E - I_B$$

$$I_B (\beta + 1) = I_E$$

$$I_B = \frac{I_E}{(\beta + 1)}$$

$$V_E = V_B + 0.7\text{V} = I_B R_B + 0.7\text{V} = \frac{I_E}{\beta + 1} R_B + 0.7\text{V}$$

$$V_E = V_{CC} - I_E R_E$$

$$\Rightarrow V_E = \frac{I_E}{\beta + 1} R_B + 0.7\text{V} = V_{CC} - I_E R_E$$

$$I_E \frac{R_B}{\beta + 1} + I_E R_E = V_{CC} - 0.7\text{V}$$

$$I_E = \frac{V_{CC} - 0.7\text{V}}{\left(R_E + \frac{R_B}{\beta + 1} \right)}$$



Problem 6.58b

In the circuit shown in Fig. P6.58, the transistor has $\beta = 50$. Find the values of V_B , V_E and V_C . If R_B is raised to $100 \text{ k}\Omega$, what voltages result? With $R_B = 100 \text{ k}\Omega$, what value of β would return the voltages to the values first calculated?

$$I_E = \frac{V_{CC} - 0.7V}{\left(R_E + \frac{R_B}{\beta + 1}\right)}$$

$$R_B = 20 \text{ k}\Omega$$

$$I_E := \frac{V_{CC} - 0.7V}{R_E + \frac{R_B}{\beta + 1}} = 855.717 \mu\text{A}$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 834.846 \mu\text{A}$$

$$I_B := I_E - I_C = 20.871 \mu\text{A}$$

$$I_B := \frac{I_C}{\beta} = 20.871 \mu\text{A}$$

$$V_B := I_B \cdot R_B = 0.417 \text{ V}$$

$$V_E := 3V - I_E \cdot 2.2 \text{ k}\Omega = 1.117 \text{ V}$$

$$V_E := V_B + 0.7 \text{ V} = 1.117 \text{ V}$$

$$V_C := -3V + I_C \cdot R_C = -1.163 \text{ V}$$

$$R_B = 100 \text{ k}\Omega$$

$$I_E := \frac{V_{CC} - 0.7V}{R_E + \frac{R_B}{\beta + 1}} = 495.794 \mu\text{A}$$

$$I_C := \frac{\beta}{\beta + 1} I_E = 483.701 \mu\text{A}$$

$$I_B := I_E - I_C = 12.093 \mu\text{A}$$

$$I_B := \frac{I_C}{\beta} = 12.093 \mu\text{A}$$

$$V_B := I_B \cdot R_B = 1.209 \text{ V}$$

$$V_E := 3V - I_E \cdot 2.2 \text{ k}\Omega = 1.909 \text{ V}$$

$$V_E := V_B + 0.7 \text{ V} = 1.909 \text{ V}$$

$$V_C := -3V + I_C \cdot R_C = -1.936 \text{ V}$$

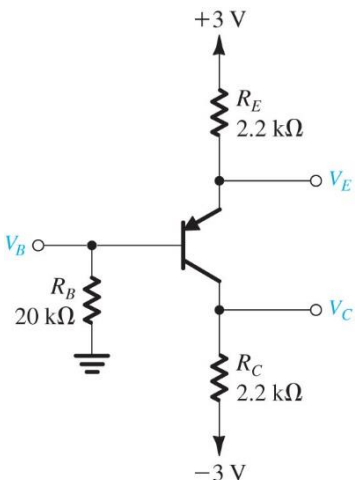


Figure P6.58



Problem 6.58b

In the circuit shown in Fig. P6.58, the transistor has $\beta = 50$. Find the values of V_B , V_E and V_C . If R_B is raised to $100\text{ k}\Omega$, what voltages result? With $R_B = 100\text{ k}\Omega$, what value of β would return the voltages to the values first calculated?

$$I_E = \frac{V_{CC} - 0.7\text{V}}{\left(R_E + \frac{R_B}{\beta + 1}\right)}$$

$$R_B = 20\text{ k}\Omega$$

$$I_E := \frac{V_{CC} - 0.7\text{V}}{R_E + \frac{R_B}{\beta + 1}} = 855.717\mu\text{A}$$

@ $R_B = 100\text{ k}\Omega$ we want the same I_E

$$\beta_{new} := \frac{100\text{ k}\Omega \cdot I_E}{(V_{CC} - 0.7\text{V}) - I_E \cdot R_E} - 1 = 204$$

$$I_E := \frac{V_{CC} - 0.7\text{V}}{R_E + \frac{100\text{ k}\Omega}{\beta_{new} + 1}} = 855.717\mu\text{A}$$

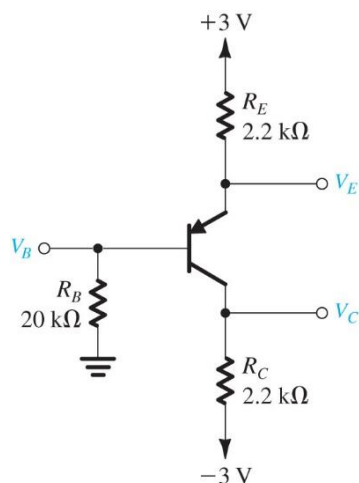


Figure P6.58



Problem 6.61

For the circuits in Fig. P6.61, find values for the labeled node voltages and branch currents, Assume β to be very high.


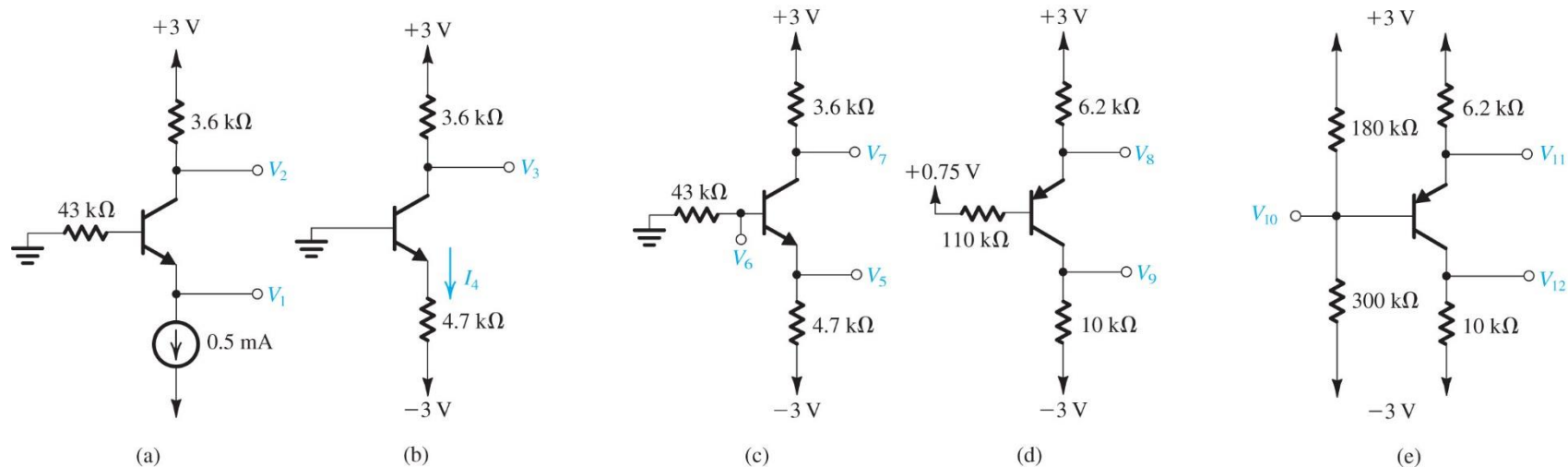


Figure P6.61

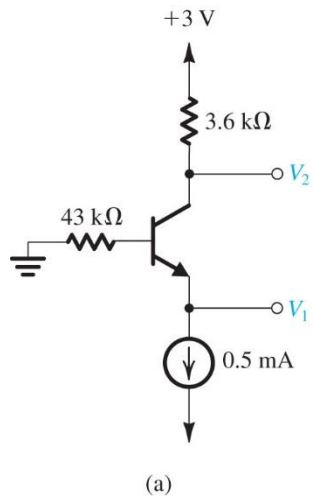Problem 6.61 a,b


For the circuits in Fig. P6.61, find values for the labeled node voltages and branch currents, Assume β to be very high.



$$V_1 = 0V - V_{BE} = -0.7V$$

$$\begin{aligned} V_2 &= 3V - I_C R_C \\ &= 3V - 0.5\text{mA} \times 3.6\text{k}\Omega \\ &= 1.2V \end{aligned}$$

Figure P6.61

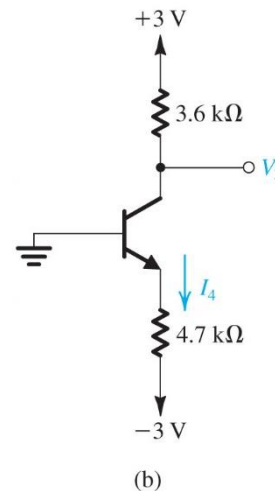

$$\begin{aligned} I_4 &= \frac{-0.7V - -3V}{4.7\text{k}\Omega} \\ &= 0.489\text{mA} \end{aligned}$$

$$\begin{aligned} V_3 &= 3V - I_C R_C \\ &= 3V - 0.489\text{mA} \times 3.6\text{k}\Omega \\ &= 1.24V \end{aligned}$$

Problem 6.61 c,d

For the circuits in Fig. P6.61, find values for the labeled node voltages and branch currents, Assume β to be very high.


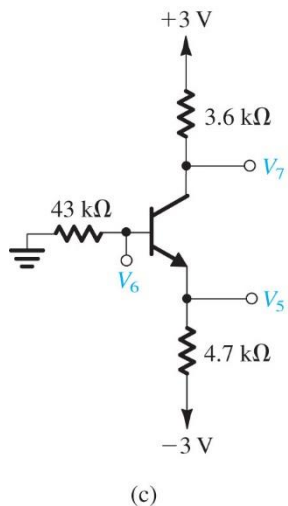


Figure P6.61
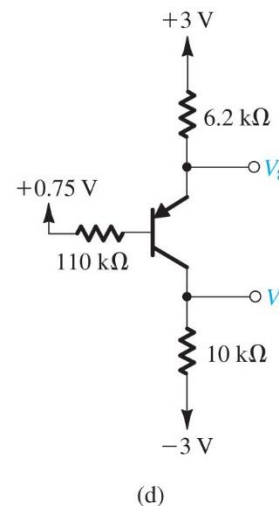
$$\begin{aligned}
 V_6 &= 0V \\
 V_5 &= 0V - V_{BE} = -0.7V \\
 I_C &= I_E = \frac{-0.7V - (-3V)}{4.7k\Omega} \\
 &= 0.489mA \\
 V_7 &= 3V - I_C R_C \\
 &= 3V - 0.489mA \times 3.6k\Omega \\
 &= 1.24V
 \end{aligned}$$



$$\begin{aligned}
 V_8 &= 0.75V + V_{BE} = 1.45V \\
 I_C &= I_E = \frac{3V - 1.45V}{6.2k\Omega} \\
 &= 0.25mA \\
 V_9 &= -3V + I_C R_C \\
 &= -3V + 0.25mA \times 10k\Omega \\
 &= -0.5V
 \end{aligned}$$

Problem 6.61 e

For the circuits in Fig. P6.61, find values for the labeled node voltages and branch currents, Assume β to be very high.

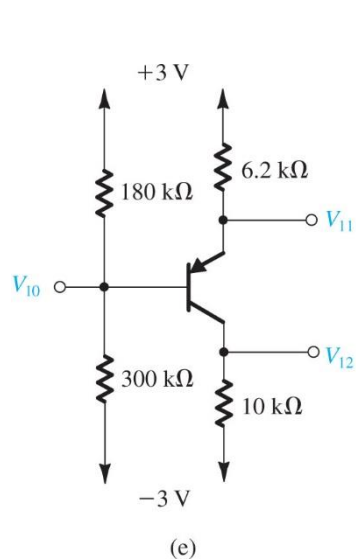


Figure P6.61

$$\begin{aligned} V_{10} &= -3V + 6V \left(\frac{300k\Omega}{300k\Omega + 180k\Omega} \right) \\ &= -3V + 6V (0.625) \\ &= 0.75V \end{aligned}$$

$$V_{11} = 0.75V + V_{BE} = 1.45V$$

$$\begin{aligned} V_{12} &= -3V - I_C R_C \\ &= -3V + 0.25mA \times 10k\Omega \\ &= -0.5V \end{aligned}$$

$$\begin{aligned} I_C = I_E &= \frac{-0.7V - -3V}{4.7k\Omega} \\ &= 0.489mA \end{aligned}$$