




# Homework #16

Problems 7.92, 7.117, 7.125,  
7.129, and 7.135
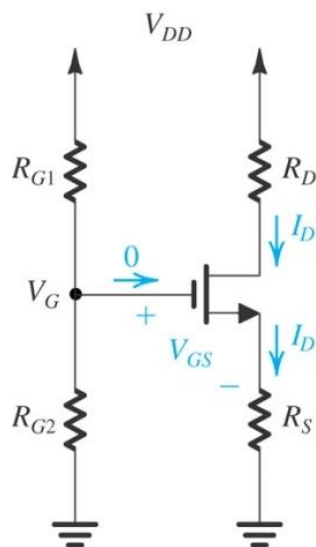
# Problem 7.92a

Consider the classical biasing scheme shown in Fig. 7.48(c), using a 9-V supply. For the MOSFET,  $V_t = 1$  V,  $\lambda = 0$ , and  $k_n = 2$  mA/V<sup>2</sup>. Arrange that the drain current is 1 mA, with about one-third of the supply voltage across each of  $R_S$  and  $R_D$ . Use 22 M $\Omega$  for the larger of  $R_{G1}$  and  $R_{G2}$ . What are the values of  $R_{G1}$ ,  $R_{G2}$ ,  $R_S$  and  $R_D$  that you have chosen? Specify them to two significant digits. For your design, how far is the drain voltage from the edge of saturation?



(c)

$$\frac{9V}{3} = 3V = 1mA \times R_D$$

$$R_D = R_S = 3k\Omega$$

$$V_{OV} = \sqrt{\frac{I_D}{\frac{1}{2}k'_n \left(\frac{W}{L}\right)}}$$

$$V_{OV} = \sqrt{\frac{1 \cdot mA}{\frac{1}{2} \cdot 2 \cdot \frac{mA}{V^2}}} = 1V$$

$$V_{GS} = V_t + V_{OV} = (1 + 1)V = 2V$$

$$V_G = V_S + V_{GS} = (3 + 2)V = 5V$$


$$\frac{5V}{9V} = \frac{22M\Omega}{22M\Omega + R_{G1}}$$

$$R_{G1} = 17.6M\Omega$$

$$R_{G2} = 22M\Omega$$
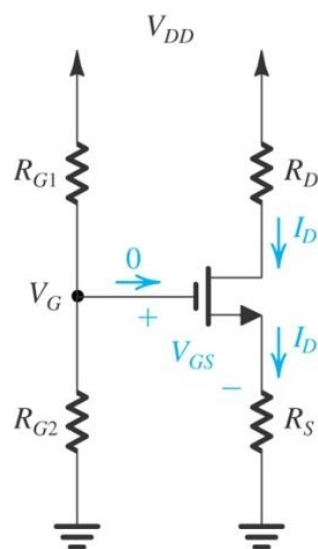
# Problem 7.92b

Consider the classical biasing scheme shown in Fig. 7.48(c), using a 9-V supply. For the MOSFET,  $V_t = 1$  V,  $\lambda = 0$ , and  $k_n = 2$  mA/V<sup>2</sup>. Arrange that the drain current is 1 mA, with about one-third of the supply voltage across each of  $R_S$  and  $R_D$ . Use 22 M $\Omega$  for the larger of  $R_{G1}$  and  $R_{G2}$ . What are the values of  $R_{G1}$ ,  $R_{G2}$ ,  $R_S$  and  $R_D$  that you have chosen? Specify them to two significant digits. For your design, how far is the drain voltage from the edge of saturation?



(c)

$$R_D = R_S = 3\text{k}\Omega$$

$$R_{G1} = 17.6\text{M}\Omega$$

$$R_{G2} = 22\text{M}\Omega$$

$$V_{GS} = V_t + V_{OV} = (1 + 1)\text{V} = 2\text{V}$$

$$V_G = V_S + V_{GS} = (3 + 2)\text{V} = 5\text{V}$$

saturation /triode boundary (B) is

$$\text{where } v_{GS} = v_{DS} + V_t$$

$$V_{GS}|_{\text{triode}} = V_{DS} + V_t = (3 + 1)\text{V} = 4\text{V}$$

Therefore the device is biased 2 V from the triode/saturation boundary



## Problem 7.117

Calculate the overall voltage gain  $G_v$  of a common source amplifier for which  $g_m = 2 \text{ mA/V}$ ,  $r_o = 50 \text{ k}\Omega$ ,  $R_o = 10 \text{ k}\Omega$ , and  $R_G = 10 \text{ M}\Omega$ . The amplifier is fed from a signal source with a Thevenin resistance of  $0.5 \text{ M}\Omega$ , and the amplifier output is coupled to a load resistance of  $20 \text{ k}\Omega$ .

$$G_v = -\frac{R_G}{R_G + R_{sig}} g_m (R_D \parallel R_L \parallel r_o)$$

$$G_v = -\frac{10\text{M}\Omega}{10\text{M}\Omega + 0.5\text{M}\Omega} 2 \frac{\text{mA}}{\text{V}} (10\text{k}\Omega \parallel 20\text{k}\Omega \parallel 50\text{k}\Omega)$$

$$R_{\text{eff}} := \left( \frac{1}{50\text{k}\Omega} + \frac{1}{10\text{k}\Omega} + \frac{1}{20\text{k}\Omega} \right)^{-1} = 5882.353 \Omega$$

$$G_v := \frac{10\text{M}\Omega}{10\text{M}\Omega + 500\text{k}\Omega} \cdot 2 \frac{\text{mA}}{\text{V}} \cdot R_{\text{eff}} = 11.204$$



## Problem 7.125

For the common-emitter amplifier shown in Fig. P7.125, let  $V_{CC} = 15\text{ V}$ ,  $R_1 = 27\text{ k}\Omega$ ,  $R_2 = 15\text{ k}\Omega$ ,  $R_E = 2.4\text{ k}\Omega$ , and  $R_C = 3.9\text{ k}\Omega$ . The transistor has  $\beta = 100$ . Calculate the dc bias current  $I_C$ . If the amplifier operates between a source for which  $R_{sig} = 2\text{ k}\Omega$  and a load of  $2\text{ k}\Omega$ , replace the transistor with its hybrid- $\pi$  model, and find the values of  $R_{in}$ , and the overall voltage gain  $v_o/v_{sig}$ .

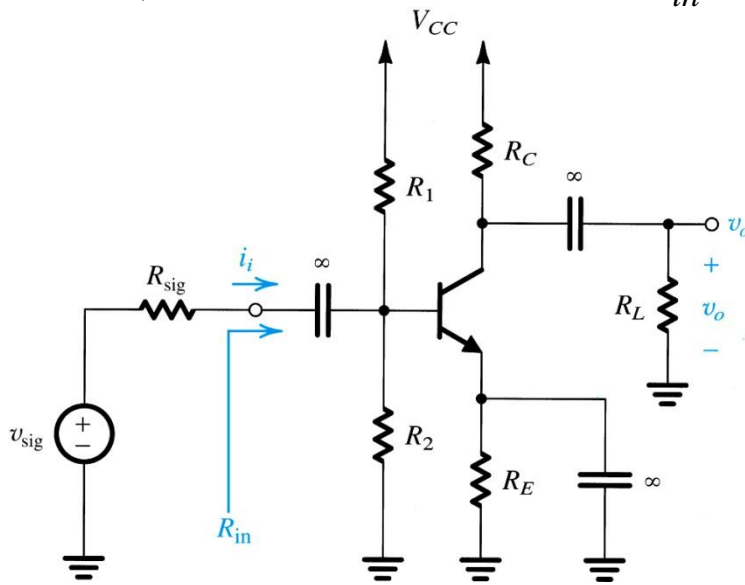


Figure P7.125

$$V_B = V_{CC} \frac{R_2}{R_2 + R_1} = 15\text{V} \frac{15\text{k}\Omega}{42\text{k}\Omega} = 5.357\text{V}$$

$$V_E = V_B - V_{BE} = 4.657\text{V}$$

$$I_E = \frac{V_E}{R_E} = \frac{4.657\text{V}}{2.4\text{k}\Omega} = 1.94\text{mA}$$


$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} 1.94\text{mA} = 1.92\text{mA}$$

$$V_C = V_{CC} - I_C R_C = 15\text{V} - 1.94\text{mA} \times 3.9\text{k}\Omega = 7.512\text{V}$$


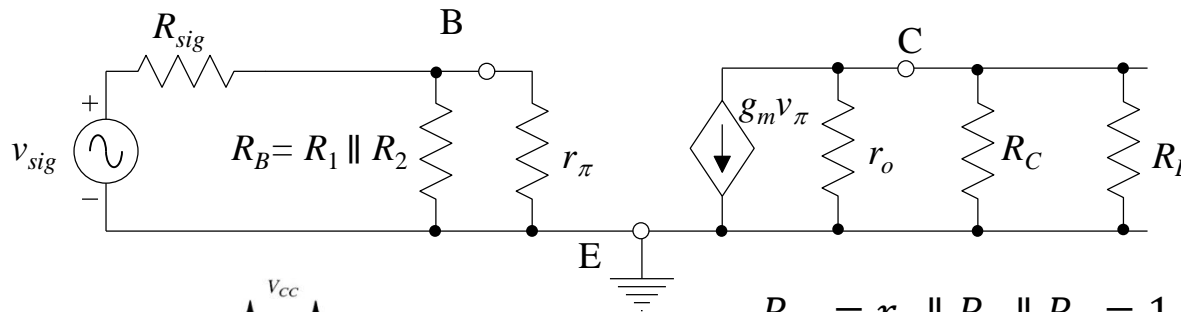
# Problem 7.125

For the common-emitter amplifier shown in Fig. P7.125, let  $V_{CC} = 15\text{ V}$ ,  $R_1 = 27\text{ k}\Omega$ ,  $R_2 = 15\text{ k}\Omega$ ,  $R_E = 2.4\text{ k}\Omega$ , and  $R_C = 3.9\text{ k}\Omega$ . The transistor has  $\beta = 100$ . Calculate the dc bias current  $I_C$ . If the amplifier operates between a source for which  $R_{sig} = 2\text{ k}\Omega$  and a load of  $2\text{ k}\Omega$ , replace the transistor with its hybrid- $\pi$  model, and find the values of  $R_{in}$ , and the overall voltage gain  $v_o/v_{sig}$ .




$$R_B = R_1 \parallel R_2 = 9.643\text{ k}\Omega$$

$$r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} = 1.302\text{ k}\Omega$$

$$R_{in} = r_\pi \parallel R_1 \parallel R_2 = 1.302\text{ k}\Omega \parallel 27\text{ k}\Omega \parallel 15\text{ k}\Omega = 1.187\text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = 76.832\text{ mA/V}$$
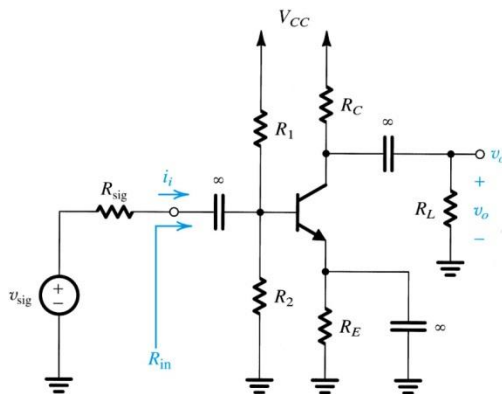
$$G_v \equiv \frac{v_o}{v_{sig}} = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L \parallel r_o) = -37.833\text{ V/V}$$





## Problem 7.129a,b

In the circuit of Fig. P6.146,  $v_{sig}$  is a small sine-wave signal with zero average. The transistor  $\beta$  is 100.

(a) Find the value of  $R_E$  to establish a dc emitter current of about 0.5 mA.

$$I_E = 0.5 \text{ mA} \quad \Rightarrow \quad I_B = \frac{I_E}{\beta + 1} = \frac{0.5 \text{ mA}}{101} = 4.95 \text{ } \mu\text{A}$$

$$R_E = \frac{V_E - V_{EE}}{I_E} = \frac{-I_B R_B - V_{BE} - V_{EE}}{I_E} = \frac{-12 \text{ mV} - 0.7 \text{ V} + 5 \text{ V}}{0.5 \text{ mA}} = 8.576 \text{ k}\Omega$$

(b) Find  $R_C$  to establish a dc collector voltage of about +1 V.

$$I_C = \alpha I_E = \frac{100}{101} 0.5 \text{ mA} = 0.495 \text{ mA}$$

$$R_E = \frac{V_{CC} - V_C}{I_C} = \frac{5 \text{ V} - 1 \text{ V}}{0.495 \text{ mA}} = 8.081 \text{ k}\Omega$$

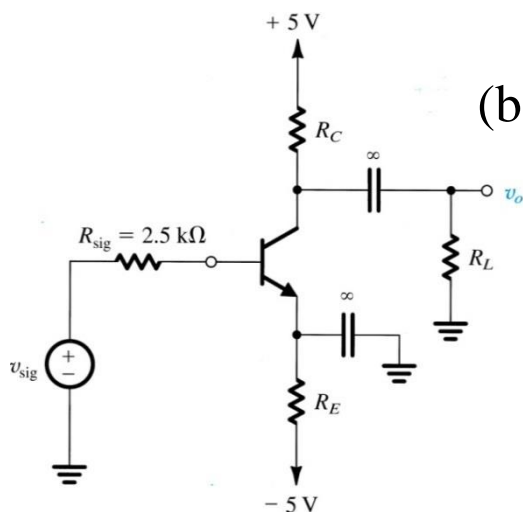


Figure P7.129



# Problem 7.129c

In the circuit of Fig. P6.146,  $v_{sig}$  is a small sine-wave signal with zero average. The transistor  $\beta$  is 100.

(c) For  $R_L = 10\text{ k}\Omega$ , draw the small-signal equivalent circuit of the amplifier and determine its overall voltage gain.


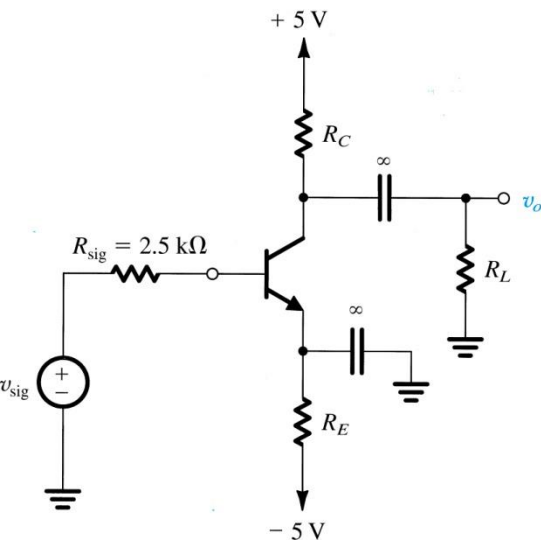


Figure P7.129

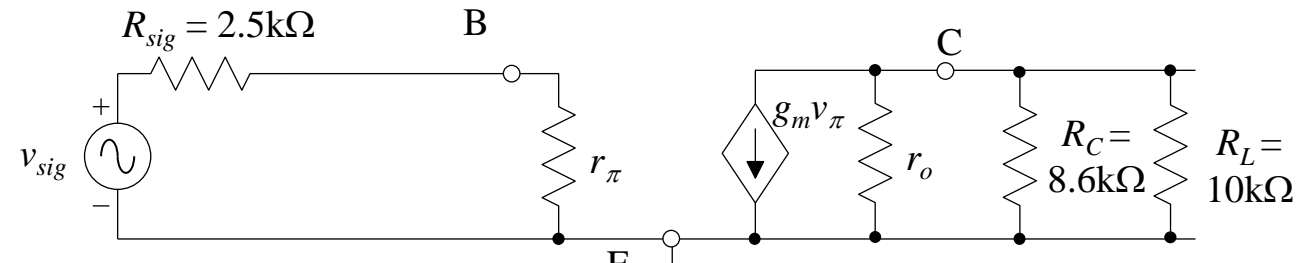

$$g_m = \frac{I_C}{V_T} = \frac{0.495\text{ mA}}{25\text{ mV}} = 19.8\text{ mA/V}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{25\text{ mV}}{4.95\text{ }\mu\text{A}} = 5.05\text{ k}\Omega$$

$$v_o = (-g_m)v_{sig} \left( \frac{r_\pi}{r_\pi + R_{sig}} \right) (R_C \parallel r_o \parallel R_L)$$

$$G_v \equiv \frac{v_o}{v_{sig}} = (-g_m) \left( \frac{r_\pi}{r_\pi + R_{sig}} \right) (R_C \parallel r_o \parallel R_L) = -19.8\text{ mA/V} \left( \frac{5.05\text{ k}\Omega}{7.55\text{ k}\Omega} \right) \left( \frac{8.576\text{ k}\Omega \times 10\text{ k}\Omega}{8.576\text{ k}\Omega + 10\text{ k}\Omega} \right)$$

$$= -61.23\text{ V/V}$$



# Problem 7.135a

For the emitter follower in Fig. P7.135, the signal source is directly coupled to the transistor base. If the dc component of  $v_{sig}$  is zero, find the dc emitter current.

Assume  $\beta = 100$ . Neglecting  $r_o$ , find  $R_{in}$ , the voltage gain  $v_o/v_{sig}$ , the current gain  $i_o/i_i$ , and the output resistance  $R_{out}$ .

$$V_B = I_B R_B = \left( \frac{1}{\beta + 1} \right) I_E R_B = \frac{100}{101} I_E [I_E \text{ in mA}]$$

$$I_E = \frac{V_{CC} - V_B - V_{BE}}{R_C} = \frac{5 - V_B - 0.7}{3.3} = \frac{1}{3.3} \left( 4.3 - \frac{100}{101} I_E \right) [I_E \text{ in mA}]$$

$$\Rightarrow I_E = \frac{4.3}{4.29} \approx 1 \text{ mA} \quad I_B = \frac{I_E}{\beta + 1} \approx 10 \text{ uA}; I_C = 0.99 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$R_{in} = (\beta + 1)(r_e + R_E \parallel R_L) = 101(25 \Omega + 3.3 \text{ k}\Omega \parallel 2 \text{ k}\Omega) = 101(1270 \Omega) = 128.3 \text{ k}\Omega$$

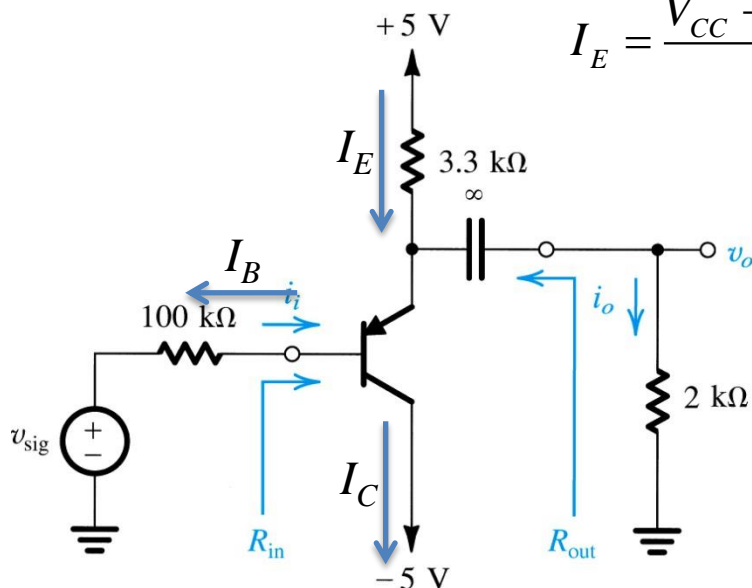


Figure P7.135



# Problem 7.135b

For the emitter follower in Fig. P7.135, the signal source is directly coupled to the transistor base. If the dc component of  $v_{sig}$  is zero, find the dc emitter current. Assume  $\beta = 100$ . Neglecting  $r_o$ , find  $R_{in}$ , the voltage gain  $v_o/v_{sig}$ , the current gain  $i_o/i_i$ , and the output resistance  $R_{out}$ .

$$I_E = 1 \text{ mA}; I_B = \frac{I_E}{\beta + 1} \approx 10 \text{ uA}; I_C = 0.99 \text{ mA}$$

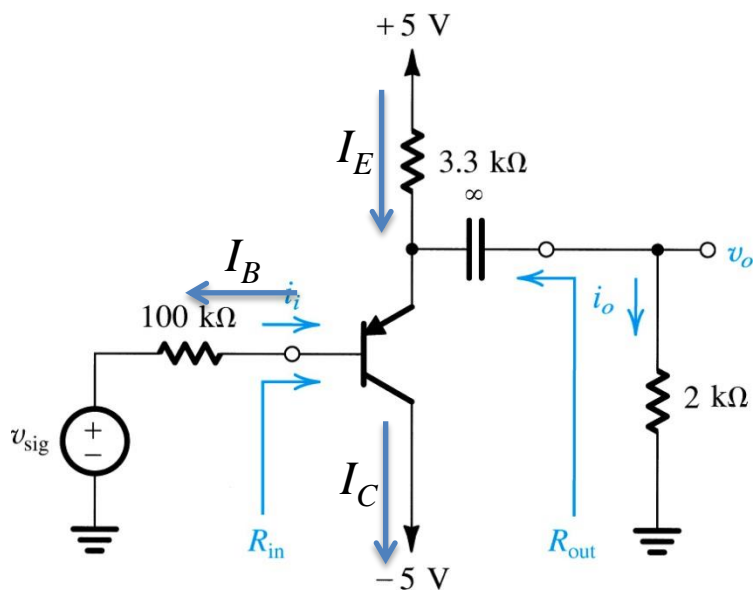



Figure P6.153

$$\begin{aligned} G_v &\equiv \frac{v_o}{v_{sig}} = \frac{(\beta + 1)(R_E \parallel R_L)}{(\beta + 1)r_e + (\beta + 1)(R_E \parallel R_L) + R_{sig}} \\ &= \frac{101(1.25 \text{ k}\Omega)}{101(25 \text{ }\Omega) + 101(1.25 \text{ k}\Omega) + 100 \text{ k}\Omega} \\ &= \frac{125.77 \text{ k}\Omega}{2.525 \text{ k}\Omega + 125.77 \text{ k}\Omega + 100 \text{ k}\Omega} \\ &= 0.551 \text{ V/V} \end{aligned}$$
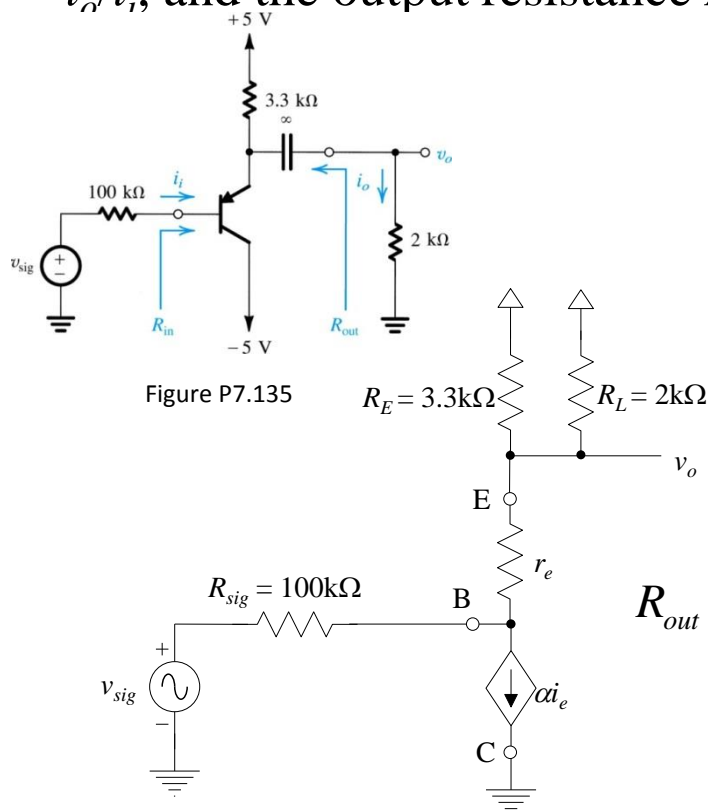
# Problem 7.135c

For the emitter follower in Fig. P7.135, the signal source is directly coupled to the transistor base. If the dc component of  $v_{sig}$  is zero, find the dc emitter current.

Assume  $\beta = 100$ . Neglecting  $r_o$ , find  $R_{in}$ , the voltage gain  $v_o/v_{sig}$ , the current gain  $i_o/i_i$ , and the output resistance  $R_{out}$ .



$$G_i \equiv \frac{i_o}{i_{sig}} = \frac{v_o/R_L}{v_{sig}/(R_{sig} + R_{in})}$$

$$= \frac{R_{sig} + R_{in}}{R_L} \frac{v_o}{v_{sig}} = \frac{R_{sig} + R_{in}}{R_L} G_v$$

$$= \frac{100 \text{ k}\Omega + 128.3 \text{ k}\Omega}{2 \text{ k}\Omega} 0.551 \text{ V/V}$$

$$= 62.9 \text{ A/A}$$

$$R_{out} = R_E \parallel R_L \parallel \left( r_e + \frac{R_{sig}}{(\beta + 1)} \right) = 3.3 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel \left( 25 \Omega + \frac{100 \text{ k}\Omega}{101} \right)$$

$$= 3.3 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 990 \Omega = 551 \Omega$$