

For an NMOS differential pair with a common-mode voltage V_{CM} applied, as shown in Fig. 9.2, let $V_{DD} = V_{SS} = 1.0 \text{ V}$, $k'_n = 0.4 \text{ mA/V}^2$, $(W/L)_{1.2} = 10$, $V_{tn} = 0.4$ V, I = 0.16 mA, $R_D = 5$ k Ω , and neglect channel-length modulation.

- (a) Find V_{OV} and V_{GS} for each transistor.
- (b) For $V_{CM} = 0$, find V_S , I_{D1} , I_{D2} , V_{D1} , and V_{D2} .
- (c) Repeat (b) for $V_{CM} = +0.4 \text{ V}$.
- (d) Repeal (b) for $V_{CM} = -0.1 \text{ V}$.
- (e) What is the highest value of V_{CM} for which Q_1 and Q_2 remain in saturation?
- (f) If current source I requires a minimum voltage of 0.2 V to operate properly, what is the lowest value allowed for V_S and hence for V_{CM} ?

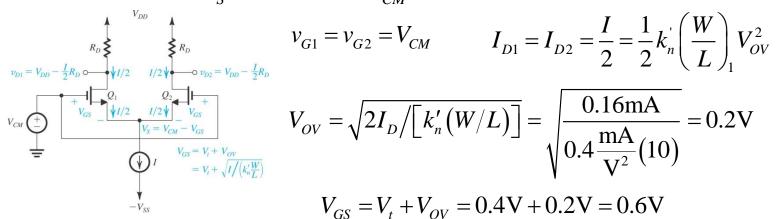


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$V_{G1} = V_{G2} = V_{CM}$$
 $I_{D1} = I_{D2} = \frac{I}{2} = \frac{1}{2} k_n \left(\frac{W}{L}\right)_1 V_{OV}^2$

$$V_{OV} = \sqrt{2I_D/[k'_n(W/L)]} = \sqrt{\frac{0.16\text{mA}}{0.4\frac{\text{mA}}{V^2}(10)}} = 0.2\text{V}$$

$$V_{GS} = V_t + V_{OV} = 0.4 \text{V} + 0.2 \text{V} = 0.6 \text{V}$$

R. Martin

Problem 9.1b,c

For an NMOS differential pair with a common-mode voltage V_{CM} applied, as shown in Fig. 9.2, let $V_{DD} = V_{SS} = 1.0 \text{ V}$, $k'_n = 0.4 \text{ mA/V}^2$, $(W/L)_{1.2} = 10$, $V_{tn} = 0.4$ V, I = 0.16 mA, $R_D = 5$ k Ω , and neglect channel-length modulation.

(b) For $V_{CM} = 0$, find V_S , I_{D1} , I_{D2} , V_{D1} , and V_{D2} .

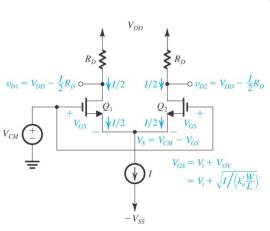


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$v_{G1} = v_{G2} = V_{CM} \qquad V_{OV} = 0.2V \qquad V_{GS} = 0.6V$$

$$V_{S} = V_{G} - V_{GS} = 0V - 0.6V = -0.6V$$

$$V_{S} = V_{CM} - V_{CS} = 0 = 0.08mA$$

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.16mA}{2} = 0.08mA$$

$$V_{CM} + V_{CM} - V_{CM} - V_{CS} - V_{CS} - V_{CM} - V_{CS} - V_{CM} - V_{CS} - V_{CM} - V_{CS} - V_{C$$

(c) Repeat (b) for
$$V_{CM} = +0.4 \text{ V}$$
.

$$V_S = V_G - V_{GS} = 0.4 \text{V} - 0.6 \text{V} = -0.2 \text{V}$$

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.16 \text{mA}}{2} = 0.08 \text{mA}$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2}R_D = 1V - 0.08\text{mA} \times 5\text{k}\Omega = 0.6V$$


Problem 9.1d,e,f

For an NMOS differential pair with a common-mode voltage V_{CM} applied, as shown in Fig. 9.2, let $V_{DD} = V_{SS} = 1.0 \text{ V}$, $k'_n = 0.4 \text{ mA/V}^2$, $(W/L)_{1.2} = 10$, $V_{tn} = 0.4$ V, I = 0.16 mA, $R_D = 5$ k Ω , and neglect channel-length modulation.

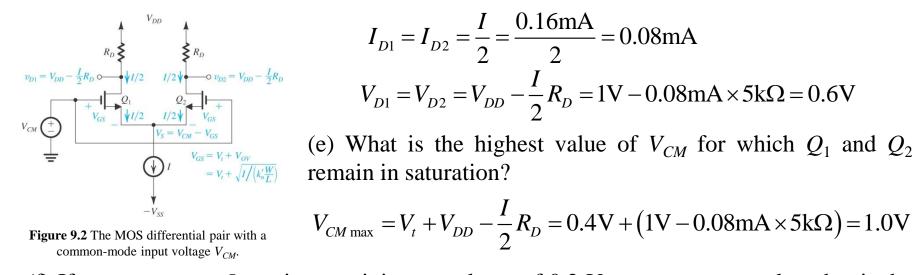(d) Repeal (b) for $V_{CM} = -0.1 \text{ V}$. $V_{c} = V_{G} - V_{GS} = -0.1 \text{V} - 0.6 \text{V} = -0.7 \text{V}$

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.16 \text{mA}}{2} = 0.08 \text{mA}$$

$$V_{D1} = V_{D2} = V_{DD} - \frac{I}{2} R_D = 1 \text{V} - 0.08 \text{mA} \times 5 \text{k}\Omega = 0.6 \text{V}$$



$$V_{CM \text{ max}} = V_t + V_{DD} - \frac{I}{2}R_D = 0.4\text{V} + (1\text{V} - 0.08\text{mA} \times 5\text{k}\Omega) = 1.0\text{V}$$

(f) If current source I requires a minimum voltage of 0.2 V to operate properly, what is the lowest value allowed for V_S and hence for V_{CM} ?

$$V_{CM \text{ min}} = -V_{SS} + V_{CS} + V_{GS} = -1V + 0.2V + 0.6V = -0.2V$$

For the differential amplifier specified in Problem 9.1 let $v_{G2} = 0$ and $v_{G1} = v_{id}$. Find the value of v_{id} that corresponds to each of the following situations:

(a)
$$i_{D1} = i_{D2} = 0.08 \text{ mA};$$

For each case, find v_s , v_{D1} , v_{D2} , and $(v_{D2} - v_{D1})$.

$$i_{D1} = i_{D2} = \frac{I}{2}$$

$$v_{G1} = v_{G2} = 0V$$

$$i_{D1} = i_{D2} = \frac{1}{2}$$
 $v_{G1} = v_{G2} = 0V$ $v_{id} = v_{G1} - v_{G2} = 0V$

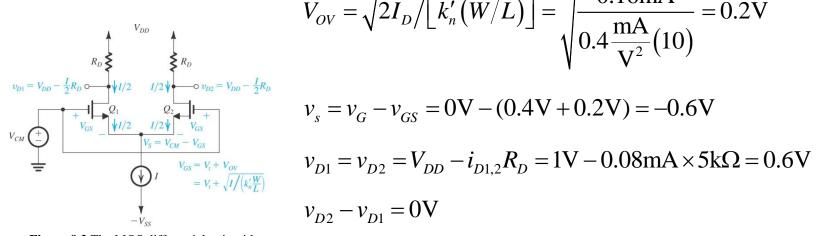


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$V_{OV} = \sqrt{2I_D/[k'_n(W/L)]} = \sqrt{\frac{0.16\text{mA}}{0.4\frac{\text{mA}}{V^2}(10)}} = 0.2\text{V}$$

$$v_s = v_G - v_{GS} = 0V - (0.4V + 0.2V) = -0.6V$$

$$v_{D1} = v_{D2} = V_{DD} - i_{D1,2}R_D = 1V - 0.08\text{mA} \times 5\text{k}\Omega = 0.6V$$

$$v_{D2} - v_{D1} = 0V$$

For the differential amplifier specified in Problem 9.1 let $v_{G2} = 0$ and $v_{G1} = v_{id}$ Find the value of v_{id} that corresponds to each of the following situations: For each case, find v_s , v_{D1} , v_{D2} , and $(v_{D2} - v_{D1})$.

(b) $i_{D1} = 0.12 \text{ mA}$ and $i_{D2} = 0.04 \text{ mA}$;

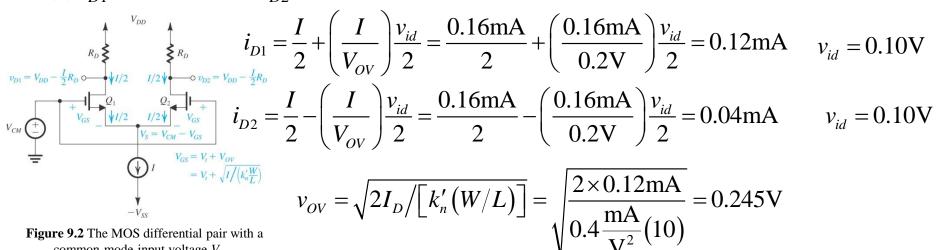


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$v_{GS} = V_t + v_{OV} = 0.4V + 0.245V = 0.645V$$


$$v_{D1} = V_{DD} - i_{D1}R_D = 1V - 0.12\text{mA} \times 5\text{k}\Omega = 0.4V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.04\text{mA} \times 5\text{k}\Omega = 0.8V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.04\text{mA} \times 5\text{k}\Omega = 0.8V$$

$$v_{D2} - v_{D1} = 0.8V - (0.4V) = 0.4V$$
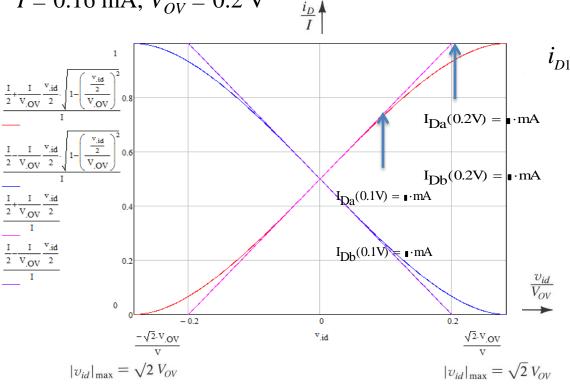
$$I = 0.16 \text{ mA}, V_{OV} = 0.2 \text{ V}$$



$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$$

$$= \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$$

Transfer characteristics nonlinear and usually linear amplification is desirable.

If we can keep $v_{id}/2 \ll V_{OV}$ (small-signal) we can say that

$$i_{D1} \approx \frac{I}{2} + i_d$$


$$i_{D1} \approx \frac{I}{2} + i_d$$
 $i_{D2} \approx \frac{I}{2} - i_d$

$$i_d = \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2}$$

7

For the differential amplifier specified in Problem 9.1 let $v_{G2} = 0$ and $v_{G1} = v_{id}$ Find the value of v_{id} that corresponds to each of the following situations: For each case, find v_s , v_{D1} , v_{D2} , and $(v_{D2} - v_{D1})$.

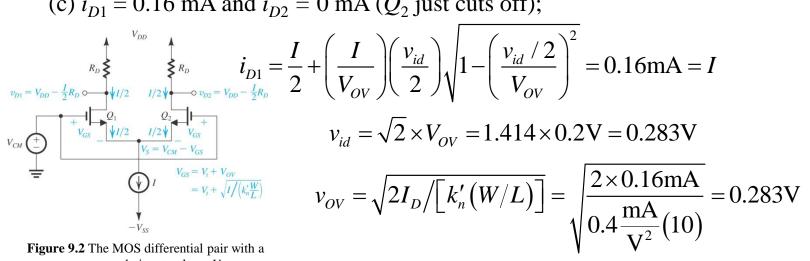(c) $i_{D1} = 0.16$ mA and $i_{D2} = 0$ mA (Q_2 just cuts off);



common-mode input voltage V_{CM} .

$$v_{GS} = V_t + v_{OV} = 0.4V + 0.283V = 0.683V$$

$$v_{D1} = V_{DD} - i_{D1}R_D = 1V - 0.16\text{mA} \times 5\text{k}\Omega = 0.2V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0\text{mA} \times 5\text{k}\Omega = 1V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0\text{mA} \times 5\text{k}\Omega = 1V$$

$$v_{D2} - v_{D1} = 1V - (0.2V) = 0.8V$$

For the differential amplifier specified in Problem 9.1 let $v_{G2} = 0$ and $v_{G1} = v_{id}$ Find the value of v_{id} that corresponds to each of the following situations: For each case, find v_s , v_{D1} , v_{D2} , and $(v_{D1} - v_{D2})$.

(d) $i_{D1} = 0.04$ mA and $i_{D2} = 0.12$ mA;

$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16 \text{mA}}{2} + \left(\frac{0.16 \text{mA}}{0.2 \text{V}}\right) \frac{v_{id}}{2} = 0.04 \text{mA} \qquad v_{id} = -0.10 \text{V}$$

$$v_{D1} = V_{D0} - \frac{I}{2}R_{D} \qquad v_{D2} = V_{DD} - \frac{I}{2}R_{D}$$

$$v_{CM} = \frac{I}{V_{CS}} \frac{I}{V_{I/2}} \frac{v_{OS}}{V_{CS}} = V_{DO} - \frac{I}{2}R_{D}$$

$$v_{D1} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16 \text{mA}}{2} - \left(\frac{0.16 \text{mA}}{0.2 \text{V}}\right) \frac{v_{id}}{2} = 0.12 \text{mA} \qquad v_{id} = -0.10 \text{V}$$

$$v_{CS} = V_{I} + V_{OV}$$

$$v_{CS} = V_{I} + V_{OV}$$

$$v_{CS} = V_{I} + V_{OV}$$

$$v_{I} = V_{I} + \frac{I}{V_{I/2}} \frac{V_{I/2}}{V_{CS}} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16 \text{mA}}{2} - \left(\frac{0.16 \text{mA}}{0.2 \text{V}}\right) \frac{v_{id}}{2} = 0.12 \text{mA} \qquad v_{id} = -0.10 \text{V}$$
Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$v_{GS} = V_t + v_{OV} = 0.4V + 0.141V = 0.541V$$

$$v_{D1} = V_{DD} - i_{D1}R_D = 1V - 0.04\text{mA} \times 5\text{k}\Omega = 0.8V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.12\text{mA} \times 5\text{k}\Omega = 0.4V$$


$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.12\text{mA} \times 5\text{k}\Omega = 0.4V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.12\text{mA} \times 5\text{k}\Omega = 0.4V$$

$$v_{D2} - v_{D2} = 0.4V - (0.8V) = -0.4V$$

For the differential amplifier specified in Problem 9.1 let $v_{G2} = 0$ and $v_{G1} = v_{id}$ Find the value of v_{id} that corresponds to each of the following situations: For each case, find v_s , v_{D1} , v_{D2} , and $(v_{D1} - v_{D2})$.

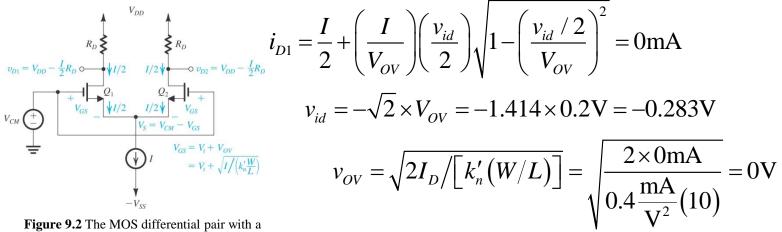(e) $i_{D1} = 0 \text{ mA}$ (Q_1 just cuts off) and $i_{D2} = 0.16 \text{ mA}$.



common-mode input voltage V_{CM} .

$$v_{GS} = V_t + v_{OV} = 0.4V + 0V = 0.4V$$

$$v_{D1} = V_{DD} - i_{D1}R_D = 1V - 0\text{mA} \times 5\text{k}\Omega = 1V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.16\text{mA} \times 5\text{k}\Omega = 0.2V$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1V - 0.16\text{mA} \times 5\text{k}\Omega = 0.2V$$

$$v_{D2} - v_{D2} = 0.2V - (1V) = -0.8V$$

Consider the differential amplifier specified in Problem 9.1 with G_2 grounded and V_{G1} = v_{id} . Let v_{id} be adjusted to the value that causes $i_{D1} = 0.09$ mA and $i_{D2} = 0.07$ mA. Find the corresponding values of v_{GS2} , v_{S} , v_{GS1} , and hence v_{id} . What is the difference output voltage v_{D2} - v_{D1} ? What is the voltage gain $(v_{D2}$ - $v_{D1})/v_{id}$? What value of v_{id} results in $i_{D1} = 0.07$ mA

and
$$i_{D2} = 0.09 \text{ mA?}$$

$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16 \text{mA}}{2} + \left(\frac{0.16 \text{mA}}{0.2 \text{V}}\right) \frac{v_{id}}{2} = 0.09 \text{mA}$$

$$v_{id} = 0.025 \text{V}$$

$$v_{D1} = V_{D0} - \frac{I}{2}R_{D} - \frac{I}{2}V_{OV} - \frac{I}{2}R_{D}$$

$$v_{CN} = \frac{I}{V_{CN}} - \frac{I}{V_{CN}} - \frac{I}{V_{CN}} - \frac{I}{V_{CN}} - \frac{I}{V_{OV}}$$

$$i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16 \text{mA}}{2} - \left(\frac{0.16 \text{mA}}{0.2 \text{V}}\right) \frac{v_{id}}{2} = 0.07 \text{mA}$$

$$v_{id} = 0.025 \text{V}$$

$$v_{CN} = \frac{V_{i} + V_{OV}}{V_{i} + V_{OV}} - \frac{I}{V_{i} + V_{i} + \frac{I}{V_{i} + V_{i} + V$$

Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$v_{GS} = V_t + v_{OV} = 0.4\text{V} + 0.212\text{V} = 0.612\text{V}$$

$$v_{D1} = V_{DD} - i_{D1}R_D = 1\text{V} - 0.09\text{mA} \times 5\text{k}\Omega = 0.55\text{V}$$

$$v_{S} = v_G - v_{GS} = 0.025\text{V} - 0.612\text{V} = -0.587\text{V}$$

$$v_{D2} = V_{DD} - i_{D2}R_D = 1\text{V} - 0.07\text{mA} \times 5\text{k}\Omega = 0.65\text{V}$$

$$\frac{v_{D2} - v_{D2}}{v_{is}} = \frac{0.1 \text{V}}{0.025 \text{V}} = 4 \text{V/V}$$

 $v_{D2} - v_{D2} = 0.65 \text{V} - (0.55 \text{V}) = 0.1 \text{V}$

Consider the differential amplifier specified in Problem 9.1 with G_2 grounded and $v_{G1} = v_{id}$. Let v_{id} be adjusted to the value that causes $i_{D1} = 0.09$ mA and $i_{D2} = 0.07$ mA. Find the corresponding values of v_{GS2} , v_S , v_{GS1} , and hence v_{id} . What is the difference output voltage v_{D2} - v_{D1} ? What is the voltage gain $(v_{D2}$ - $v_{D1})/v_{id}$? What value of v_{id} results in $i_{D1} = 0.07$ mA and $i_{D2} = 0.09$ mA?

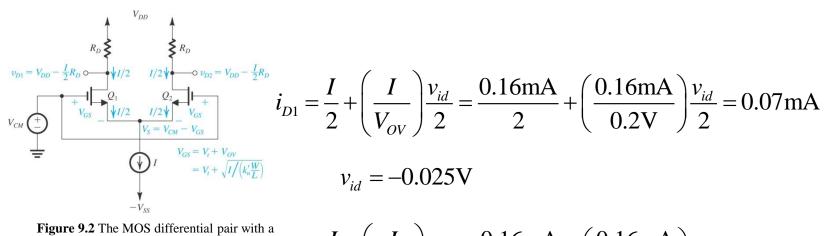


Figure 9.2 The MOS differential pair with a common-mode input voltage V_{CM} .

$$i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \frac{v_{id}}{2} = \frac{0.16\text{mA}}{2} - \left(\frac{0.16\text{mA}}{0.2\text{V}}\right) \frac{v_{id}}{2} = 0.09\text{mA}$$

$$v_{id} = -0.025 \text{V}$$

Homework

An NMOS differential amplifier is operated at a bias current I of 0.2 mA and has a W/L ratio of 32, $\mu_n C_{ox} = 200 \mu A/V^2$, $V_A = 10$ V, and $R_D = 10$ k Ω . Find V_{OV} , g_m , r_o , and A_d .

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.2 \text{mA}}{2} = \frac{1}{2} \mu_n c_{ox} \left(\frac{W}{L}\right)_1 V_{OV}^2$$

$$V_{OV} = \sqrt{2I_D/[\mu_c c_{ox}(W/L)]} = \sqrt{\frac{0.2\text{mA}}{0.2\frac{\text{mA}}{V^2}(32)}} = 0.176\text{V}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{0.2\text{mA}}{0.176\text{V}} = 1.14\text{mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{10 \text{V}}{0.1 \text{mA}} = 100 \text{k}\Omega$$

$$A_d = g_m(r_o || R_D) = 1.14 \text{mA/V} \times (100 \text{k}\Omega || 10 \text{k}\Omega) = 10.36 \text{V/V}$$

Problem 9.19a

Figure P9.19 shows a MOS differential amplifier with the drain resistors R_D implemented using diode connected PMOS transistors, Q_3 and Q_4 . Let Q_1 and Q_2 be matched, and Q_3 and Q_4 be matched.

(a) Find the differential half-circuit and use it to derive an expression for A_d in terms of $g_{m1,2}$, $g_{m3,4}$, $r_{o1,2}$, and $r_{o3,4}$.

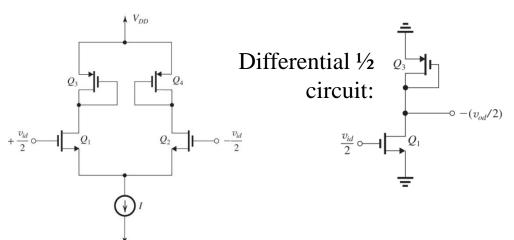


Figure P9.19

The gate to source resistance of a "diode" connected FET is $1/g_m||r_o|$


$$G \circ \longrightarrow G \circ$$

$$A_{d} = g_{m1}(r_{o1} || R_{D}) = g_{m1}(r_{o1} || \frac{1}{g_{m3}} || r_{o3})$$

Problem 9.19b

Figure P9.19 shows a MOS differential amplifier with the drain resistors R_D implemented using diode connected PMOS transistors, Q_3 and Q_4 . Let Q_1 and Q_2 be matched, and Q_3 and Q_4 be matched.

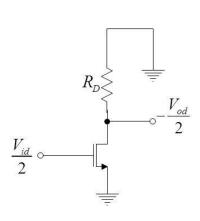(b) Neglecting the effect of the output resistances r_o , find A_d in terms of μ_n , μ_p , $(W/L)_{1,2}$, and $(W/L)_{3,4}$.



$$R_{D} = \frac{1}{g_{m3}} || r_{o3} \simeq \frac{1}{g_{m3}}$$

$$A_{d} = g_{m1} (r_{o1} || R_{D}) \simeq g_{m1} R_{D} = \frac{g_{m1}}{g_{m3}}$$


$$g_m = \sqrt{2\mu_{n,p}C_{ox}(W/L)I_D}$$

$$A_{d} = \frac{g_{m1}}{g_{m3}} = \frac{\sqrt{2\mu_{n}C_{ox}(W/L)_{1}I_{D}}}{\sqrt{2\mu_{p}C_{ox}(W/L)_{3}I_{D}}} = \sqrt{\frac{\mu_{n}(W/L)_{1}}{\mu_{p}(W/L)_{3}}}$$

Problem 9.19c

Figure P9.19 shows a MOS differential amplifier with the drain resistors R_D implemented using diode connected PMOS transistors, Q_3 and Q_4 . Let Q_1 and Q_2 be matched, and Q_3 and Q_4 be matched.

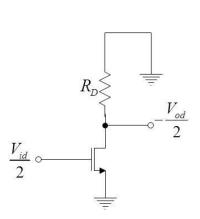(c) If $\mu_n = 4\mu_p$ and all four transistors have the same channel length, find $(W_{1,2}/W_{3,4})$ that results in $A_d = 10 \text{ V/V}$.



$$A_{d} = \frac{g_{m1}}{g_{m3}} = \frac{\sqrt{2\mu_{n}C_{ox}(W/L)_{1}I_{D}}}{\sqrt{2\mu_{p}C_{ox}(W/L)_{3}I_{D}}} = \sqrt{\frac{\mu_{n}(W/L)_{1}}{\mu_{p}(W/L)_{3}}}$$

$$A_d = 10\text{V/V} = \sqrt{\frac{4\mu_p (W/L)_1}{\mu_p (W/L)_3}}$$

$$\frac{(W/L)_{1}}{(W/L)_{3}} = 5^{2} = 25$$

For the differential amplifier of Fig. 9.15(a) let I = 0.4 mA, $V_{CC} = V_{EE} = 2.5$ V, $V_{CM} = -1 \text{ V}, R_C = 5 \text{ k}\Omega$, and $\beta = 100$. Assume that the BJTs have $v_{BE} = 0.7 \text{ V}$ at i_C = 1mA. Find the voltage at the emitters and at the outputs.

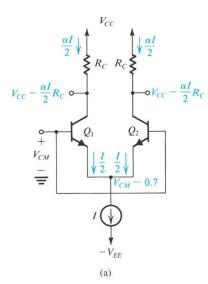


Figure 9.15: Different modes of operation of the BJT differential pair: (a) the differential pair with a common-mode input voltage V_{CM} .

$$i_{E} = \frac{I}{2} = \frac{0.4 \text{ mA}}{2} = 0.2 \text{mA}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.990$$

$$i_{C} = \alpha I_{E} = 0.99 \cdot 0.20 \text{ mA} = 0.198 \text{mA}$$

$$v_{BE} = 0.7 \text{ V at } i_{C} = 1 \text{ mA, need } v_{BE} \text{ at } i_{C} = 0.198 \text{ mA}$$

$$i_{C} = I_{S}e^{v_{BE}/V_{T}} \qquad \ln\left(\frac{i_{C1}}{i_{C2}}\right) = \frac{v_{BE1} - v_{BE2}}{V_{T}} \qquad v_{BE1} = v_{BE2} + V_{T} \ln\left(\frac{i_{C1}}{i_{C2}}\right)$$

$$i_{C} = I_{S}e^{v_{BE}/V_{T}} \qquad \ln\left(\frac{i_{C1}}{i_{C2}}\right) = \frac{v_{BE1} - v_{BE2}}{V_{T}} \qquad v_{BE1} = v_{BE2} + V_{T}\ln\left(\frac{i_{C1}}{i_{C2}}\right)$$

$$v_{BE} = 0.7V + 0.025V \times \ln\left(\frac{0.198\text{mA}}{1\text{mA}}\right) = 0.660V$$

$$v_E = v_B - v_{BE} = -1V - 0.660V = -1.660V$$

$$v_{o1,2} = v_{C1,2} = V_{CC} - \alpha R_C (I/2) = 2.5 \text{V} - (0.99) 5 \text{k}\Omega \left(\frac{0.4 \text{mA}}{2}\right) = 1.51 \text{V}$$

An *npn* differential amplifier with I = 0.4 mA, $V_{CC} = V_{EE} = 2.5$ V, and $R_C = 5$ k Ω utilizes BJTs with $\beta = 100$ and $v_{BE} = 0.7$ V at $i_C = 1$ mA. Assuming that the bias current is obtained by a simple current source and that all transistors require a minimum of 0.3 V for operation in the active mode, find the input common-mode range.

R. Martin

$$V_{CM\text{max}} \approx V_C + 0.4 = V_{CC} - \alpha \frac{I}{2} R_C + 0.3$$

$$V_{CM\text{max}} = 2.5 \text{V} - (0.99) \left(\frac{0.4 \text{mA}}{2} \right) 5 \text{k}\Omega + 0.3 \text{V} = 1.81 \text{V}$$

$$V_{\rm CMmin} = -V_{\rm EE} + V_{\rm CS} + V_{\rm BE}$$

$$v_{BE} = 0.7 \text{ V at } i_C = 1 \text{ mA}$$

$$v_{BE} = 0.7\text{V} + 0.025\text{V} \times \ln\left(\frac{0.198\text{mA}}{1\text{mA}}\right) = 0.660\text{V}$$

$$V_{CM_{\text{min}}} = -2.5\text{V} + 0.3\text{V} + 0.660\text{V} = -1.54\text{V}$$

Homework

Design the circuit of Fig. 9.14 to provide a differential output voltage (i.e., one taken between the two collectors) of 1 V when the differential input signal is 10 mV. A current source of 1 mA and a positive supply of +5 V are available. What is the largest possible input common-mode voltage for which operation is as required? Assume $\alpha \approx 1$.

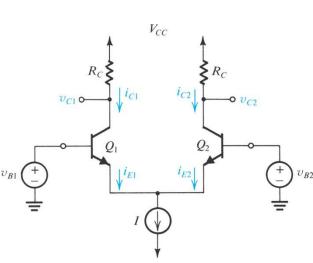


Figure 9.14: The basic BJT differentialpair configuration.

$$i_{E1} = \frac{1}{1 + e^{(v_{B2} - v_{B1})/V_{T}}} \qquad i_{E1} = \frac{I}{1 + e^{-v_{id}/V_{T}}}$$

$$i_{E1} = \frac{I}{1 + e^{-v_{id}/V_{T}}}$$

$$i_{E1} = \frac{ImA}{1 + e^{-0.01V/0.025V}} = 0.599mA$$

$$i_{E2} = I - i_{E1} = 1mA - 0.599mA = 0.401mA$$

$$v_{od} = R_{C}(i_{C1} - i_{C2}) \approx R_{C}(i_{E1} - i_{E2}) = 1V$$

$$R_{C} = \frac{1V}{(i_{E1} - i_{E2})} = \frac{1V}{0.198mA} = 5.05k\Omega$$

$$v_{c1} = V_{CC} - i_{c1}R_C = 5V - (0.599 \text{mA})5.05 \text{k}\Omega = 1.975 \text{V}$$

 $v_{c2} = V_{CC} - i_{c2}R_C = 5V - (0.401 \text{mA})5.05 \text{k}\Omega = 2.975 \text{V}$
 $V_{CM\text{max}} = v_{C1} + 0.4 = 2.375 \text{V}$