

Problem 1

$$\text{KCL: } -i_1(t) + i_2(t) + i_3(t) = 0 \Rightarrow +i_3(t) = i_1(t) - i_2(t)$$

$$\begin{aligned} i_3(t) &= 141.4 \cos(\omega t + 135^\circ) \text{ mA} - 50 \sin(\omega t - 53.13^\circ) \text{ mA} = \\ &= 141.4 \cos(\omega t + 135^\circ) \text{ mA} - 50 \cos(\omega t - 53.13^\circ - 90^\circ) \text{ mA} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_3 &= 141.4 \text{ mA} \angle 135^\circ - 50 \text{ mA} \angle -143.13^\circ = \\ &= (-99.98 + j \cdot 99.98) \text{ mA} - (-40.00 - j \cdot 30.00) \text{ mA} = \\ &= (-59.98 + j \cdot 129.98) \text{ mA} = 143.2 \text{ mA} \angle 114.8^\circ \end{aligned}$$

$$i_3(t) = 143.2 \cos(\omega t + 114.8^\circ) \text{ mA}$$

If sine functions were used, the result in phasor notation would differ in phase by 90 degrees.

Problem 2


Solution:

Known quantities:

The values of the impedance, $R_s = 50 \Omega$, $R_c = 40 \Omega$, $L = 20 \mu\text{H}$, $C = 1.25 \text{ nF}$, and the voltage applied to the circuit shown in Figure P4.53,

$$v_s(t) = V_0 \cos(\omega t + 0^\circ) \quad V_0 = 10 \text{ V}, \quad \omega = 6 \text{ M} \frac{\text{rad}}{\text{s}}.$$

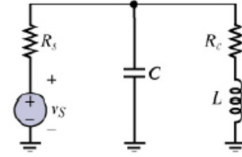Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Find:

The current supplied by the source.

Analysis:

Assume clockwise currents:

$$X_L = \omega L = \left(6 \text{ M} \frac{\text{rad}}{\text{s}}\right)(20 \mu\text{H}) = 1203 \Omega \Rightarrow Z_L = 0 + j120 \Omega = 120 \angle 90^\circ \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{\left(6 \text{ M} \frac{\text{rad}}{\text{s}}\right)(1.25 \text{ nF})} = 133.3 \Omega \Rightarrow Z_C = 0 - j133.3 \Omega = 133.3 \angle -90^\circ \Omega$$

$$Z_{R_c} = 40 - j \Omega = 40 \angle 0^\circ \Omega, \quad Z_{R_s} = 50 - j \Omega = 50 \angle 0^\circ \Omega$$

Equivalent impedances:

$$Z_{eq1} = Z_{R_c} + Z_L = 40 + j120 \Omega = 126.5 \angle 71.56^\circ \Omega$$

$$\begin{aligned} Z_{eq} &= Z_{R_s} + \frac{Z_C \cdot Z_{eq1}}{Z_C + Z_{eq1}} = 50 + j0 \Omega + \frac{(133.3 \angle -90^\circ \Omega)(126.5 \angle 71.56^\circ \Omega)}{133.3 \angle -90^\circ \Omega + 126.5 \angle 71.56^\circ \Omega} = \\ &= 50 + j0 \Omega + \frac{16.87 \angle -18.44^\circ \text{ k}\Omega^2}{42.161 \angle -18.44^\circ \Omega} = 50 \angle 0^\circ \Omega + 400 \angle 0^\circ \Omega = 450 \angle 0^\circ \Omega \end{aligned}$$

$$\text{OL: } \mathbf{I}_s = \frac{\mathbf{V}_s}{Z_{eq}} = \frac{10 \angle 0^\circ \text{ V}}{450 \angle 0^\circ \Omega} = 22.22 \angle 0^\circ \text{ mA} \Rightarrow i_s(t) = 22.22 \cos(\omega t + 0^\circ) \text{ mA}$$

Note:

The equivalent impedance of the parallel combination is purely resistive; therefore, the frequency given is the resonant frequency of this network.

Problem 3

Solution:

Known quantities:

The values of the impedance and the current source for the circuit shown in Figure P4.56.

Find:

The current I_1 .

Analysis:


Specifying the positive directions of the currents as in figure P4.45:

$$Z_{eq} = \frac{1}{\frac{1}{2} + \left(\frac{1}{-j4}\right)} = 1.79 \angle 26.56^\circ \Omega$$

$$V_S = I_S Z_{eq} = (10 \angle -\pi/8) \text{ A} \cdot (1.79 \angle 26.56^\circ) \Omega = 17.9 \angle 4.06^\circ \text{ V}$$

$$I_1 = \frac{V_S}{R} = 8.95 \angle 4.06^\circ \text{ A}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

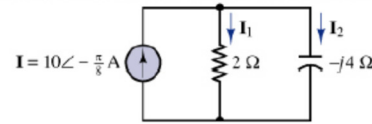

Problem 4

Solution:

Known quantities:

The values of the impedance and the voltage source for circuit shown in Figure P4.57.

Find:

The voltage V_2 .


Analysis:

Specifying the positive directions as in figure P4.57:

$$Z_L = j\omega L = j12 \Omega$$

$$V_2 = \frac{R_{6\Omega}}{R_{12\Omega} + Z_L + R_{6\Omega}} V = \frac{6 \Omega}{(12 + j12 + 6) \Omega} 25 \angle 0^\circ \text{ V} = \frac{150 \angle 0^\circ \Omega}{18 + j12 \Omega} \text{ V} = 6.93 \angle -33.7^\circ \text{ V}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

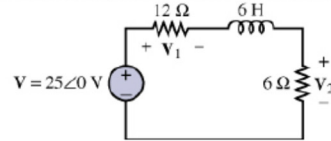

Problem 5

Solution:

Known quantities:

The circuit shown in Figure P4.61, the values of the resistance, $R = 2 \Omega$, capacitance, $C = 1/8 \text{ F}$, inductance,

$L = 1/4 \text{ H}$, and the frequency $\omega = 4 \frac{\text{rad}}{\text{s}}$.

Find:

The impedance Z .


Analysis:

$$Z_L = j\omega L = j4 \frac{1}{4} \Omega = j \Omega, \quad Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C} = -j \frac{1}{4 \cdot (1/8)} = -j2 \Omega$$

$$Z = Z_L + Z_C \parallel R = Z_L + \frac{1}{\frac{1}{Z_C} + \frac{1}{R}} = j + \frac{1}{\frac{1}{-j2} + \frac{1}{2}} = j + \frac{j2}{-1+j} = j + \frac{(j2)(-1-j)}{(-1+j)(-1-j)}$$

$$= j + \frac{j2(-1-j)}{1+1} = j - j + 1 = 1 \Omega$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

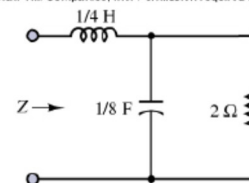

Problem 6

Solution:

Known quantities:

Circuit shown in Figure P4.72 the values of the resistance, $R_1 = 4\ \Omega$, $R_2 = 4\ \Omega$, capacitance, $C = 1/4\ \text{F}$, inductance, $L = 2\ \text{H}$, and the voltage source $v_s(t) = 2\cos(2t)\ \text{V}$.

Find:

The current in the circuit $i_L(t)$ using phasor techniques.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Analysis:

$$V_S(t) = 2\angle 0^\circ\ \text{V}$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2 \cdot \frac{1}{4}} = -j2\ \Omega$$

$$Z_L = j\omega L = j2 \cdot 2 = j4\ \Omega$$

Applying the voltage divider rule:

$$V_L = \frac{(Z_L \parallel (Z_C + Z_2))}{Z_1 + (Z_L \parallel (Z_C + Z_2))} V_S = \frac{4\angle 36.8^\circ}{4\angle 0^\circ + 4\angle 36.8^\circ} 2\angle 0^\circ = 1.05\angle 18.4^\circ\ \text{V}$$

Therefore, the current is:

$$I_L = \frac{V_L}{Z_L} = \frac{1.05\angle 18.4^\circ}{4\angle 90^\circ} = 0.2635\angle -71.6^\circ\ \text{A}$$

$$i_L(t) = 0.2635\cos(2t - 71.6^\circ)\ \text{A}$$

