

UNIVERSITY *of* DELAWARE

Chapter 4

Diodes





IN THIS CHAPTER YOU WILL LEARN

1. The characteristics of the ideal diode and how to analyze and design circuits containing multiple ideal diodes together with resistors and dc sources to realize useful and interesting nonlinear functions.
2. The details of the i - v characteristic of the junction diode (which was derived in Chapter 3) and how to use it to analyze diode circuits operating in the various bias regions: forward, reverse, and breakdown.
3. A simple but effective model of the diode i - v characteristic in the forward direction; the constant-voltage-drop model.



IN THIS CHAPTER YOU WILL LEARN

4. A powerful technique for the application and modeling of the diode (and in later chapters, transistors): dc-biasing the diode and modeling its operation for small signals around the dc operating point by means of the small-signal model.
5. The use of a string of forward-biased diodes and of diodes operating in the breakdown region (zener diodes), to provide constant dc voltages (voltage regulators).
6. Application of the diode in the design of rectifier circuits, which convert ac voltages to dc as needed for powering electronic equipment.
7. A number of other practical and important applications of diodes.



4.1 THE IDEAL DIODE



The Ideal Diode

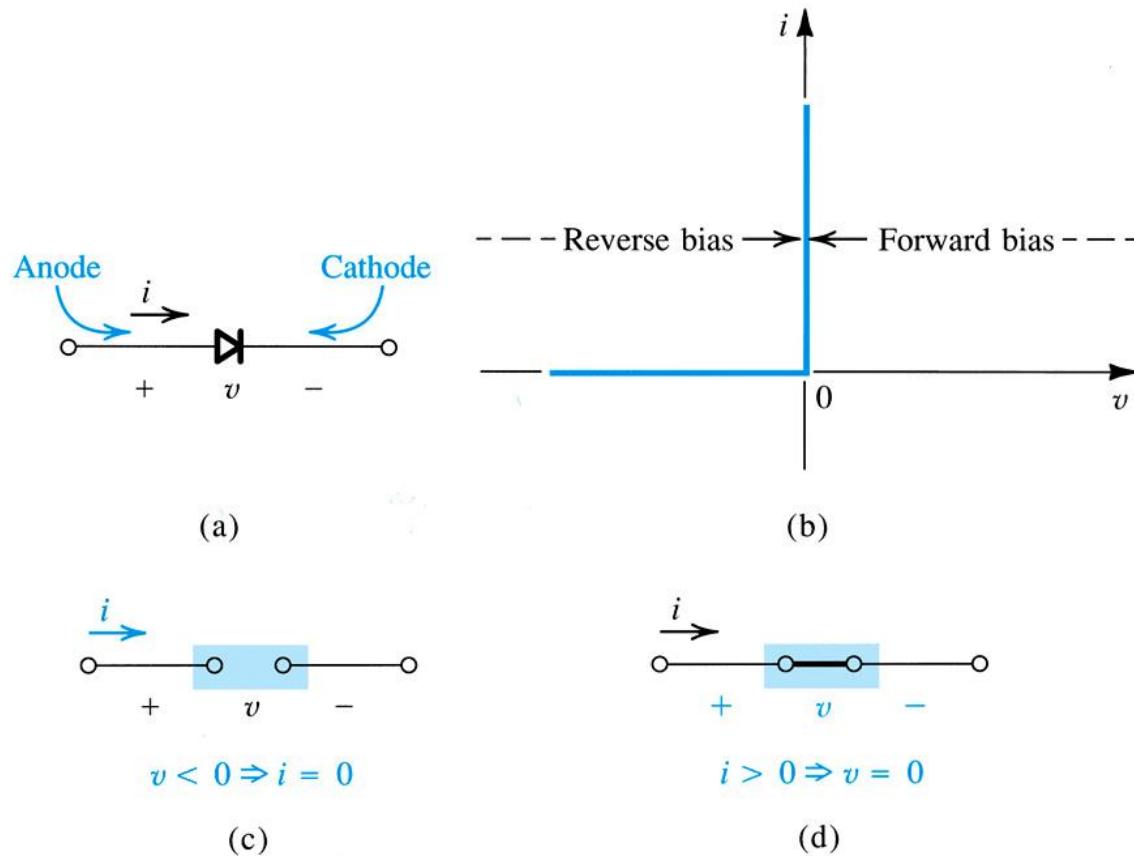


Figure 4.1 The ideal diode: (a) diode circuit symbol; (b) i - v characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction.



Modes of Operation

- Forward Bias
 - Current limited by bias voltage and series resistance.
 - On, turned-on
- Reverse Bias
 - Voltage limited by bias voltage
 - Off, cut-off

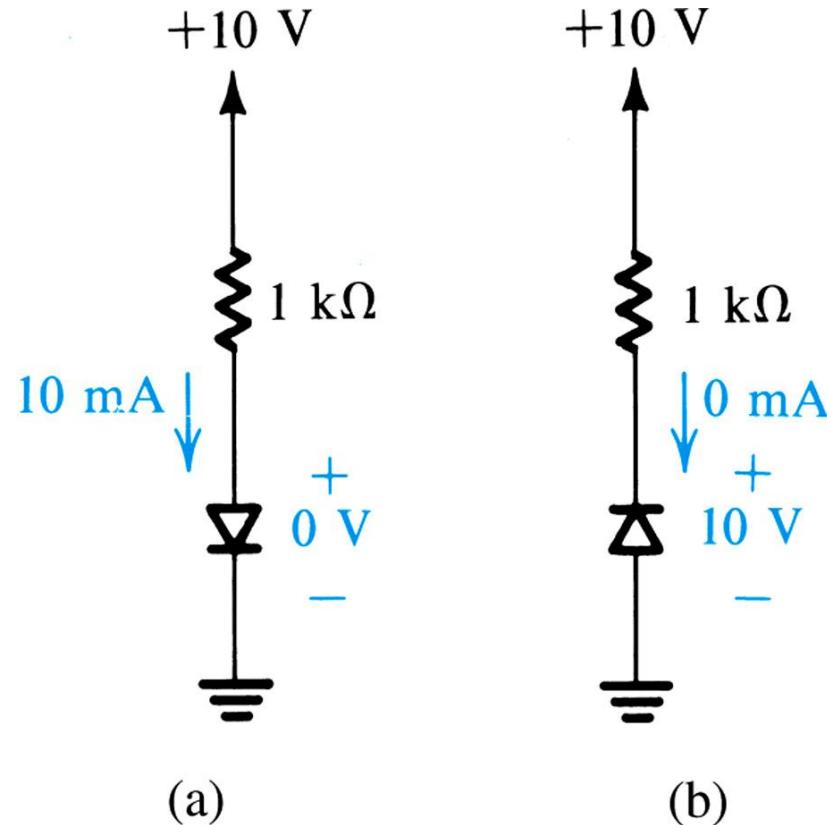


Figure 4.2 The two modes of operation of ideal diodes and the use of an external circuit to limit (a) the forward current and (b) the reverse voltage.



Uses of Diodes

- Rectification
- Switching
- Logic
- Reference Voltages
- Limiting and clamping
- Generating and detecting optical signals



Rectification

A **rectifier** is an electrical device that converts alternating current (AC), which periodically reverses direction, to direct current (DC), which flows in only one direction. The process is known as **rectification**. Physically, rectifiers take a number of forms, including vacuum tube diodes, mercury-arc valves, solid-state diodes, silicon-controlled rectifiers and other silicon-based semiconductor switches. Historically, even synchronous electromechanical switches and motors have been used. Early radio receivers, called crystal radios, used a "cat's whisker" of fine wire pressing on a crystal of galena (lead sulfide) to serve as a point-contact rectifier or "crystal detector".

Rectifiers have many uses, but are often found serving as components of DC power supplies and high-voltage direct current power transmission systems. Rectification may serve in roles other than to generate direct current for use as a source of power. As noted, detectors of radio signals serve as rectifiers. In gas heating systems *flame rectification* is used to detect presence of flame.

<http://en.wikipedia.org/wiki/Rectifier>



Application: Rectifier Circuit


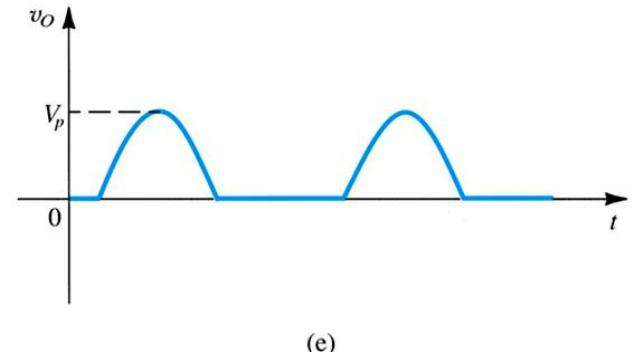
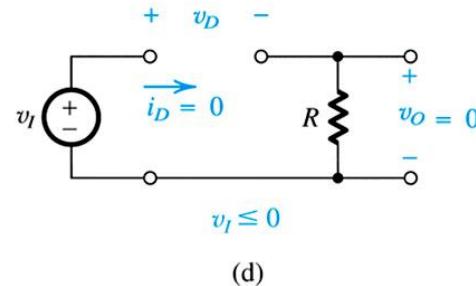
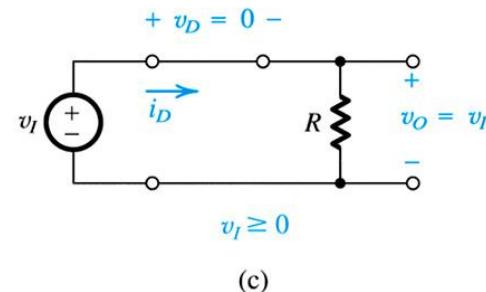
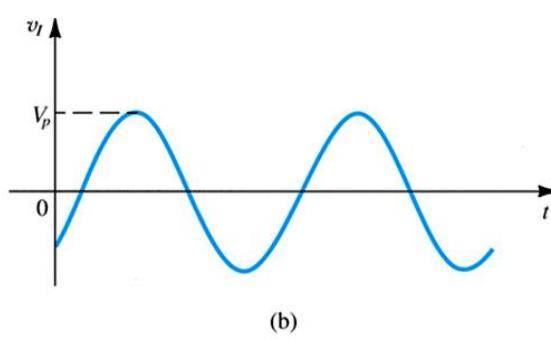


Figure 4.3 (a) Rectifier circuit. (b) Input waveform. (c) Equivalent circuit when $v_i \geq 0$.
(d) Equivalent circuit when $v_i \leq 0$. (e) Output waveform.

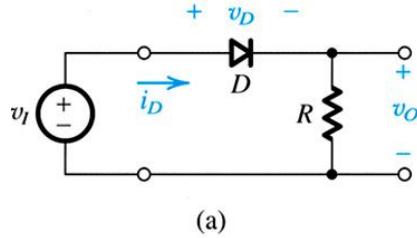

Rectifier Circuit

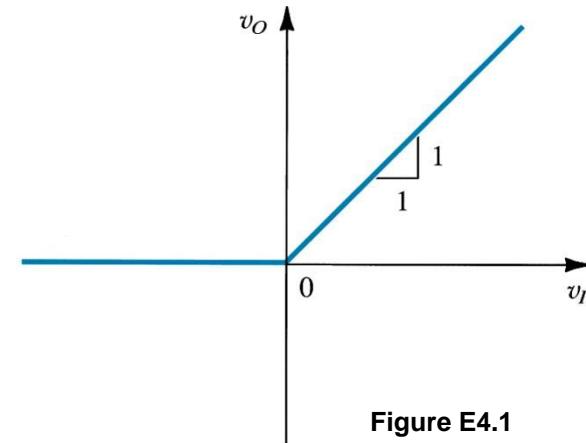
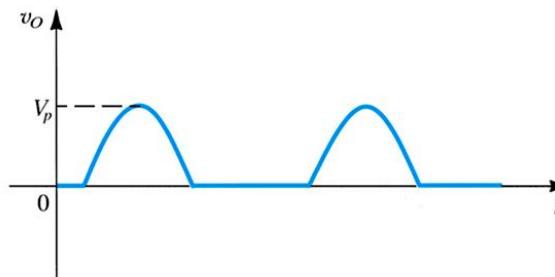
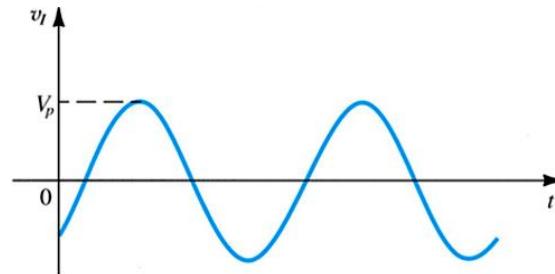
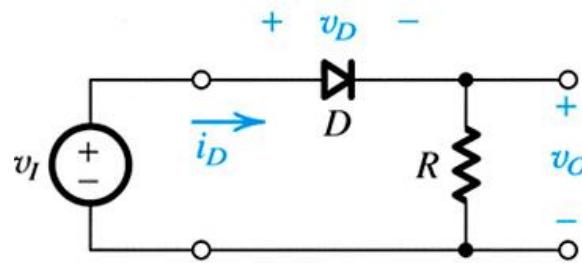


Figure E4.1

Transfer characteristic

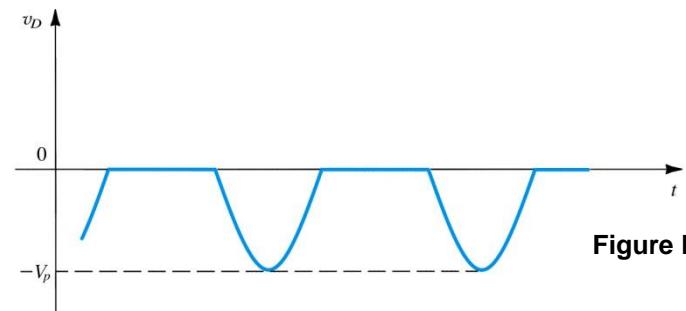


Figure E4.2

Voltage across the diode



Example 4.1 (p. 180)

Figure 4.4 shows a circuit for charging a 12-V battery. If v_S is a sinusoid with 24-V peak amplitude, find the fraction of each cycle during which the diodes conduct. Also, find the peak value of the diode current and the maximum reverse-bias that appears across the diode.


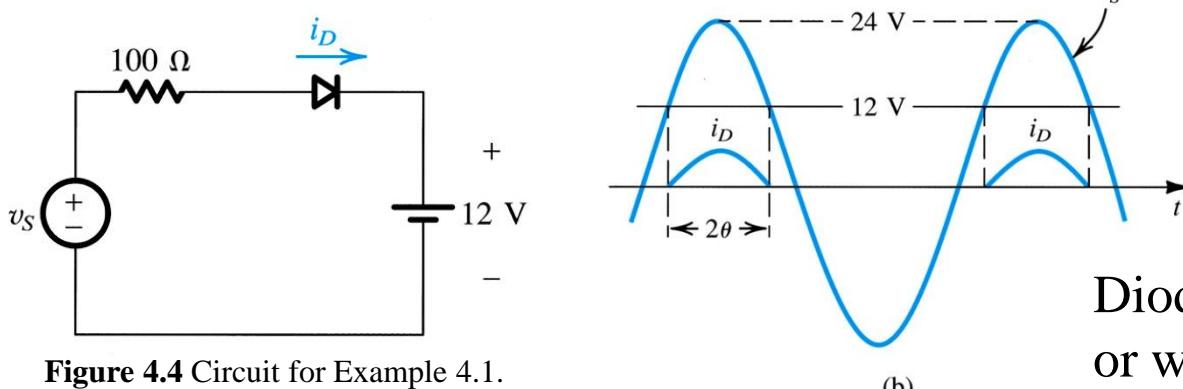


Figure 4.4 Circuit for Example 4.1.

$$v_S = 24 \sin \theta$$

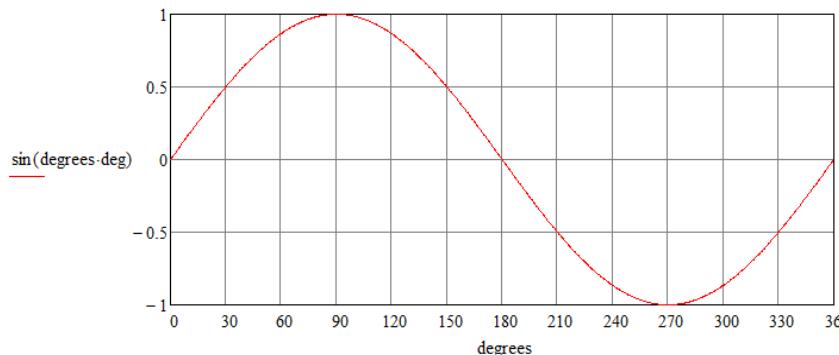Diode conducts when $v_S \geq 12 \text{ V}$ or when $\sin \theta \geq 0.5$.



$\sin \theta \geq 0.5$ when $30^\circ \leq \theta \leq 150^\circ$
so the diode is conducting
 $120^\circ/360^\circ$ or $1/3$ of a cycle.



Example 4.1 (p. 180)

Figure 4.4 shows a circuit for charging a 12-V battery. If v_S is a sinusoid with 24-V peak amplitude, find the fraction of each cycle during which the diodes conduct. Also, find the peak value of the diode current and the maximum reverse-bias voltage that appears across the diode.


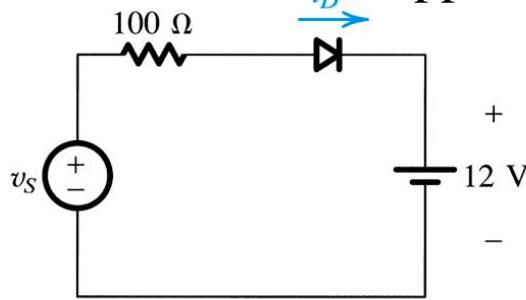


Figure 4.4 Circuit for Example 4.1.

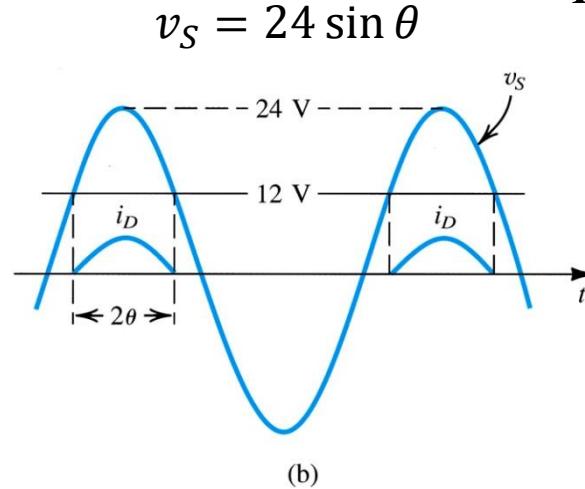


Peak current is when $v_S = 24 \text{ V}$

$$I_d = \frac{24\text{V} - 12\text{V}}{100\Omega} = 0.12\text{A}$$

The maximum reverse bias voltage is when $v_S = -24 \text{ V}$ so the total reverse voltage across the diode is $24 \text{ V} + 12 \text{ V} = 36 \text{ V}$



Application: Diode Logic Gates

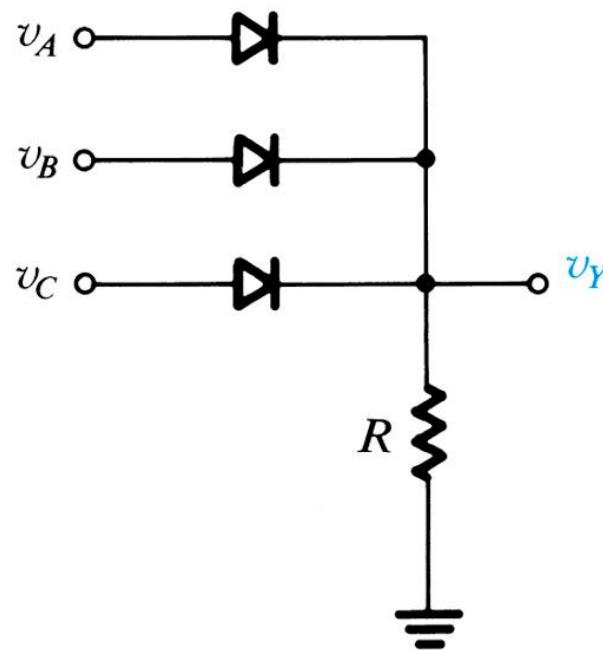

v_A	v_B	v_C	v_Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
...			
1	1	0	1
1	1	1	1


$$Y = A + B + C$$

Figure 4.5 Diode logic gates: (a) OR gate;.

logic OR function



Application: Diode Logic Gates

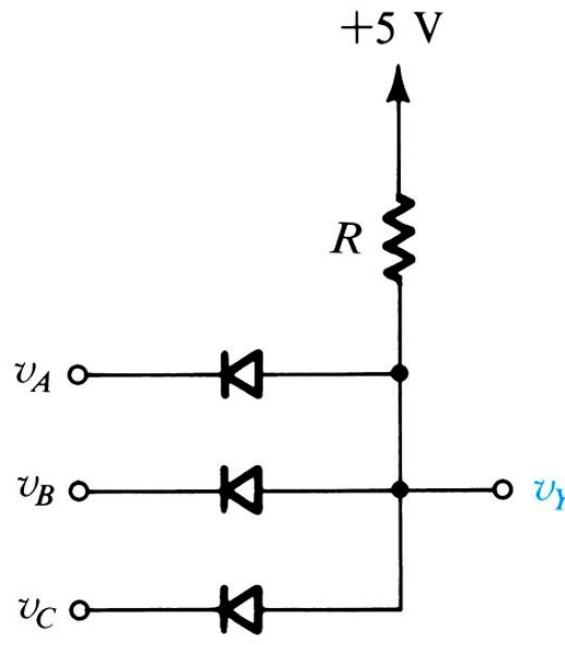

v_A	v_B	v_C	v_Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
...			
1	1	0	0
1	1	1	1

Figure 4.5 Diode logic gates: (b) AND gate (in a positive-logic system).


$$Y = A \cdot B \cdot C$$

logic AND function



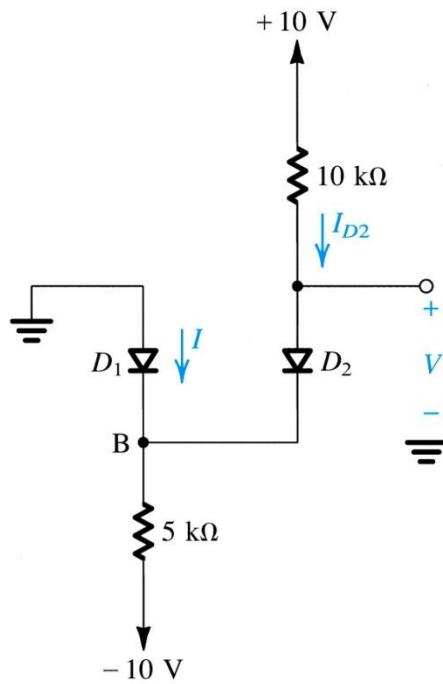Example 4.2a

Assuming the diodes to be ideal, find the values of I and V in the circuits of Fig. 4.6.



Assume D_1 is conducting, then the voltage at node B is 0 V and D_2 is also conducting and the output voltage, $V = 0$ V.

$$I_{D2} = \frac{10V}{10k\Omega} = 1mA$$

$$I + I_{D2} = \frac{10V}{5k\Omega} = 2mA$$


$$I = 1mA$$

Figure 4.6 Circuits for Example 4.2.



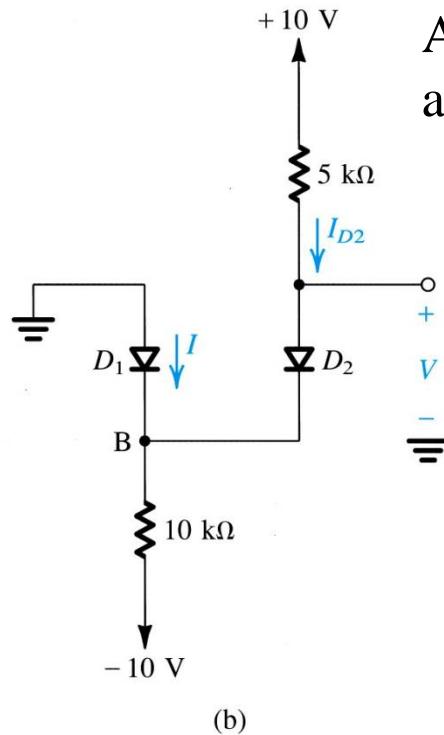Example 4.2b

Assuming the diodes to be ideal, find the values of I and V in the circuits of Fig. 4.6.



Assume D_1 is conducting, then the voltage at node B is 0 V and D_2 is also conducting and the output voltage, $V = 0$ V.

$$I_{D2} = \frac{10V}{5k\Omega} = 2mA$$

$$I + I_{D2} = \frac{10V}{10k\Omega} = 1mA \quad I = -1mA$$

Which can't be correct so D_1 can't be conducting, which means that the current, $I = 0$ A. The voltage at node B is

$$V = V_B = -10V + 20V \frac{10k\Omega}{15k\Omega} = 3.33V$$


$$I_{D2} = \frac{10V - 3.33V}{5k\Omega} = 1.33mA$$

Figure 4.6 Circuits for Example 4.2.




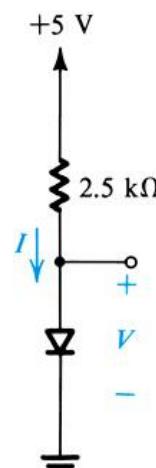Exercise 4.4 (a-c)


Find the values of I and V in the circuits shown in Fig. E4.4



(a)

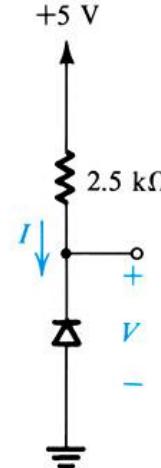

(b)

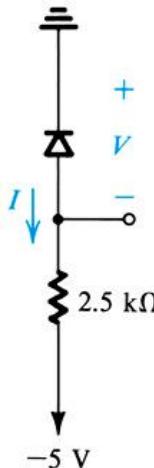

(c)

Figure E4.4

$$I = \frac{5V}{2.5k\Omega} = 2mA$$

$$V = 0V$$

$$I = 0A$$

$$V = +5V$$

$$I = 0A$$

$$V = -5V$$



Exercise 4.4 (d-f)

Find the values of I and V in the circuits shown in Fig. E4.4

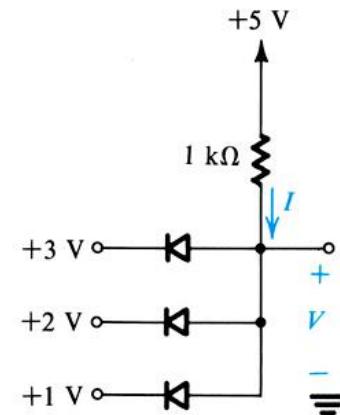
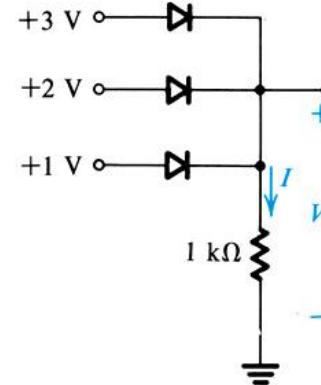
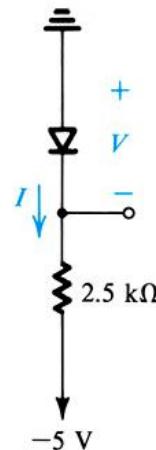


Figure E4.4

$$I = \frac{5V}{2.5k\Omega} = 2mA$$


$$V = 0V$$

$$I = \frac{3V}{1k\Omega} = 3mA$$

$$V = +3V$$

$$I = \frac{5V - 1V}{1k\Omega} = 4mA$$

$$V = +1V$$

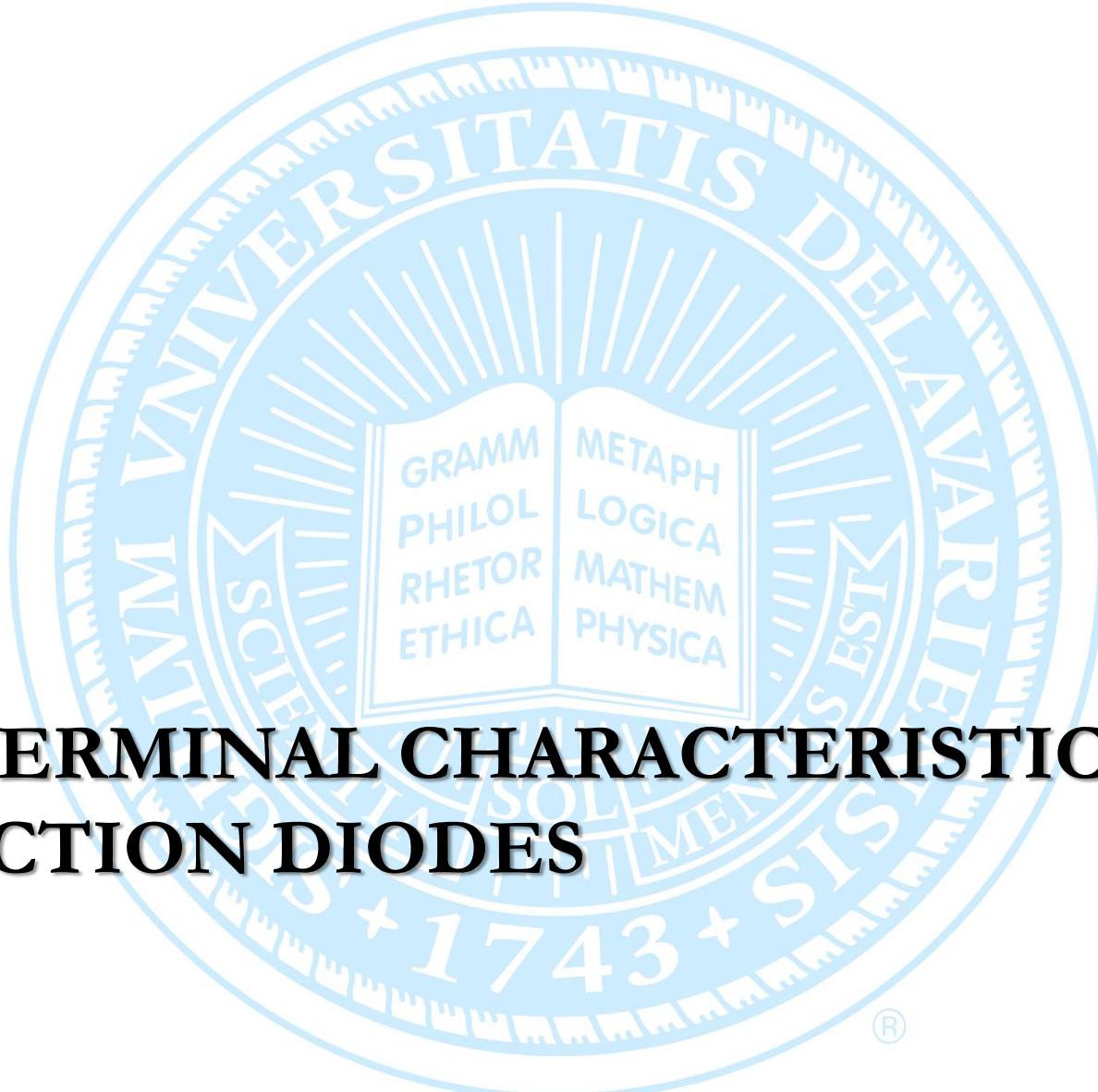

4.2 TERMINAL CHARACTERISTICS OF JUNCTION DIODES



i - v characteristic of a silicon junction diode


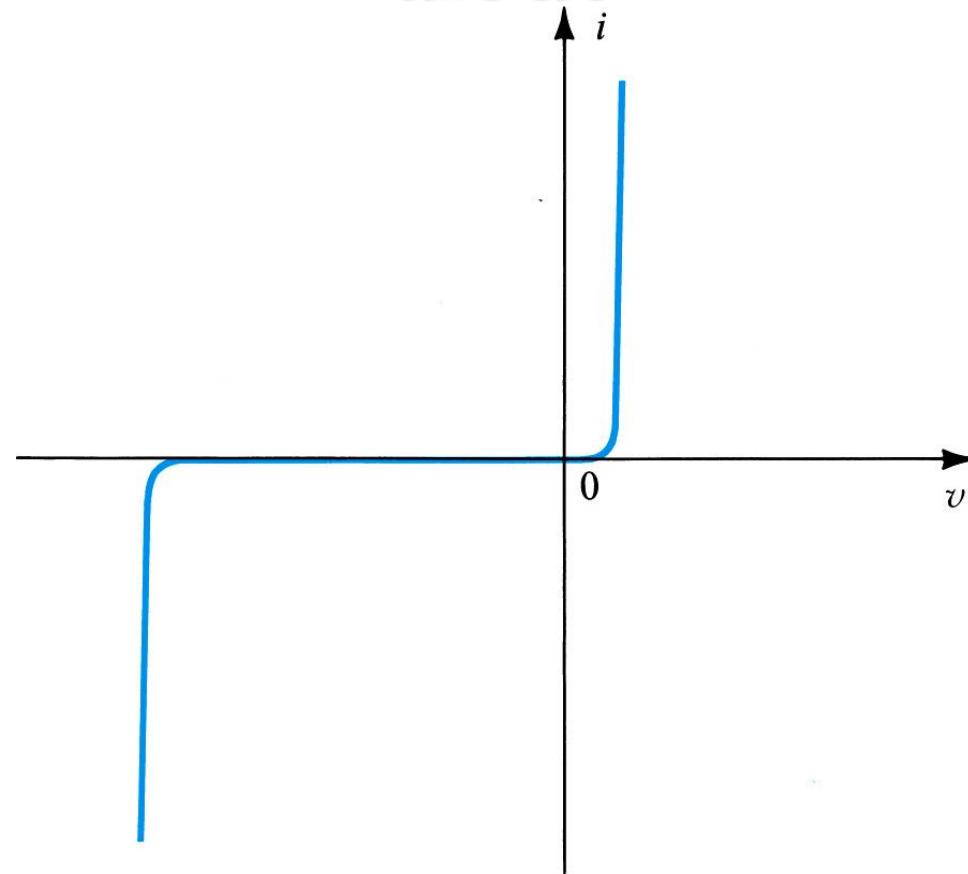


Figure 4.7 The i - v characteristics of a silicon junction diode.

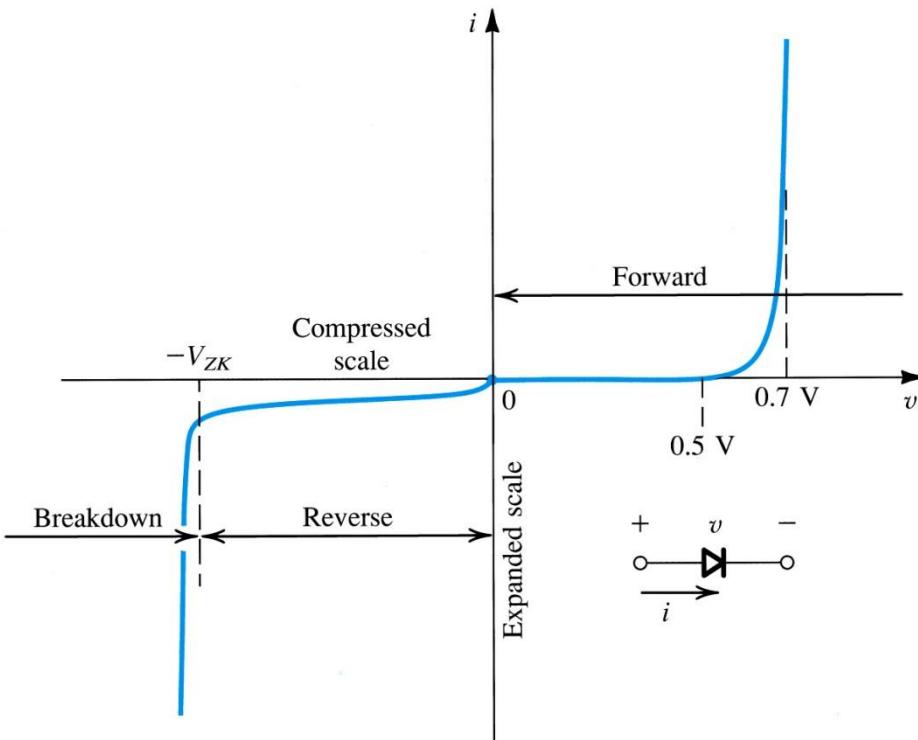

i - v characteristic of a silicon junction diode



The characteristic curve consists of three distinct regions:

- 1 The forward-bias region, determined by $v > 0$
2. The reverse-bias region, determined by $v < 0$
3. The breakdown region, determined by $v < -V_{ZK}$

Figure 4.8 The diode i - v relationship with some scales expanded and others compressed in order to reveal details.



The Forward-Bias Region

From Chapter 3: $I = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) (e^{V/V_T} - 1)$

If we define the saturation current or scale current, I_S , as:

$$I_S = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

$$i = I_S (e^{v/V_T} - 1)$$

The current I_S is usually called the saturation current (for reasons that will become apparent shortly). Another name for I_S is the scale current. This name arises from the fact that I_S is directly proportional to the cross-sectional area of the diode. Thus doubling of the junction area results in a diode with double the value of I_S and, as the diode equation indicates, double the value of current i for a given forward voltage v . For "small-signal" diodes, which are small-size diodes intended for low-power applications, I_S is on the order of 10 fA. The value of I_S is, however, a very strong function of temperature. As a rule of thumb, I_S doubles in value for every 5°C rise in temperature.



The Forward-Bias Region

$$i = I_S(e^{v/V_T} - 1)$$

Where $V_T = \frac{kT}{q}$ is known as the thermal voltage

k is the Boltzmann constant [8.617×10^{-5} eV/K]

T is the temperature in Kelvin

q is the magnitude of the electrical charge on the electron [1.602×10^{-19} C]

$$V_T = 0.0862T \text{ mV}$$

At 20°C (293.15 K, 68°F, room temperature) $V_T = 25.3 \text{ mV} \approx 25.0 \text{ mV}$

A slightly higher ambient temperature (25°C or so) is usually assumed for electronic equipment operating inside a cabinet. At this temperature, $V_T \sim 25.8 \text{ mV}$. Nevertheless, for the sake of simplicity and to promote rapid circuit analysis, we shall use the more arithmetically convenient value of $V_T \sim 25 \text{ mV}$ throughout the rest of this book/class.



The Forward-Bias Region

$$i = I_S(e^{v/V_T} - 1)$$

For case where $i \gg I_S$ the curve can be approximated by $i \simeq I_S e^{v/V_T}$

$$v = V_T \ln \frac{i}{I_S}$$

At diode voltage V_1 $I_1 = I_S e^{V_1/V_T}$

$$\frac{I_2}{I_1} = e^{(V_2-V_1)/V_T}$$



At diode voltage V_2 $I_2 = I_S e^{V_2/V_T}$

$$V_2 - V_1 = V_T \ln \frac{I_2}{I_1} = 2.3V_T \log \frac{I_2}{I_1}$$

This equation simply states that for a decade change in current, the diode voltage drop changes by $2.3 V_T$ which is approximately 60 mV. This also suggests that the diode i - v relationship is most conveniently plotted on semilog paper. Using the vertical, linear axis for v and the horizontal, log axis for i , one obtains a straight line with a slope of 60 mV per decade of current.



Linear, Semilog $v-i$ Plot

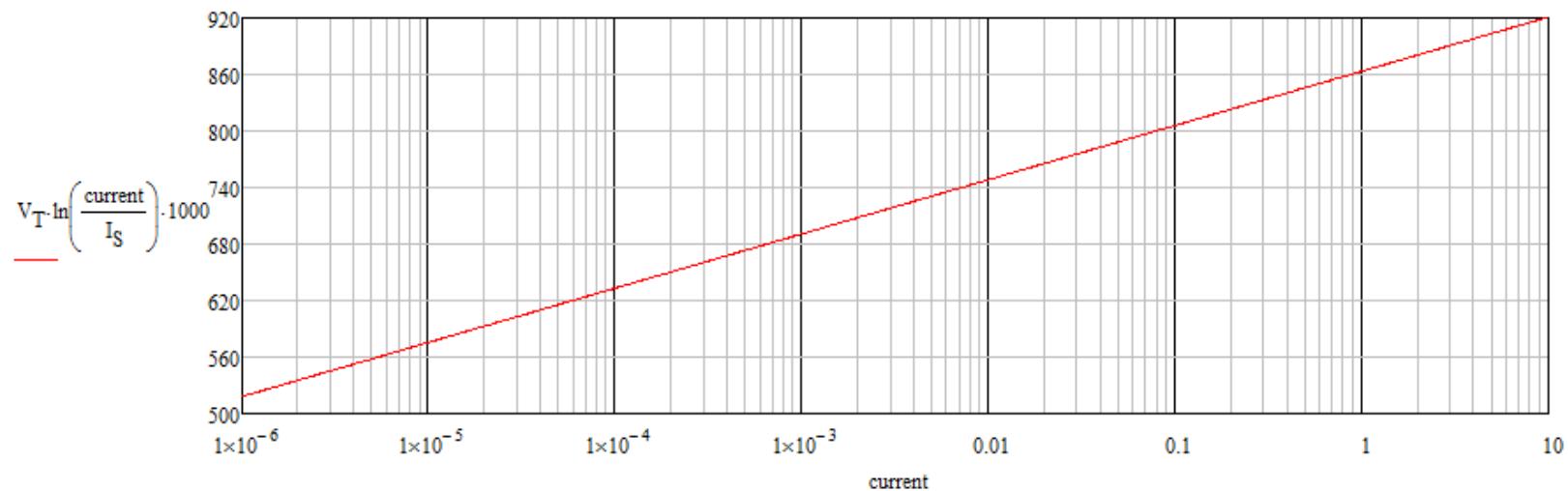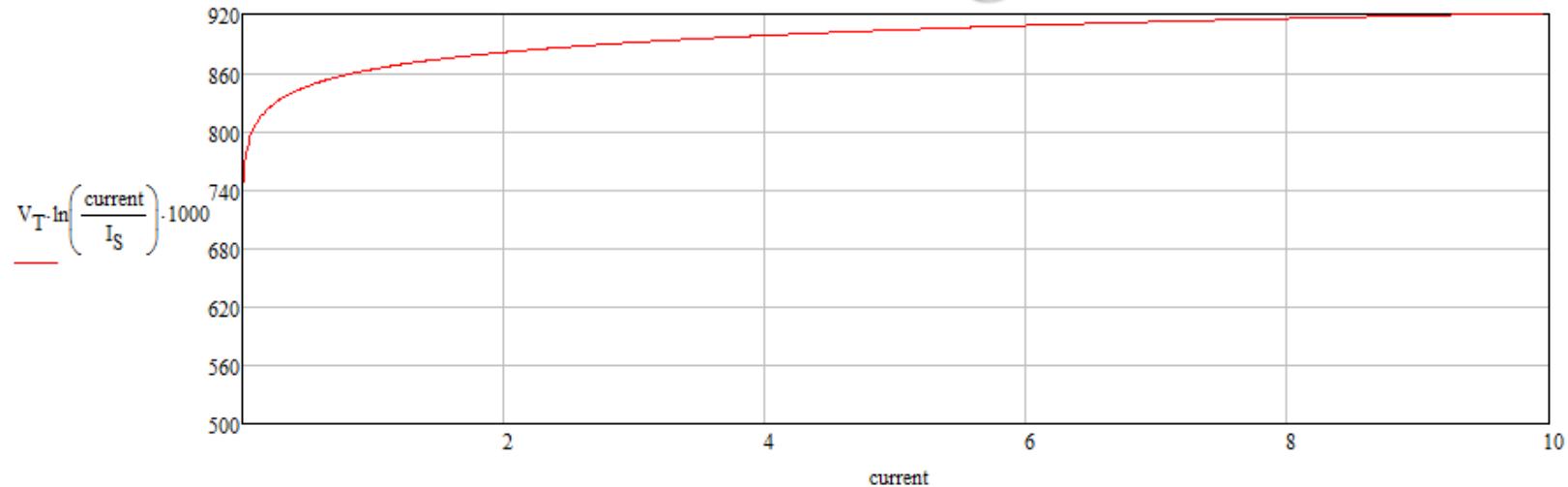



Example 4.3

A silicon diode said to be a 1-mA device displays a forward voltage of 0.7 V at a current of 1 mA. Evaluate the junction scaling constant I_S . What scaling constants would apply for a 1-A diode of the same manufacture that conducts 1 A at 0.7 V?

$$i = I_S e^{v/V_T}$$

$$I_S = \frac{i}{e^{v/V_T}} = i e^{-v/V_T}$$
$$I_S := 1\text{mA} \cdot e^{\frac{-0.7\text{V}}{V_T}} = 0.691\text{fA}$$

$$I_S := 1\text{A} \cdot e^{\frac{-0.7\text{V}}{V_T}} = 691.44\text{fA}$$



Forward Bias – Temperature Effects

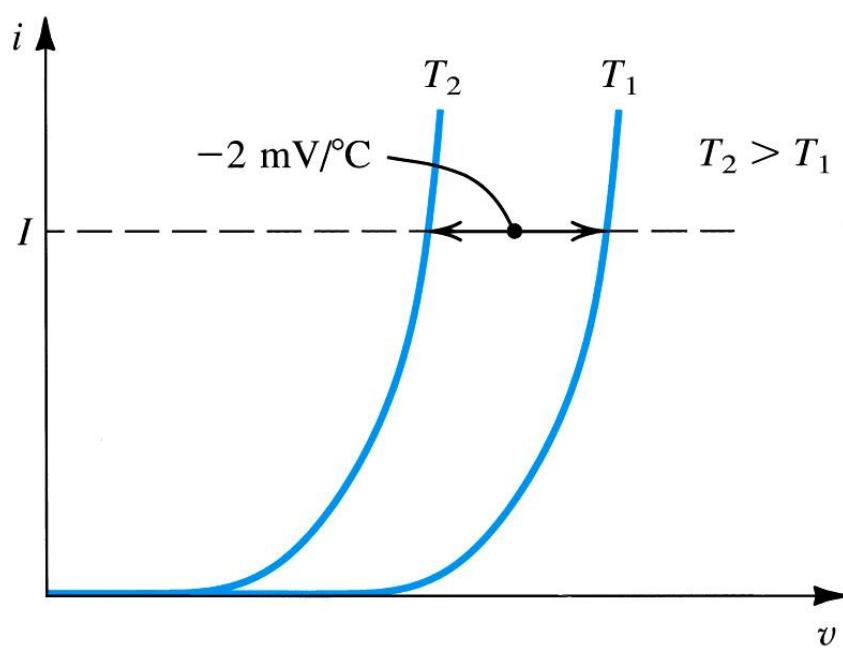


Figure 4.9 Temperature dependence of the diode forward characteristic. At a constant current, the voltage drop decreases by approximately 2 mV for every 1°C increase in temperature.

$$V_T = \frac{kT}{q} \quad I_S = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$

Since both I_S and V_T are functions of temperature, the forward $i-v$ characteristic varies with temperature, as illustrated in Fig. 4.9. At a given constant diode current, the voltage drop across the diode decreases by approximately 2 mV for every 1°C increase in temperature. The change in diode voltage with temperature has been exploited in the design of electronic thermometers.



The Reverse-Bias Region

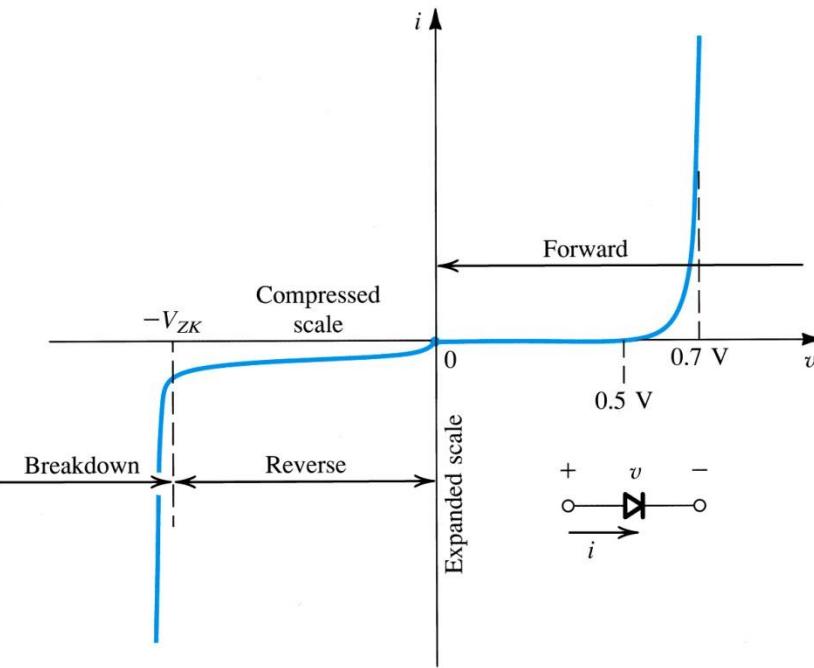


Figure 4.8 The diode i - v relationship with some scales expanded and others compressed in order to reveal details.

For case where $v > V_T$ and is negative the curve can be approximated by $i \simeq -I_S$

The current in the reverse direction is constant and equal to I_S . This constancy is the reason behind the term **saturation current**.

Real diodes exhibit reverse currents that, though quite small, are much larger than I_S . For instance, a small-signal diode whose I_S is on the order of 10^{-14} to 10^{-15} Amps could show a reverse current on the order of 1 nA. The rule of thumb for the temperature dependence of the reverse current is that it doubles for every 10°C rise in temperature.



Reverse Current

NXP Semiconductors
Product data sheet

High-speed diodes 1N4148; 1N4448

LIMITING VALUES
In accordance with the Absolute Maximum Rating System (IEC 60134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
V_{RRM}	repetitive peak reverse voltage		–	100	V
V_R	continuous reverse voltage		–	100	V
I_F	continuous forward current	see Fig.2; note 1	–	200	mA
I_{FPM}	repetitive peak forward current		–	450	mA
I_{FSM}	non-repetitive peak forward current	square wave; $T_j = 25^\circ\text{C}$ prior to surge; see Fig.4	–	4	A
		$t = 1 \mu\text{s}$	–	1	A
		$t = 1 \text{ ms}$	–	0.5	A
P_{tot}	total power dissipation	$T_{amb} = 25^\circ\text{C}$; note 1	–	500	mW
T_{stg}	storage temperature		–85	+200	°C
T_j	junction temperature		–	200	°C

Note

- Device mounted on an FR4 printed-circuit board; lead length 10 mm.

ELECTRICAL CHARACTERISTICS
 $T_j = 25^\circ\text{C}$ unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
V_F	forward voltage 1N4148 1N4448	see Fig.3 $I_F = 10 \text{ mA}$ $I_F = 5 \text{ mA}$ $I_F = 100 \text{ mA}$	–	1 0.62 1	V V V
I_R	reverse current	$V_R = 20 \text{ V}$; see Fig.5	25	nA	
I_R	reverse current	$V_R = 20 \text{ V}; T_j = 150^\circ\text{C}$; see Fig.5	–	50	μA
C_d	diode capacitance	$f = 1 \text{ MHz}; V_R = 0 \text{ V}$; see Fig.6	–	4	pF
t_{fr}	reverse recovery time	when switched from $I_F = 10 \text{ mA}$ to $I_F = 80 \text{ mA}$; $R_L = 100 \Omega$; measured at $I_A = 1 \text{ mA}$; see Fig.7	–	4	ns
V_{fr}	forward recovery voltage	when switched from $I_F = 50 \text{ mA}$; $t_r = 20 \text{ ns}$; see Fig.8	–	2.5	V

THERMAL CHARACTERISTICS

SYMBOL	PARAMETER	CONDITIONS	VALUE	UNIT
$R_{th(j-to-p)}$	thermal resistance from junction to tie-point	lead length 10 mm	240	K/W
$R_{th(j-to-A)}$	thermal resistance from junction to ambient	lead length 10 mm; note 1	350	K/W

Note

- Device mounted on a printed-circuit board without metallization pad.

2004 Aug 10 3

May 2009

FAIRCHILD SEMICONDUCTOR®

1N4001 - 1N4007
General Purpose Rectifiers

Features

- Low forward voltage drop.
- High surge current capability.


DO-41
COLOR BAND DENOTES CATHODE

Absolute Maximum Ratings * $T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value							Units
		4001	4002	4003	4004	4005	4006	4007	
V_{RRM}	Peak Repetitive Reverse Voltage	50	100	200	400	600	800	1000	V
$I_{F(AV)}$	Average Rectified Forward Current .375" lead length @ $T_A = 75^\circ\text{C}$							1.0	A
I_{FSM}	Non-Repetitive Peak Forward Surge Current 8.3ms Single Half-Sine-Wave							30	A
I^*	Rating for Fusing (1-8.3ms)							3.7	A ² sec
T_{STG}	Storage Temperature Range							-55 to +175	°C
T_J	Operating Junction Temperature							-55 to +175	°C

* These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

Thermal Characteristics

Symbol	Parameter	Value	Units
P_D	Power Dissipation	3.0	W
R_{thJA}	Thermal Resistance, Junction to Ambient	50	°CW

Electrical Characteristics $T_A = 25^\circ\text{C}$ unless otherwise noted


Symbol	Parameter	Value	Units
V_F	Forward Voltage @ 1.0A	1.1	V
I_{fr}	Maximum Full Load Reverse Current, Full Cycle $T_A = 75^\circ\text{C}$	30	μA
I_R	Reverse Current @ Rated V_R , $T_A = 25^\circ\text{C}$ $T_A = 100^\circ\text{C}$	5.0 50	μA μA
C_T	Total Capacitance $V_R = 4.0\text{V}$, $f = 1.0\text{MHz}$	15	pF

© 2009 Fairchild Semiconductor Corporation
1N4001 - 1N4007 Rev. C2 1 www.fairchildsemi.com



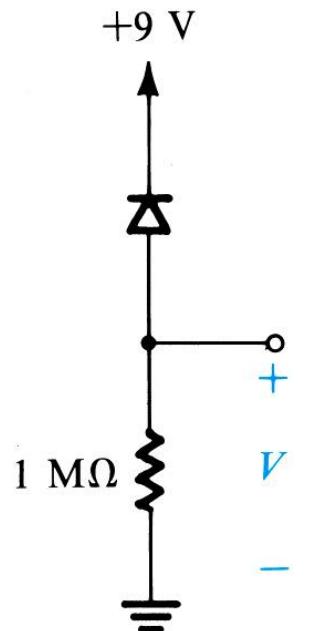Exercise 4.9

The diode in the circuit of Fig. E4.9 is a large high-current device whose reverse leakage is reasonably independent of voltage. If $V = 1\text{ V}$ at 20°C , find the value of V at 40°C and at 0°C .



The rule of thumb for the temperature dependence of the reverse current is that it doubles for every 10°C rise in temperature.

$$40^\circ\text{C} = 2 \times 10^\circ\text{C} \text{ increase} \rightarrow V = 4 \times 1\text{ V} = 4\text{V}$$

$$0^\circ\text{C} = 2 \times 10^\circ\text{C} \text{ decrease} \rightarrow V = \frac{1}{4} \times 1\text{ V} = 0.25\text{ V}$$



Figure E4.9



The Breakdown Region

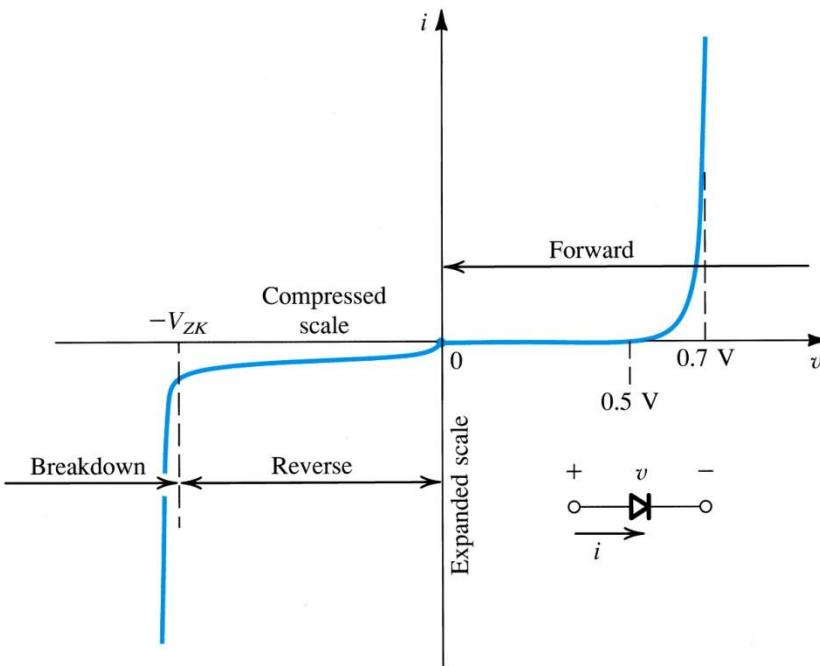


Figure 4.8 The diode i - v relationship with some scales expanded and others compressed in order to reveal details.

The breakdown region is entered when the magnitude of the reverse voltage exceeds a threshold value that is particular to a specific diode, called the **breakdown voltage**. This is the voltage at the “knee” of the i - v curve and designated as V_{ZK} .


The fact that the diode i - v characteristic in breakdown is almost a vertical line enables it to be used in voltage regulation.



Homework #7

- Read Chapter 4
- Chapter 4 Problems:
 - 4.2*
 - 4.3*
 - 4.9*
 - 4.17*
 - 4.23*

* Answers in Appendix L

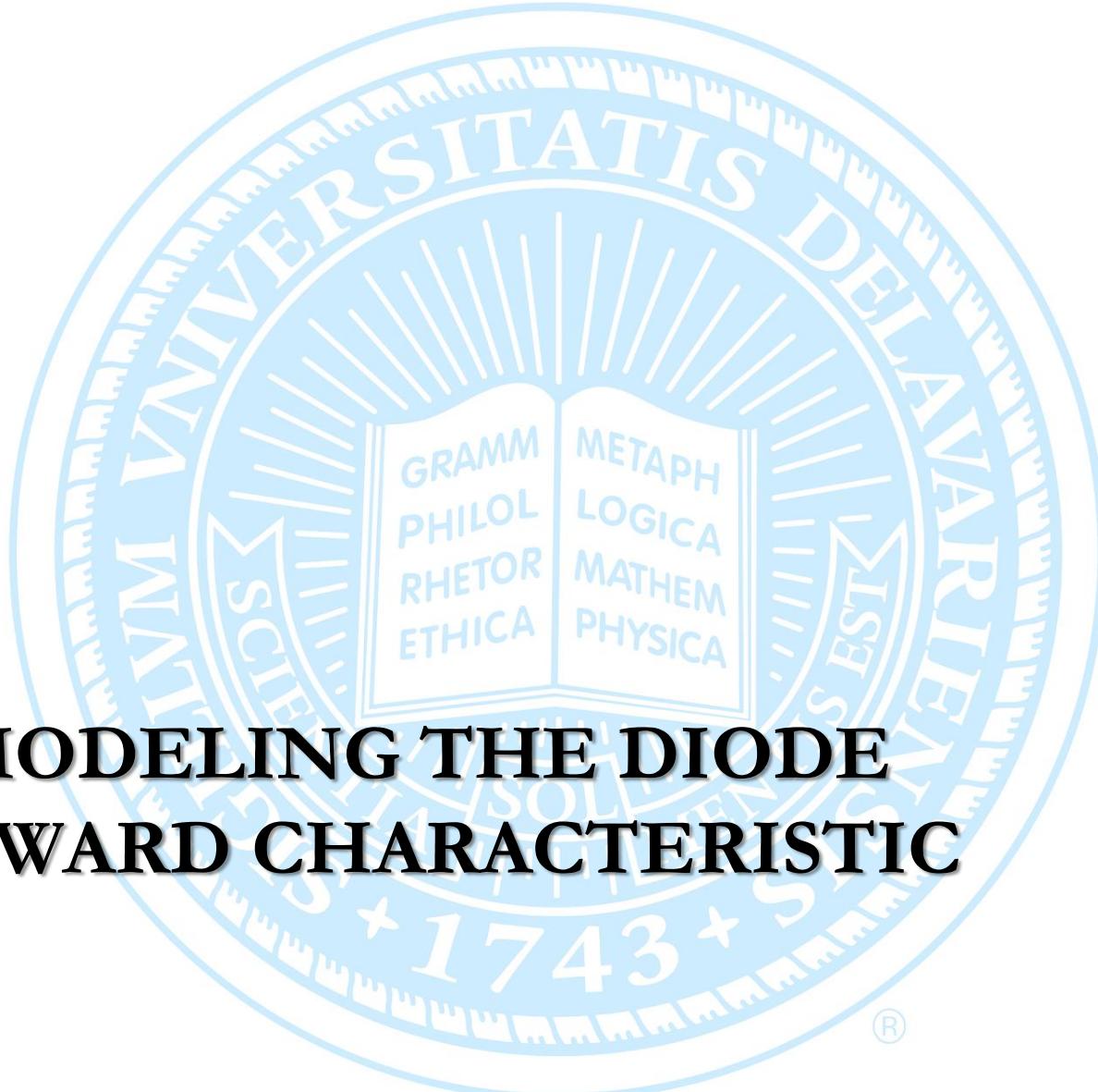

4.3 MODELING THE DIODE FORWARD CHARACTERISTIC



The Exponential Model

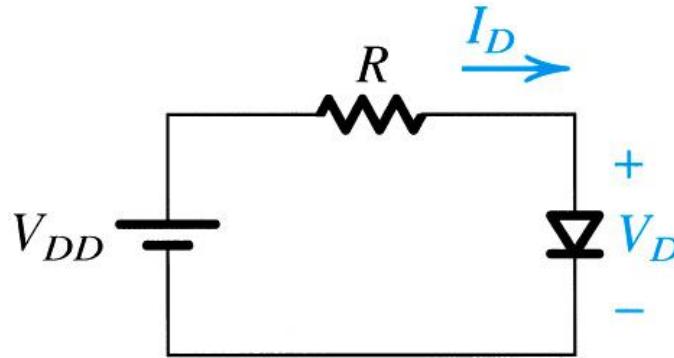


Figure 4.10 A simple circuit used to illustrate the analysis of circuits in which the diode is forward conducting.

Assuming that V_{DD} is greater than 0.5 V or so, the diode current will be much greater than I_S ,

$$I_D = I_S(e^{V_D/V_T} - 1) \cong I_S e^{V_D/V_T}$$

and we can represent the diode *i-v* characteristic by the exponential relationship, resulting in

$$I_D = I_S e^{V_D/V_T}$$

From Kirchhoff's loop equation:


$$I_D = \frac{V_{DD} - V_D}{R}$$

If we know V_T , V_{DD} , and I_S we have 2 equations with 2 unknowns (I_D and V_D) which we can solve in two ways:

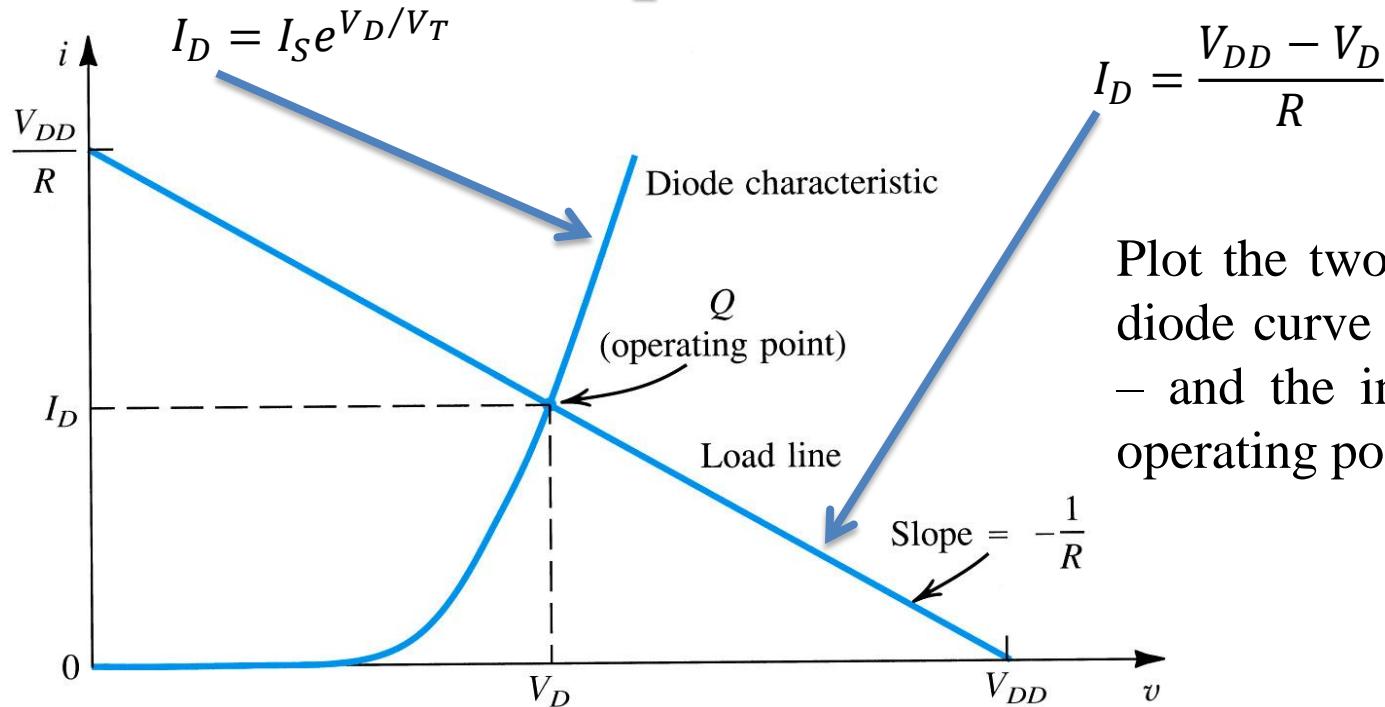1. graphical analysis
2. iterative analysis



Graphical Analysis Using the Exponential Model



Plot the two i - v curves – the diode curve and the load line – and the intersection is the operating point (Q).

Figure 4.11 Graphical analysis of the circuit in Fig. 4.10 using the exponential diode model.



Iterative Example 4.4 (p.192)

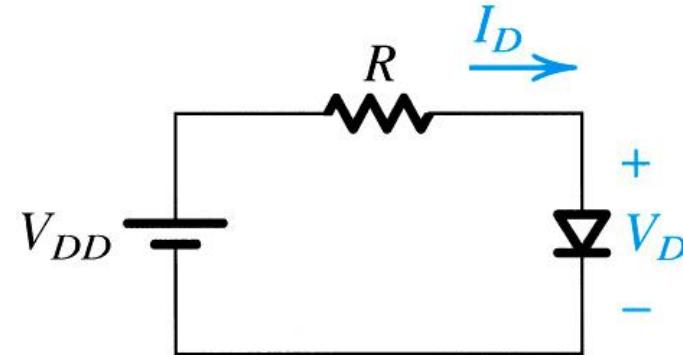


Figure 4.10 A simple circuit used to illustrate the analysis of circuits in which the diode is forward conducting.

Determine the current I_D and the diode voltage V_D for the circuit in Fig 4.10 with $V_{DD} = 5$ V and $R = 1$ k Ω . Assume that the diode has a current of 1 mA at a voltage of 0.7 V.

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5V - 0.7V}{1k\Omega} = 4.3\text{mA}$$

But 4.3 mA is 4.3x the 1 mA specification current $V_2 - V_1 = 2.3V_T \log \frac{I_2}{I_1}$

$$V_2 = V_1 + 2.3V_T \log \frac{I_2}{I_1}$$


$$V_2 = 0.7V + 2.3(.025V) \log \frac{4.3\text{mA}}{1\text{mA}} = 0.736V$$

$$I_D = \frac{5V - 0.736V}{1k\Omega} = 4.264\text{mA}$$

$$V_2 = 0.736V + 2.3(.025V) \log \frac{4.264\text{mA}}{4.3\text{mA}} = 0.736V$$



The Constant Voltage Drop Model

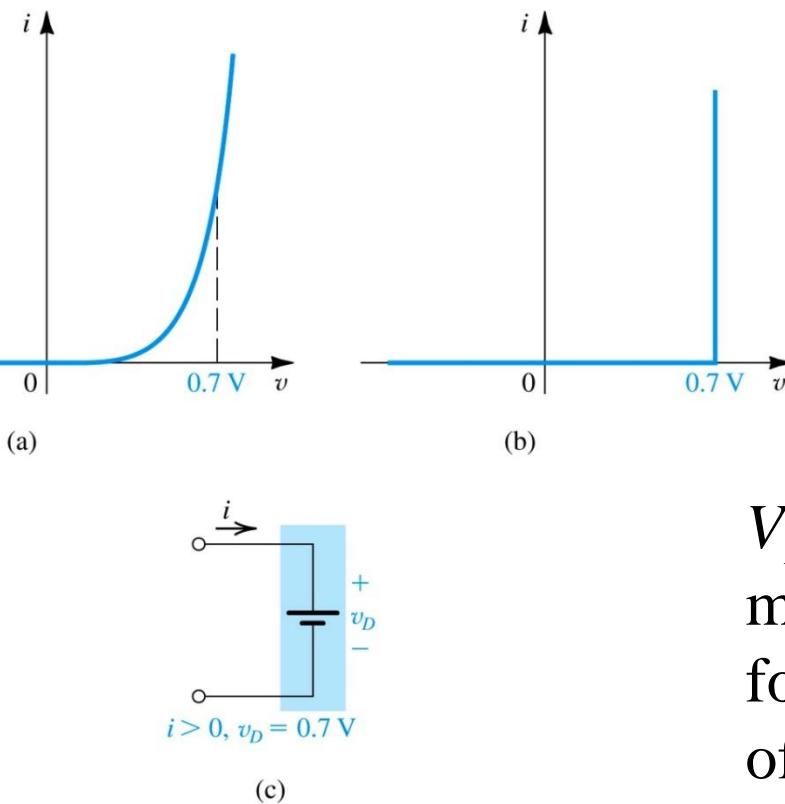

To speed up the circuit analysis we can use SPICE or approximate the diode as a constant voltage drop.

$$V_D = 0.7 \text{ V}$$

V_D depends on doping, material, and temperature and for Si is typically in the range of 0.6 to 0.8 V.

Figure 4.12 Development of the diode constant-voltage-drop model: (a) the exponential characteristic; (b) approximating the exponential characteristic by a constant voltage, usually about 0.7 V; (c) the resulting model of the forward-conducting diodes.



The Constant Voltage Drop Model


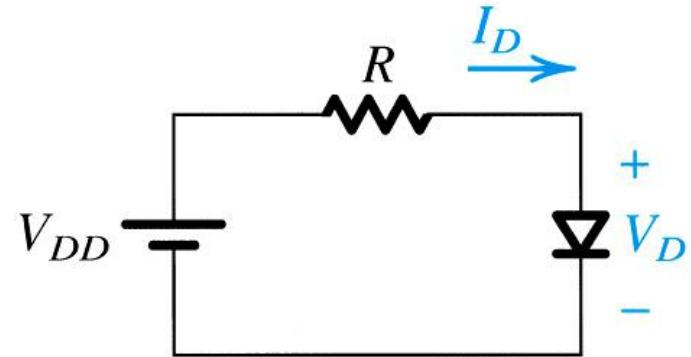
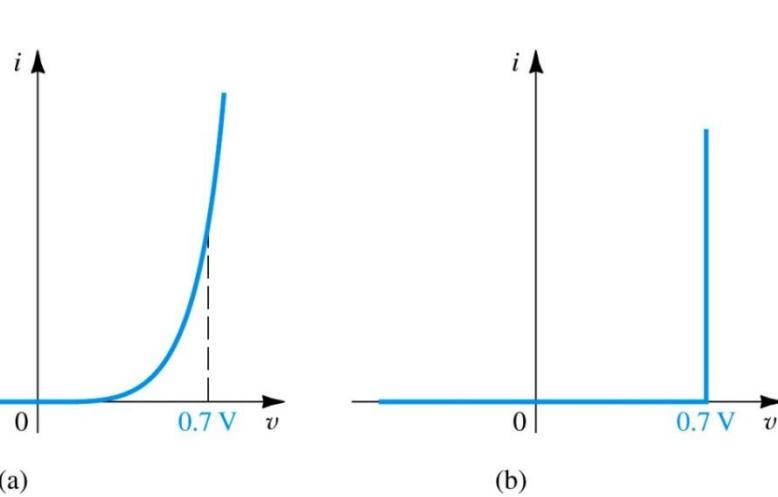


Figure 4.10 A simple circuit used to illustrate the analysis of circuits in which the diode is forward conducting.

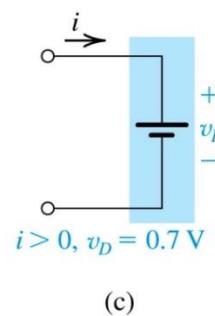

Re-examining the circuit in Fig 4.10 yields:


$$I_D = \frac{V_{DD} - 0.7}{R} = \frac{(5 - 0.7)V}{1\text{k}\Omega}$$

$$I_D = 4.3 \text{ mA}$$

Figure 4.12 Development of the diode constant-voltage-drop model: (a) the exponential characteristic; (b) approximating the exponential characteristic by a constant voltage, usually about 0.7 V; (c) the resulting model of the forward-conducting diodes.



Exercise 4.11

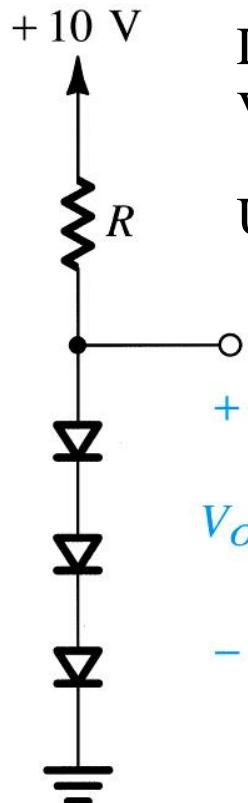

Design the circuit in Fig. E4.11 to provide an output voltage of 2.4 V. Assume that the diodes available have 0.7-V drop at 1 mA.

Use the iterative technique to find the current at $V_D = 0.8$ V.

$$V_2 - V_1 = 2.3V_T \log \frac{I_2}{I_1}$$

$$0.8V - 0.7V = 2.3(.025V) \log \frac{I_2}{1\text{mA}}$$

$$\frac{0.1V}{0.0575V} = \log \frac{I_2}{1\text{mA}} \quad I_2 = 1\text{mA} \cdot 10^{1.739} = 54.83\text{mA}$$

Figure E4.11

$$R = \frac{V_{DD} - V_D}{I_D} = \frac{10V - 2.4V}{0.05483A} = 138.6\Omega$$



The Small-Signal (AC) Model

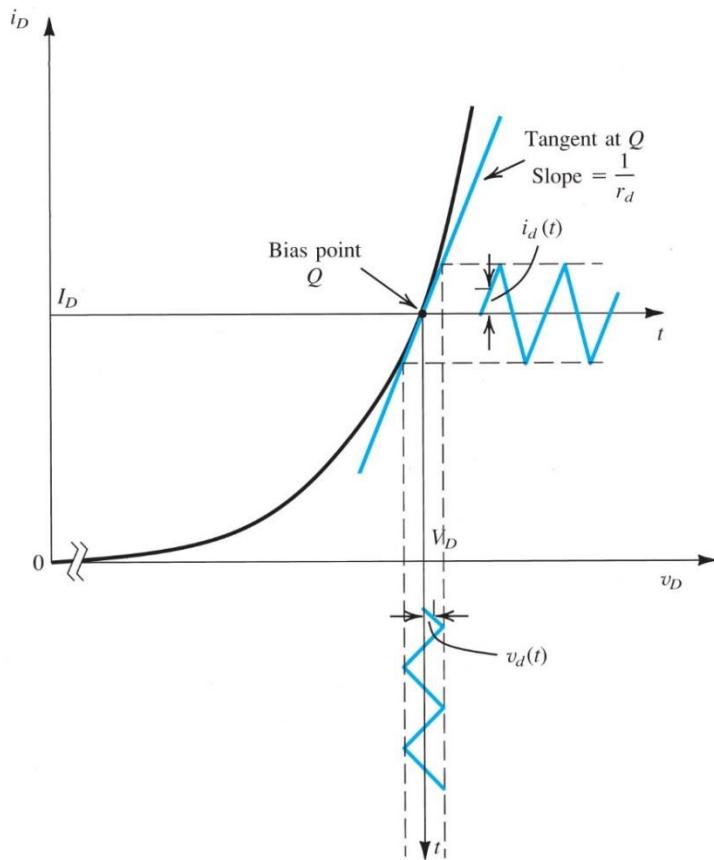


Figure 4.14 Development of the diode small-signal model.

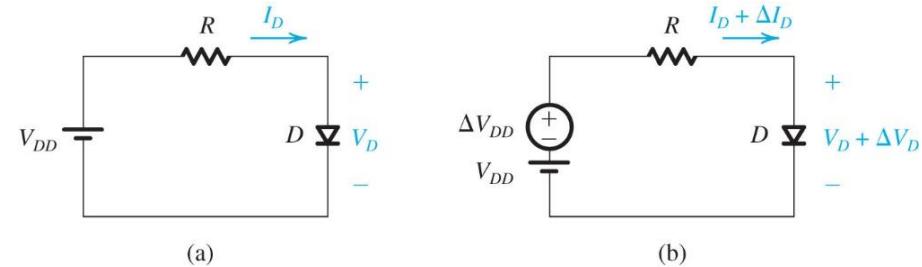


Figure 4.13 (a) A simple diode circuit; (b) the situation when V_{DD} changes by ΔV_{DD} .

There are applications in which a diode is biased to operate at a point on the forward i - v characteristic and a small ac signal is superimposed on the dc quantities. In this case we first solve for the dc operating point, Q , and then treat the diode as a resistor for the small ac signal.



Quiescent

<http://www.merriam-webster.com/dictionary/quiescent>

- 1: marked by inactivity or repose : tranquilly at rest
- 2: causing no trouble or symptoms

 i_c

From Chapter 1

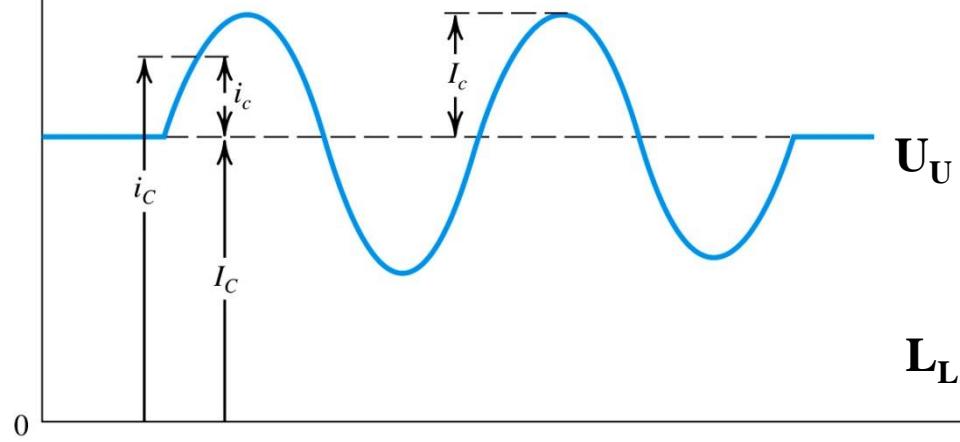


Figure 1.15 Symbol convention employed throughout the book.

Total instantaneous current

$$i_C(t) = I_C + i_c(t)$$

Signal current

$$i_c(t) = I_c \omega t$$

 L_U U_U L_L U_L U_{UU}

Total instantaneous quantities are denoted by a lowercase symbol with uppercase subscript(s).

Direct-current, (dc) quantities are denoted by a uppercase symbol with uppercase subscript(s).

Incremental signal quantities are denoted by a lowercase symbol with lowercase subscript(s).

If the signal is a sine wave, then its amplitude is denoted by an uppercase symbol with lowercase subscript(s).

Finally, power supply voltages and currents are denoted by an uppercase letter with a double-letter uppercase subscript.



The Small-Signal (AC) Model

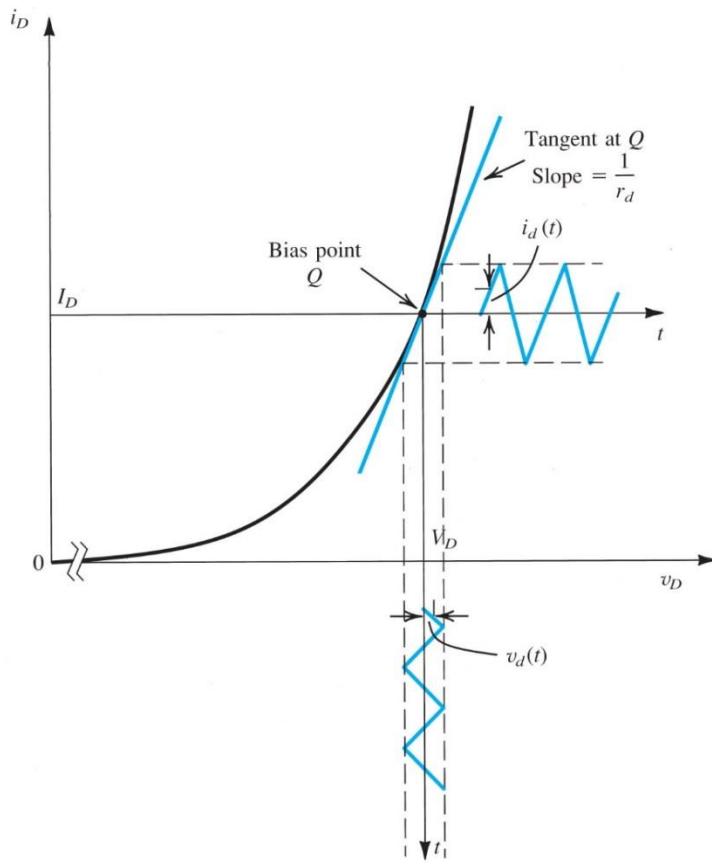


Figure 4.14 Development of the diode small-signal model.

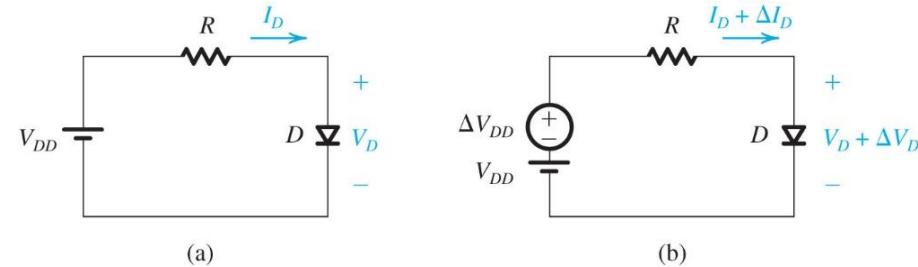


Figure 4.13 (a) A simple diode circuit; (b) the situation when V_{DD} changes by ΔV_{DD} .

With just the dc component (i.e. no small ac signal):

$$I_D = I_S e^{V_D/V_T}$$

Adding the small ac signal:

$$v_D(t) = V_D + v_d(t)$$

The total instantaneous diode current is then:

$$i_D = I_S e^{v_D/V_T} = I_S e^{(V_D+v_d)/V_T}$$

$$i_D = I_S e^{V_D/V_T} e^{v_d/V_T} = I_D e^{v_d/V_T}$$



The Small-Signal (AC) Model

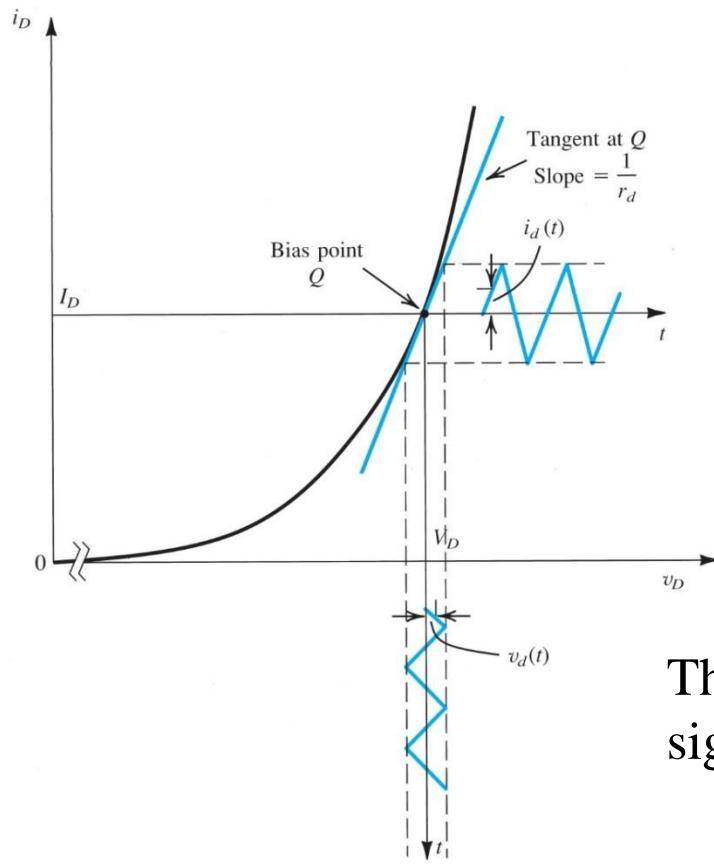


Figure 4.14 Development of the diode small-signal model.

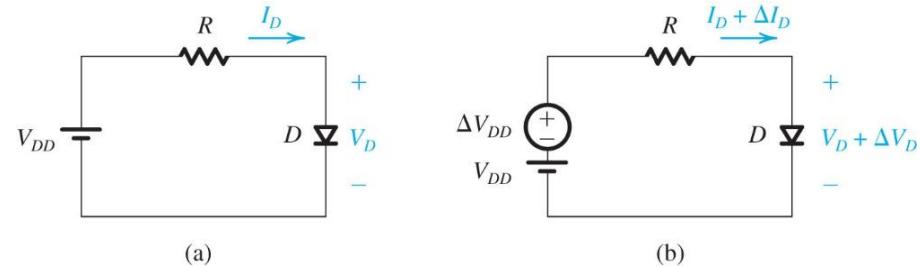


Figure 4.13 (a) A simple diode circuit; (b) the situation when V_{DD} changes by ΔV_{DD} .

The total instantaneous diode current is then:

$$i_D = I_D e^{v_d/V_T}$$

If $v_d(t)$ is small, i.e. much less than V_T :


$$i_D \simeq I_D \left(1 + \frac{v_d}{V_T} \right)$$

This is the **small-signal approximation**. It is valid for signals whose amplitudes are smaller than about 5 mV.

$$i_D = I_D + i_d \quad \text{where} \quad i_d = \frac{I_D}{V_T} v_d$$



e^x Power Series Expansion

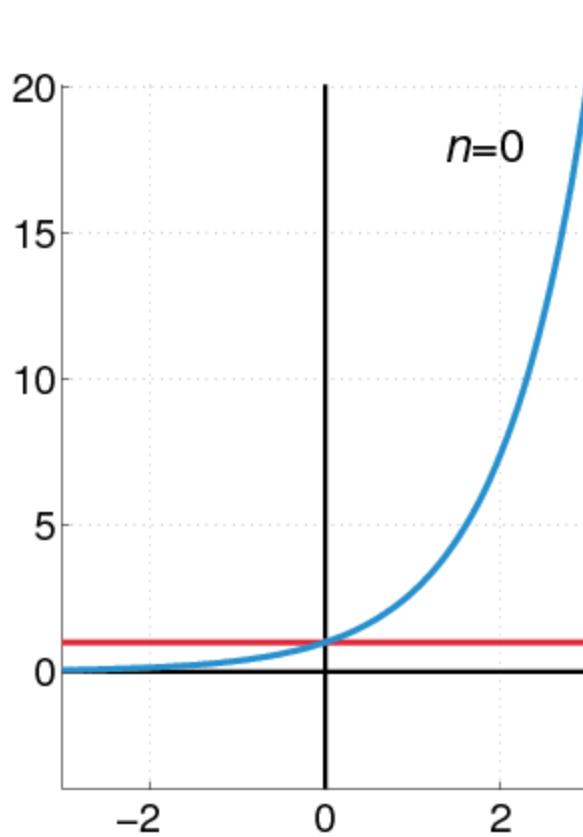

$$e^x = \sum_{n=0}^{\infty} \frac{x^n}{n!} = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$$

$$e^x = \lim_{n \rightarrow \infty} \left(1 + \frac{x}{n}\right)^n$$

$$x = \frac{v_d}{V_T} \ll 1$$

For $v_d = 5$ mV, $v_d/V_T = 0.2$.

Thus the next term in the series expansion of the exponential will be $(0.2)^2/2 = 0.02$, a factor of 10 lower than the linear term we kept.

http://en.wikipedia.org/wiki/Exponential_function



The Small-Signal (AC) Model

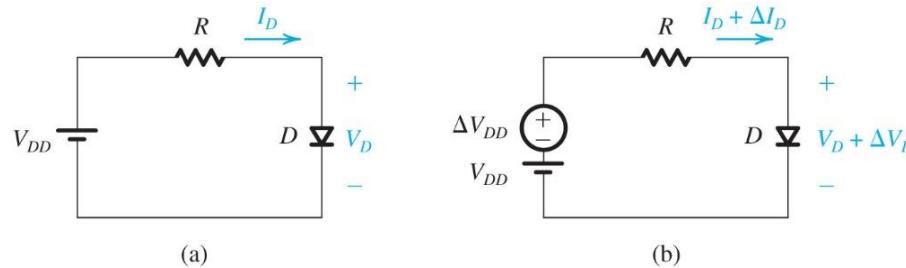


Figure 4.13 (a) A simple diode circuit; (b) the situation when V_{DD} changes by ΔV_{DD} .

The small-signal approximation.

$$i_D = I_D + i_d$$

where

$$i_d = \frac{I_D}{V_T} v_d$$

I_D/V_T is the **diode small-signal conductance** (mhos or Siemens)

V_T/I_D is the **diode small-signal resistance** or **incremental resistance** (ohms)

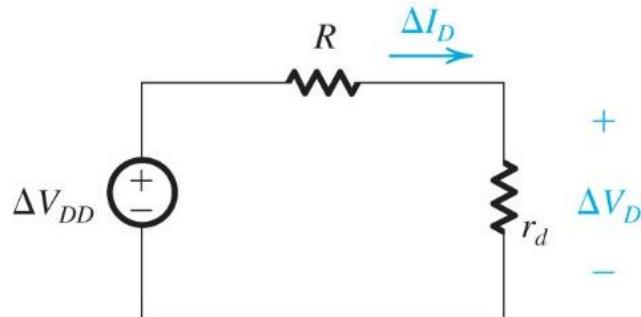


Figure 4.15 Circuit for determining the incremental quantities ΔI_D and ΔV_D for the circuit in Figure 4.13(b).


Note that replacing the diode with its small-signal resistance r_d results in a linear circuit.

$$r_d = \frac{V_T}{I_D}$$




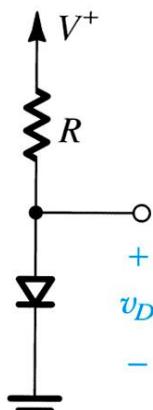Example 4.5

Consider the circuit shown in Fig. 4.16(a) for the case in which $R = 10 \text{ k}\Omega$. The power supply V has a dc value of 10 V on which is superimposed a 60-Hz sinusoid of 1-V peak amplitude. (This "signal" component of the power-supply voltage is an imperfection in the power-supply design. It is known as the power-supply ripple. More on this later.) Calculate both the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it. Assume the diode to have a 0.7-V drop at 1-mA current.



(a)

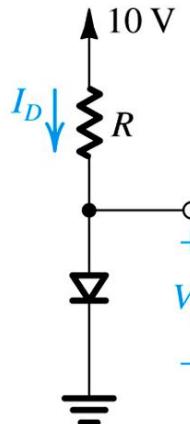

(b)

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{10\text{V} - 0.7\text{V}}{10\text{k}\Omega} = 0.93\text{mA}$$


which is very close to 1 mA

Figure 4.16 (a) Circuit for Example 4.5.



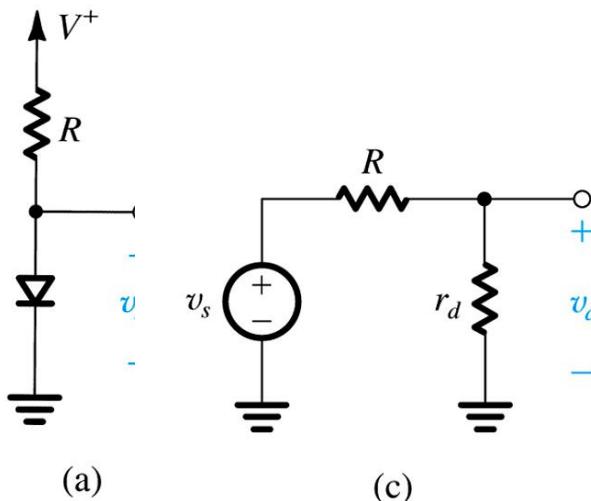Example 4.5

Consider the circuit shown in Fig. 4.16(a) for the case in which $R = 10 \text{ k}\Omega$. The power supply V has a dc value of 10 V on which is superimposed a 60-Hz sinusoid of 1-V peak amplitude. (This "signal" component of the power-supply voltage is an imperfection in the power-supply design. It is known as the power-supply ripple. More on this later.) Calculate both the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it. Assume the diode to have a 0.7-V drop at 1-mA current.



$$r_d = \frac{V_T}{I_D} = \frac{25\text{mV}}{0.93\text{mA}} = 26.9\Omega$$

$$v_{dpeak} = 1.0 \text{ V} \frac{r_d}{R + r_d} = 1.0 \text{ V} \frac{26.9\Omega}{10000\Omega + 26.9\Omega}$$

$$v_{dpeak} = 2.68 \text{ mV}$$

Figure 4.16 (a) Circuit for Example 4.5.




Voltage Regulator Example 4.6

Consider the circuit shown in Fig 4.17. A string of three diodes is used to provide a constant voltage of about 2.1 V. We want to calculate the percentage change in this regulated voltage caused by (a) a $\pm 10\%$ change in the power-supply voltage and (b) connection of a $1\text{-k}\Omega$ load resistance.

$10 \pm 1 \text{ V}$

with no load:

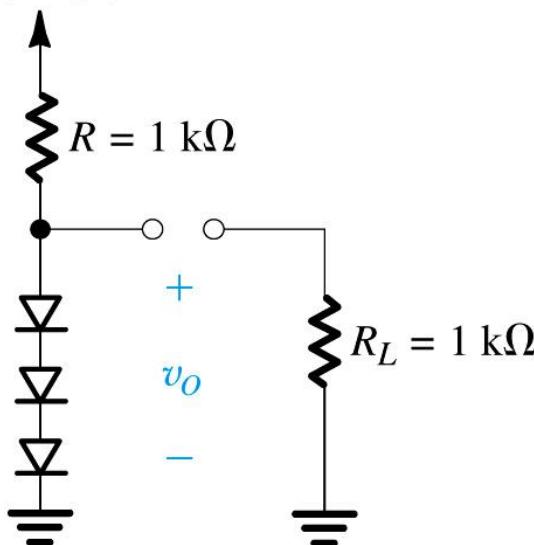

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{10\text{V} - 2.1\text{V}}{1\text{k}\Omega} = 7.9\text{mA}$$

$$r_d = \frac{V_T}{I_D} = \frac{25\text{mV}}{7.9\text{mA}} = 3.165\Omega \text{ per diode}$$

$$r_{dtotal} = 9.5\Omega$$


$$v_{Op-p} = 2.0 \text{ V} \frac{r_{dtotal}}{R + r_{dtotal}} = 19.0 \text{ mV}$$

Figure 4.17 Circuit for Example 4.6.



Voltage Regulator Example 4.6

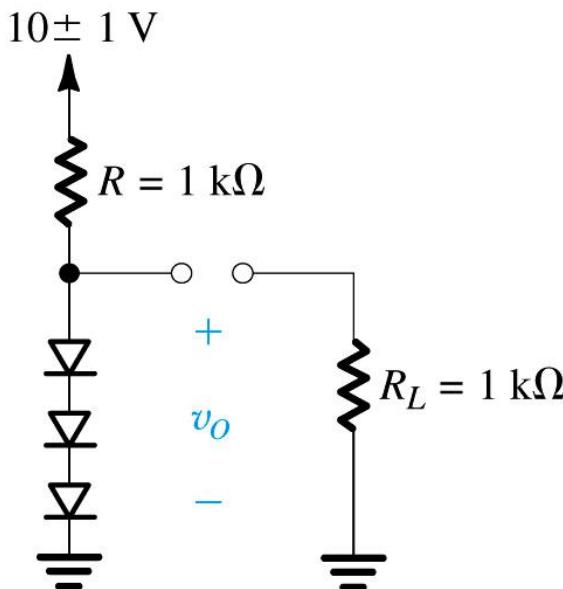Consider the circuit shown in Fig 4.17. A string of three diodes is used to provide a constant voltage of about 2.1 V. We want to calculate the percentage change in this regulated voltage caused by (a) a $\pm 10\%$ change in the power-supply voltage and (b) connection of a $1\text{-k}\Omega$ load resistance.



with $1\text{k}\Omega$ load: $I_L = \frac{v_O}{R_L} = \frac{2.1\text{V}}{1\text{k}\Omega} = 2.1\text{mA}$

with no load: $I_D = 7.9\text{mA}$

with $1\text{k}\Omega$ load: $I_D = 7.9\text{mA} - 2.1\text{mA} = 5.8\text{mA}$

$$r_d = \frac{V_T}{I_D} = \frac{25\text{mV}}{5.8\text{mA}} = 4.31\Omega \text{ per diode}$$

$$r_{dtotal} = 12.9\Omega$$

$$v_{dp-p} = 2.0\text{ V} \frac{r_{dtotal}}{R + r_{dtotal}} = 25.0\text{ mV}$$


Figure 4.17 Circuit for Example 4.6.



Exercise 4.15

Design the circuit of Fig. E4.15 so that $V_O = 3$ V when $I_L = 0$, and V_O changes by 20 mV per 1 mA of load current.

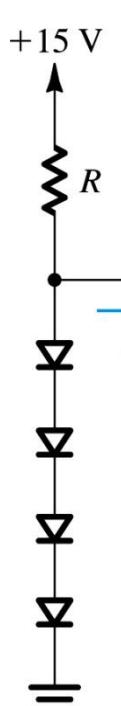- (a) Use the small-signal model of the diode to find the value of R .



$$r_{dtotal} = \frac{\Delta V_O}{\Delta I_D} = \frac{20\text{mV}}{1\text{mA}} = 20\Omega \quad r_d = \frac{r_{dtotal}}{4} = 5\Omega$$

$$I_D = \frac{V_T}{r_d} = \frac{25\text{mV}}{5\Omega} = 5\text{mA} \quad R = \frac{V_{CC} - V_O}{I_D} = \frac{12\text{V}}{5\text{mA}} = 2.4\text{k}\Omega$$

- (b) Specify the value of I_S of each of the diodes.


$$V_D = \frac{3\text{V}}{4} = 750\text{mV} \quad i_D = I_S e^{V/V_T} \Rightarrow I_S = \frac{i_D}{e^{V_D/V_T}} = \frac{5\text{mA}}{e^{750\text{mV}/25\text{mV}}} = 4.679 \times 10^{-16} \text{ A}$$

- (c) For this design, use the diode exponential model to determine the actual change in V_O when a current $I_L = 1$ mA is drawn from the regulator.

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right) = 25\text{mV} \times \ln\left(\frac{5\text{mA} - 1\text{mA}}{4.679 \times 10^{-16} \text{ A}}\right) = 0.7444\text{V}$$

$$\Delta V_O = 3\text{V} - 4V_D = 3\text{V} - 4(0.7444\text{V}) = 0.0223\text{V}$$


Figure E4.15

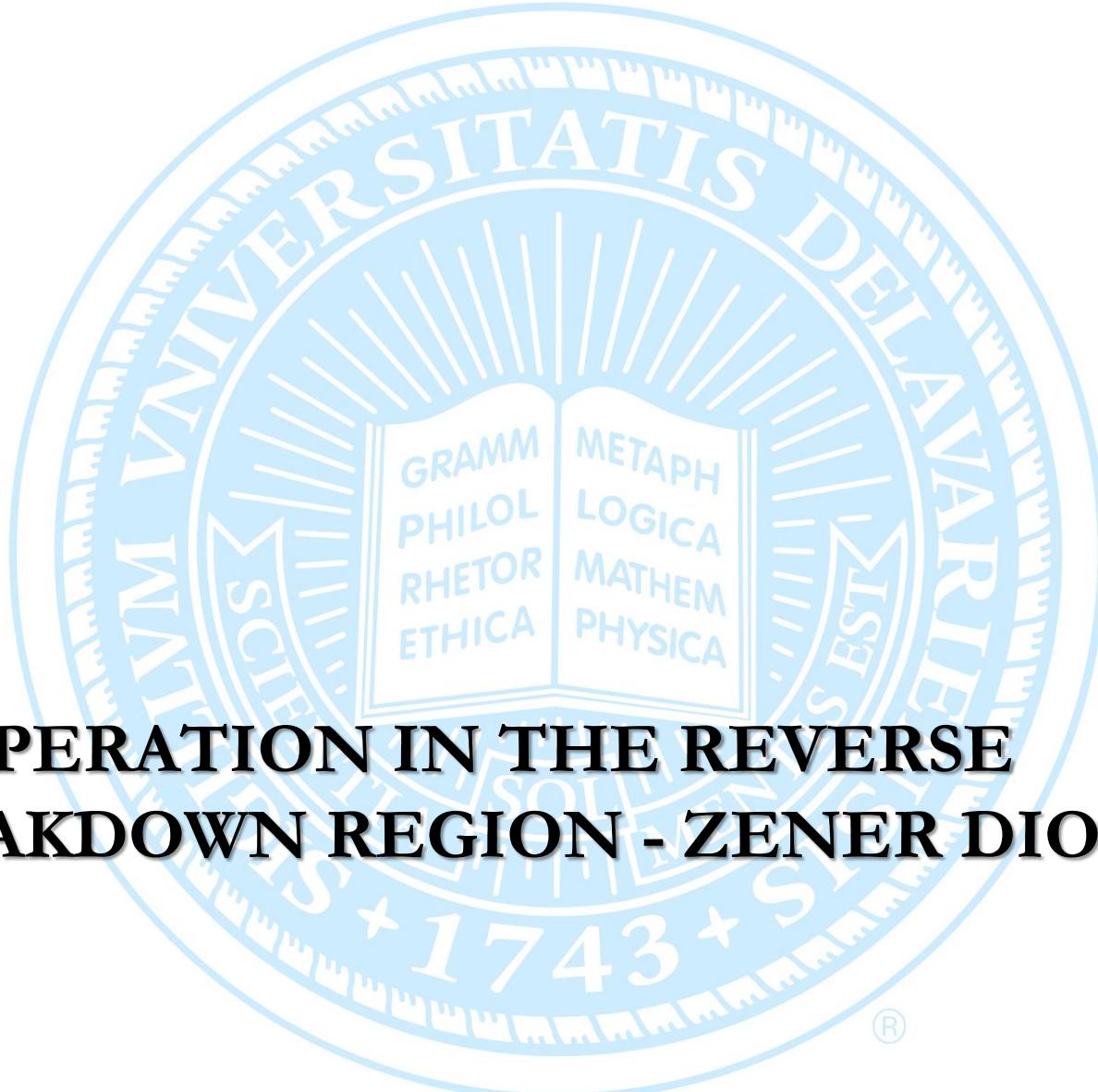

4.4 OPERATION IN THE REVERSE BREAKDOWN REGION - ZENER DIODES



Breakdown Region – Zener Diodes

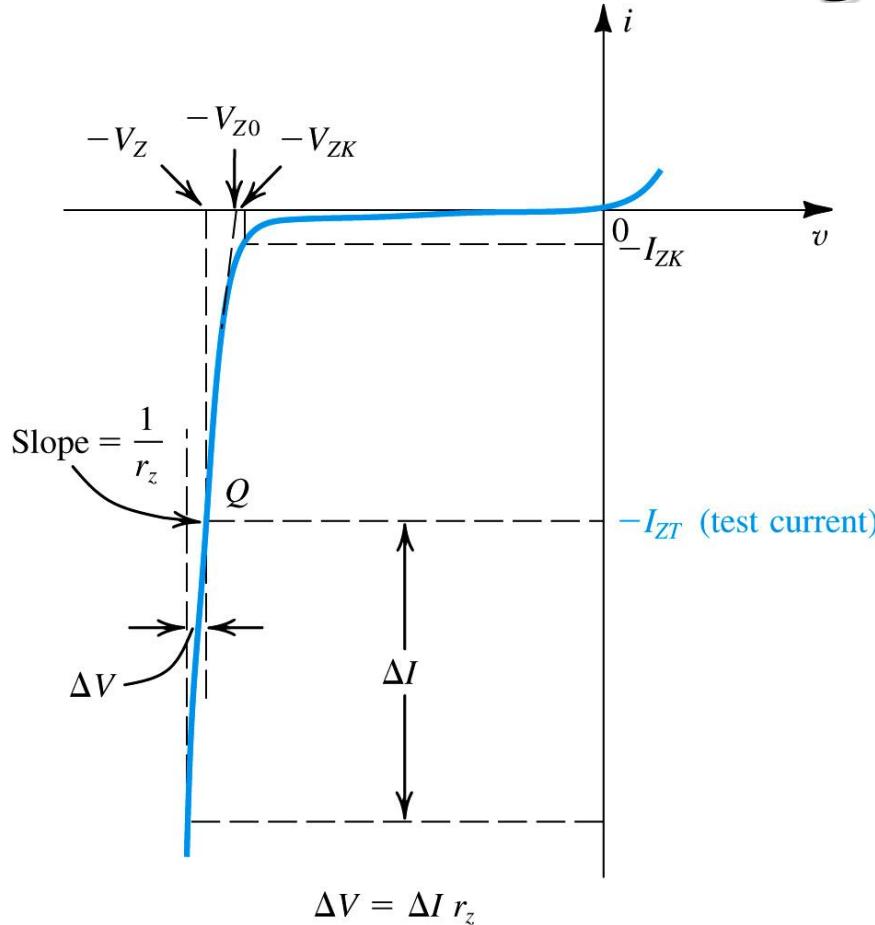

For currents greater than the knee current I_{ZK} (specified on the data sheet of the zener diode), the i - v characteristic is almost a straight line. The manufacturer usually specifies the voltage across the zener diode V_Z at a specified test current, I_{ZT} . We have indicated these parameters in Fig. 4.19 as the coordinates of the point labeled Q . Thus a 6.8-V zener diode will exhibit a 6.8-V drop at a specified test current of, say, 10 mA.

Figure 4.19 The diode i - v characteristic with the breakdown region shown in some detail.



Breakdown Region – Zener Diodes

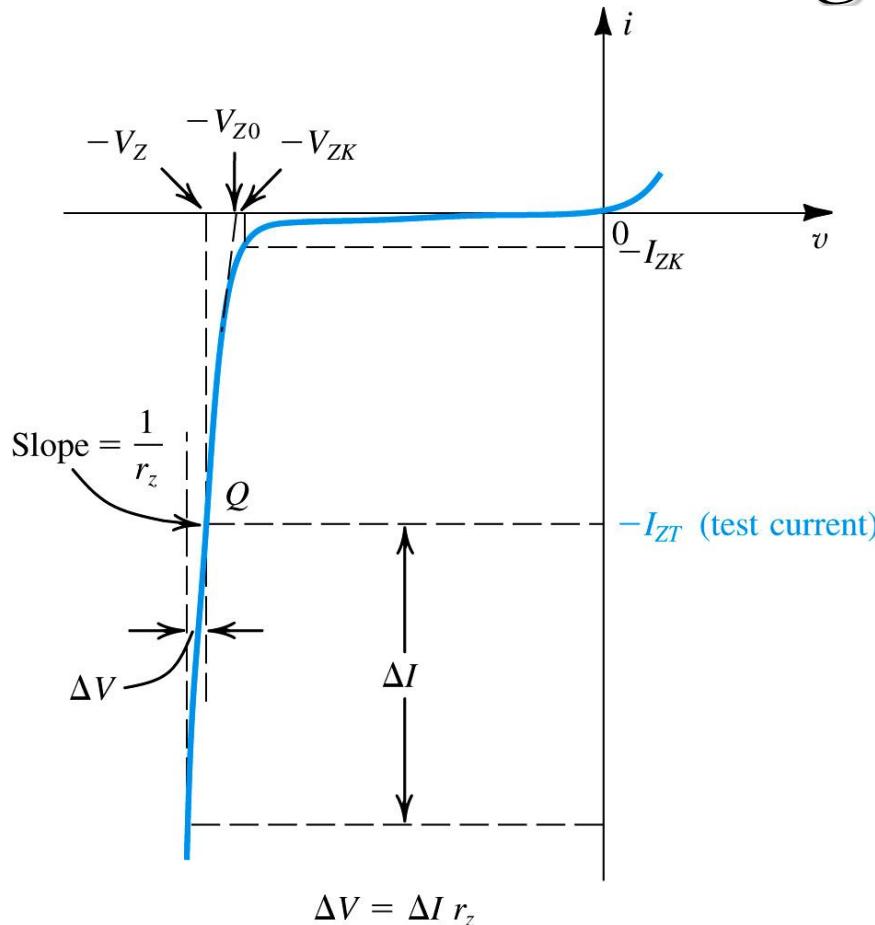


Figure 4.19 shows that corresponding to current change ΔI the zener voltage changes by ΔV , which is related to ΔI by

$$\Delta V = r_z \Delta I$$

where r_z is the inverse of the slope of the almost-linear i - v curve at point Q . Resistance r_z is the **incremental resistance** of the zener diode at operating point Q . It is also known as the **dynamic resistance** of the zener, and its value is specified on the device data sheet. Typically, r_z is in the range of a few ohms to a few tens of ohms.

Figure 4.19 The diode i - v characteristic with the breakdown region shown in some detail.



NXP Semiconductors

1N4728A to 1N4749A

Voltage regulator diodes

Table 8. Characteristics per type
 $T_j = 25^\circ\text{C}$ unless otherwise specified.

Type number	Working voltage V _Z (V) ^[1] at I _{test}	Test current I _{test} (mA)	Differential resistance r _{diff} (Ω)			Reverse current I _R (μA)		Working current I _Z (mA)		Non-repetitive peak reverse current I _{ZSM} (mA) ^[2]	
			at I _{test}		at I _Z	I _Z (mA)	Max	V _R (V)	Max	Max	Max
			Max	Max	Max	Max	Max	Max	Max	Max	Max
1N4728A	3.3	76	10	400	1	100	1	276	1380		
1N4729A	3.6	69	10	400	1	100	1	252	1260		
1N4730A	3.9	64	9	400	1	50	1	234	1190		
1N4731A	4.3	58	9	400	1	10	1	217	1070		
1N4732A	4.7	53	8	500	1	10	1	193	970		
1N4733A	5.1	49	7	550	1	10	1	178	890		
1N4734A	5.6	45	5	600	1	10	2	162	810		
1N4735A	6.2	41	2	700	1	10	3	146	730		
1N4736A	6.8	37	3.5	700	1	10	4	133	660		
1N4737A	7.5	34	4	700	0.5	10	5	121	605		
1N4738A	8.2	31	4.5	700	0.5	10	6	110	550		
1N4739A	9.1	28	5	700	0.5	10	7	100	500		
1N4740A	10	25	7	700	0.25	10	7.6	91	454		
1N4741A	11	23	8	700	0.25	5	8.4	83	414		
1N4742A	12	21	9	700	0.25	5	9.1	76	380		
1N4743A	13	19	10	700	0.25	5	9.9	69	344		
1N4744A	15	17	14	700	0.25	5	11.4	61	304		
1N4745A	16	15.5	16	700	0.25	5	12.2	57	285		
1N4746A	18	14	20	750	0.25	5	13.7	50	250		
1N4747A	20	12.5	22	750	0.25	5	15.2	45	225		
1N4748A	22	11.5	23	750	0.25	5	16.7	41	205		
1N4749A	24	10.5	25	750	0.25	5	18.2	38	190		

[1] V_Z is measured with device at thermal equilibrium while held in clips at 10 mm from body in still air at 25 °C.[2] Half square wave or equivalent sine wave pulse 1/120 second duration superimposed on I_{test}.

Electrical Characteristics

@T_A = 25°C unless otherwise specified

Type Number	Nominal Zener Voltage (Note 3) (V)	Test Current I _{ZT} (mA)	Maximum Zener Impedance (Note 4)			Maximum Reverse Leakage Current			Max Surge Current 8.3ms (mA)	Temperature Coefficient @ I _{ZT} (%/°C)
			Z _{ZT} @ I _{ZT} (Ω)	Z _{ZK} @ I _{ZK} (Ω)	I _{ZK} (mA)	I _R (@ V _R) (μA)	(V)			
1N4728A	3.3	76	10	400	1	100	1	100	1.0	-0.08 to -0.05
1N4729A	3.6	69	10	400	1	100	1	100	1.0	-0.08 to -0.05
1N4730A	3.9	64	9	400	1	50	1	100	1.0	-0.07 to -0.02
1N4731A	4.3	58	9	400	1	10	1	10	1.0	-0.07 to -0.01
1N4732A	4.7	53	8	500	1	80	1	10	1.0	-0.03 to +0.04
1N4733A	5.1	49	7	550	1	70	1	10	1.0	-0.01 to +0.04
1N4734A	5.6	45	6	600	1	60	1	10	2.0	0 to +0.045
1N4735A	6.2	41	5	700	1	50	1	10	3.0	+0.01 to +0.055
1N4736A	6.8	37	4.5	700	1	40	1	10	4.0	+0.015 to +0.06
1N4737A	7.5	34	4.0	700	1	30	0.5	10	5.0	+0.02 to +0.065
1N4738A	8.2	31	3.5	700	1	25	0.5	10	6.0	0.03 to 0.07
1N4739A	9.1	28	3.0	700	1	20	0.5	10	7.0	0.035 to 0.075
1N4740A	10	25	2.5	700	1	15	0.5	10	7.6	0.04 to 0.08
1N4741A	11	23	2.0	700	1	12	0.5	10	8.4	0.045 to 0.08
1N4742A	12	21	1.8	700	1	10	0.25	5.0	9.1	0.045 to 0.085
1N4743A	13	19	1.6	700	1	8	0.25	5.0	9.9	0.05 to 0.085
1N4744A	15	17	1.4	700	1	6	0.25	5.0	11.4	0.055 to 0.09
1N4745A	16	15.5	1.3	700	1	5	0.25	5.0	12.2	0.055 to 0.09
1N4746A	18	14	1.2	750	1	4	0.25	5.0	13.7	0.06 to 0.09
1N4747A	20	12.5	1.1	750	1	3	0.25	5.0	15.2	0.06 to 0.09
1N4748A	22	11.5	1.0	750	1	2.5	0.25	5.0	16.7	0.06 to 0.095
1N4749A	24	10.5	0.9	750	1	2	0.25	5.0	18.2	0.06 to 0.095
1N4750A	27	9.5	0.8	750	1	1.5	0.25	5.0	20.6	0.06 to 0.095
1N4751A	30	8.5	0.7	1000	1	1	0.25	5.0	22.8	0.06 to 0.095
1N4752A	33	7.5	0.6	1000	1	0.5	0.25	5.0	25.1	0.06 to 0.095
1N4753A	36	7.0	0.5	1000	1	0.4	0.25	5.0	27.4	0.06 to 0.095
1N4754A	39	6.5	0.4	1000	1	0.3	0.25	5.0	29.7	0.06 to 0.095
1N4755A	43	6.0	0.3	1500	1	0.2	0.25	5.0	32.7	0.06 to 0.095
1N4756A	47	5.5	0.2	1500	1	0.15	0.25	5.0	35.8	0.06 to 0.095
1N4757A	51	5.0	0.15	1500	1	0.1	0.25	5.0	38.8	0.06 to 0.095
1N4758A	56	4.5	0.1	2000	1	0.05	0.25	5.0	42.6	0.06 to 0.095
1N4759A	62	4.0	0.05	2000	1	0.02	0.25	5.0	47.1	0.06 to 0.095
1N4760A	68	3.7	0.02	2000	1	0.01	0.25	5.0	51.7	0.06 to 0.095
1N4761A	75	3.3	0.01	2000	1	0.005	0.25	5.0	56.0	0.06 to 0.095

Notes: 3. Measured under thermal equilibrium and dc (I_{ZT}) test conditions.4. The Zener impedance is derived from the 60 Hz ac voltage which results when an ac current having an rms value equal to 10% of the Zener current (I_{ZT} or I_{ZK}) is superimposed on I_{ZT} or I_{ZK}. Zener impedance is measured at two points to insure a sharp knee on the breakdown curve and to eliminate unstable units.



The Zener Diode Symbol and Model

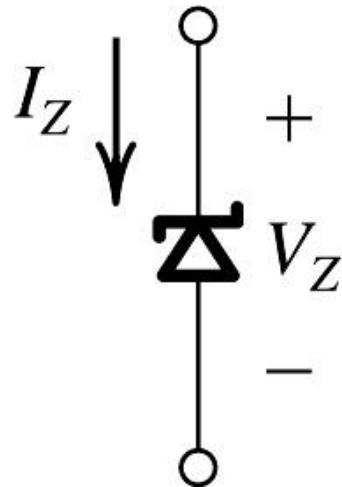


Figure 4.18 Circuit symbol for a zener diode.

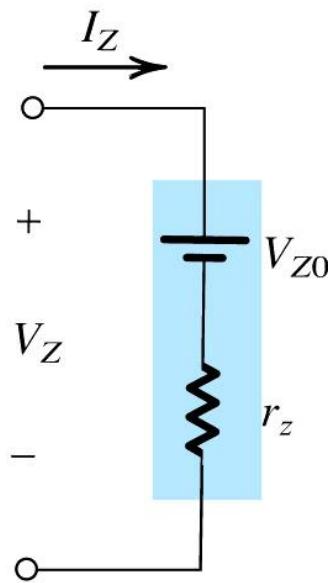


Figure 4.20 Model for the zener diode.

The almost-linear i - v characteristic of the zener diode suggests that the device can be modeled as indicated in Fig. 4.20. Here V_{Z0} denotes the point at which the straight line of slope $1/r_z$ intersects the voltage axis. Although V_{Z0} is shown in Fig. 4.19 to be slightly different from the knee voltage V_{ZK} , in practice their values are almost equal. The equivalent circuit model of Fig. 4.20 can be analytically described by

$$V_Z = V_{Z0} + r_z I_Z$$

and it applies for $I_Z > I_{ZK}$ and, obviously, $V_Z > V_{Z0}$.



Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

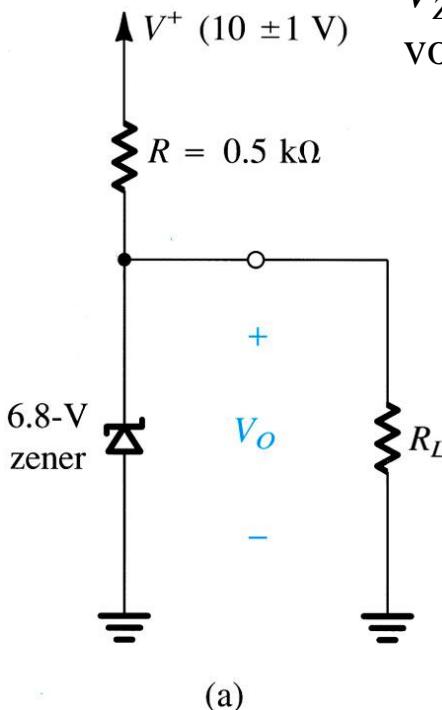


Figure 4.21 (a) Circuit for Example 4.7.



- Find V_O with no load and with V^+ at its nominal value.
- Find the change in V_O resulting from the $\pm 1\text{-V}$ change In V^+ .
Note that $(\Delta V_O / \Delta V^+)$, usually expressed in mV/V, is known as **line regulation**.
- Find the change in V_O resulting from connecting a load resistance R_L that draws a current $I_L = 1 \text{ mA}$, and hence find the **load regulation** $(\Delta V_O / \Delta I_L)$ in mV/mA.
- Find the change in V_O when $R_L = 2 \text{ k}\Omega$.
- Find the change in V_O when $R_L = 0.5 \text{ k}\Omega$.
- What is the minimum value of R_L for which the diode still operates in the breakdown region?



Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

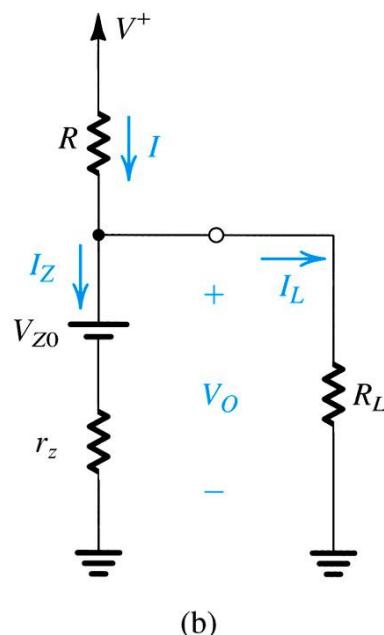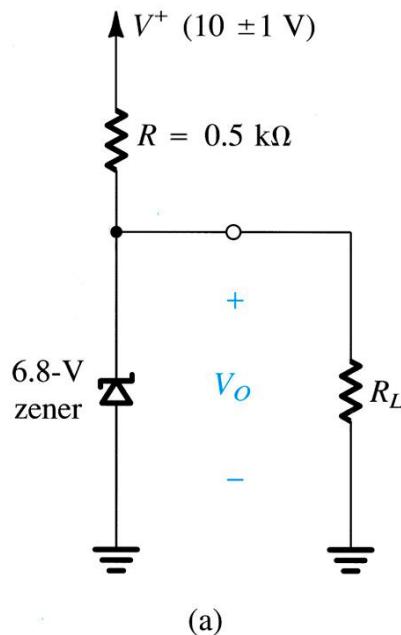(a) Find V_O with no load and with V^+ at its nominal value.



$$V_Z = V_{Z0} + r_z I_Z$$

$$V_{Z0} = V_Z - r_z I_Z = 6.8 - (20)(.005) = 6.7 \text{ V}$$

$$I_Z = \frac{V^+ - V_{Z0}}{R + r_z} = \frac{10V - 6.7V}{500 + 20} = 6.35 \text{ mA}$$

$$V_O = V_{Z0} + r_z I_Z = 6.7 + (20)(.00635) = 6.83 \text{ V}$$

Figure 4.21 (a) Circuit for Example 4.7. (b) The circuit with the zener diode replaced with its equivalent circuit model.




Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

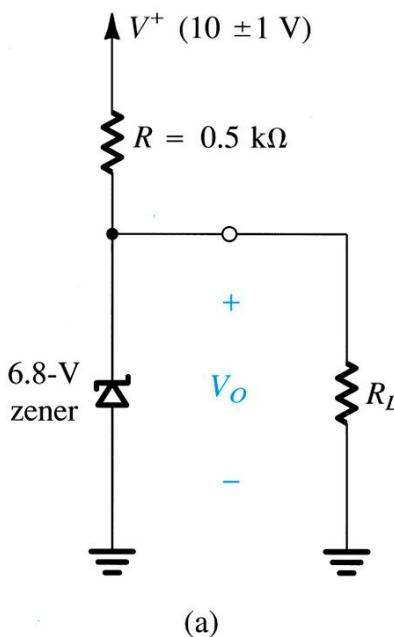
(b) Find the change in V_O resulting from the $\pm 1\text{-V}$ change in V^+ . Note that $(\Delta V_O / \Delta V^+)$, usually expressed in mV/V, is known as **line regulation**.

$$\Delta V_O = \Delta V^+ \frac{r_z}{R + r_z} = \pm 1 \frac{20}{520} = \pm 38.5 \text{ mV}$$

the **line regulation** in mV/V is 38.5 mV/V



(a)

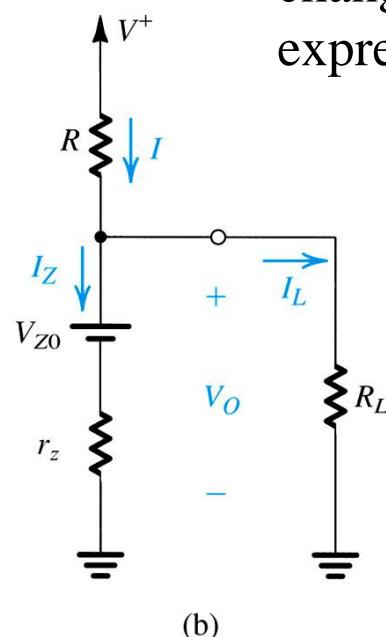

(b)

Figure 4.21 (a) Circuit for Example 4.7. (b) The circuit with the zener diode replaced with its equivalent circuit model.




Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

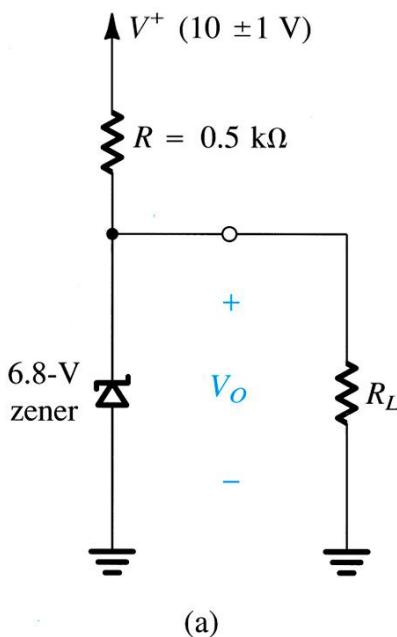
(c) Find the change in V_O resulting from connecting a load resistance R_L that draws a current $I_L = 1 \text{ mA}$, and hence find the **load regulation** ($\Delta V_O / \Delta I_L$) in mV/mA.

$$\Delta V_O = r_z \Delta I_Z = 20 \times -0.001 = -20 \text{ mV}$$

the **load regulation** in mV/mA is -20 mV/mA



(a)

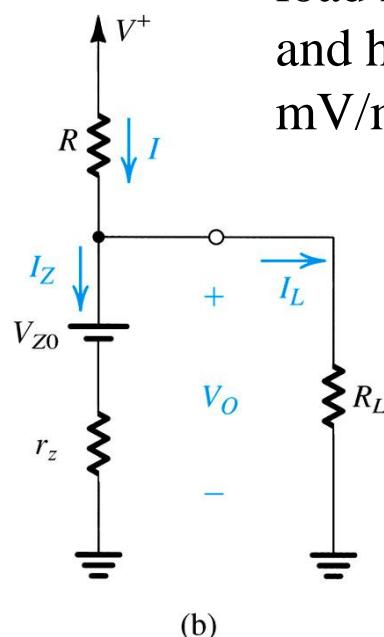

(b)



Figure 4.21 (a) Circuit for Example 4.7. (b) The circuit with the zener diode replaced with its equivalent circuit model.



Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

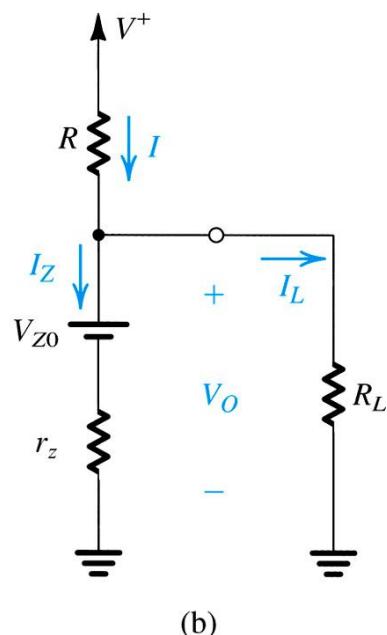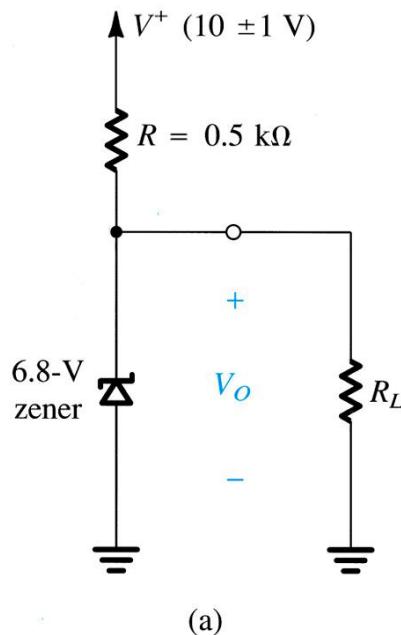(d) Find the change in V_O when $R_L = 2 \text{ k}\Omega$.



$$I_L = \frac{6.8\text{V}}{2000\Omega} = 3.4\text{mA}$$

$$\Delta V_O = r_z \Delta I_Z = 20 \times -0.0034 = -68\text{mV}$$

(e) Find the change in V_O when $R_L = 0.5 \text{ k}\Omega$.

$$I_L = \frac{6.8\text{V}}{500\Omega} = 13.6\text{mA}$$

But $I_Z = 6.4 \text{ mA}$ so the zener must be cut-off !

$$V_O = 10\text{V} \frac{500\Omega}{1000\Omega} = 5\text{V}$$

Figure 4.21 (a) Circuit for Example 4.7. (b) The circuit with the zener diode replaced with its equivalent circuit model.



Use as a Shunt Regulator (Example 4.7)

The 6.8-V zener diode in the circuit of Fig. 4.21(a) is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.

(f) What is the minimum value of R_L for which the diode still operates in the breakdown region?

$$I_Z = I_{ZK} = 0.2 \text{ mA}$$

$$V_Z = V_{ZK} = 6.7 \text{ V}$$

Worst case $V^+ = 9 \text{ V}$.

$$I = \frac{9 - 6.7 \text{ V}}{500 \Omega} = 4.6 \text{ mA}$$

$$I_L = I - I_Z = 4.6 \text{ mA} - 0.2 \text{ mA} = 4.4 \text{ mA}$$

$$R_L = \frac{V_O}{I_L} = \frac{6.7 \text{ V}}{4.4 \text{ mA}} = 1523 \Omega$$


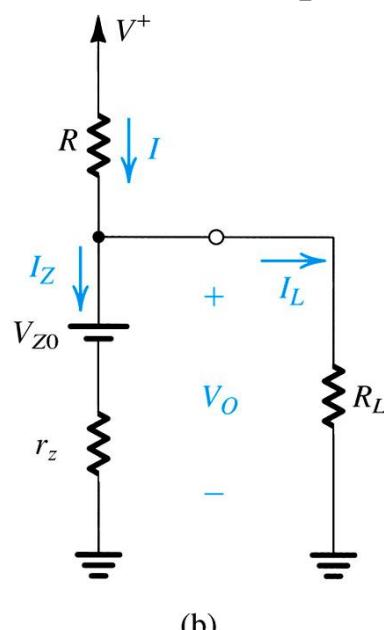



Figure 4.21 (a) Circuit for Example 4.7. (b) The circuit with the zener diode replaced with its equivalent circuit model.

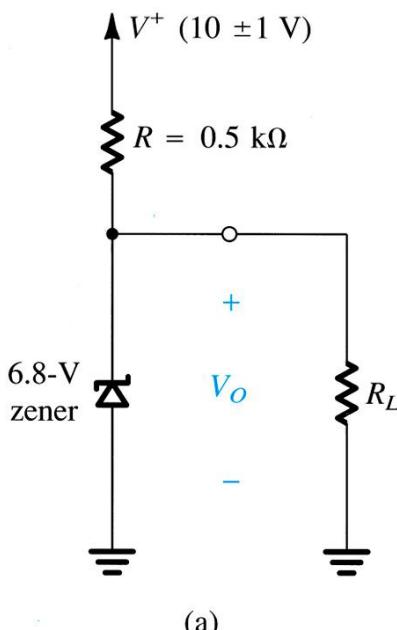

Temperature Effects

The dependence of the zener voltage V_Z on temperature is specified in terms of its **temperature coefficient TC**, or **temco**, which is usually expressed in mV/ $^{\circ}\text{C}$. Zener diodes whose V_Z are lower than about 5 V exhibit a negative TC while zeners with higher voltages exhibit a positive TC.

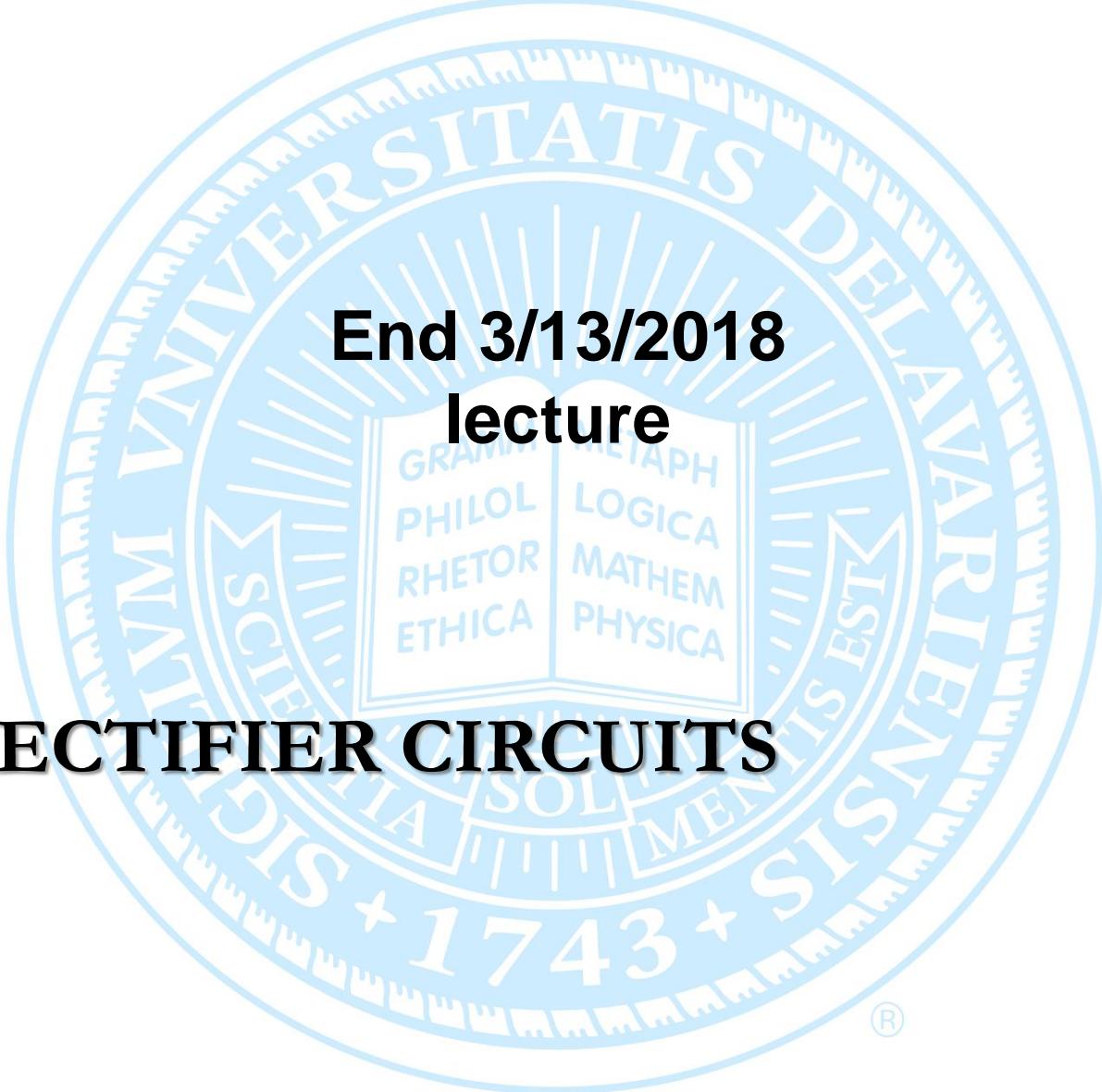A commonly used technique to obtain a reference voltage with a low TC is to use a forward biased diode (-2 mV/ $^{\circ}\text{C}$) in series with a reverse biased zener ($\sim 2\text{mV } ^{\circ}\text{C}$).



A large, faint watermark of the University of Delaware seal is centered behind the text. The seal is circular with the outer ring containing the text "UNIVERSITATIS DELAVARIEENSIS" at the top and "SIGIS * 1743 * SISAG" at the bottom. Inside the ring is a book with Latin inscriptions: "GRAMMATICA", "RHETOR", "ETHICA" on the left page, and "LOGICA", "MATHEM", "PHYSICA" on the right page. The center of the seal features a sunburst design with radiating lines.

**End 3/13/2018
lecture**

4.5 RECTIFIER CIRCUITS



Rectifier Circuits


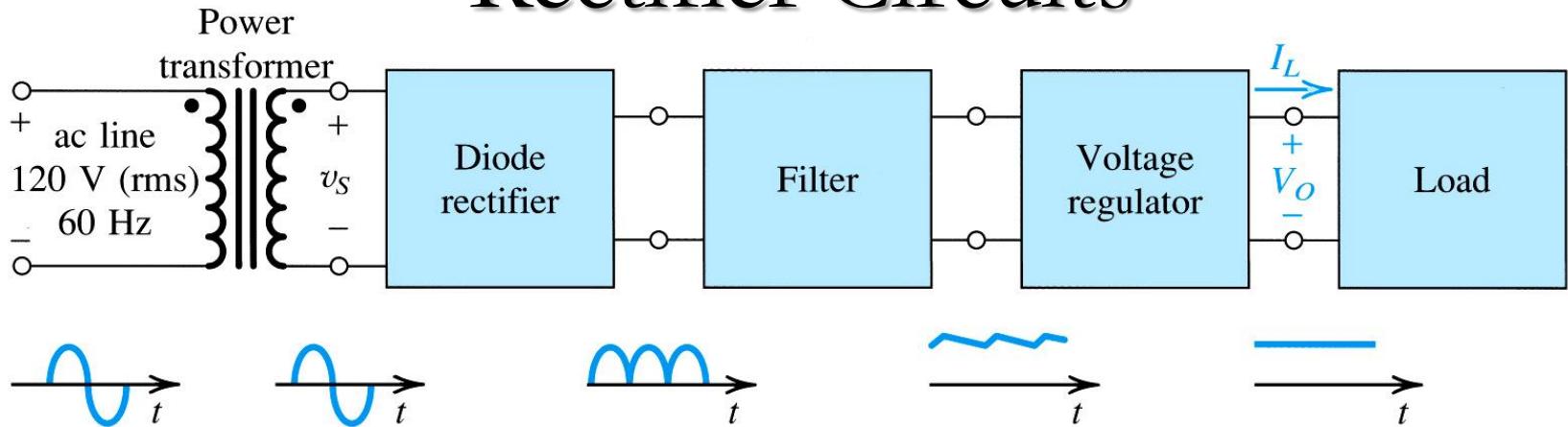


Figure 4.22 Block diagram of a dc power supply.

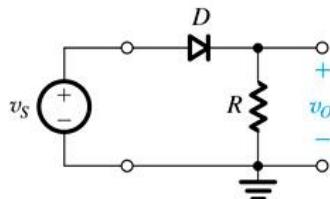
- Power transformer
 - Primary (N_1) and secondary (N_2) windings
 - $v_S = 120 \frac{N_2}{N_1} V_{\text{rms}}$
 - Isolates electronics
- Diode Rectifier
 - Converts AC to DC
 - Half-Wave
 - Full-Wave




Half-Wave Rectifier



(a)

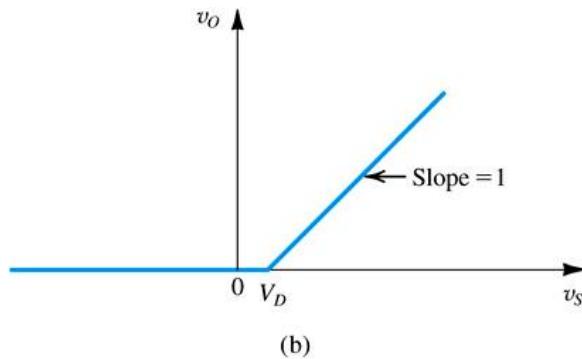

(b)

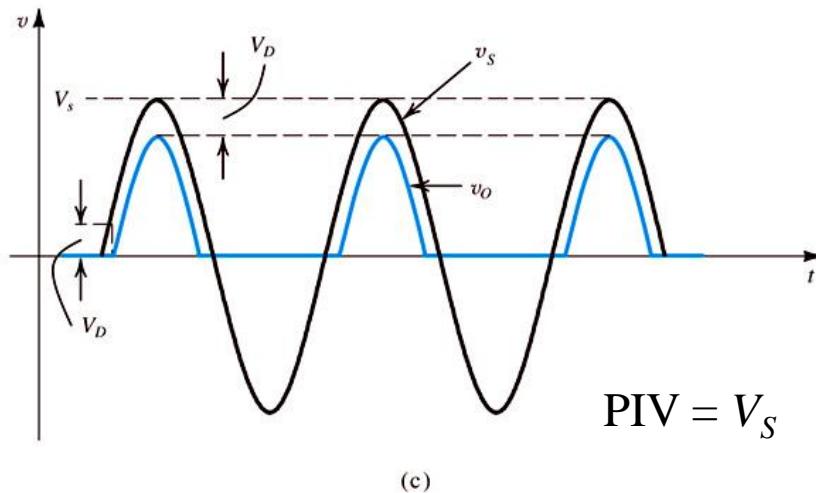

(c)

Figure 4.23 (a) Half-wave rectifier. (b) Transfer characteristic of the rectifier circuit. (c) Input and output waveforms.

Using a constant voltage drop model


$$v_o = 0; v_s < V_D$$

$$v_o = v_s - V_D; v_s \geq V_D$$

In selecting diodes for rectifier design, two important parameters must be specified: the current-handling capability required of the diode, determined by the largest current the diode is expected to conduct, and the **peak inverse voltage (PIV)** that the diode must be able to withstand without breakdown. determined by the largest reverse voltage that is expected to appear across the diode.



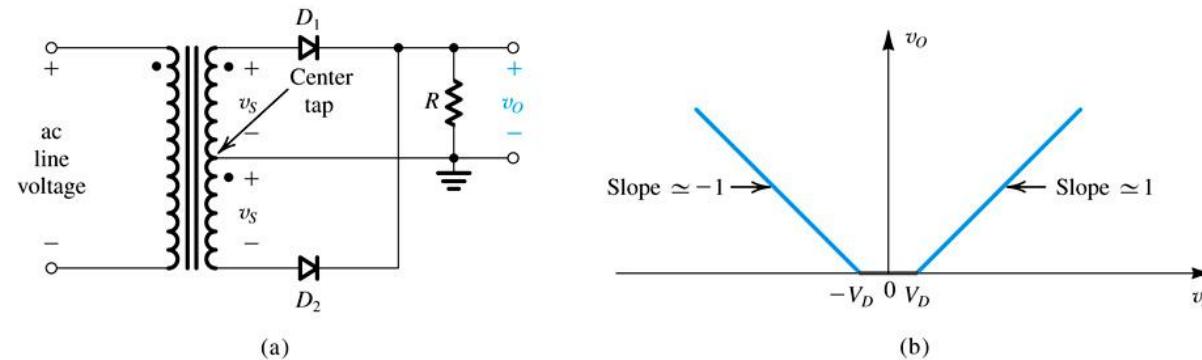Full-Wave Rectifier using a Center-Tapped Transformer




Center-tapped
transformer generates
two outputs 180° out
of phase

$$\text{PIV} = 2V_S - V_D$$

Figure 4.24 Full-wave rectifier utilizing a transformer with a center-tapped secondary winding: (a) circuit; (b) transfer characteristic assuming a constant-voltage-drop model for the diodes; (c) input and output waveforms.



Bridge Full-Wave Rectifier

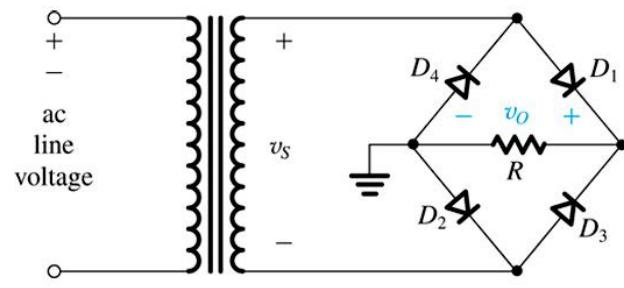

(a)

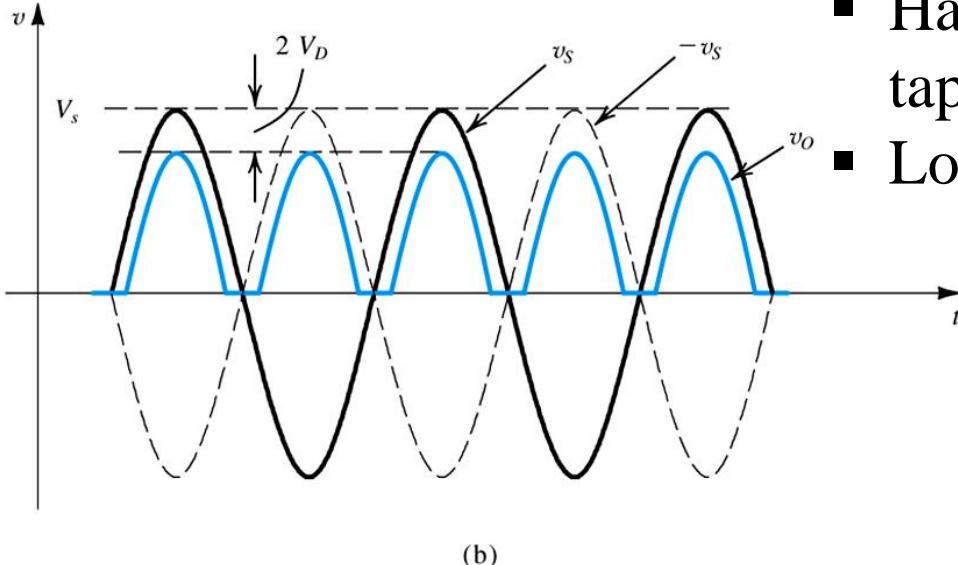



Figure 4.25 The bridge rectifier: (a) circuit; (b) input and output waveforms.

- Bridge rectifier requires 4 diodes instead of 2
- Conduction paths have two diode drops
- Half as many windings as a center-tapped transformer
- Lower peak inverse voltage


$$\text{PIV} = V_S - V_D$$



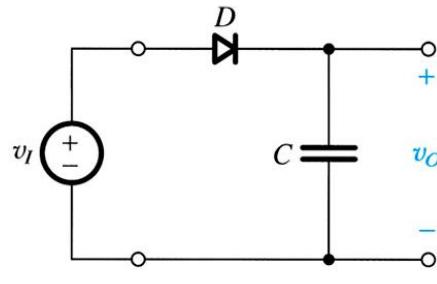The Half-Wave Rectifier with a Filter Capacitor



(a)

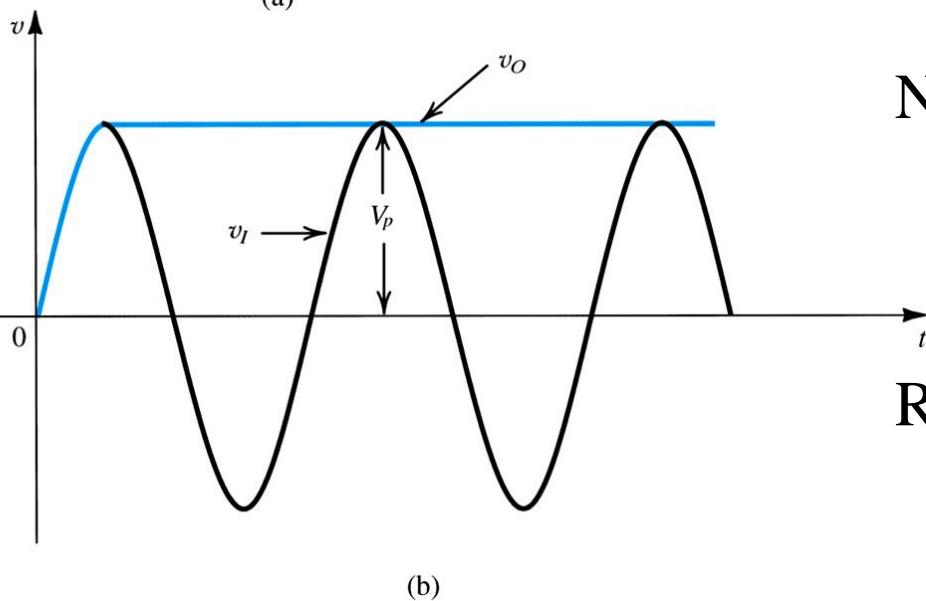


(b)

Assume an ideal diode.
Diode is only forward biased for the first $\frac{1}{4}$ cycle.
No load so there is no way for the capacitor to discharge.

Results in $v_O = V_p$ and is known as a **peak rectifier** or **peak detector**.

Figure 4.26 (a) A simple circuit used to illustrate the effect of a filter capacitor.
(b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*.

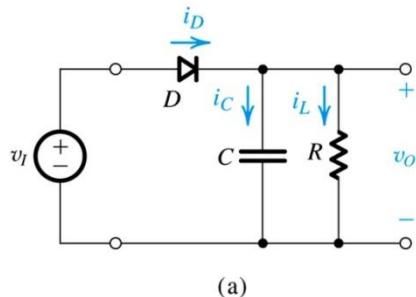

Half-Wave Rectifier with a Load


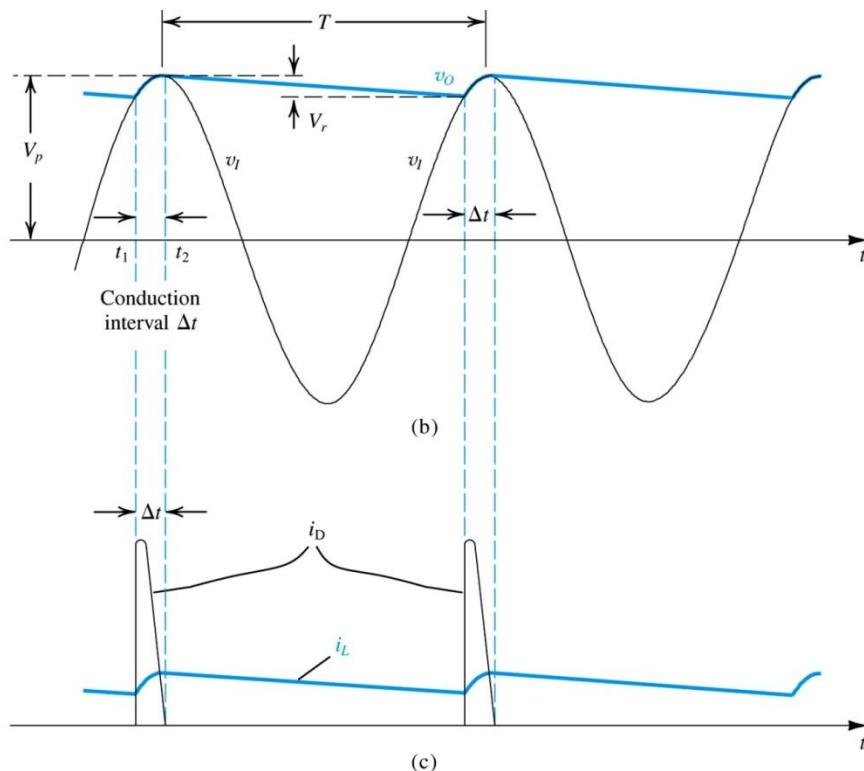


Figure 4.27 Voltage and current waveforms in the peak-rectifier circuit with $CR \gg T$. The diode is assumed ideal.

Assume an ideal diode.
Diode is only forward biased for a brief period in each cycle.
The capacitor charges during forward conduction and then discharges through the load resistor.

Choose a capacitor such that

$$\tau_{RC} \gg T$$

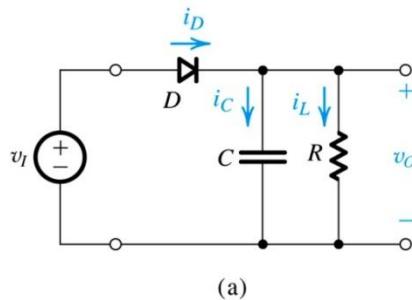

Half-Wave Rectifier with a Load

During the diode-off interval:

$$v_o = V_P e^{-t/RC}$$

At the end of the discharge

$$V_P - V_r \cong V_P e^{-T/RC}$$

But $RC \gg T$ so $e^{-T/RC} \cong 1 - T/RC$

$$V_r \cong V_P \frac{T}{RC}$$

Therefore, to keep the **ripple voltage**, V_r , low we need to select a capacitor such that $RC \gg T$.


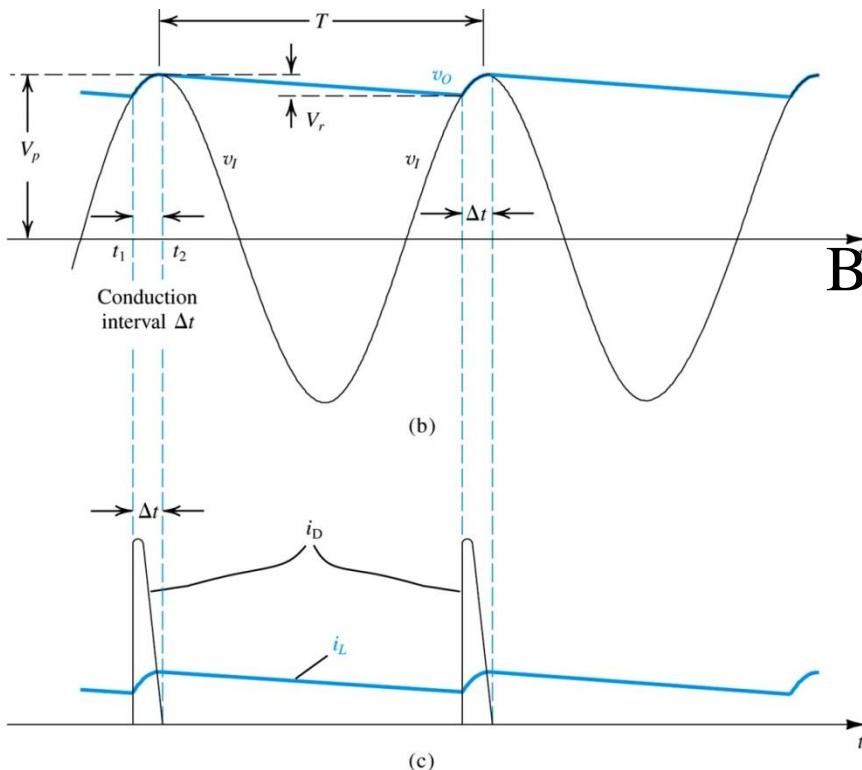


Figure 4.27 Voltage and current waveforms in the peak-rectifier circuit

with $CR \gg T$. The diode is assumed ideal.

Ch 4. Diodes


R. Martin

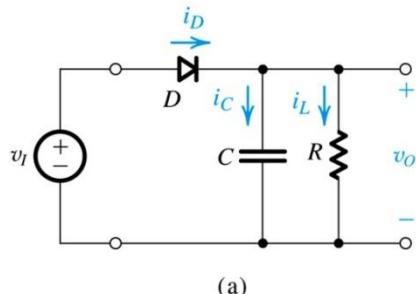

Half-Wave Rectifier with a Load

The ripple voltage in terms of the frequency is


$$V_r = \frac{V_p}{fRC}$$

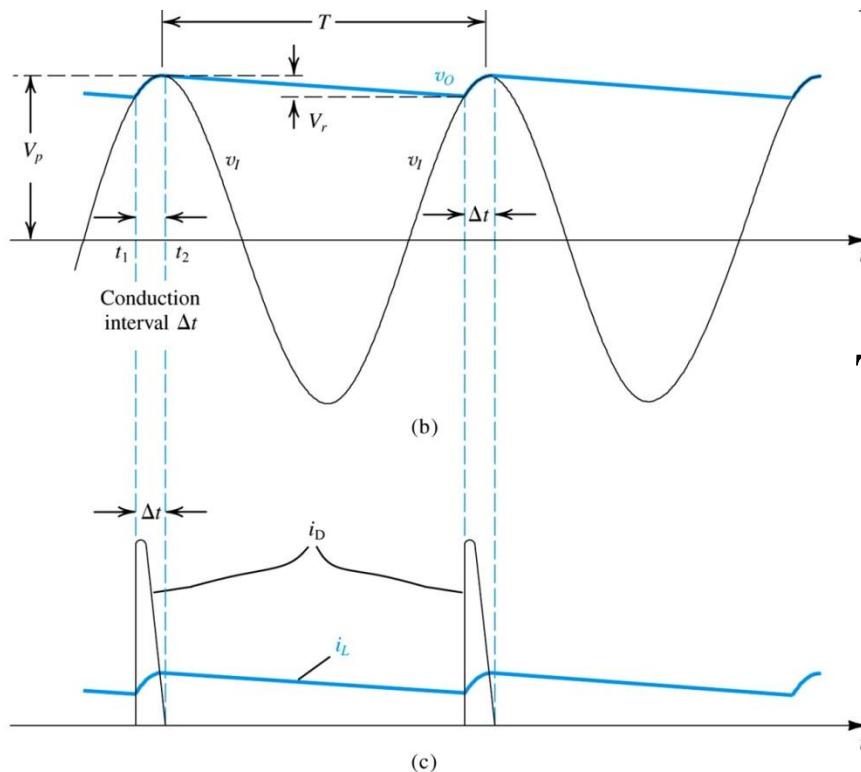

The DC component of the load current is

$$I_L = \frac{V_p}{R} \quad \text{so} \quad V_r = \frac{I_L}{fC}$$

Figure 4.27 Voltage and current waveforms in the peak-rectifier circuit with $CR \gg T$. The diode is assumed ideal.

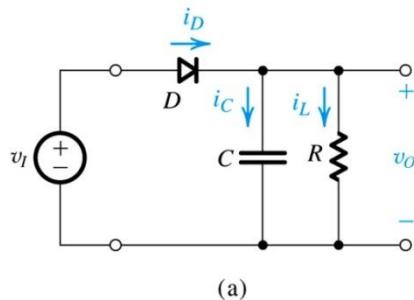

Half-Wave Rectifier with a Load

Assuming that diode conduction ceases almost at the peak of v_l , we can determine the **conduction interval** Δt from

$$V_P \cos(\omega\Delta t) \cong V_P - V_r$$

Using the small angle approximation

$$\omega\Delta t = \sqrt{2V_r/V_P}$$

To determine the average and peak diode current during conduction we equate the charge that the diode supplies to the capacitor (see p. 217).

$$I_{Dav} = I_L \left(1 + \pi \sqrt{2V_P/V_r} \right)$$

$$I_{Dmax} = I_L \left(1 + 2\pi \sqrt{2V_P/V_r} \right)$$

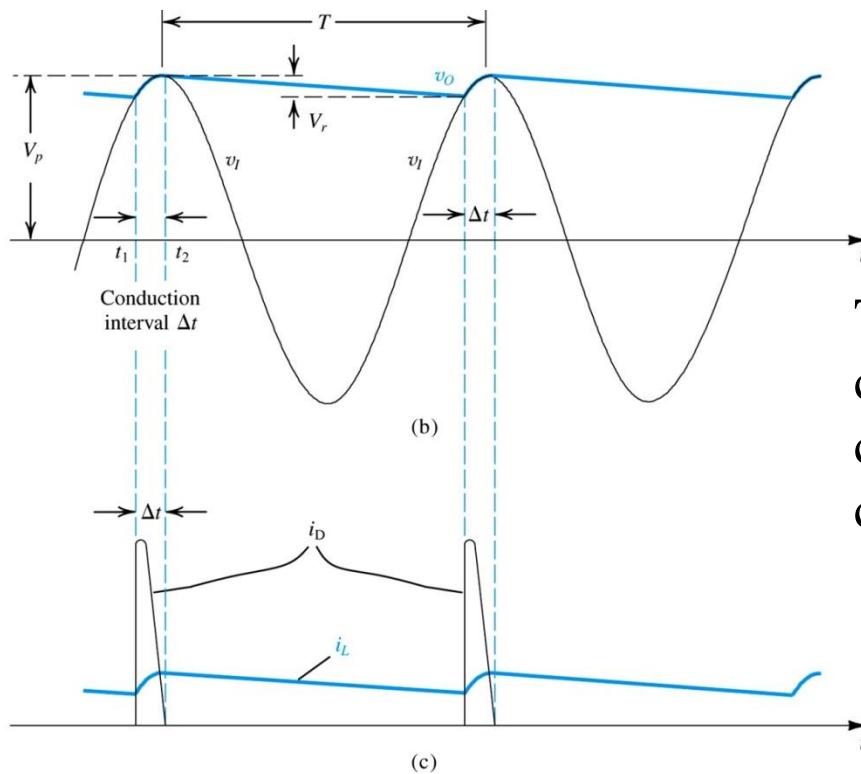


Figure 4.27 Voltage and current waveforms in the peak-rectifier circuit

with $CR \gg T$. The diode is assumed ideal.

R. Martin



Full-Wave Peak Rectifier

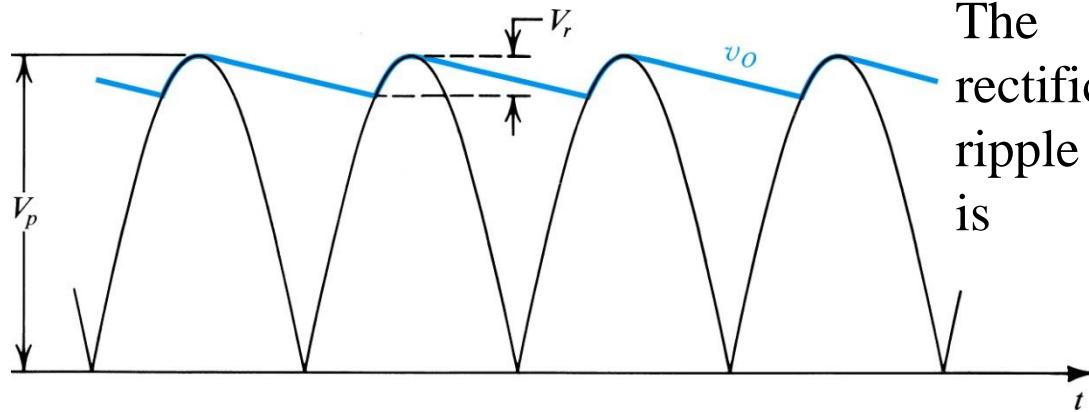


Figure 4.28 Waveforms in the full-wave peak rectifier.

The period in the half-wave rectification is replaced by $T/2$. The ripple voltage in terms of the frequency is

$$V_r = \frac{V_P}{2fRC}$$

$$\omega\Delta t = \sqrt[2]{2V_r/V_P}$$

$$I_{Dav} = I_L \left(1 + \pi \sqrt{V_P/2V_r} \right)$$

$$I_{Dmax} = I_L \left(1 + 2\pi \sqrt{V_P/2V_r} \right)$$

Comparing these expressions with the corresponding ones for the half-wave case, we note that for the same values of V_P , f , R , and V_r (and thus the same I_L), we need a capacitor half the size of that required in the half-wave rectifier. Also, the current in each diode in the full-wave rectifier is approximately half that which flows in the diode of the half-wave circuit.



Precision Half-Wave Rectifier, the “Superdiode”


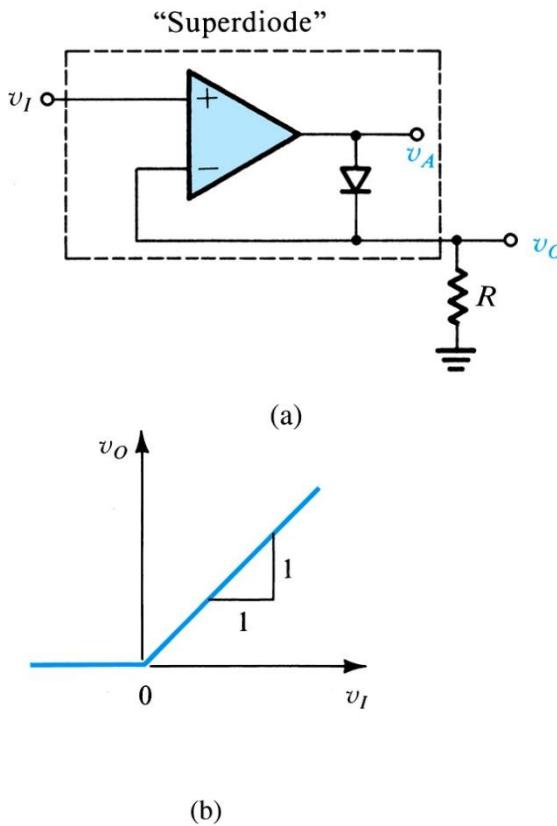


Figure 4.29 (a)The “superdiode” precision half-wave rectifier and (b) its almost-ideal transfer characteristic. Note that when $v_I > 0$ and the diode conducts, the op amp supplies the load current, and the source is conveniently buffered, an added advantage. Not shown are the op-amp power supplies.

Ch 4. Diodes

The rectifier circuits studied thus far suffer from having one or two diode drops in the signal paths. Thus these circuits work well only when the signal to be rectified is much larger than the voltage drop of a conducting diode (0.7 V or so). In such a case, the details of the diode forward characteristics or the exact value of the diode voltage do not play a prominent role in determining circuit performance.

Figure 4.29(a) shows a precision half-wave rectifier circuit consisting of a diode placed in the negative-feedback path of an op amp, with R being the rectifier load resistance. The combination of diode and op amp, shown in the dotted box in Fig. 4.29(a), is appropriately referred to as a "superdiode."

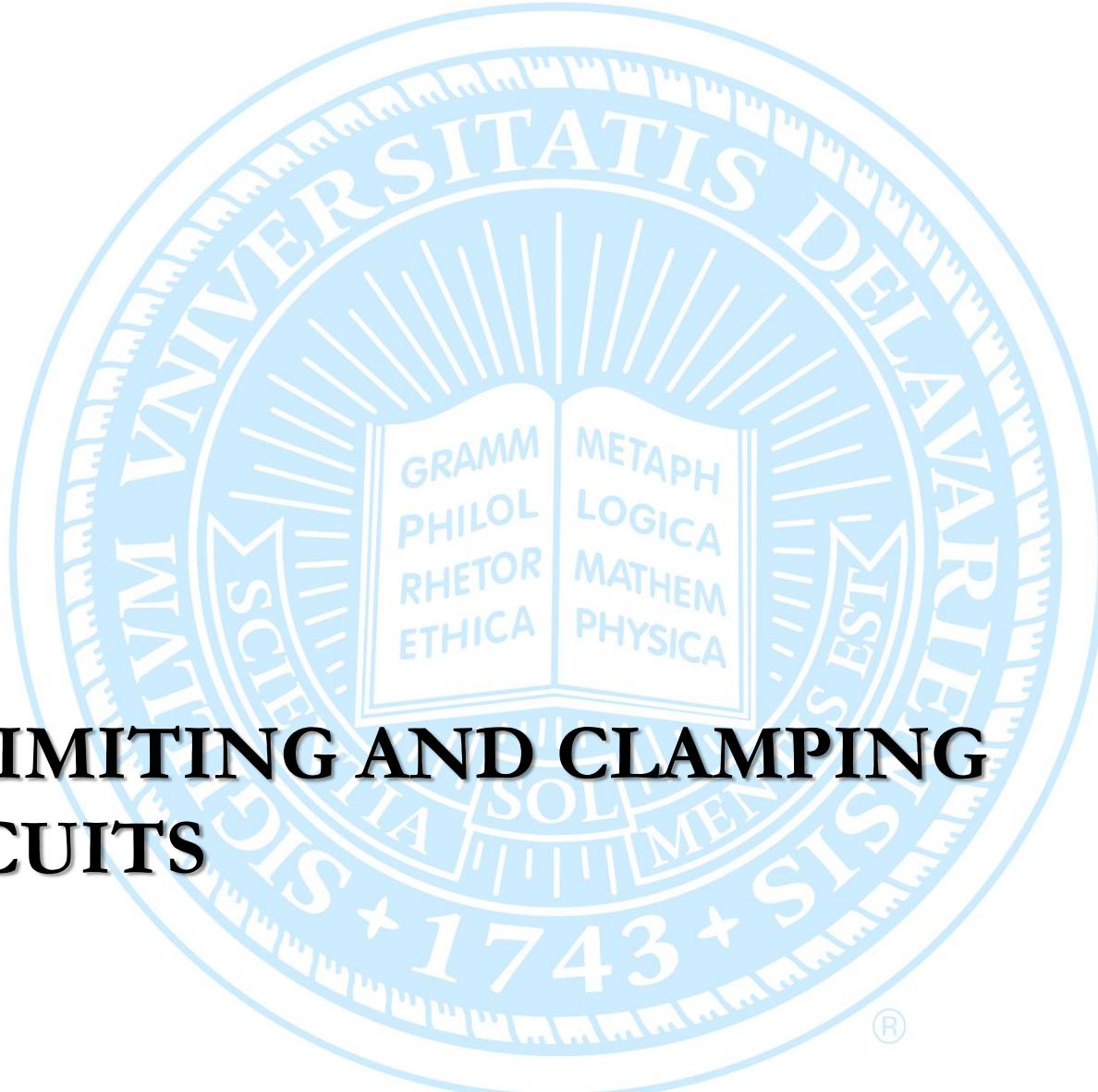


4.6 LIMITING AND CLAMPING CIRCUITS



The Limiter Circuit

Figure 4.30 shows the general transfer characteristic of a double limiter circuit.

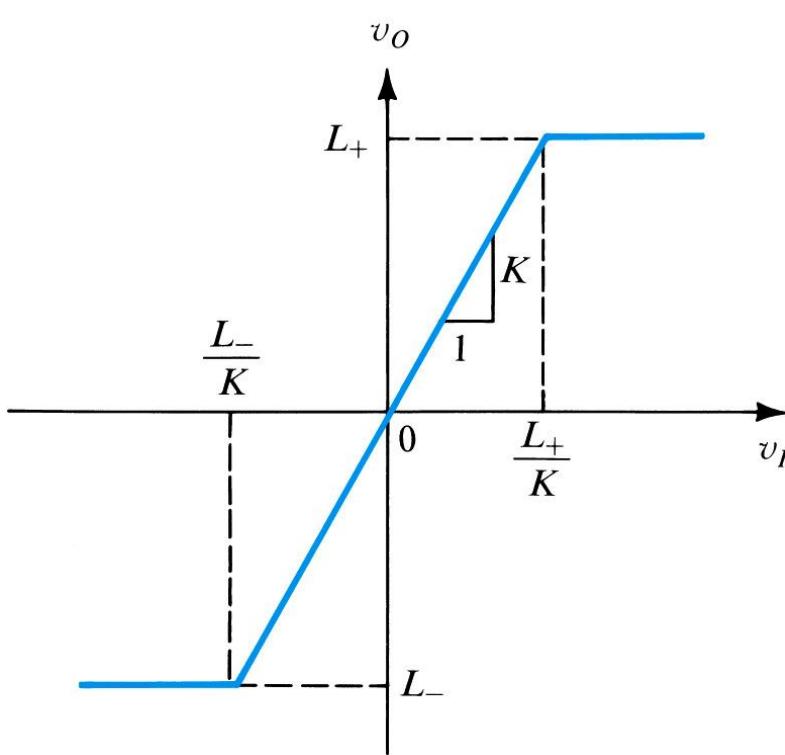

$$v_O = K v_I \quad \text{if} \quad L_-/K \leq v_I \leq L_+/K$$

$$v_O = L_+ \quad \text{if} \quad v_I > L_+/K$$

$$v_O = L_- \quad \text{if} \quad v_I < L_-/K$$

Although in general K can be greater than 1, the circuits discussed in this section have $K \leq 1$ and are known as **passive limiters**.

Figure 4.30 General transfer characteristic for a limiter circuit.



Results of a Double Limiter, or Clipper Circuit

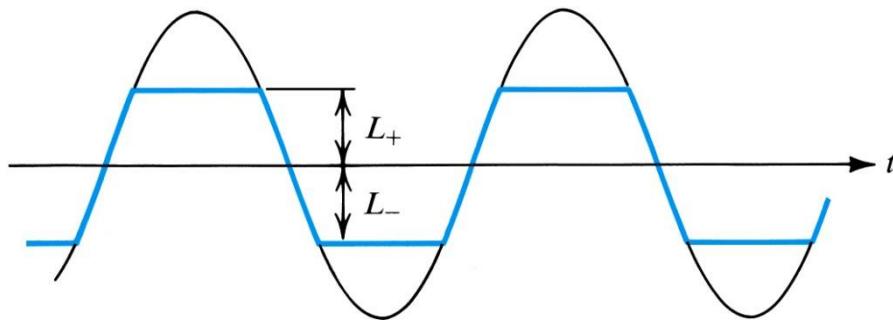


Figure 4.31 Applying a sine wave to a limiter can result in clipping off its two peaks.


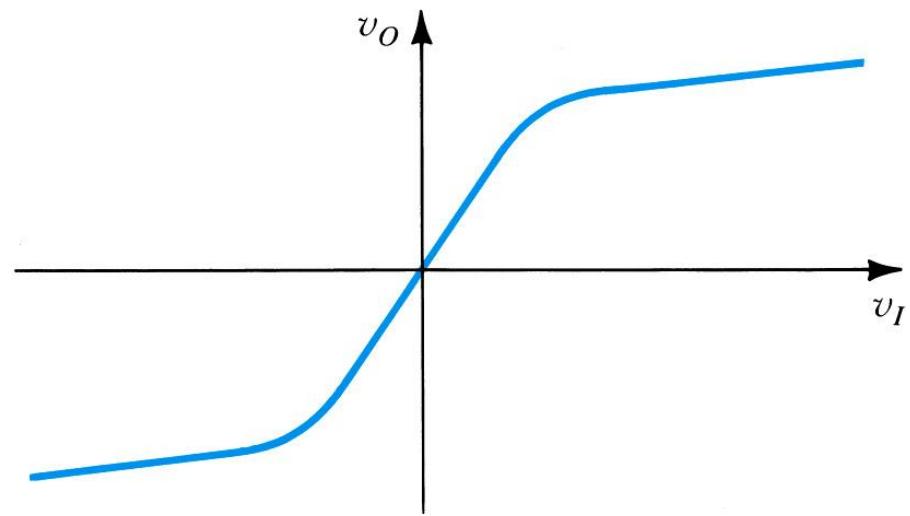


Figure 4.32 Soft limiting.

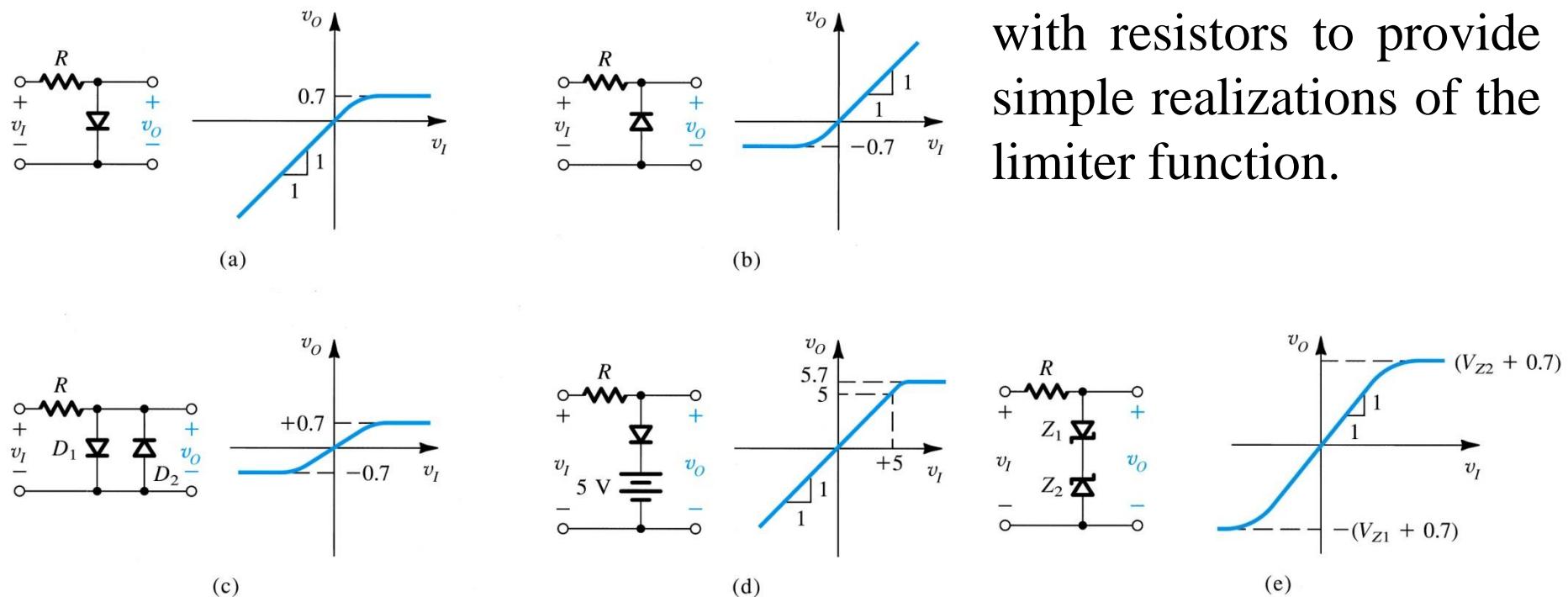

Basic Limiting Circuits



Diodes can be combined with resistors to provide simple realizations of the limiter function.

Figure 4.33 A variety of basic limiting circuits.



Exercise 4.26

Assuming the diodes to be ideal, describe the transfer characteristic of the circuit shown in Fig. E4.26.


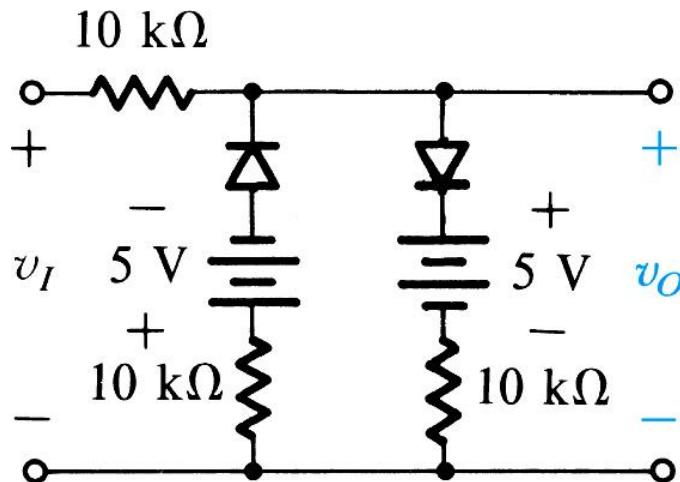


Figure E4.26

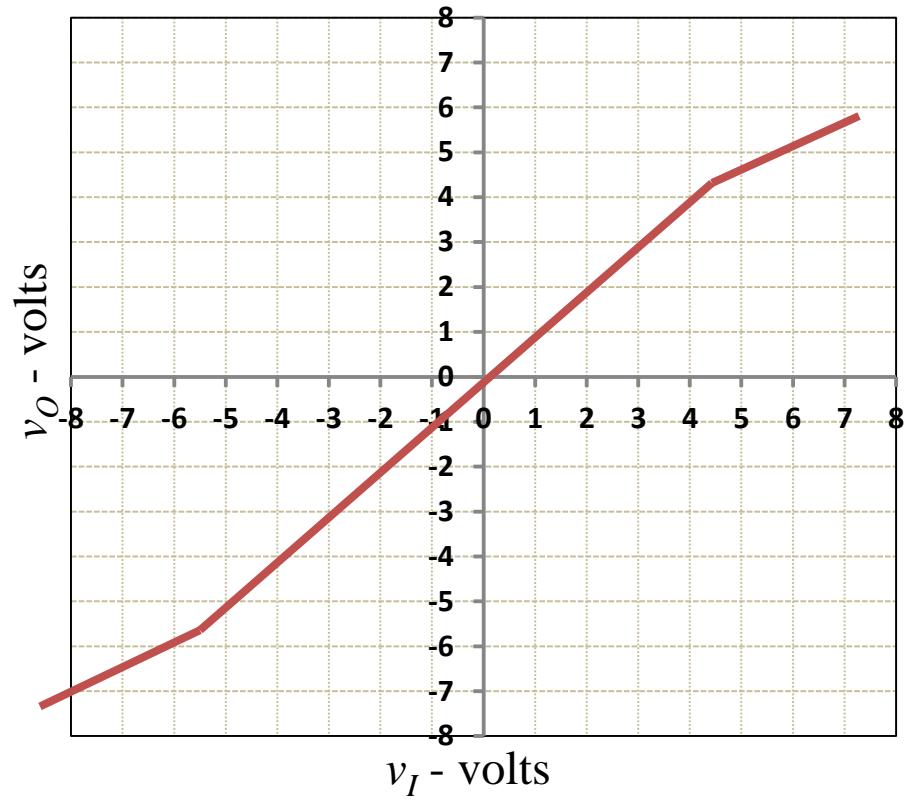



The Clamped Capacitor or DC Restorer

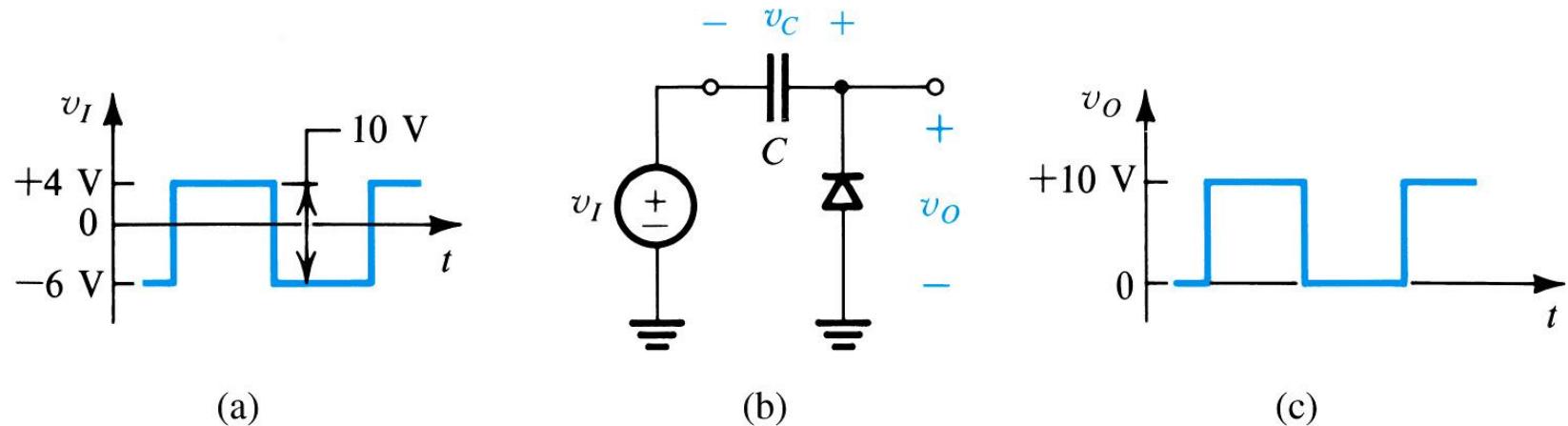


Figure 4.34 The clamped capacitor or dc restorer with a square-wave input and no load.

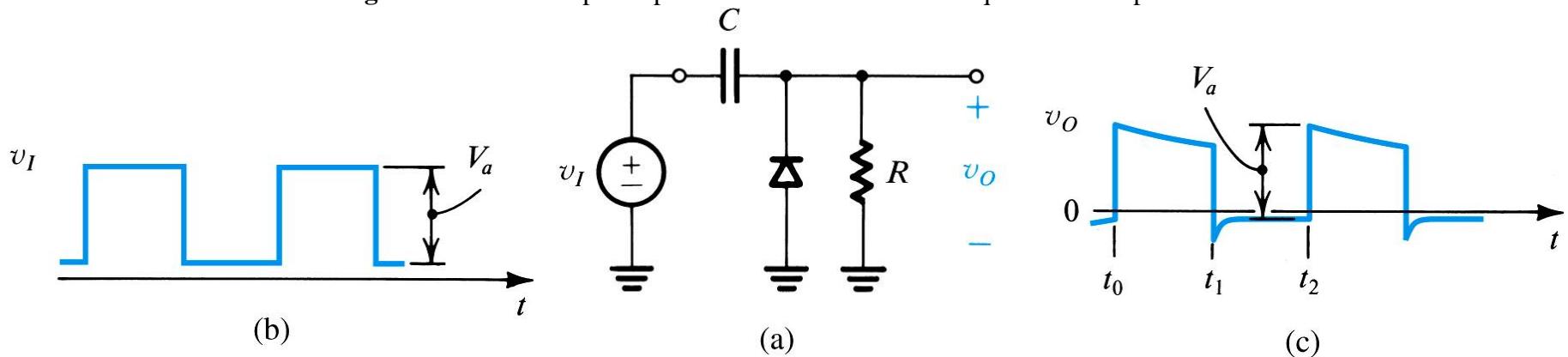


Figure 4.35 The clamped capacitor with a load resistance R .



The Voltage Doubler (Lab #4)

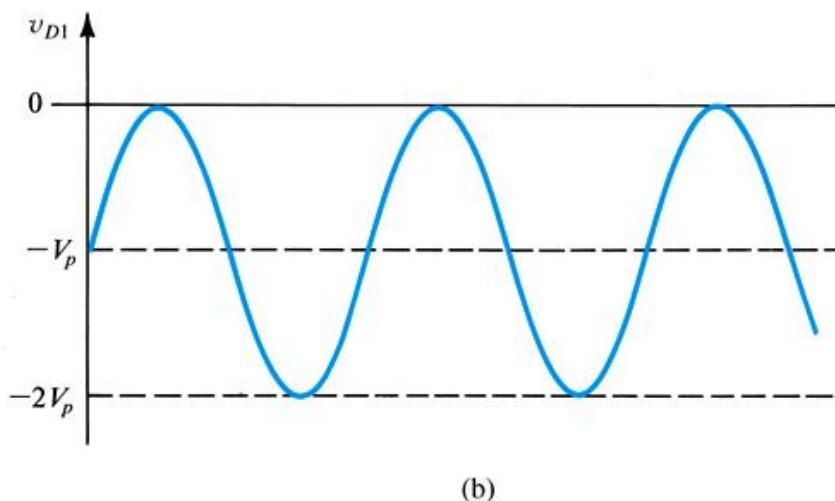
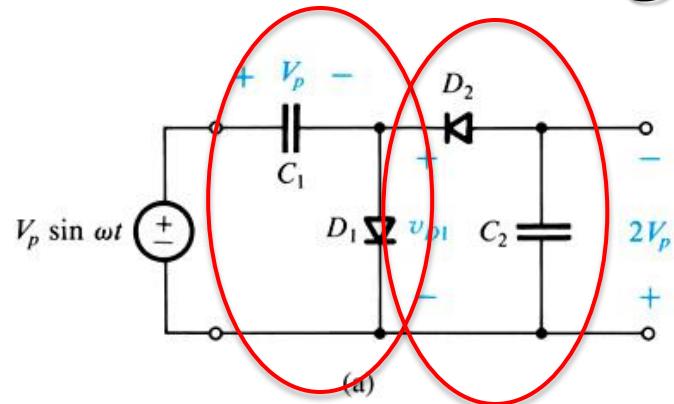


Figure 4.36 Voltage doubler: (a) circuit; (b) waveform of the voltage across D_1 .

C_1 and D_1 form a clamped capacitor

C_2 and D_2 form a peak rectifier

When excited by a sinusoid of amplitude V_P the clamping section provides the voltage waveform shown, assuming ideal diodes.


Note that while the positive peaks are clamped to 0 V, the negative peak reaches $-2V_P$.




Homework #8

- Finish reading Chapter 4
- Chapter 4 Problems:
 - 4.35*
 - 4.59*
 - 4.62
 - 4.70
 - 4.72
 - 4.87

* Answers in Appendix L

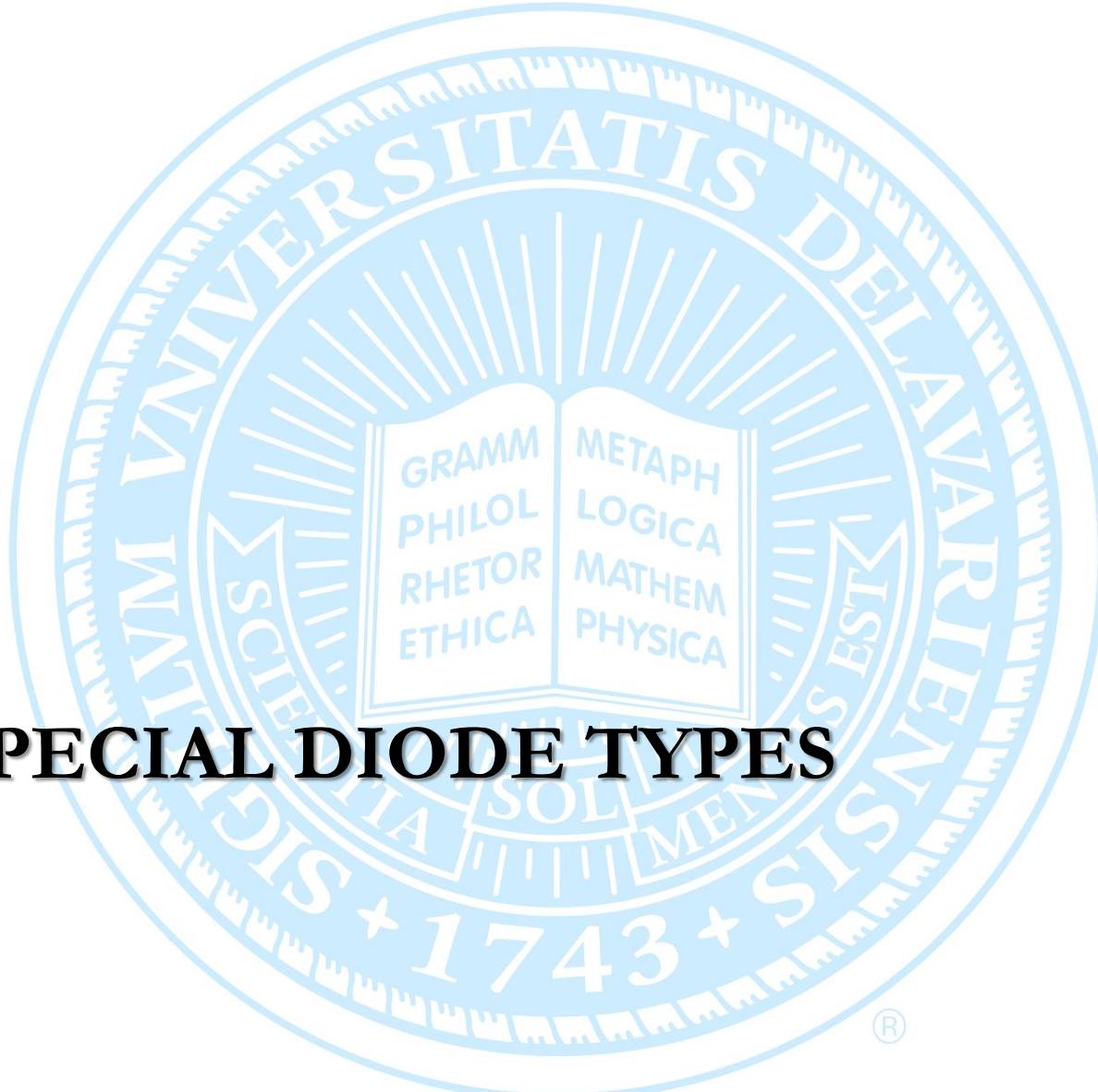


4.7 SPECIAL DIODE TYPES

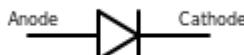

Special Diode Types



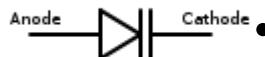- The Schottky-Barrier Diode (SBD)
 - Uses metal-semiconductor junctions
 - Faster (only majority carriers) and lower voltage drop



- Varactors
 - Voltage-variable capacitor (used for tuning frequency)



- Photodiodes/Solar Cells (Lab #3)
 - Convert photons to current



- Light-Emitting Diodes (LEDs), Laser Diodes (Lab #3)
 - Convert current to photons



- Zener Diode
- Tunnel Diode



Diode symbols from <https://en.wikipedia.org/wiki/Diode>



Summary

- In the forward direction, the ideal diode conducts any current forced by the external circuit while displaying a zero voltage drop. The ideal diode does not conduct in the reverse direction; any applied voltage appears as reverse bias across the diode.
- The unidirectional-current-flow property makes the diode useful in the design of rectifier circuits.
- The forward conduction of practical silicon-junction diodes is accurately characterized by the relationship $i = I_s e^{v/V_T}$.
- A silicon diode conducts a negligible current until the forward voltage is at least 0.5 V. Then the current increases rapidly, with the voltage drop increasing by 60 mV for every decade of current change.



Summary

- In many applications, a conducting diode is modeled as having a constant voltage drop, usually approximately 0.7 V.
- A diode biased to operate at a dc current I_D has a small-signal resistance $r_d = V_T / I_D$.
- Rectifiers convert ac voltages into unipolar voltages. Half-wave rectifiers do this by passing the voltage in half of each cycle and blocking the opposite-polarity voltage in the other half of the cycle. Full-wave rectifiers accomplish the task by passing the voltage in half of each cycle and inverting the voltage in the other half-cycle.
- The bridge-rectifier circuit is the preferred full-wave rectifier configuration.



Summary

- The variation of the output waveform of the rectifier is reduced considerably by connecting a capacitor C across the output load resistance R. The resulting circuit is the peak rectifier. The output waveform then consists of a dc voltage almost equal to the peak of the input sine wave, V_p , on which is superimposed a ripple component of frequency $2f$ (in the full-wave case) and of peak-to-peak amplitude $V_r = V_p/2fCR$. To reduce this ripple voltage further, a voltage regulator is employed.
- Combination of diodes, resistors, and possibly reference voltages can be used to design voltage limiters that prevent one or both extremities of the output wave form from going beyond predetermined values, the limiting level(s).



Summary

- Applying a time-varying waveform to a circuit consisting of a capacitor in series with a diode and taking the output across the diode provides a clamping function. Specifically, depending on the polarity of the diode, either the positive or negative peaks of the signal will be clamped to the voltage at the other terminal of the diode (usually ground). In this way the output waveform has a nonzero average or dc component, and the circuit is known as a dc restorer.
- By cascading a clamping circuit with a peak-rectifier circuit, a voltage doubler is realized.