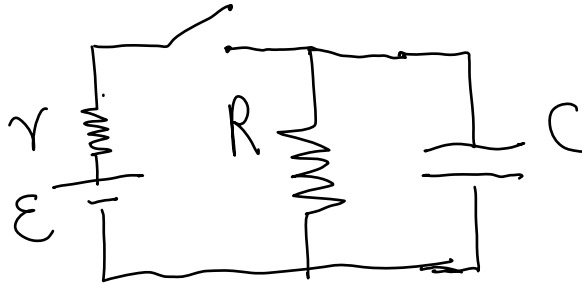


### Problem 1

In the figure below, let  $\varepsilon = 12 \text{ V}$ ,  $r = 2 \Omega$ ,  $R = 6 \Omega$ , and  $C = 4.5 \mu\text{F}$ . The capacitor is uncharged initially. The switch is connected at  $t = 0$ . (a) At  $t = 0^+$  find the initial current through each resistor and the charge on the capacitor. (b) Find the current through each resistor and the charge on the capacitor a long time after the battery is connected to the circuit.



### Problem 2

Ch. 26, #44

### Problem 3

Ch. 26, #46

### Problem 4


Ch. 26, #49

### Problem 5

At  $t < 0$ , the circuit shown in the Figure below is at steady state. The switch is changed as shown at  $t = 0$ .


$V_{S1} = 35 \text{ V}$ ,  $V_{S2} = 130 \text{ V}$ ,  $C = 11 \mu\text{F}$ ,  $R_1 = 17 \text{ k}\Omega$ ,  $R_2 = 7 \text{ k}\Omega$ , and  $R_3 = 23 \text{ k}\Omega$ .

Determine at  $t = 0^+$  the initial current through  $R_3$  just after the switch is changed.

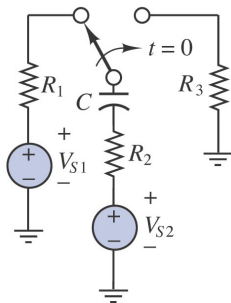

**Problem 6**

Steady-state conditions exist in the circuit shown below at  $t < 0$ . The switch is closed at  $t = 0$ .  $V_1 = 12\text{ V}$ ,  $R_1 = 0.68\text{ k}\Omega$ ,  $R_2 = 2.2\text{ k}\Omega$ ,  $R_3 = 1.8\text{ k}\Omega$ ,  $C = 0.47\text{ }\mu\text{F}$ . Determine the current through the capacitor at  $t = 0^+$ , just after the switch is closed.

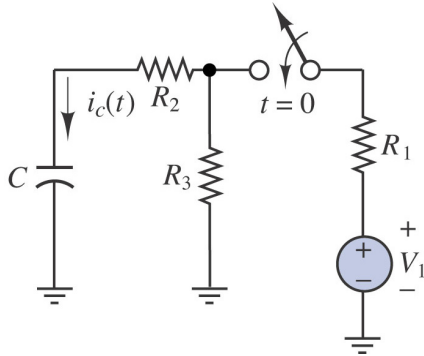
**Problem 7**

Ch. 26, #89

**Problem 8**

Determine the voltage across the inductor just before and just after the switch is changed in the figure below. Assume steady-state conditions exist for  $t < 0$ .

$V_S = 12\text{ V}$ ,  $R_S = 0.7\text{ }\Omega$ ,  $R_1 = 22\text{ k}\Omega$ , and  $L = 100\text{ mH}$ .

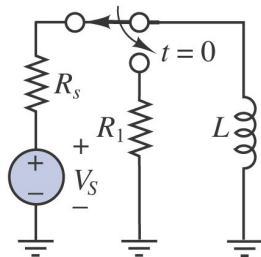**Problem 9**

The circuit in the figure below is a simple model of an automotive ignition system. The switch models the “points” that switch electric power to the cylinder when the fuel-air mixture is compressed. And  $R$  is the resistance between the electrodes (i.e., the “gap”) of the spark plug.  $V_G = 12\text{ V}$ ,  $R_G = 0.37\text{ }\Omega$ , and  $R = 1.7\text{ k}\Omega$ .

Determine the value of  $L$  and  $R_1$  so that the voltage across the spark plug gap just after the switch is changed is  $23\text{ kV}$  and so that this voltage will change exponentially with a time constant  $\tau = 13\text{ ms}$ .

