

Homework R. Martin

Problem 9.61

The differential amplifier circuit of Fig. P9.61 utilizes a resistor connected to the negative power supply to establish the bias current *I*.

- (a) For $v_{B1} = v_{id}/2$ and $v_{B2} = -v_{id}/2$, where v_{id} is a small signal with zero average, find the magnitude of the differential gain, $|v_o/v_{id}|$.
- (b) For $v_{B1} = v_{B2} = v_{icm}$, where v_{icm} has a zero average, find the magnitude of the common-mode gain, $|v_o/v_{icm}|$.
- (c) Calculate the CMRR.
- (d) If $v_{B1} = 0.1 \sin(2\pi \times 60t) + 0.005 \sin(2\pi \times 1000t)$, volts, and $v_{B2} = 0.1 \sin(2\pi \times 60t) 0.005 \sin(2\pi \times 1000t)$, volts, find v_o .

$$V_{B1} = V_{B2} = 0V \qquad V_{E} = V_{B} - V_{BE} = 0V - 0.7V = -0.7V$$

$$I = \frac{V_{E} - V_{EE}}{R_{E}} = \frac{-0.7V + 5V}{4.3k\Omega} = \frac{4.3V}{4.3k\Omega} = 1mA$$

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{1mA}{2} = 0.5mA$$

Figure P9.61

R. Martin


Problem 9.61a

The differential amplifier circuit of Fig. P9.61 utilizes a resistor connected to the negative power supply to establish the bias current *I*.

(a) For $v_{B1} = v_{id}/2$ and $v_{B2} = -v_{id}/2$, where v_{id} is a small signal with zero average, find the magnitude of the differential gain, $|v_o/v_{id}|$.

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{1 \text{mA}}{2} = 0.5 \text{mA}$$
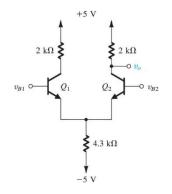
$$r_{e1} = r_{e2} = \frac{V_T}{I_E} = \frac{25\text{mV}}{0.5\text{mA}} = 50\Omega$$



$$A_{d} \equiv \frac{v_{o}}{v_{id}} = \alpha \frac{\text{total resistance across } v_{o}}{\text{total emitter resistance}} = \alpha \frac{R_{C}}{r_{e1} + r_{e2}} \simeq \frac{2k\Omega}{0.1k\Omega} = 20 \frac{V}{V}$$

Figure P9.61

Problem 9.61b,c

The differential amplifier circuit of Fig. P9.61 utilizes a resistor connected to the negative power supply to establish the bias current *I*.

(b) For $v_{B1} = v_{B2} = v_{icm}$, where v_{icm} has a zero average, find the magnitude of the common-mode gain, $|v_o/v_{icm}|$.

(c) Calculate the CMRR.

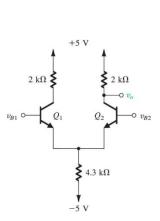


Figure P9.61

$$\frac{1}{R_C} \qquad A_{cm} \equiv \frac{v_o}{v_{icm}} = \alpha \frac{\text{total resistance across } v_o}{\text{total emitter resistance}}$$

$$= -\alpha \frac{R_C}{2R_{SS} + r_{e2}} \simeq \frac{-2k\Omega}{8.6k\Omega + 0.05k\Omega}$$

$$= -0.23 \frac{V}{V}$$

$$CMRR = 20\log\left(\frac{|A_d|}{|A_{cm}|}\right) = 20\log\left(\frac{20\text{ V/V}}{0.23\text{ V/V}}\right) = 38.8\text{dB}$$

Problem 9.61d

The differential amplifier circuit of Fig. P9.61 utilizes a resistor connected to the negative power supply to establish the bias current *I*.

(d) If
$$v_{B1} = 0.1 \sin(2\pi \times 60t) + 0.005 \sin(2\pi \times 1000t)$$
, volts, and $v_{B2} = 0.1 \sin(2\pi \times 60t) - 0.005 \sin(2\pi \times 1000t)$, volts, find v_o .

$$v_{icm} = 0.1 \sin(2\pi \times 60t)$$

$$A_{cm} = -0.23 \frac{V}{V}$$

$$v_{B2} = 2 \times 0.005 \sin(2\pi \times 1000t) = 0.01 \sin(2\pi \times 1000t)$$

$$A_d = 20 \frac{V}{V}$$


$$\Rightarrow v_o = A_{cm}v_{icm} + A_dv_{id}$$

$$= (-0.23)(0.1\sin(2\pi 60t)) + (20)(0.01\sin(2\pi 1000t))$$

$$= -0.023\sin(2\pi 60t) + 0.2\sin(2\pi 1000t)$$

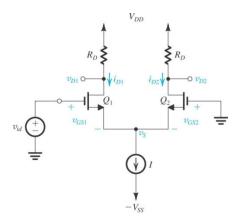Problem 9.73a

An NMOS differential pair operating at a bias current I of 100 μ A uses transistors for which $k'_n = 200 \text{ uA/V}^2$ and W/L = 10. Find the three components of input offset voltage under the conditions that $\Delta R_D/R_D = 4\%$, $\Delta (W/L)/(W/L) = 4\%$, and $\Delta V_t = 5$ mV. In the worst case, what might the total offset be? For the usual case of the three effects being independent, what is the offset likely to be?



$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{OV}^2$$

$$V_{OV} = \sqrt{I/[k_n'(W/L)]} = \sqrt{\frac{0.1 \text{mA}}{V^2}(10)} = 0.224 \text{V}$$

$$\Delta R_D/R_D = 4\%$$

$$V_{OS} = \frac{V_O}{A_d} = \left(\frac{V_{OV}}{2}\right) \left(\frac{\Delta R_D}{R_D}\right) = \left(\frac{0.224 \text{V}}{2}\right) (0.04) = 4.5 \text{mV}$$

Homework R. Martin

Problem 9.73b

An NMOS differential pair operating at a bias current I of 100 μ A uses transistors for which $k'_n = 200 \text{ uA/V}^2$ and W/L = 10. Find the three components of input offset voltage under the conditions that $\Delta R_D/R_D = 4\%$, $\Delta(W/L)/(W/L) = 4\%$, and $\Delta V_t = 5 \text{ mV}$. In the worst case, what might the total offset be? For the usual case of the three effects being independent, what is the offset likely to be?

$$V_{DD}$$

$$V_{DD}$$

$$V_{DV} = 0.2V$$

$$V_{UD1}$$

$$V_{UD1}$$

$$V_{UD1}$$

$$V_{UD2}$$

$$V_{UD2}$$

$$V_{UD2}$$

$$V_{UD3}$$

$$\Delta(W/L)/(W/L) = 4\%$$

$$V_{OS} = \left(\frac{V_{OV}}{2}\right) \left(\frac{\Delta(W/L)}{(W/L)}\right) = \left(\frac{0.224 \text{V}}{2}\right) (0.04) = 4.5 \text{mV}$$

$$\Delta V_t = 5 \text{ mV}$$

$$V_{OS} = \Delta V_t = 5 \text{mV}$$

worst case offset: $V_{OS} = V_{OS\Delta R} + V_{OS\Delta(W/L)} + V_{OS\Delta V_t} = 4.5 \text{mV} + 4.5 \text{mV} + 5 \text{mV} = 14 \text{mV}$

likely offset:
$$V_{OS} = \sqrt{V_{OS\Delta R}^2 + V_{OS\Delta(W/L)}^2 + V_{OS\Delta V_t}^2} = \sqrt{(4.5 \text{mV})^2 + (4.5 \text{mV})^2 + (5 \text{mV})^2} = 8.1 \text{mV}$$

Homework R. Martin

Problem 9.74

A bipolar differential amplifier uses two well-matched transistors but collector load resistors that are mismatched by 10%. What input offset voltage is required to reduce the differential output voltage to zero?

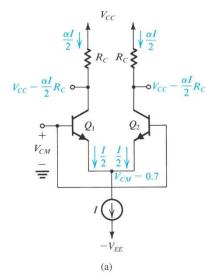


Figure 8.16: Different modes of operation of the BJT differential pair: (a) the differential pair with a common-mode input voltage V_{CM} .

$$V_{O} = V_{C2} - V_{C1} = \alpha \left(\frac{I}{2}\right) \Delta R_{C}$$
 $A_{d} = \frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = g_{m}R_{C}$

$$V_{O} = V_{C2} - V_{C1} = \alpha \left(\frac{I}{2}\right) \Delta R_{C}$$

$$V_{O} = V_{C2} - V_{C1} = \alpha \left(\frac{I}{2}\right) \Delta R_{C}$$

$$A_{d} = \frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = g_{m}R_{C}$$

$$V_{CC} - \frac{\alpha I}{2}R_{C}$$

$$V_{CC} - \frac{\alpha I}{2}R_{C}$$

$$V_{CS} = \frac{V_{O}}{A_{d}} = \frac{\alpha \frac{I}{2}\Delta R_{C}}{g_{m}R_{C}}$$


$$g_{m} = \frac{I_{C}}{V_{T}} = \frac{\alpha I_{E}}{V_{T}} \rightarrow V_{T} = \frac{\alpha I_{E}}{g_{m}}$$

$$V_{OS} = \frac{\alpha I_E}{g_m} \left(\frac{\Delta R_C}{R_C} \right) = V_T \left(\frac{\Delta R_C}{R_C} \right)$$

$$\left|V_{OS}\right| = V_T \left(\frac{\Delta R_C}{R_C}\right) = 25 \text{mV} (0.1) = 2.5 \text{mV}$$

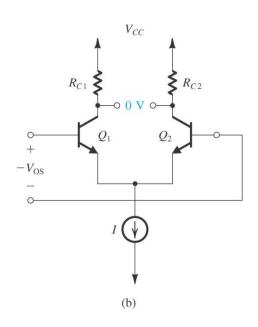Problem 9.77a

A differential amplifier uses two transistors whose β values are β_1 and β_2 . If everything else is matched, show that the input offset voltage is approximately $V_T[(1/\beta_1) - (1/\beta_2)]$. Evaluate V_{OS} for $\beta_1 = 50$ and $\beta_2 = 100$. Assume the differential source resistance to be zero.



$$V_{C1} = V_{CC} - \frac{\alpha_{1}I}{2}R_{C} \qquad V_{C2} = V_{CC} - \frac{\alpha_{2}I}{2}R_{C}$$

$$V_{O} = V_{C2} - V_{C1} = (\alpha_{1} - \alpha_{2})\left(\frac{IR_{C}}{2}\right)$$


$$V_{O} = \left(\frac{IR_{C}}{2}\right)\left(\frac{\beta_{1}}{\beta_{1} + 1} - \frac{\beta_{2}}{\beta_{2} + 1}\right) = \left(\frac{IR_{C}}{2}\right)\left(\frac{\beta_{1} - \beta_{2}}{\beta_{1}\beta_{2} + \beta_{1} + \beta_{2} + 1}\right)$$

$$V_{O} = \left(\frac{IR_{C}}{2}\right)\left(\frac{\beta_{1} - \beta_{2}}{\beta_{1}\beta_{2}}\right) = \left(\frac{IR_{C}}{2}\right)\left(\frac{1}{\beta_{2}} - \frac{1}{\beta_{1}}\right)$$

$$A_{d} = \frac{v_{od}}{v_{id}} = \frac{v_{o2} - v_{o1}}{v_{id}} = g_{m}R_{C} = \left(\frac{\alpha I/2}{V_{T}}\right)R_{C}$$

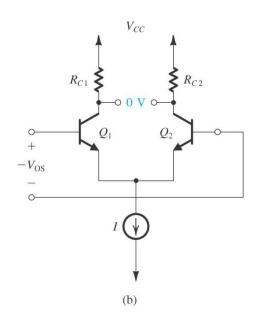Problem 9.77b

A differential amplifier uses two transistors whose β values are β_1 and β_2 . If everything else is matched, show that the input offset voltage is approximately $V_T[(1/\beta_1) - (1/\beta_2)]$. Evaluate V_{OS} for $\beta_1 = 50$ and $\beta_2 = 100$. Assume the differential source resistance to be zero.



$$V_{o} = \left(\frac{IR_{c}}{2}\right) \left(\frac{1}{\beta_{2}} - \frac{1}{\beta_{1}}\right) \qquad A_{d} = g_{m}R_{c} = \left(\frac{\alpha I/2}{V_{T}}\right)R_{c}$$

$$V_{os} = \frac{V_{o}}{A_{d}} = \frac{\left(\frac{IR_{c}}{2}\right) \left(\frac{1}{\beta_{1}} - \frac{1}{\beta_{2}}\right)}{\left(\frac{\alpha I/2}{V_{T}}\right)R_{c}} = \frac{V_{T}}{\alpha} \left(\frac{1}{\beta_{1}} - \frac{1}{\beta_{2}}\right) \approx V_{T} \left(\frac{1}{\beta_{1}} - \frac{1}{\beta_{2}}\right)$$

$$V_{os} = V_{T} \left(\frac{1}{\beta_{2}} - \frac{1}{\beta_{1}}\right) = 25\text{mV} \left(\frac{1}{100} - \frac{1}{50}\right) = -250\mu\text{V}$$

Problem 9.81a

One approach to "offset correction" involves the adjustment of the values of R_{C1} and R_{C2} so as to reduce the differential output voltage to zero when both input terminals are grounded. This offset-nulling process can be accomplished by utilizing a potentiometer in the collector circuit, as shown in Fig. P9.81. We wish to find the potentiometer setting, represented by the fraction x of its value connected in series with R_{C1} , that is required for nulling the output offset voltage that results from:

- (a) R_{C1} being 4% higher than nominal and R_{C2} 4% lower than nominal
- (b) Q_1 having an area 5% larger than nominal, while Q_2 has area 5% smaller than nominal.

$$R_{C1} + (x \times 1k\Omega) = R_{C2} + [(1-x)\times 1k\Omega]$$

$$(5k\Omega\times1.04) + (x\times1k\Omega) = (5k\Omega\times0.96) + 1k\Omega - (x\times1k\Omega)$$

$$2(x\times1k\Omega) = 4.8k\Omega - 5.2k\Omega + 1k\Omega = 0.6k\Omega$$

$$x = 0.3$$

Figure P9.81

Problem 9.81b

One approach to "offset correction" involves the adjustment of the values of R_{C1} and R_{C2} so as to reduce the differential output voltage to zero when both input terminals are grounded. This offset-nulling process can be accomplished by utilizing a potentiometer in the collector circuit, as shown in Fig. P9.81. We wish to find the potentiometer setting, represented by the fraction x of its value connected in series with R_{C1} , that is required for nulling the output offset voltage that results from:

(b) Q_1 having an area 5% larger than nominal, while Q_2 has area 5% smaller than nominal.

$$I_{C1}\left[R_C + (x \times 1k\Omega)\right] = I_{C2}\left[R_C + (1-x) \times 1k\Omega\right]$$

$$I_{C1} = \alpha I_{E1} \simeq 1.05 I_C = 1.05 (0.5 \text{mA}) = 0.525 \text{mA}$$

$$I_{C2} \simeq \alpha I_{E2} = 0.95 I_C = 0.95 (0.5 \text{mA}) = 0.475 \text{mA}$$

$$x \times 1 \text{k}\Omega = \frac{I_{C2} \left(5 \text{k}\Omega + 1 \text{k}\Omega\right) R_C - \left(I_{C1} \times 5 \text{k}\Omega\right)}{\left(I_{C1} + I_{C2}\right)} = \frac{2.85 \text{V} - 2.625 \text{V}}{1 \text{mA}} = .225 \text{k}\Omega$$

$$x = 0.225$$

Figure P9.81

Problem 9.82a

A differential amplifier for which the total emitter bias current is 400 μ A uses transistors for which β is specified to lie between 80 and 200. What is the largest possible input bias current? The smallest possible input bias current? The largest possible input offset current?

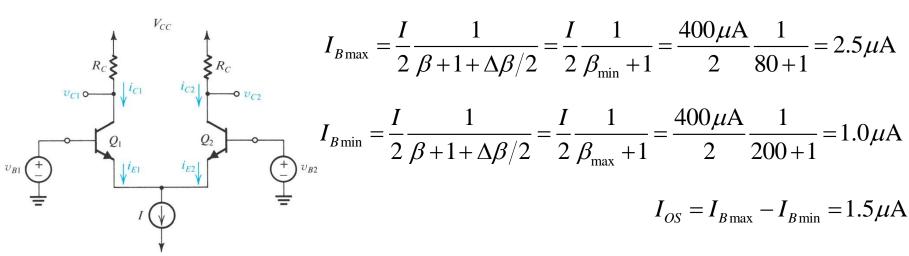


Figure 9.14: The basic BJT differential-pair configuration.

$$I_{OS} = \frac{I}{2(\beta+1)} \left(\frac{\Delta\beta}{\beta}\right) = \frac{400\mu\text{A}}{2(140+1)} \left(\frac{120}{140}\right) = 1.22\mu\text{A}$$

Homework R. Martin