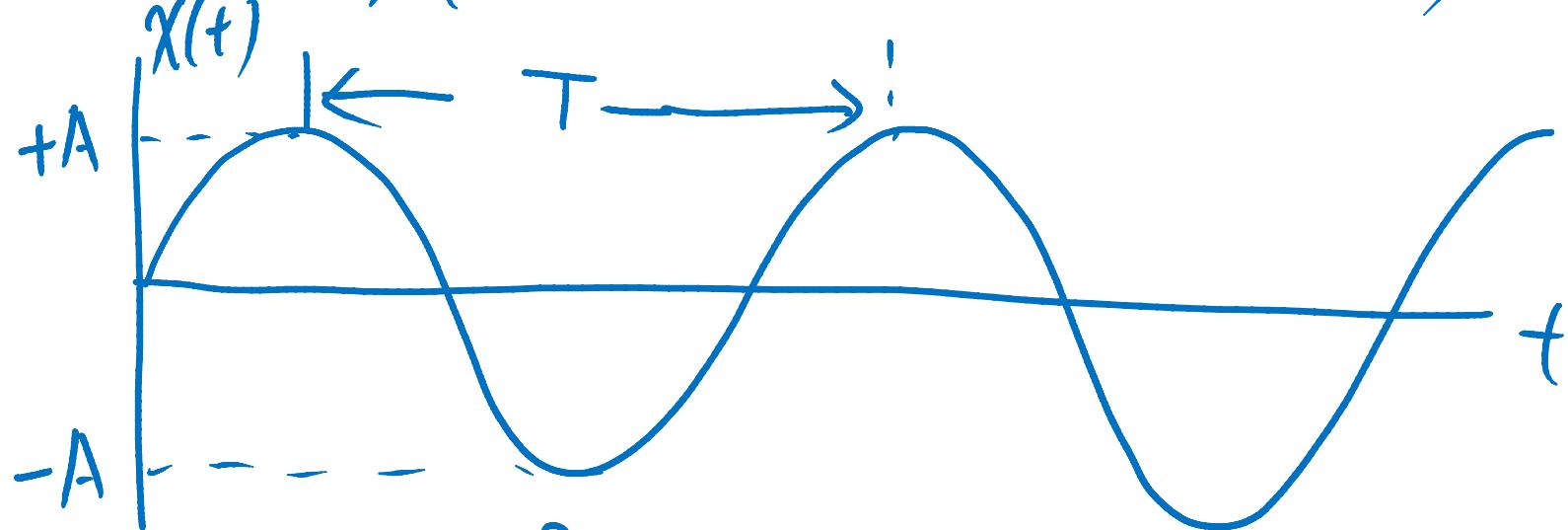


## Chapter 3. A.C. circuits


### \* Sinusoidal waves

$$x(t) = A \sin \omega t = A \cos \left( \omega t - \frac{\pi}{2} \right)$$



Why sinusoids?  
fundamental waves

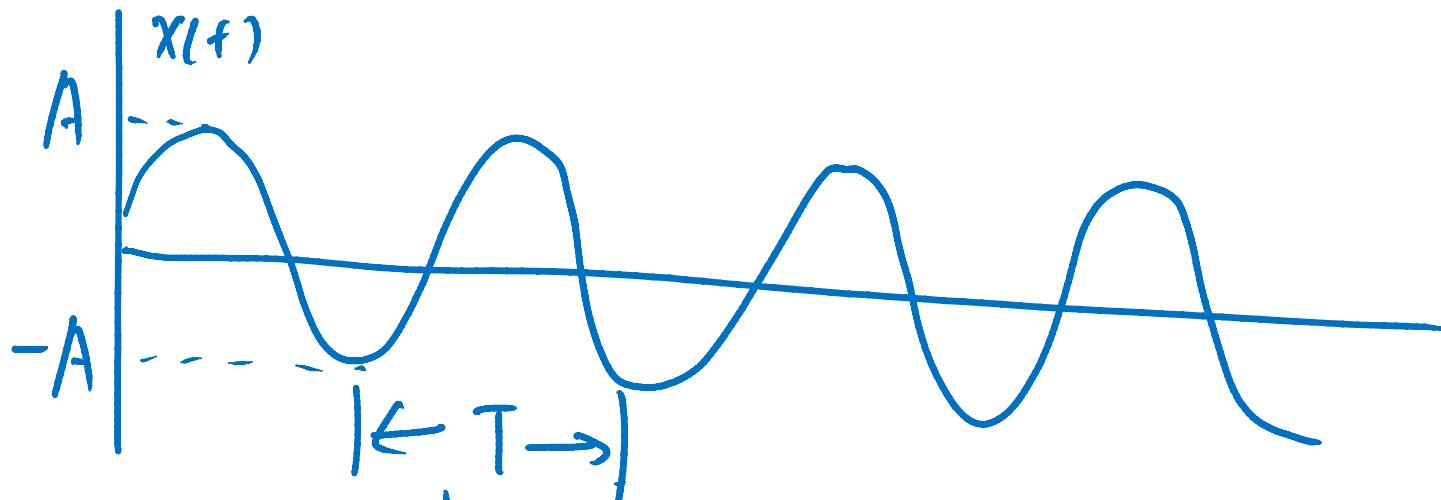Arbitrary periodic function can be constructed by using  
sinusoids with different frequencies)  
(Fourier transform)



In general  $x(t) = A \cos(\omega t + \varphi)$

$A$ : amplitude

$T$ : period. unit : s


$$f = \frac{1}{T} \quad \text{frequency. unit: } \frac{1}{s} \text{ or Hz}$$

$$\text{angular frequency } \omega = 2\pi f = \frac{2\pi}{T} \quad \begin{matrix} \text{unit: rad/s} \\ \text{or } 1/s \end{matrix}$$

Average and RMS values of a.c. signal.

— average
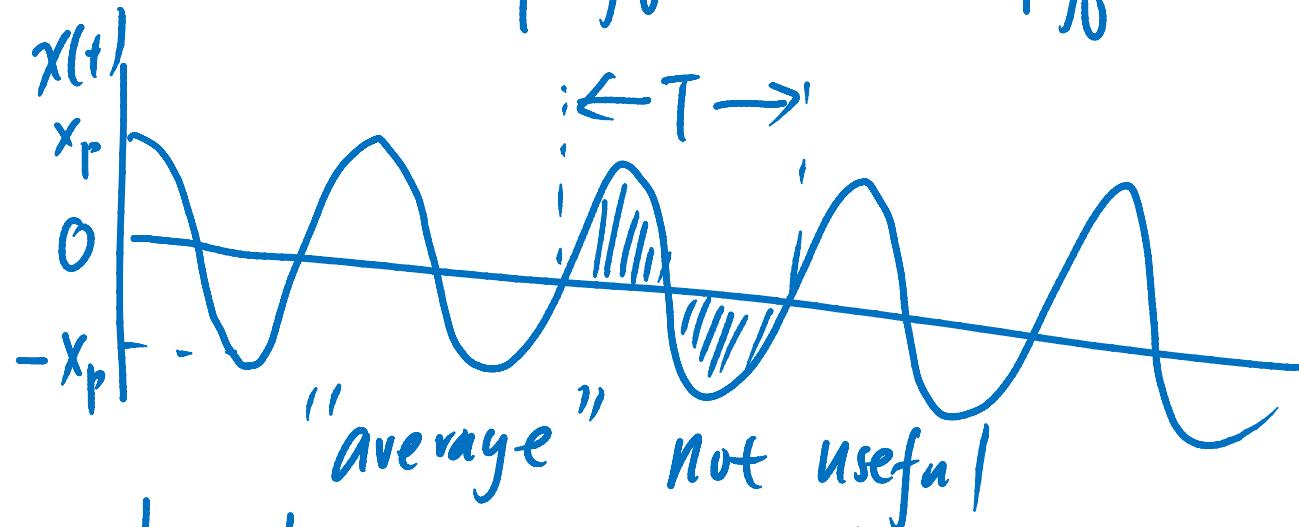
$$\langle x(t) \rangle = \frac{1}{T} \int_0^T x(t) dt = \frac{1}{T} \int_0^T A \cos(\omega t + \varphi) dt = 0$$



— peak value  $x_p$  is useful

— root-mean-square (rms) values

$$X_{\text{rms}} = \sqrt{\overline{x^2(t)}} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$x(t) = A \sin \omega t$$

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T A^2 \sin^2 \omega t dt}$$

$$= \sqrt{\frac{A^2}{T} \int_0^T \left( \frac{1 - \cos 2\omega t}{2} \right) dt}$$

$$= \sqrt{\frac{A^2}{T} \cdot \frac{\pi}{2}} = \frac{A}{\sqrt{2}}$$

If  $A = V_p$ ,  $V_{rms} = \frac{V_p}{\sqrt{2}}$ . If  $A = I_p$ ,  $I_{rms} = \frac{I_p}{\sqrt{2}}$

$$p(t) = i^2(t) R$$

$$P_{\text{ave}} = \overline{p(t)} = \overline{i^2(t)} R = I_{\text{rms}}^2 R,$$

$$P_{\text{ave}} = I_{\text{rms}}^2 R \quad (\text{resistive})$$

general  $P_{\text{ave}} = I_{\text{rms}} (I_{\text{rms}} R) = I_{\text{rms}} \cdot V_{\text{rms}}$

$$P_{\text{ave}} = \frac{V_{\text{rms}}^2}{R} \quad (\text{resistive})$$

## \* Complex Number Review

- A.C. Signal  $x(t) = A \cos(\omega t + \varphi)$   
 $\omega$  does not change in circuits with R, C, L.
- A and  $\varphi$  characterize an A.C. Signal
- Complex number has two components, and can be used to represent A.C. Signals.

Rectangular form:  $a + jb$        $j^2 = -1$   
(Cartesian)      real part      imaginary part

$$a + jb = \sqrt{a^2 + b^2} \left( \frac{a}{\sqrt{a^2 + b^2}} + j \frac{b}{\sqrt{a^2 + b^2}} \right)$$

$$A = \sqrt{a^2 + b^2}$$

modulus


$$\frac{a}{\sqrt{a^2 + b^2}} = \cos \theta$$

$$\frac{b}{\sqrt{a^2 + b^2}} = \sin \theta$$

$$\theta = \tan^{-1} \left( \frac{b}{a} \right)$$

$$a + jb = A (\cos \theta + j \sin \theta) = Ae^{j\theta} = A \angle \theta \text{ (polar form)}$$
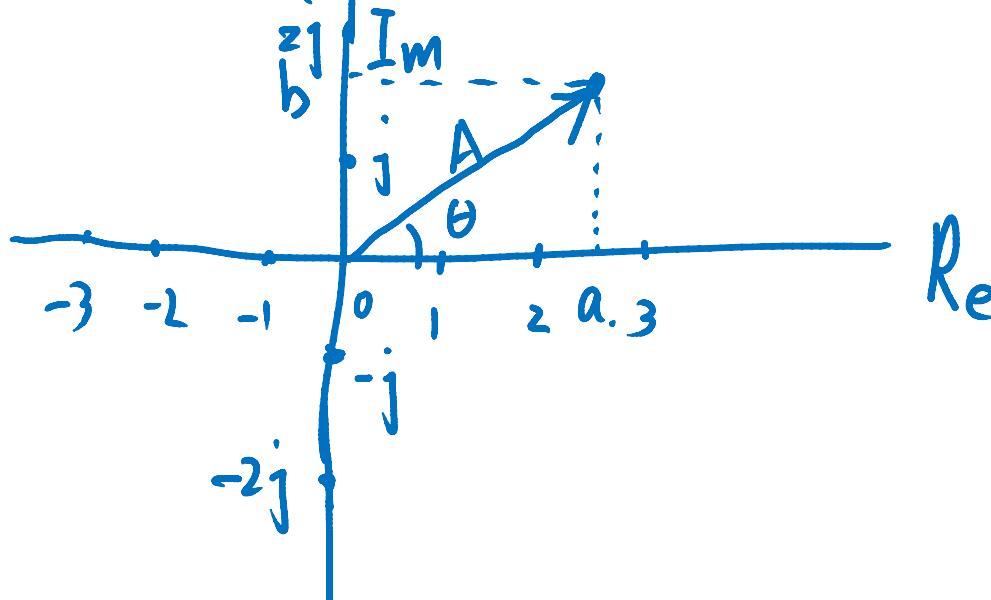
$$a+jb = A e^{j\theta} = A \angle \theta = A \cos \theta + j A \sin \theta$$




$$A = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

$$a = A \cos \theta$$

$$b = A \sin \theta$$

unit modulus ( $A=1$ )

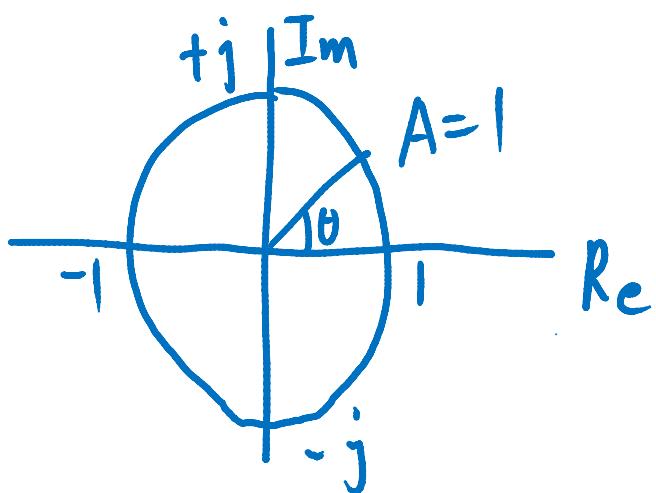

$$1 \angle \theta = 1 e^{j\theta} \\ = \cos \theta + j \sin \theta$$

$$a = \cos \theta$$

$$b = \sin \theta$$

Operations of complex numbers  
add or subtract: use rectangular form

$$C_1 = a_1 + j b_1 \quad C_2 = a_2 + j b_2$$

$$C_1 + C_2 = (a_1 + a_2) + j(b_1 + b_2)$$

Multiply or divide: more convenient to use polar form.

$$A_1 = \sqrt{a_1^2 + b_1^2}$$

$$\theta_1 = \tan^{-1} \left( \frac{b_1}{a_1} \right)$$

$$A_2 = \sqrt{a_2^2 + b_2^2}$$

$$\theta_2 = \tan^{-1} \left( \frac{b_2}{a_2} \right)$$

$$C_1 = A_1 e^{j\theta_1} = A_1 \angle \theta_1$$

$$C_2 = A_2 e^{j\theta_2} = A_2 \angle \theta_2$$

$$C_1 \times C_2 = A_1 A_2 e^{j(\theta_1 + \theta_2)} = A_1 A_2 \angle (\theta_1 + \theta_2)$$

$$\frac{C_1}{C_2} = \frac{A_1}{A_2} e^{j(\theta_1 - \theta_2)} = \frac{A_1}{A_2} \angle (\theta_1 - \theta_2)$$

Multiply or Divide in rectangular form

$$C_1 = a_1 + j b_1 \quad C_2 = a_2 + j b_2$$

$$C_1 \times C_2 = (a_1 + j b_1)(a_2 + j b_2)$$


$$= a_1 a_2 + a_1 (j b_2) + (j b_1) a_2 + (j b_1)(j b_2)$$

$$= a_1 a_2 + j a_1 b_2 + j a_2 b_1 + (-b_1 b_2)$$

$$= (a_1 a_2 - b_1 b_2) + j(a_1 b_2 + a_2 b_1)$$

$$\frac{C_1}{C_2} = \frac{(a_1 + j b_1)}{(a_2 + j b_2)} = \frac{(a_1 + j b_1)(a_2 - j b_2)}{(a_2 + j b_2)(a_2 - j b_2)} = \frac{(a_1 a_2 + b_1 b_2) + (a_2 b_1 - a_1 b_2)}{a_2^2 + b_2^2} j$$

\* phasor

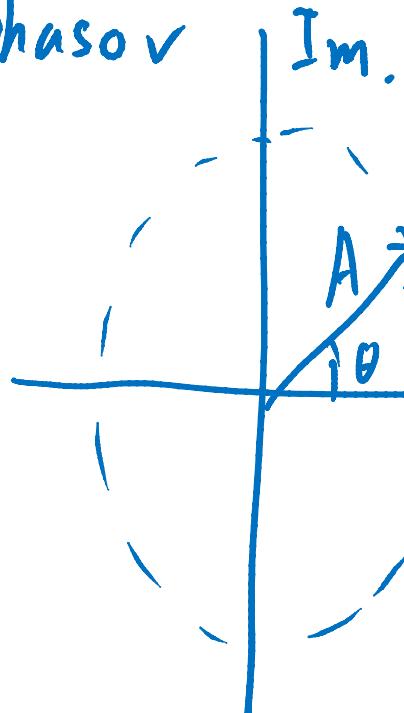


$$\theta = \omega t + \varphi \quad \omega = \frac{2\pi}{T}$$

$$A e^{j\theta} = A \angle \theta \\ = A e^{j(\omega t + \varphi)}$$

$$= \underbrace{A \cos(\omega t + \varphi)}_{\text{real part}} + j A \sin(\omega t + \varphi)$$

↳ real part is an a.c. signal

# Phasor Animation

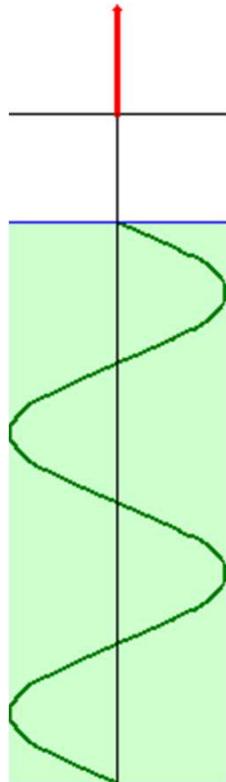

sinPlotting1.swf

$$A \cos(\omega t + \varphi) = \operatorname{Re} [A e^{j(\omega t + \varphi)}]$$

$$= \operatorname{Re} [A e^{j\omega t} \cdot e^{j\varphi}]$$


$e^{j\omega t}$  is same for all signals in the same circuit.

$$A \cos(\omega t + \varphi) \rightarrow A \underline{e^{j\omega t}} e^{j\varphi} \Rightarrow A e^{j\varphi} = A L \varphi$$

$A L \varphi \rightarrow$  phasor representation (amplitude and phase)  
of an a.c. signal

- Phasor is a complex number in polar form used to assist the calculation of a.c. circuits.
- Note the specific frequency  $\omega$  of the a.c. signal, since this is not explicit in a phasor.

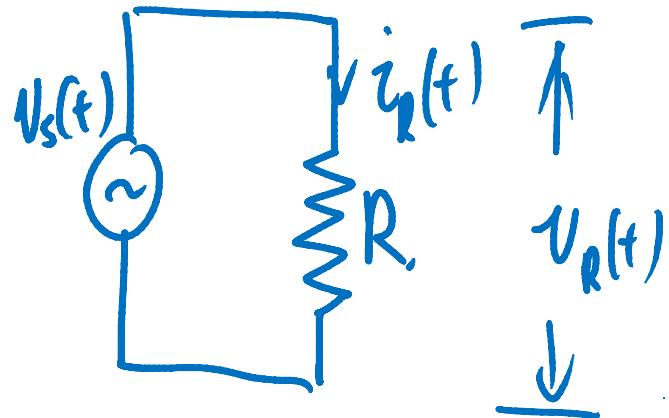\* A.C.  $i-v$  relationship for R, L, and C.



$$\text{Source } V_s(t) = A \sin \omega t$$


$$V_R(t) = V_s(t) = A \sin \omega t$$

$$V_R(t) = A \cos \left( \omega t - \frac{\pi}{2} \right)$$

$$i_R(t) = \frac{V_R(t)}{R} = \frac{A}{R} \cos \left( \omega t - \frac{\pi}{2} \right)$$

$\hookrightarrow 90^\circ$
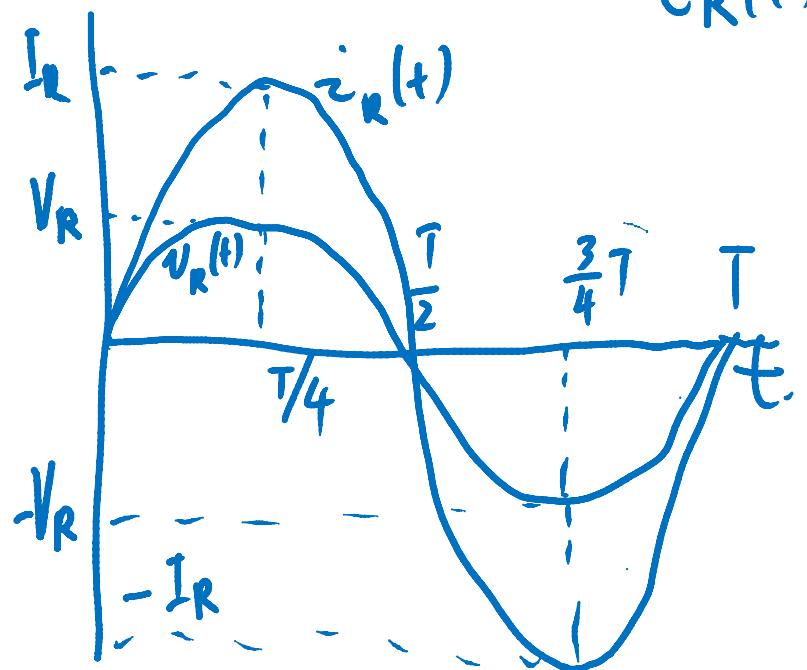
$$\varphi = -90^\circ = -\frac{\pi}{2} \text{ rad.}$$



$V_R(t)$  and  $i_R(t)$  are in phase.

Phasor representation

$$V_R(t) = A \cos(\omega t - 90^\circ)$$

$$V_R(j\omega) = A \angle -90^\circ = A \angle (-\frac{\pi}{2})$$

$$i_R(t) = \frac{A}{R} \cos(\omega t - 90^\circ)$$

$$I_R(j\omega) = \frac{A}{R} \angle -90^\circ = \frac{A}{R} \angle (-\frac{\pi}{2})$$

Impedance: phasor form of resistance.


$$Z_R = \frac{V_R(j\omega)}{I_R(j\omega)} = \frac{A \angle -90^\circ}{\frac{A}{R} \angle -90^\circ} = R \angle 0^\circ = R$$

Generalized Ohm's law

$$V(j\omega) = Z I(j\omega)$$

$$Z = \frac{V(j\omega)}{I(j\omega)}$$

Capacitors.

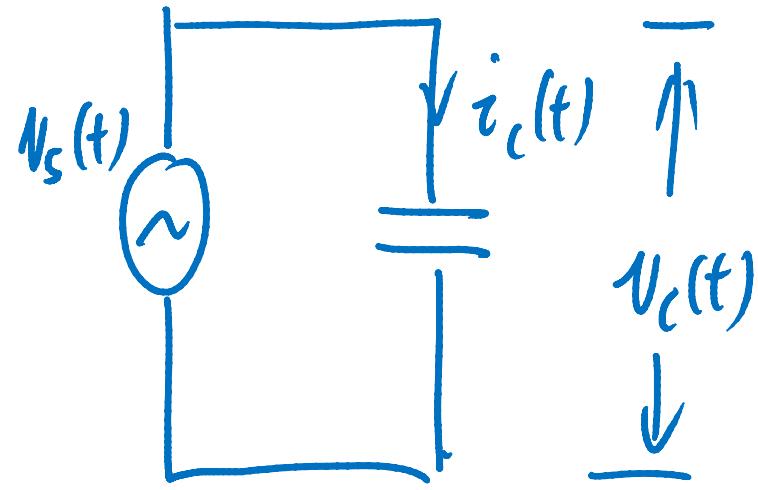


$$V_s(t) = A \sin \omega t$$

$$V_c(t) = V_s(t) = A \sin \omega t$$

$$i_c = C \frac{dV_c}{dt} = \omega C A \cos \omega t$$

$$V_c(t) = A \cos(\omega t - 90^\circ)$$

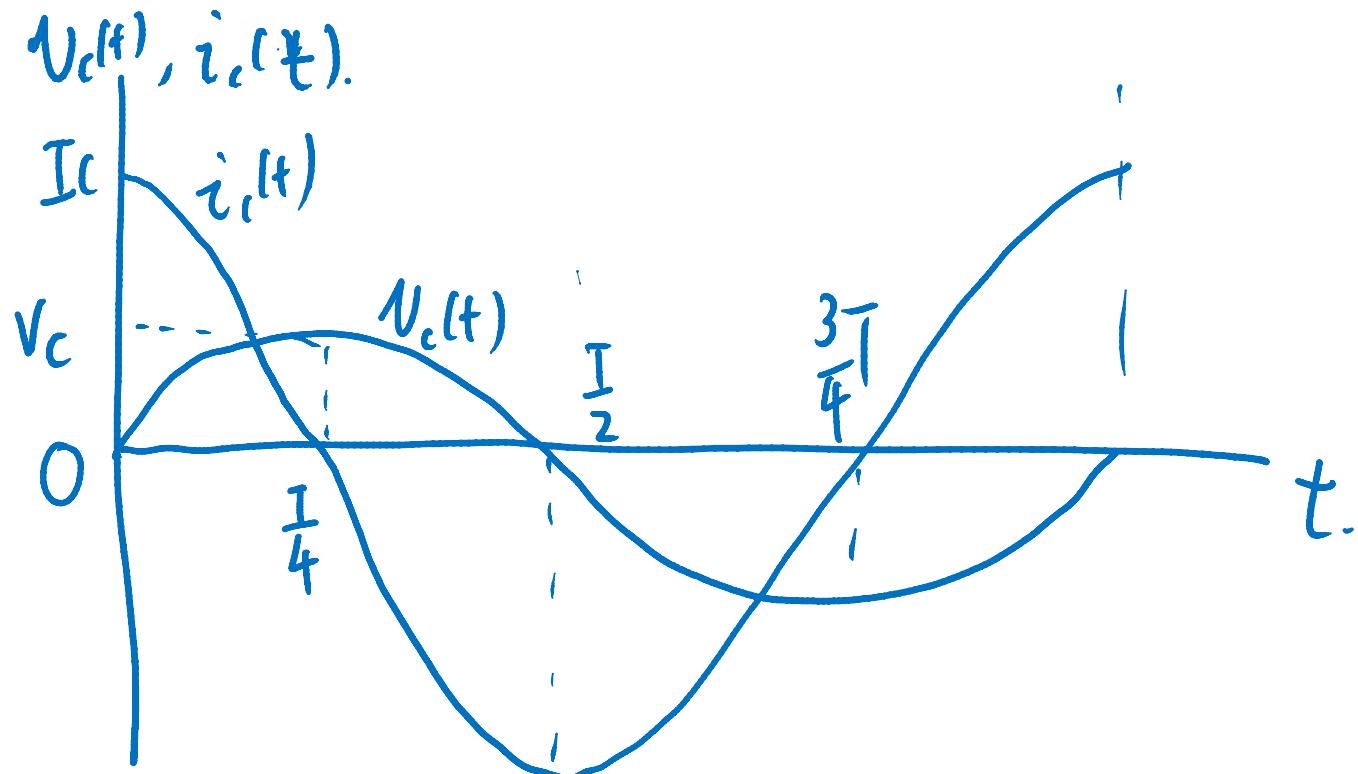

current leads voltage by  $\frac{\pi}{2}$  ( $90^\circ$ )

use "ICE" to remember

current  $\leftarrow$   $\downarrow$  voltage  
capacitor


phasors

$$V_c(j\omega) = A \angle -90^\circ$$

$$I_c(j\omega) = wCA \angle 0^\circ$$

Impedance
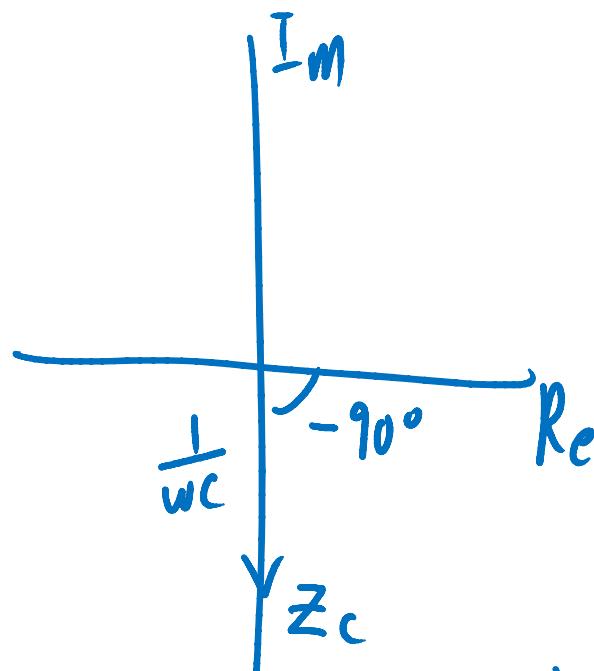
$$Z_c = \frac{V_c(j\omega)}{I_c(j\omega)} = \frac{A \angle -90^\circ}{wCA \angle 0^\circ} = \frac{1}{wC} \angle -90^\circ$$




$$j\frac{1}{wC} = \frac{-jj}{jwC} = -\frac{j}{wC}$$

$$Z_c = \frac{1}{jwC} = \frac{1}{wC} \angle -90^\circ$$

$|Z_c| = \frac{1}{wC}$        $w \uparrow |Z_c| \downarrow$   
when  $w=0$        $w=\infty$        $|Z_c| = \infty$

$$|Z_c| = 0$$

## Inductive Load.

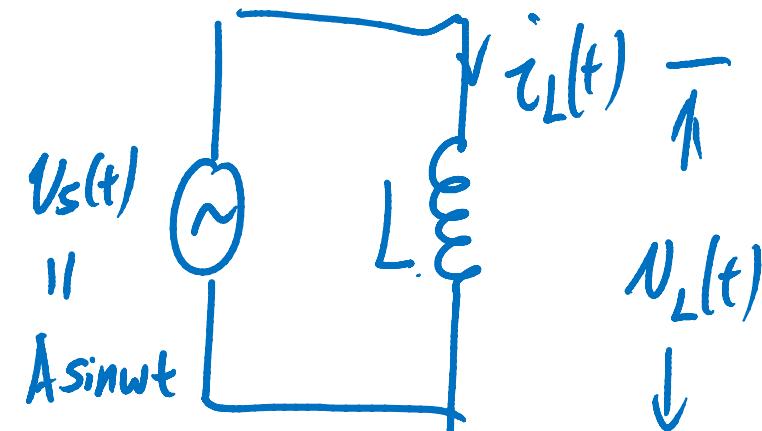

$$V_L(t) = V_s(t) = A \sin \omega t$$

$$\boxed{V_L(t) = A \cos(\omega t - 90^\circ)}$$


$$V_L = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{N_L}{L} = \frac{A}{L} \sin \omega t$$

$$i_L = \int \frac{A}{L} \sin \omega t \, dt$$

$$= \frac{A}{L} \frac{(-\cos \omega t)}{\omega} = \frac{A}{L \omega} \cos(\omega t - 180^\circ)$$
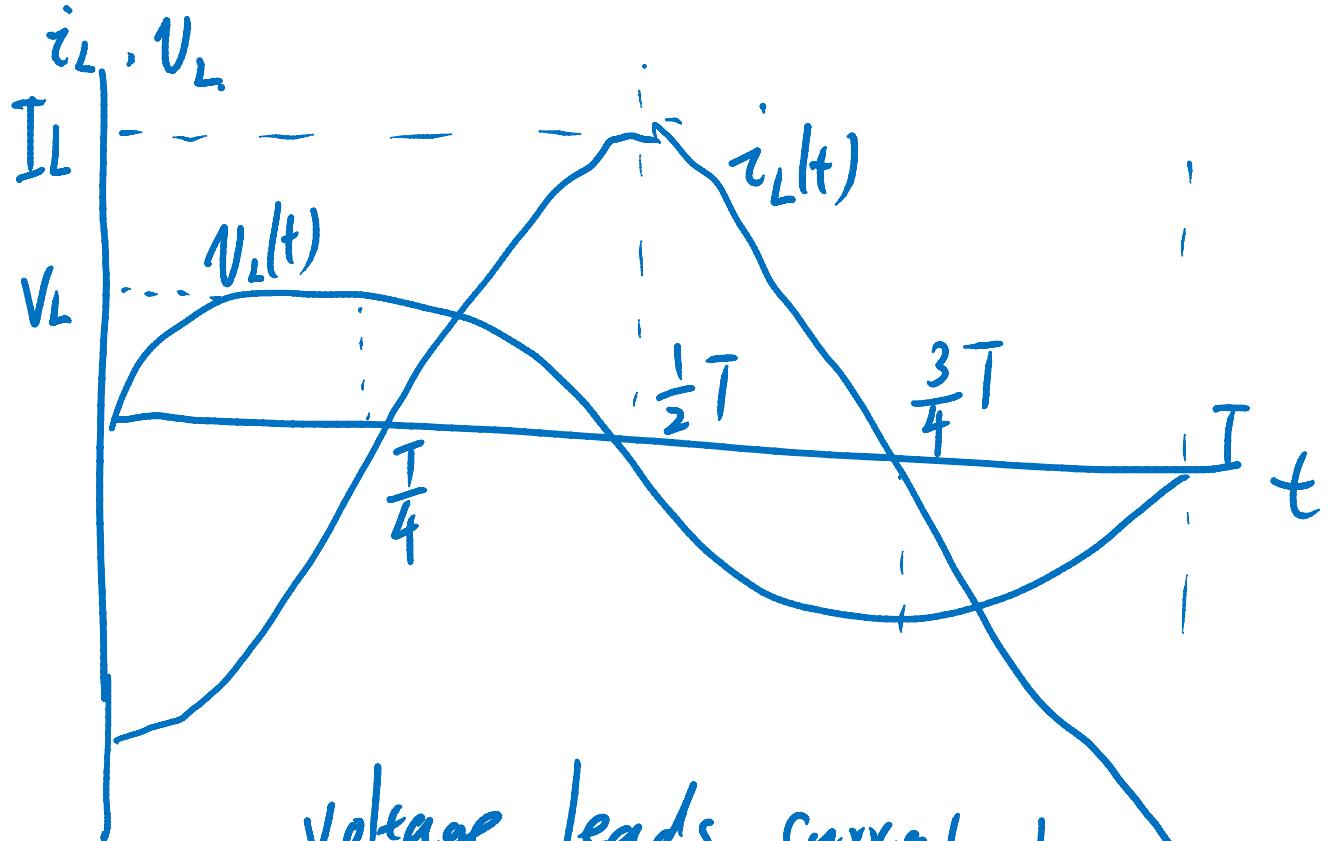
$$\boxed{i_L(t) = \frac{A}{L \omega} \cos(\omega t - 180^\circ)}$$



voltage leads current by  $\frac{\pi}{2}$  ( $90^\circ$ )

remember it as "ELI"

voltage  $\leftarrow$   $\downarrow$  current  
inductor


phasors

$$V_L(j\omega) = A L - 90^\circ$$

$$I_L(j\omega) = \frac{A}{\omega L} L - 180^\circ$$

Impedance :
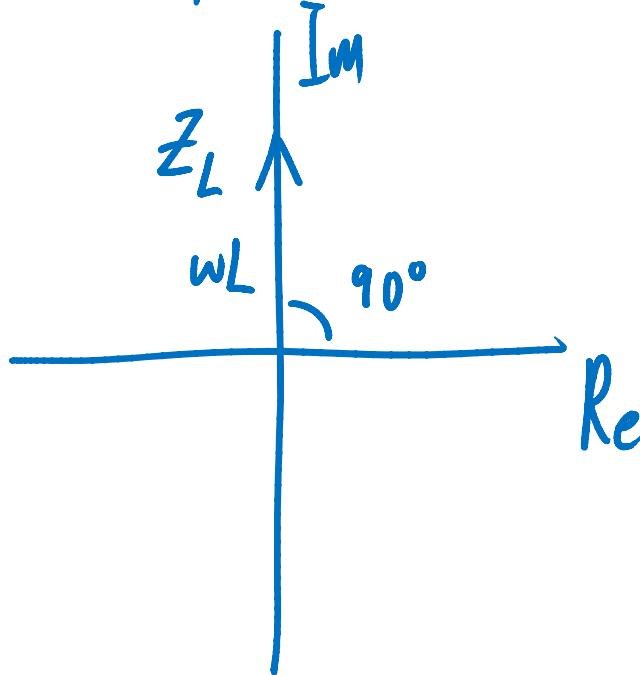
$$Z_L = \frac{V_L(j\omega)}{I_L(j\omega)} = \frac{AL - 90^\circ}{\frac{A}{\omega L} L - 180^\circ} = \omega L / 90^\circ$$



$$Z_L = j\omega L$$

$$|Z_L| = \omega L \quad \omega \uparrow \quad |Z_L| \uparrow$$

when  $\omega = 0$

$\omega = \infty$

$$|Z_L| = 0$$

$$|Z_L| \rightarrow \infty$$

## \* Impedance


$$Z_R = R \quad Z_C = \frac{1}{j\omega C} = -\frac{1}{\omega C} \quad Z_L = j\omega L$$

$$V(j\omega) = I(j\omega) Z \quad \text{generalized Ohm's law}$$

- polar angle of  $Z$  reflects phase difference between  $V(j\omega)$  and  $I(j\omega)$
- $Z_C, Z_L$  are related to  $\omega$
- Everything we learnt from dc circuits can be used for phasors

- \* a.c. phasor current analysis procedure:
  - Identify the sinusoidal and note the  $\omega$
  - Convert sources to phasor forms
  - represent each circuit element by its impedance.
  - Solve the phasor circuit using previously learnt methods (Combination rules, mesh, kirchhoff laws, Thevenin & Norton)

## Example

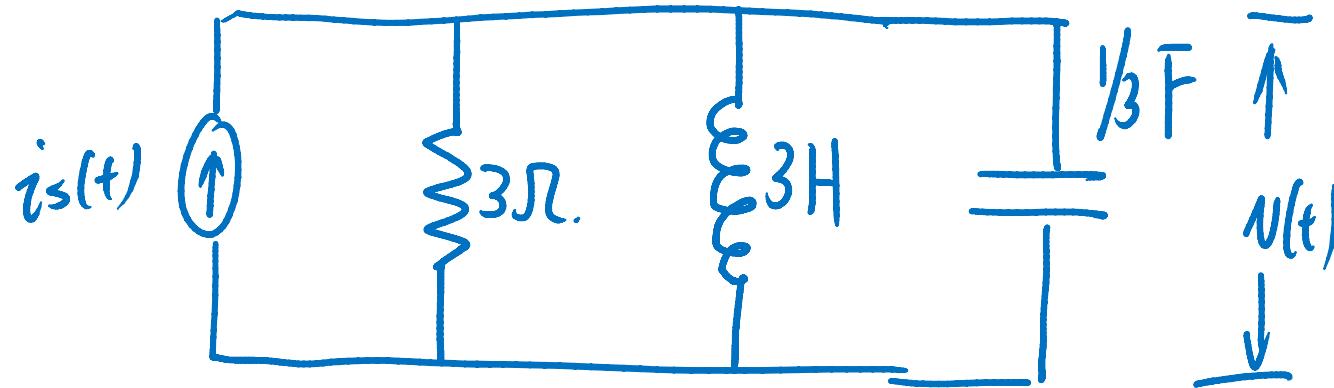

a.c. Source current  $i_s(t) = 10 \cos 2t$  (A)

$$I_s(j\omega) = 10 \angle 0^\circ = 10 e^{j0^\circ} \quad \omega = 2 \text{ rad/s}$$

$$Z_R = R = 3\Omega \quad Z_L = j\omega L = j \cdot 2 \cdot 3 = 6j \Omega$$

$$Z_C = \frac{1}{j\omega C} = -\frac{1}{\omega C} = -\frac{j}{2 \cdot \frac{1}{3}} = -1.5j \Omega$$

$$Z_{eq} = ? \quad \frac{1}{Z_{eq}} = \frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L}$$

$$Z_{eq} = \frac{1}{\left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L}\right)}$$

$$= \frac{1}{\left(\frac{1}{3} + \frac{1}{(-1.5j)}j + \frac{1}{6j}j\right)} = \frac{1}{\frac{1}{3} + \frac{j}{1.5} - \frac{1}{6}j}$$

$$= \frac{1}{0.333 + 0.6667j - 0.1667j} = \frac{1}{0.333 + 0.5j}$$

$$= \frac{1 \angle 0^\circ}{0.6007 \angle 56.3^\circ}$$

$$A = \sqrt{(0.333)^2 + (0.5)^2} = 0.6007$$

$$\Theta = \tan^{-1}\left(\frac{0.5}{0.333}\right) = 56.3^\circ$$

$$Z_{eq} = 1.667 \angle (-56.3^\circ)$$


$$V(j\omega) = I(j\omega) Z_{eq}$$

$$= (10 \angle 0^\circ) (1.667 \angle -56.3^\circ)$$

$$V(j\omega) = 16.67 \angle -56.3^\circ$$

$$v(t) = 16.67 \cos(2t - 56.3^\circ) \quad (V)$$

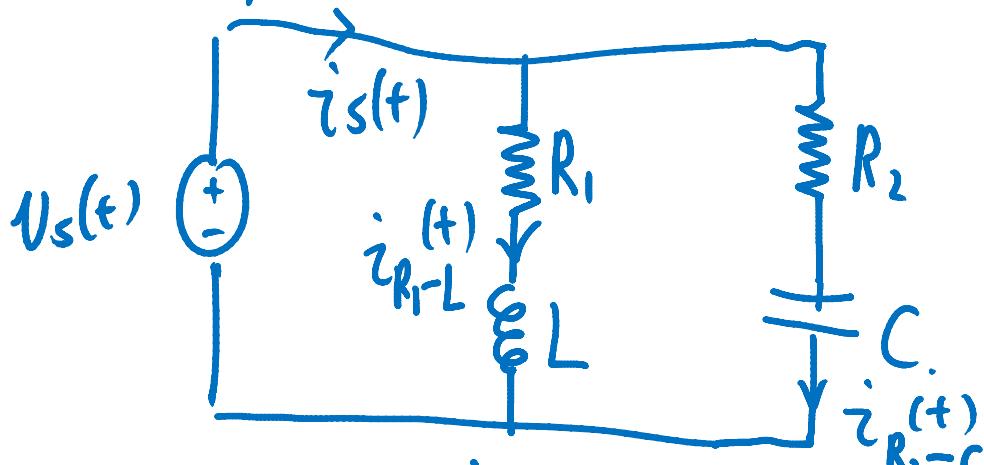Example Determine the current in each branch.



$$i_s(t) = ? \quad i_{R_1-L}(t) = ? \quad i_{R_2-C}(t) = ?$$

$$V_s(j\omega) = 636 \angle 15^\circ$$

$$Z_{R_1} = 3300 \Omega \quad Z_{R_2} = 22000 \Omega$$

$$Z_L = j\omega L = j(3000 \times 1.9) = 5700 j \Omega$$

$$Z_C = -\frac{1}{j\omega C} = -\frac{1}{(3000) \times (6.8 \times 10^{-9})} = -4.9 \times 10^4 j \Omega$$

$$V_s(t) = 636 \cos\left(3000t + \frac{\pi}{12}\right) V$$

$$R_1 = 3.3 k\Omega \quad R_2 = 22 k\Omega \quad \frac{\pi}{12} = 15^\circ$$

$$L = 1.9 H \quad C = 6.8 nF$$

$$= 6.8 \times 10^{-9} F$$

$$\begin{aligned}
 Z_{eq} &= (Z_C + Z_{R_2}) // (Z_L + Z_{R_1}) \\
 &= \frac{(Z_C + Z_{R_2})(Z_L + Z_{R_1})}{Z_C + Z_{R_2} + Z_L + Z_{R_1}} \\
 &= \frac{(22000 - 4.9 \times 10^4 j)(5700j + 3300)}{22000 + 3000 - 4.9 \times 10^4 j + 5700j} \\
 &= \frac{(53712 \angle -65.8^\circ)(6586 \angle 59.9^\circ)}{(50149 \angle -59.7^\circ)}
 \end{aligned}$$

$$Z_{eq} = 7054 \angle 53.8^\circ (\Omega)$$

$$I_S(j\omega) = \frac{V_S(j\omega)}{Z_{eq}} = \frac{636 \angle 15^\circ}{7054 \angle 53.8^\circ} = 0.090 \angle -38.8^\circ$$

$$i_s(t) = 0.090 \cos(3000t - 38.8^\circ) \text{ (A)}$$

$$i_{R_1-L}(t) = ?$$

$$I_{R_1-L}(j\omega) = \frac{V_s(j\omega)}{Z_L + Z_{R_1}} = \frac{636 \angle 15^\circ}{6586 \angle 59.9^\circ} = 0.096 \angle -44.9^\circ$$

$$i_{R_1-L}(t) = 0.096 \cos(3000t - 44.9^\circ)$$


$$i_{R_2-C} = ?$$

$$I_{R_2-C}(j\omega) = \frac{V_s(j\omega)}{Z_C + Z_{R_2}} = \frac{636 \angle 15^\circ}{53712 \angle -65.8^\circ} = 0.012 \angle 80.8^\circ$$

$$i_{R_2-C}(t) = 0.012 \cos(3000t + 80.8^\circ)$$

Also try current divider rule as exercise.

Same circuit. use mesh analysis.

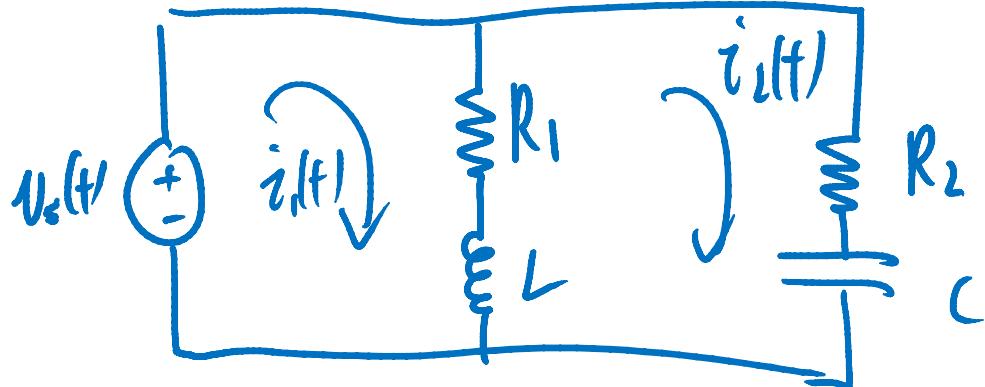

$$V_s(j\omega) = 636 \angle 15^\circ$$

$$I_1(j\omega) = ? \quad I_2(j\omega) = ?$$

$$(Z_{R_1} + Z_L) I_1(j\omega) - (Z_{R_1} + Z_L) I_2(j\omega) = V_s(j\omega) \quad (1)$$

$$(Z_{R_1} + Z_L + Z_{R_2} + Z_C) I_2(j\omega) - (Z_{R_1} + Z_L) I_1(j\omega) = 0 \quad (2)$$

$$(1) + (2) \quad (Z_{R_2} + Z_C) I_2(j\omega) = V_s(j\omega)$$

$$I_2(j\omega) = \frac{V_s(j\omega)}{Z_{R_2} + Z_C} = \frac{636 \angle 15^\circ}{537.12 \angle -65.8^\circ} = 0.012 \angle 80.8^\circ$$

$$i_2(t) = 0.012 \cos(300\pi t + 80.8^\circ) = i_{R_2+C}(t)$$

$$\begin{aligned}
 I_1(j\omega) &= \frac{V_s(j\omega)(Z_{R_1} + Z_L + Z_{R_2} + Z_C)}{(Z_{R_2} + Z_C)(Z_{R_1} + Z_L)} \\
 &= \frac{(636 \angle 15^\circ)(50149 \angle -59.7^\circ)}{(53712 \angle -65.8^\circ)(6586 \angle 59.9^\circ)} \\
 &= 0.090 \angle -38.8^\circ
 \end{aligned}$$


$$i_1(t) = 0.090 \cos(3000t - 38.8^\circ) = i_s(t)$$

$$\begin{aligned}
 I_{R_1-L}(j\omega) &= I_1(j\omega) - I_2(j\omega) = 0.090 \angle -38.8^\circ - 0.012 \angle 80.8^\circ \\
 &= (0.070 - 0.056 j) - (0.0019 + 0.00118 j) \\
 &= 0.068 - 0.068 j = 0.096 \angle -45^\circ
 \end{aligned}$$

$$i_{R_1-L} = 0.096 \cos(3000t - 45^\circ)$$
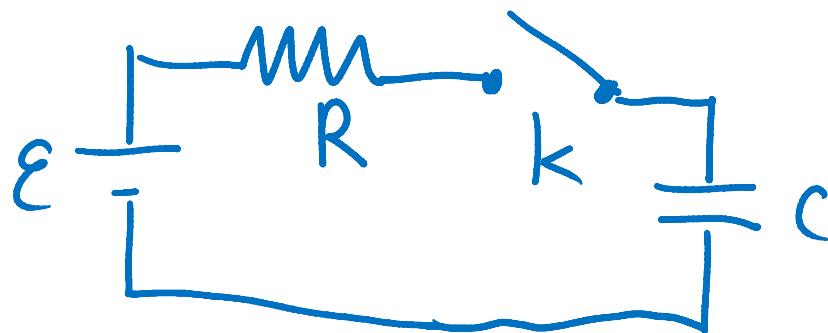
## \* Transient Circuits

— transient: transition region between two steady states.



initially no charge on  $C$

$$V_C = \frac{Q_C}{C} = 0$$

$t < 0$  Switch is open

at  $t=0$  switch is closed,

What happens at  $t=0^+$ ?

What happens at  $t=\infty$ ? (steady state)

What happens in between  $t=0^+$  and  $t=\infty$ ?

$$i_c = \frac{dq_c}{dt} = C \frac{dv_c}{dt}$$


if  $v_c$  suddenly changes

$$i_c = C \frac{dv_c}{dt} = \infty$$

(unphysical)

No sudden jump of voltage on capacitor

At  $t = 0^+$  what happens

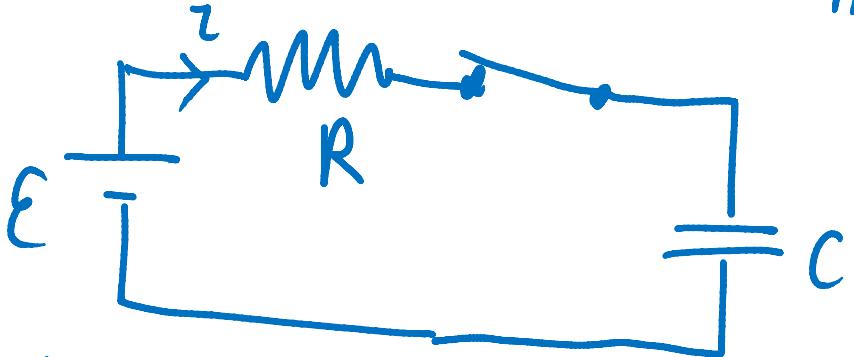

kVL

$$E - iR - V_C = 0$$

At  $t < 0$   $V_C = 0$


At  $t = 0^+$   $V_C = 0$  (no sudden jump)

$$E - iR = 0$$

$$i(t=0^+) = \frac{E}{R}$$

$$i \Big|_{t=0^+} = \frac{\epsilon}{R} \quad \text{at } t=0^+$$

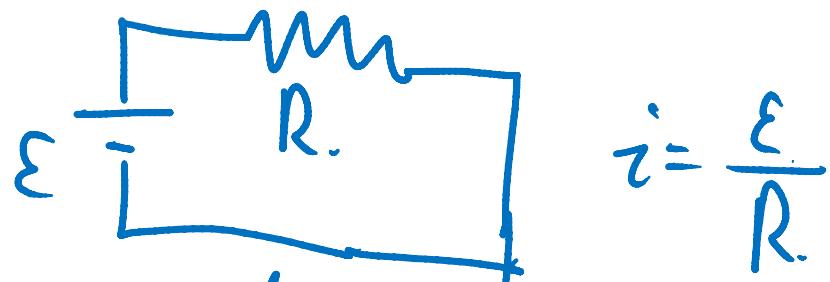At  $t=0^+$  the capacitor is equivalent to a piece of wire.




From impedance perspective:

$$Z_C = \frac{1}{j\omega C} \quad |Z_C| = \frac{1}{\omega C}$$

sudden change  $\leftrightarrow \omega = \infty$

$|Z_C| = 0$   
only true for  $t < 0^+$

At  $t=\infty$  what happens?

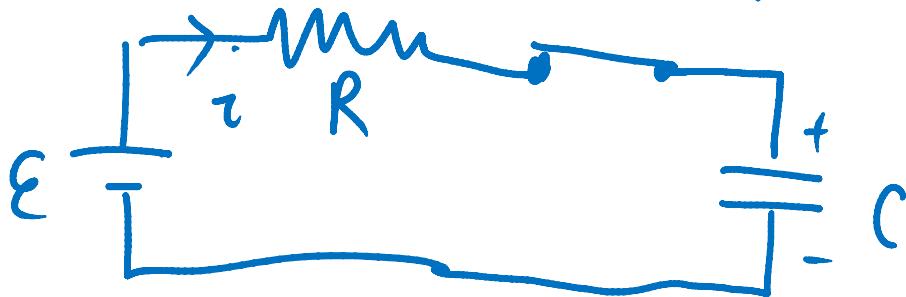

At  $t=\infty$   $C$  is fully charged.

$$q_C = \text{const}$$


$$i = \frac{dq_C}{dt} = 0 \quad (t=\infty)$$

KVL       $E - iR - V_C = 0$

$\stackrel{i=0}{\parallel}$        $V_C = E \quad \text{at } t=\infty$

$$Q_C = C \cdot V_C = CE$$

between  $t = 0^+$  and  $t = \infty$

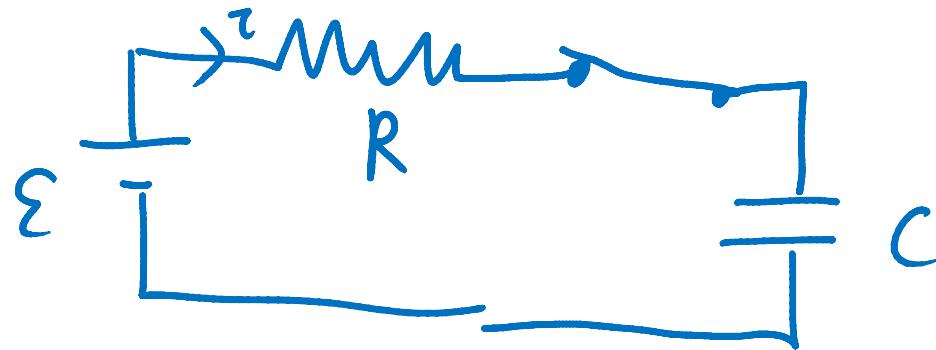

$$\text{KVL} \quad \epsilon - iR - V_C = 0$$

$$i = \frac{\epsilon - V_C}{R} \quad (1)$$

$$i = C \frac{dV_C}{dt} \quad (2)$$

$$\frac{\epsilon - V_C}{R} = C \frac{dV_C}{dt} \quad V_C(t) = ?$$

$$\frac{dV_C}{\epsilon - V_C} = \frac{dt}{RC} \quad \frac{d(\epsilon - V_C)}{\epsilon - V_C} = - \frac{dt}{RC}$$

$$\ln(\varepsilon - V_c) = -\frac{t}{RC} + A$$

$$\varepsilon - V_c = e^A \cdot e^{-t/RC}$$

Let  $e^A = B$

$$\varepsilon - V_c = B \cdot e^{-t/RC}$$

$$\text{At } t=0^+ \quad V_c = 0, \quad B = \varepsilon$$


$$\varepsilon - V_c = \varepsilon e^{-t/RC}$$

$$V_c = \varepsilon (1 - e^{-t/RC})$$

$$i_c = C \frac{dV_c}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$


$$V_c = \epsilon(1 - e^{-t/RC}) \quad t = \tau = RC$$
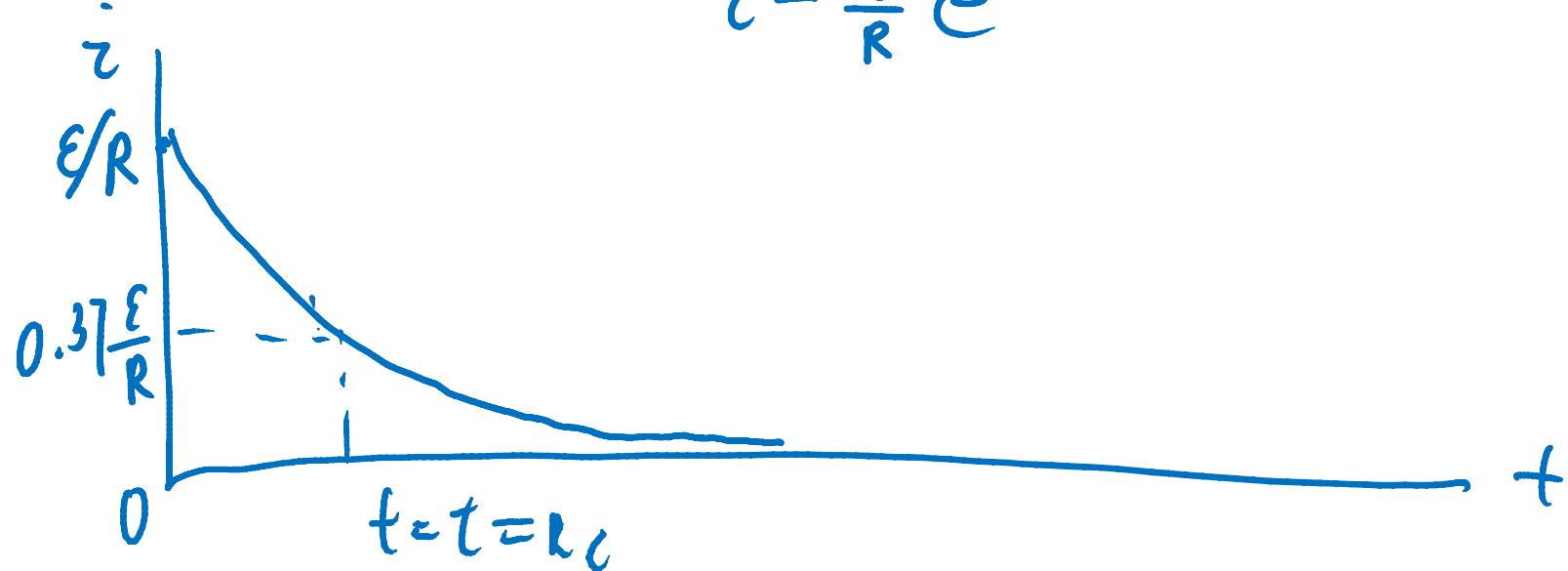
$$V_c = \epsilon(1 - e^{-1}) = 0.63 \epsilon$$



- Time constant  $\tau = RC$   
time to charge a capacitor to 63% of its full  
charge capacity
- The larger the  $\tau = RC$ , the longer it takes to  
charge the capacitor.  
( large R means smaller charging current  
larger C ~~means~~ more charge )

Discharging a capacitor.

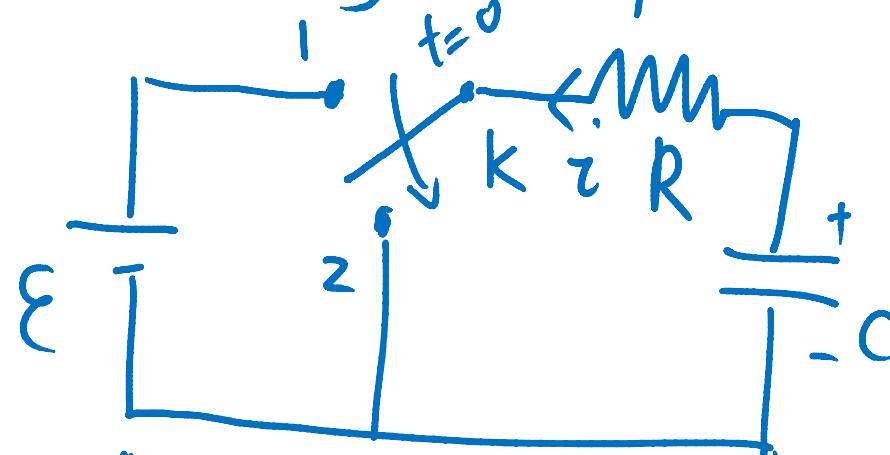

Switch to 1.

charging  $V_C = \epsilon$   
( $t < 0$ ,  $V_C = \epsilon$ )

At  $t=0$ , switch to 2 : discharging

at  $t=0^+$  (right after switching to 2)

$V_C = \epsilon$  (no sudden jump of  $V$  on  $C$ )


$$kVL \quad V_C - iR = 0$$

$$i|_{t=0^+} = \frac{V_C}{R} = \frac{\epsilon}{R}$$

$$\text{At } t=\infty \quad i|_{t=\infty} = 0 \quad V_C|_{t=\infty} = 0$$

completely  
discharged

Between  $t = 0^+$  and  $t = \infty$

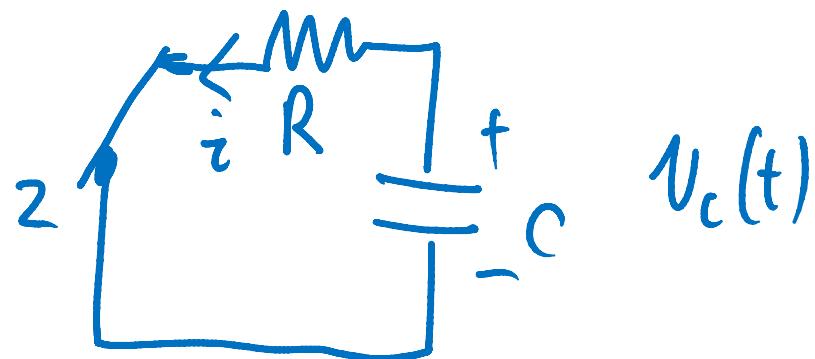

$$V_c - iR = 0$$

$$i = \frac{V_c}{R} \quad (1)$$

$$i = -\frac{dq_c}{dt} = -C \frac{dV_c}{dt} \quad (2)$$

$$-C \frac{dV_c}{dt} = \frac{V_c}{R}$$

$$\frac{dV_c}{V_c} = -\frac{dt}{RC}$$

$$\ln V_c = -\frac{t}{RC} + A$$

$$V_c = e^{-t/RC} \cdot e^A$$

$$\text{Let } e^A = B$$


$$V_c = Be^{-t/RC}$$

At  $t=0^+$   $V_C = \varepsilon$

$$B = \varepsilon$$

$$V_C(t) = \varepsilon \cdot e^{-t/RC}$$

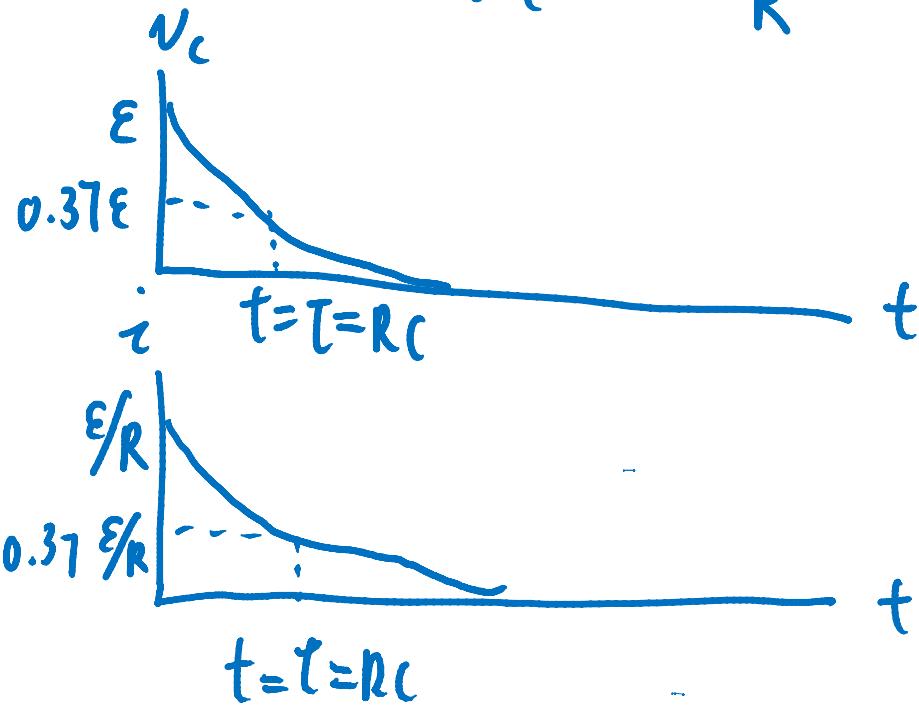
$$i = -C \frac{dV_C}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$



General form of transient variables in circuits

$$x(t) = x(\infty) + (x(0^+) - x(\infty))e^{-t/\tau}$$

Example

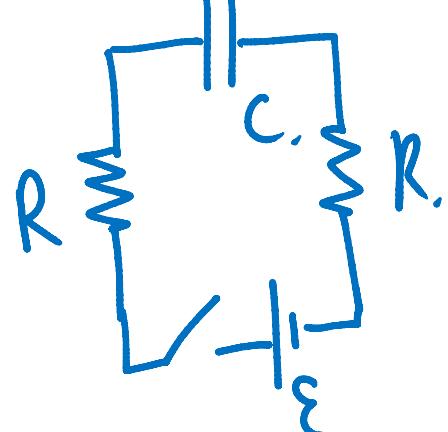

C initially uncharged.

$$i|_{t=0^+} = \frac{\epsilon}{2R}$$

$$i|_{t=\infty} = 0$$

$$v_c|_{t=0^+} = 0$$


$$v_c|_{t=\infty} = \epsilon$$

$$\tau = 2RC$$

$$i = \frac{\epsilon}{2R} e^{-t/2RC}$$

$$v_c = \epsilon \left(1 - e^{-t/2RC}\right)$$


Example

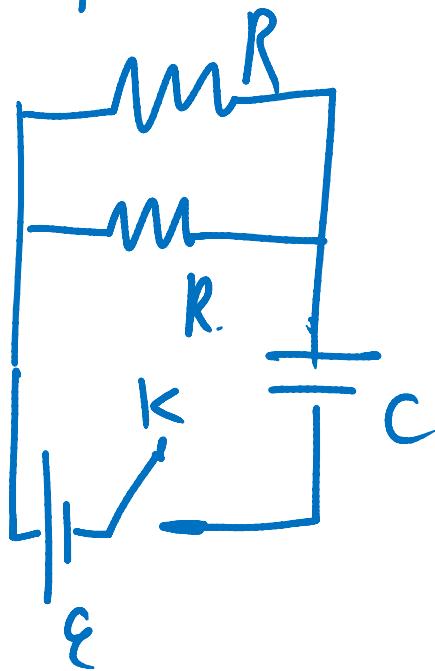

$$i|_{t=0^+} = \frac{\epsilon}{(R/Z)}$$

time constant

$$\tau = \frac{RC}{2}$$

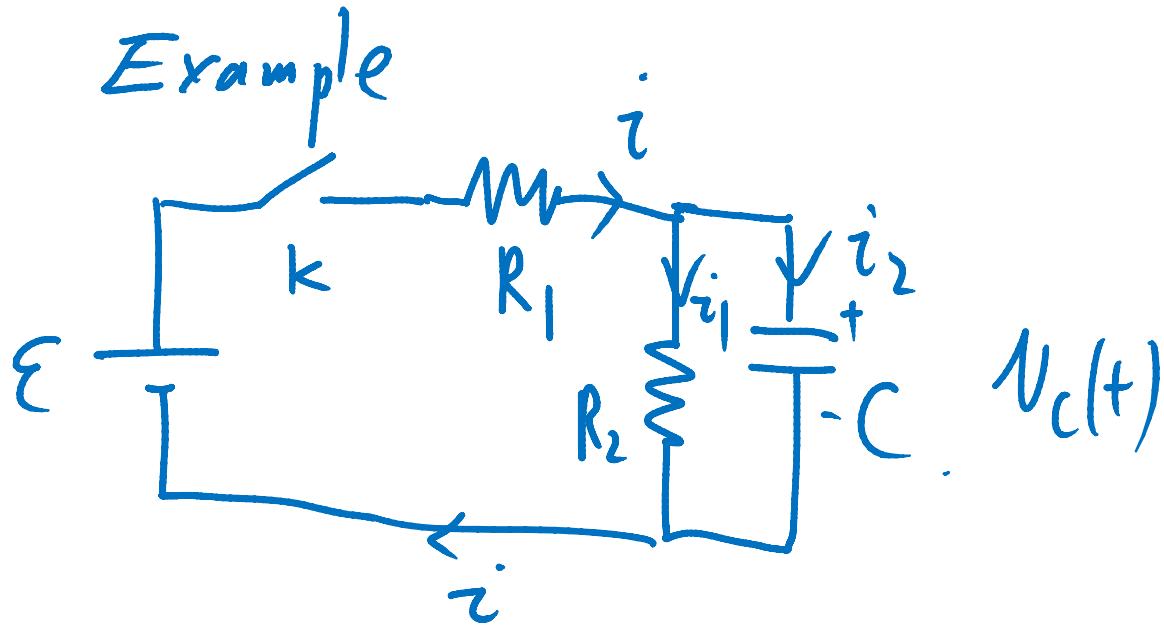

(1) into (3)

$$\left\{ \begin{array}{l} i = i_1 + i_2 \quad (1) \\ i_2 = C \frac{dV_c}{dt} \quad (2) \\ \epsilon - i_1 R_1 - i_2 R_2 = 0 \quad (3) \\ i_1 R_2 = V_c \quad (4) \end{array} \right.$$

$\epsilon - (i_1 + i_2)R_1 - i_1 R_2 = 0 \quad (5)$

(2) (4) into (5)

$$\mathcal{E} - \frac{V_c}{R_2} R_1 - C \frac{dV_c}{dt} R_1 - V_c = 0$$

$$-CR_1 \frac{dV_c}{dt} - \frac{R_1 + R_2}{R_2} V_c + \mathcal{E} = 0$$

$$CR_1 \frac{dV_c}{dt} = -\frac{R_1 + R_2}{R_2} V_c + \mathcal{E}$$

$$\frac{dV_c}{-\frac{R_1 + R_2}{R_2} V_c + \mathcal{E}} = \frac{dt}{CR_1}$$

$$\frac{d\left(-\frac{R_1 + R_2}{R_2} V_c + \mathcal{E}\right)}{-\frac{R_1 + R_2}{R_2} V_c + \mathcal{E}} = -\frac{dt}{C \left(\frac{R_1 R_2}{R_1 + R_2}\right)}$$

$$\ln \left[-\frac{R_1 + R_2}{R_2} V_c + \mathcal{E}\right] = -\frac{t}{C \left(\frac{R_1 R_2}{R_1 + R_2}\right)} + A$$

$$\text{Let } B = e^A - \frac{e}{C\left(\frac{R_1 R_2}{R_1 + R_2}\right)}$$

$$\epsilon - \frac{R_1 + R_2}{R_2} V_C = B e^{-\frac{t}{C\left(\frac{R_1 R_2}{R_1 + R_2}\right)}}$$

$$t=0^+ \quad V_C = 0$$


$$B = \epsilon$$

$$V_C(t) = \frac{R_2}{R_1 + R_2} \epsilon \left( 1 - e^{-\frac{t}{C\left(\frac{R_1 R_2}{R_1 + R_2}\right)}} \right)$$


$$t=0^+ \quad V_C = 0$$

$$t=\infty \quad V_C = \frac{R_2}{R_1 + R_2} \epsilon$$
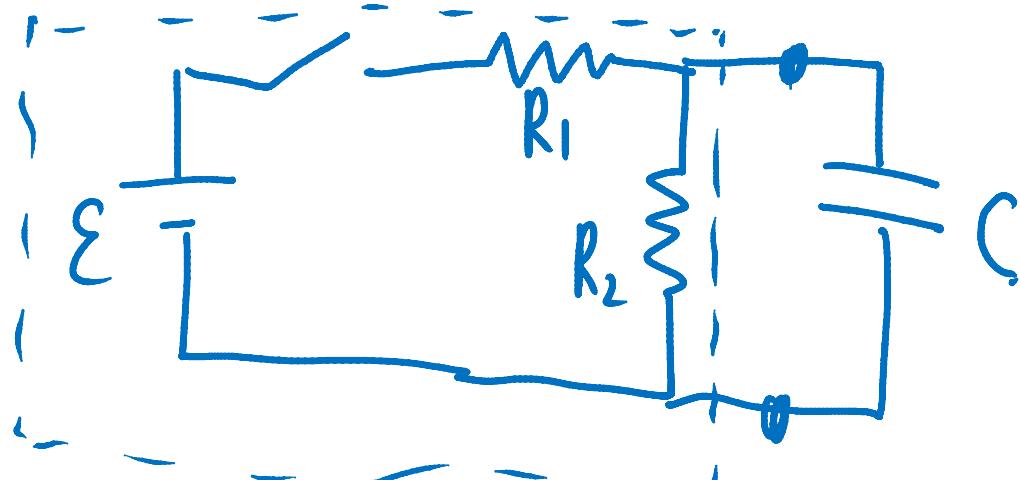
$$T = \left( \frac{R_1 R_2}{R_1 + R_2} \right) C$$




Thevenin equivalent.

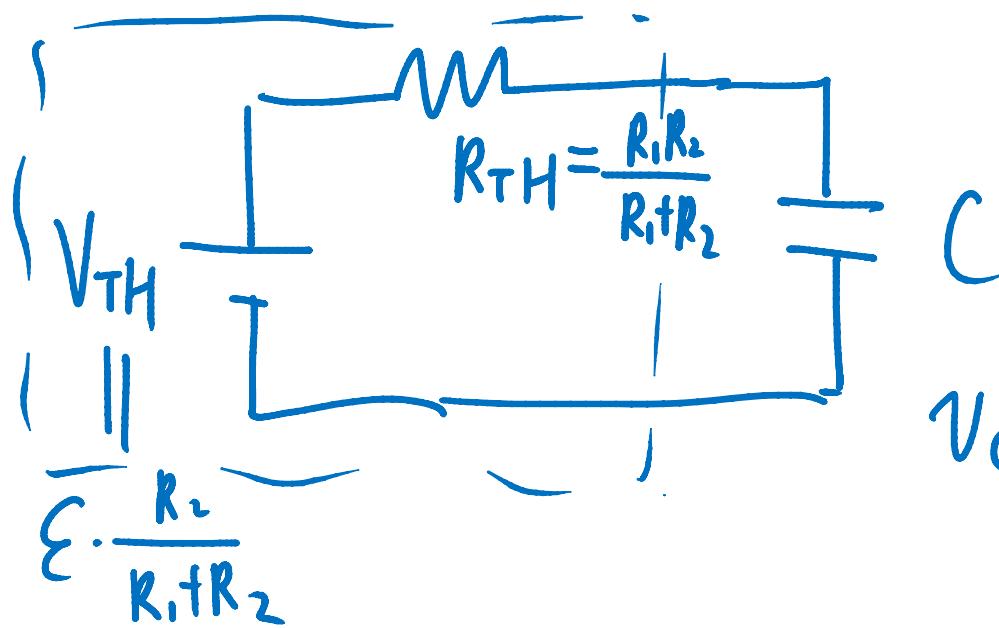

$$V_C = V_T \left( 1 - e^{-\frac{t}{R_T C}} \right)$$

$$V_C = E \frac{R_2}{R_1 + R_2} \left( 1 - e^{-\frac{t}{C \left( \frac{R_1 R_2}{R_1 + R_2} \right)}} \right)$$

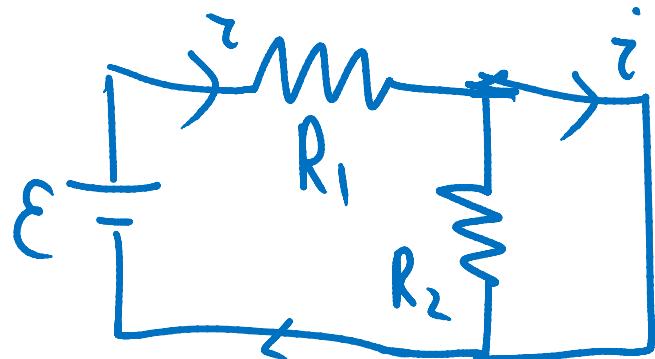
At  $t = 0^+$  and  $t = \infty$  What is the current through the battery  $\epsilon$



$t = 0^+$


$$\dot{i} \Big|_{t=0^+} = \frac{\epsilon}{R_1}$$

At  $t = \infty$

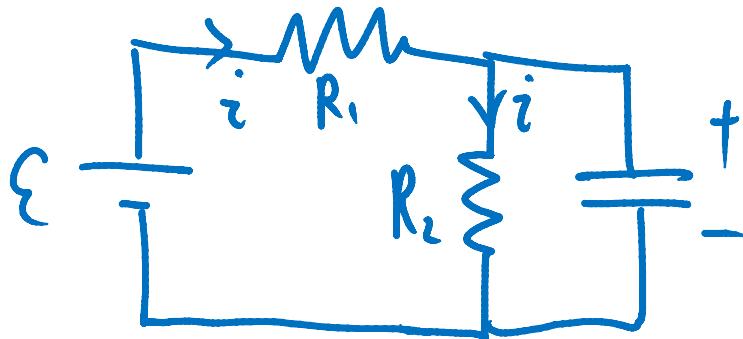

$$\dot{i} \Big|_{t=\infty} = \frac{\epsilon}{R_1 + R_2}$$

Example

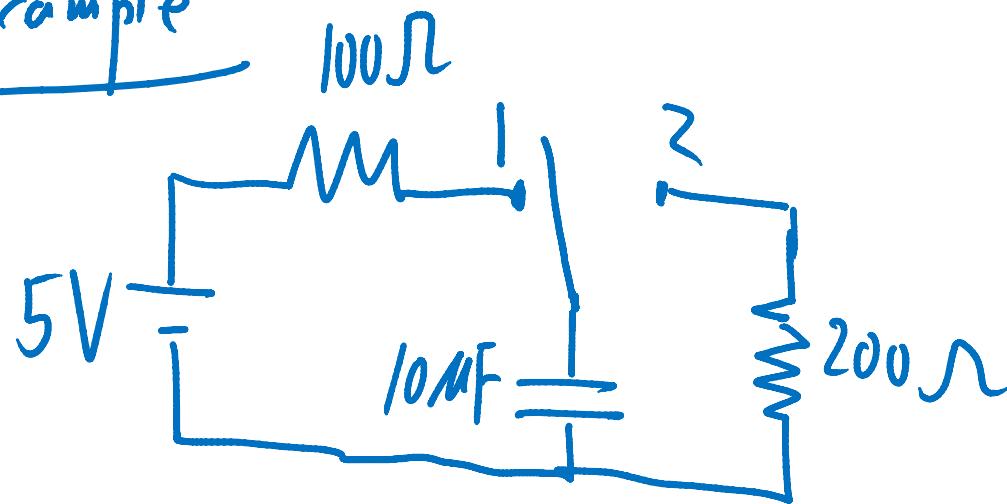


switch to 1 charging:  $T_1 = R_1 C$


$$= (100 \Omega) \times (10 \times 10^{-6} F)$$
$$= 1 \times 10^{-3} (s) = 1 \text{ ms}$$

switch to 2 discharge:  $T_2 = R_2 C$

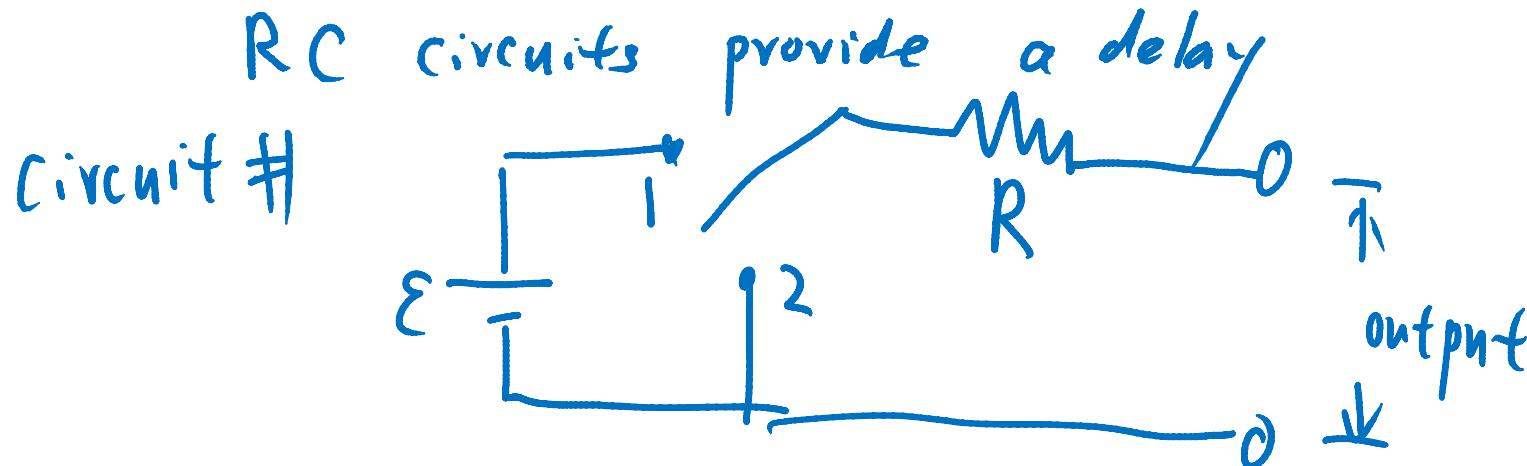
$$= 200 \times 10 \times 10^{-6}$$
$$= 2 \text{ ms}$$



toggles between 1 and 2 periodically

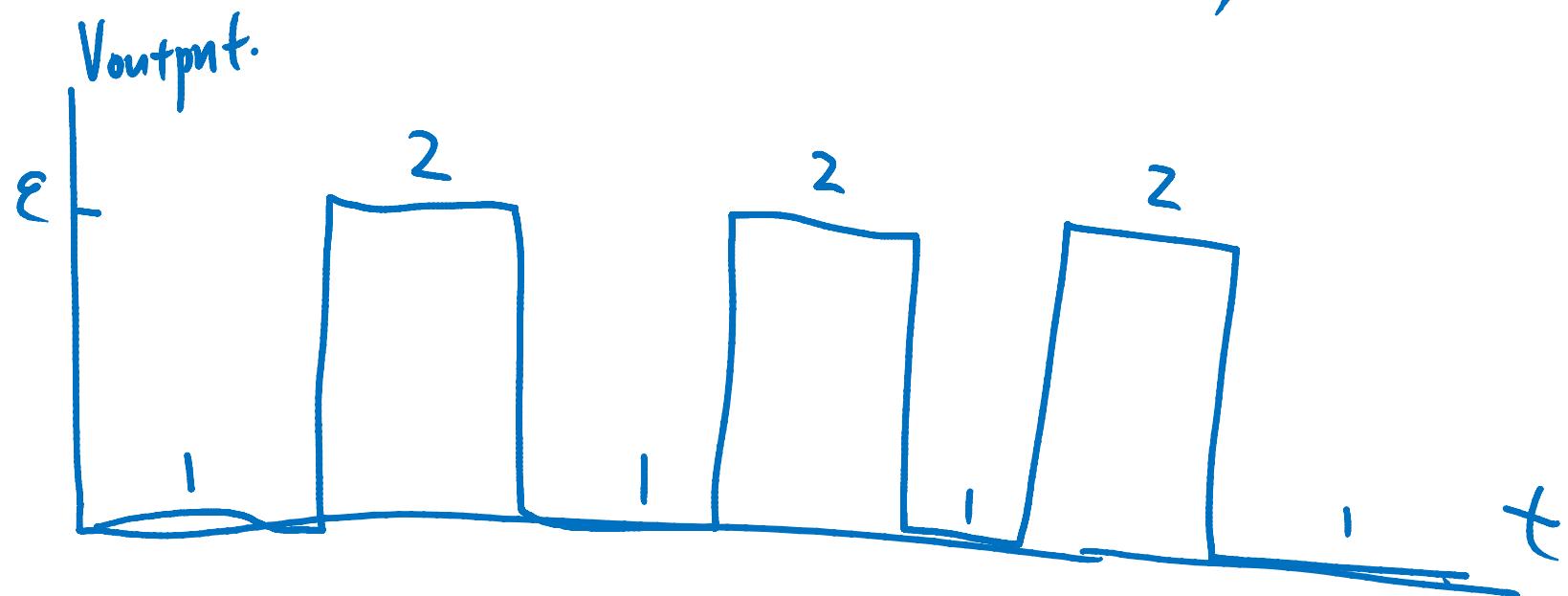


Circuit #2

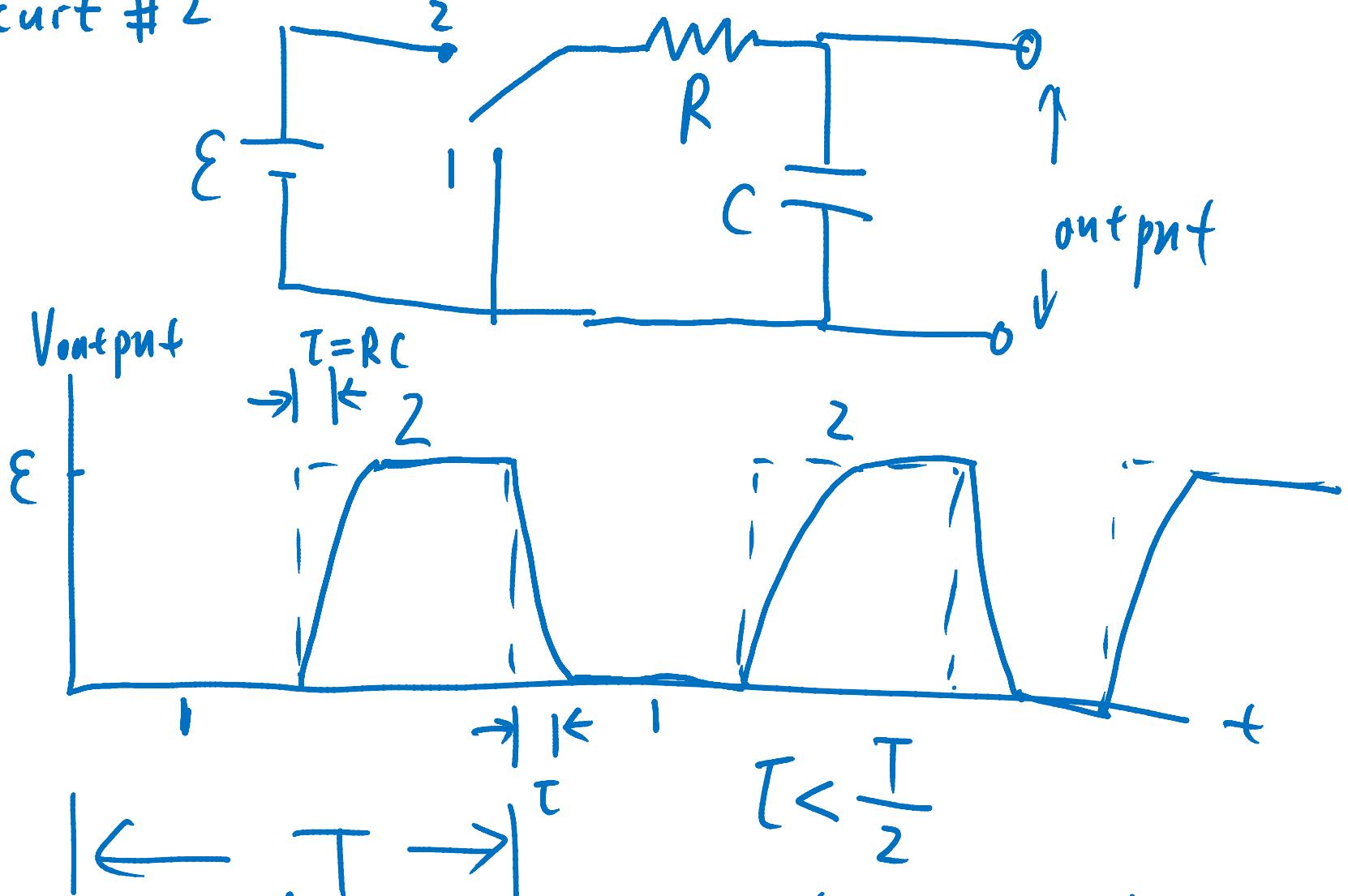


Response is delayed in RC circuit. Because there is no abrupt jump of voltage on capacitor.

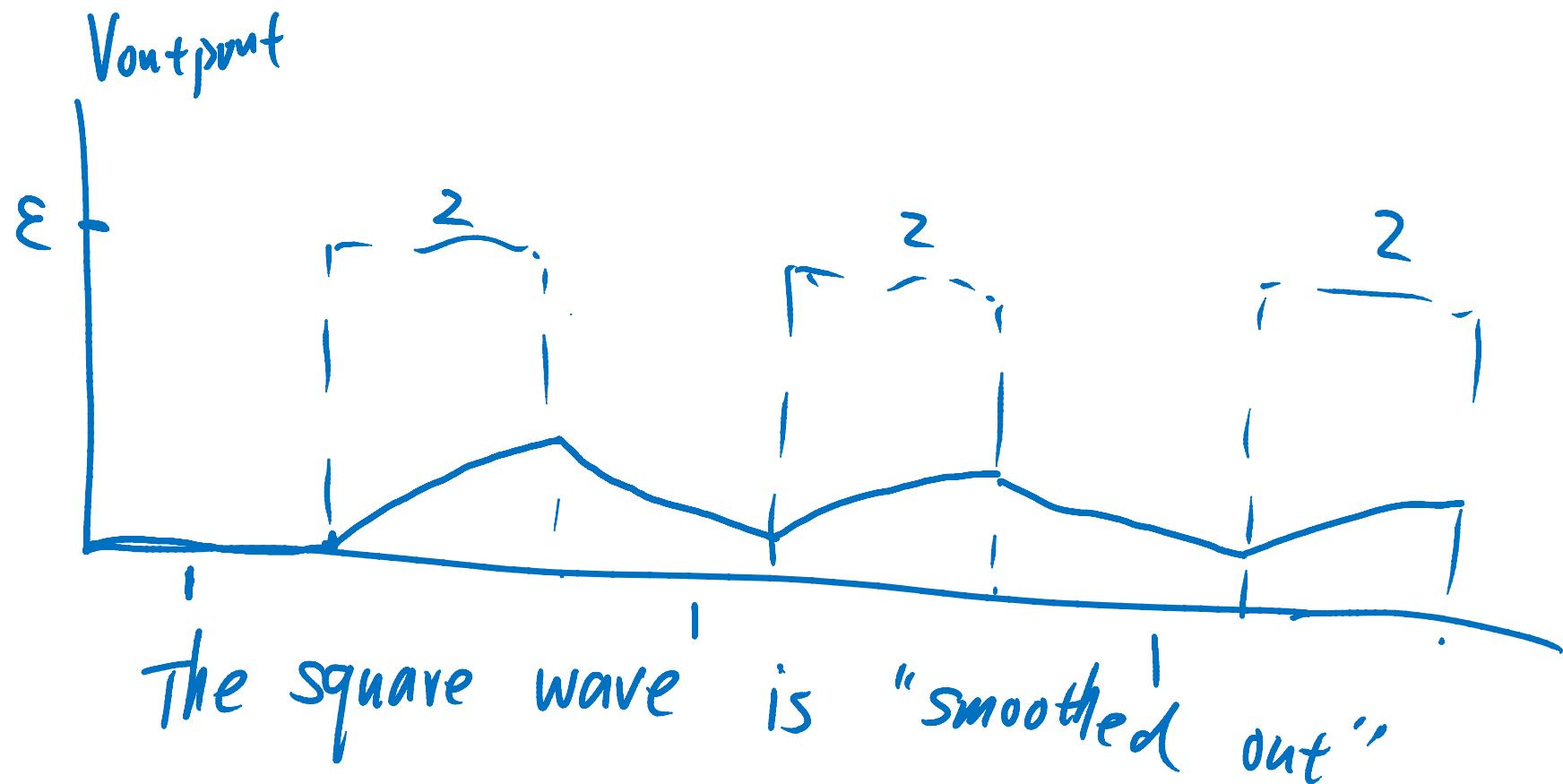Imagine RC value increases so that  $T=RC > \frac{T}{2}$



In Lab.

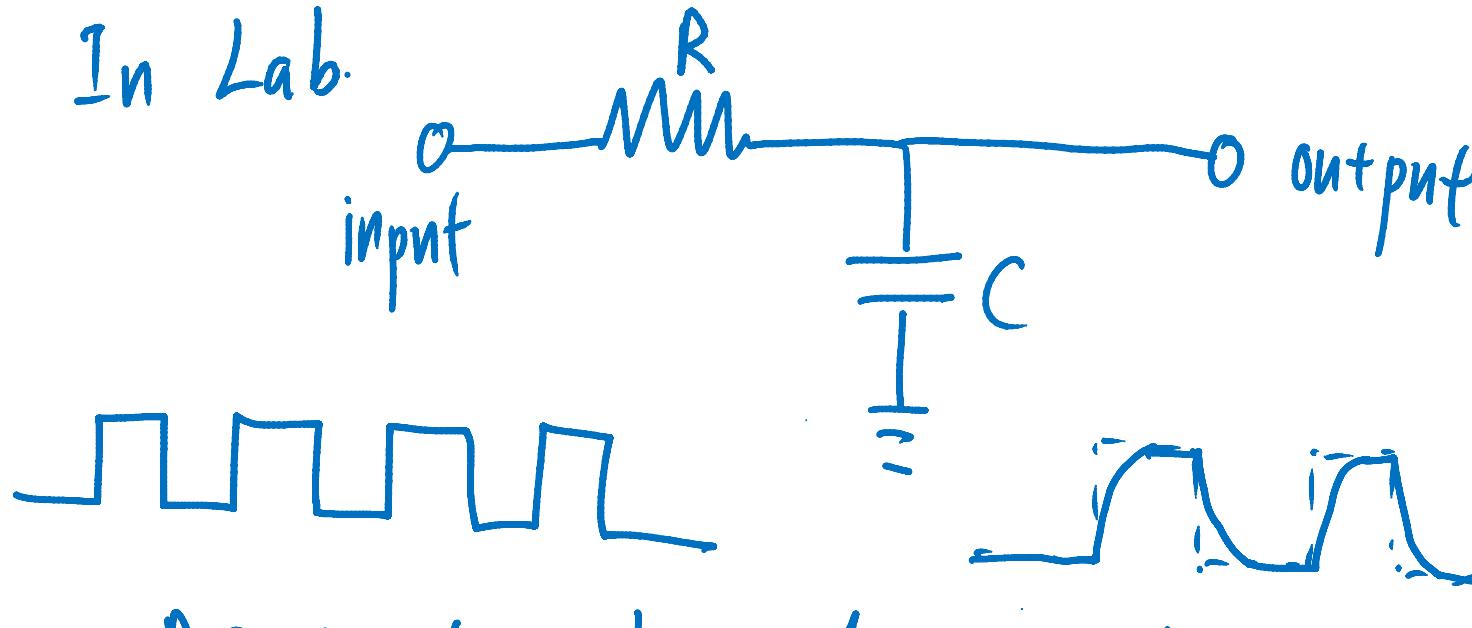


RC circuit can be used to smooth out "voltage spikes"


input:



output:

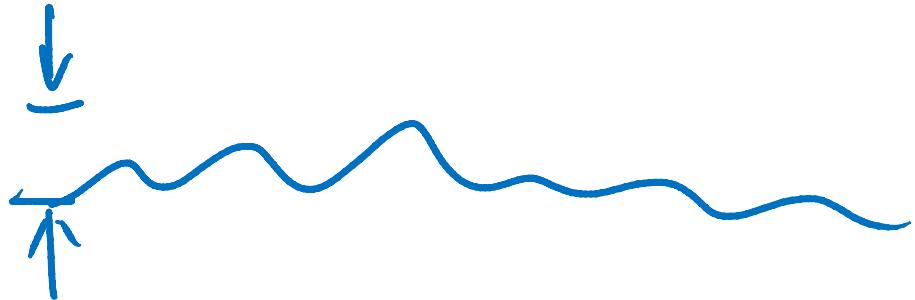

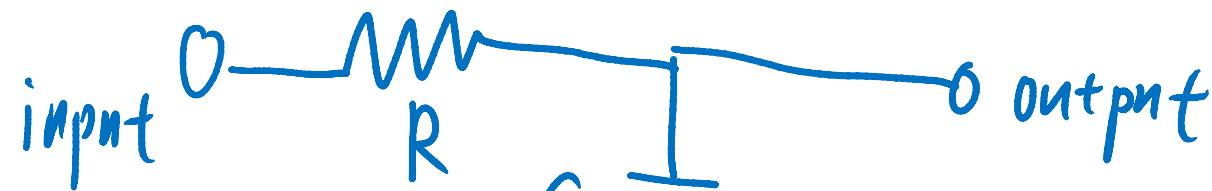RC circuits can be used as low pass filter



$$V_{in}(t) = A \cos(\omega t + \phi)$$

phasor  $\tilde{V}_{in}(j\omega)$

$$V_{out}(t) = A' \cos(\omega t + \phi')$$

phasor  $\tilde{V}_{out}(j\omega)$

$$\tilde{V}_{out}(j\omega) = \tilde{V}_{in}(j\omega) \cdot \frac{Z_C}{Z_C + Z_R} = \tilde{V}_{in}(j\omega) \frac{1}{1 + Z_R/Z_C}$$

$$Z_R = R \quad Z_C = \frac{1}{j\omega C}$$

$$\begin{array}{ll} \omega \downarrow & |Z_C| \uparrow \quad |\tilde{V}_{out}| \uparrow \\ \omega \uparrow & |Z_C| \downarrow \quad |\tilde{V}_{out}| \downarrow \end{array}$$

$$\begin{array}{ll} \omega \rightarrow 0 & |\tilde{V}_{out}| = |\tilde{V}_{in}| \\ \omega \rightarrow \infty & |\tilde{V}_{out}| = 0 \end{array}$$

## RL circuits


$$V_L = L \frac{di}{dt}$$

if  $i$  changes abruptly  $\frac{di}{dt} \rightarrow \infty$

then  $V_L = \infty$  (physically impossible)

KVL can not be satisfied.

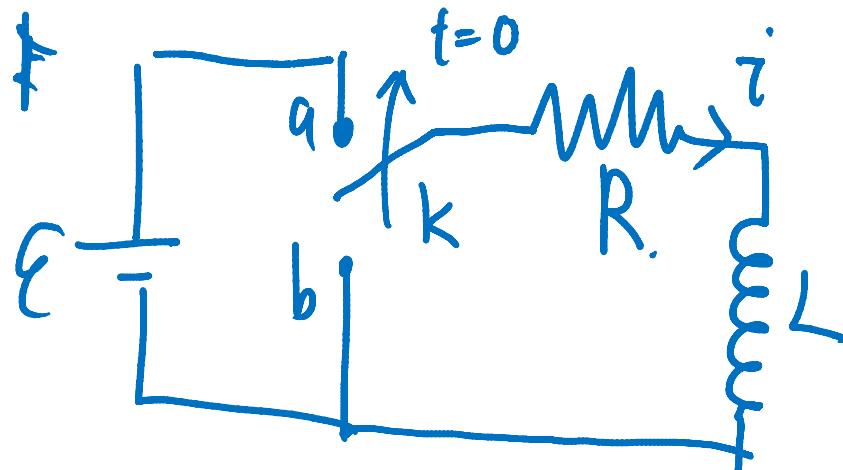So there should be no abrupt change of current in  $L$ .



At  $t=0$  switch to a.  
charge the inductor

$$t < 0 \quad i = 0$$

$$v_L = 0$$

$$\text{at } t=0^+ \quad i = ? \quad v_L = ?$$

$$i|_{t=0^+} = i|_{t<0} = 0$$

$$\text{kVL} \quad \mathcal{E} - iR - v_L = 0$$

$$v_L \Big|_{t>0^+} = \mathcal{E}$$

The initially uncharged inductor behaves like an open circuit

at  $t=0^+$

At  $t=\infty$   $i=?$   $V_L=?$

eventually circuit stabilizes  $i=\text{const}$

$$V_L = L \frac{di}{dt} = 0$$

KVL  $\mathcal{E} - iR - V_L = 0$


"0"

$$\mathcal{E} = iR$$

$$i \Big|_{t=\infty} = \frac{\mathcal{E}}{R} \quad V_L \Big|_{t=\infty} = 0$$

At  $t=\infty$ , inductor behaves like a short circuit

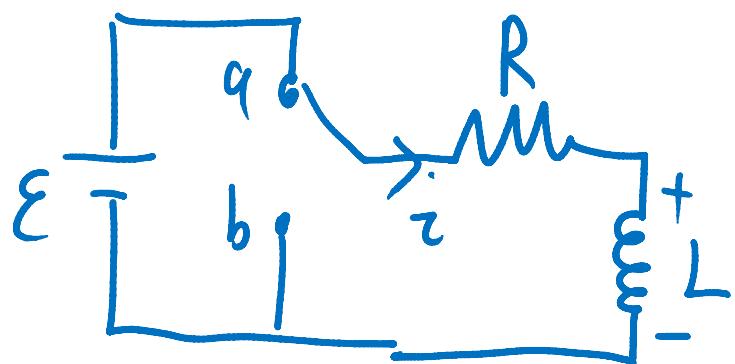What happens between  $t=0^+$  and  $t=\infty$



$$\text{kVL} \quad \mathcal{E} - iR - V_L = 0$$

$$V_L = \mathcal{E} - iR$$

$$V_L = L \frac{di}{dt}$$

$$L \frac{di}{dt} = \mathcal{E} - iR$$

$$\frac{di}{\mathcal{E} - iR} = \frac{dt}{L}$$

$$\frac{d(\mathcal{E} - iR)}{\mathcal{E} - iR} = - \frac{dt}{\left(\frac{L}{R}\right)}$$

$$\ln(\mathcal{E} - iR) = - \frac{t}{\left(\frac{L}{R}\right)} + A$$

$$\mathcal{E} - iR = e^{-t/(L/R)} \cdot e^A$$

$$\text{Let } e^A = B$$

$$\mathcal{E} - iR = B \cdot e^{-t/(L/R)}$$

$$i=0 \quad \text{at} \quad t=0^+$$

$$B = \mathcal{E}$$



$$\mathcal{E} - iR = \mathcal{E} \cdot e^{-t/(L/R)}$$


$$T = \frac{L}{R}$$

$$i(t) = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/(L/R)} \right)$$

$$V_L = \mathcal{E} - iR = \mathcal{E} \cdot e^{-t/(L/R)}$$
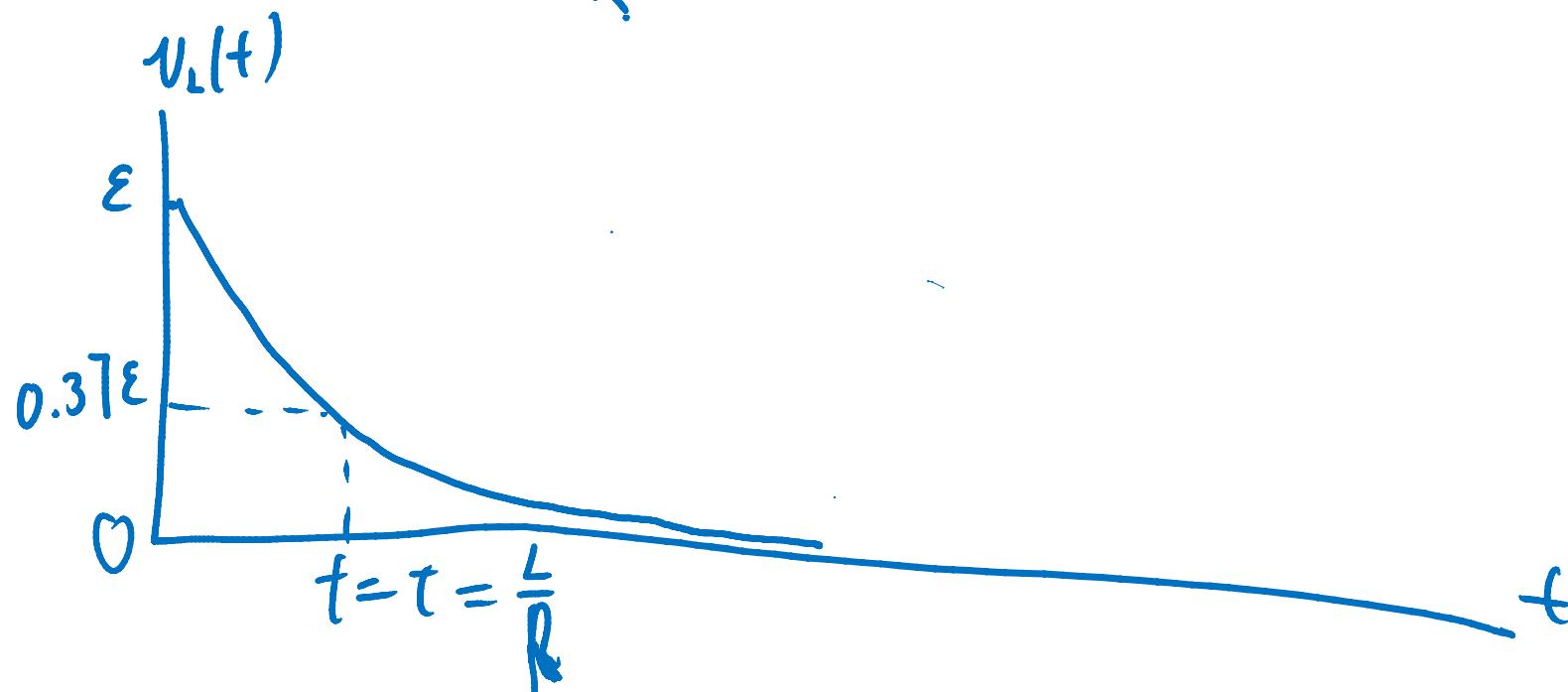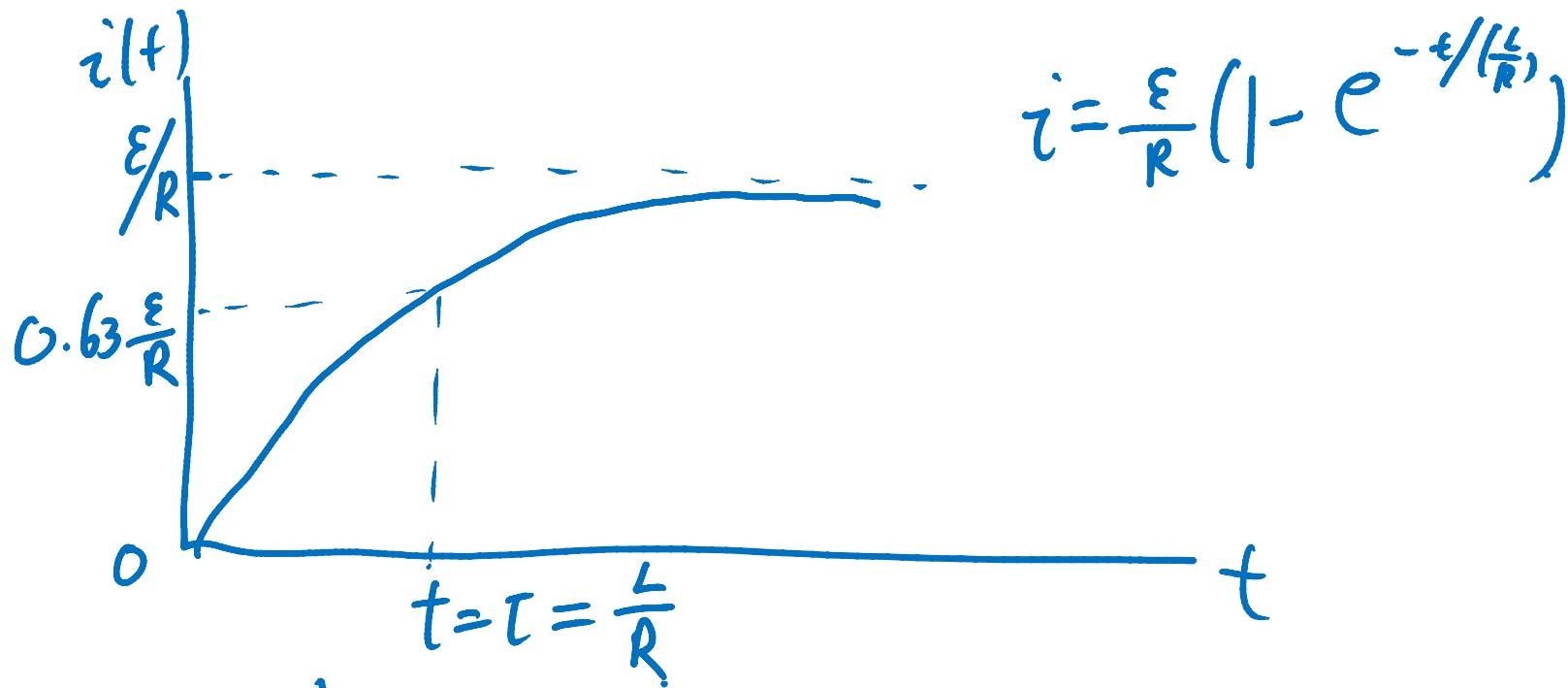
$$\text{Satisfy general form } x(t) = x(\infty) + (x(0^+) - x(\infty)) e^{-t/T}$$



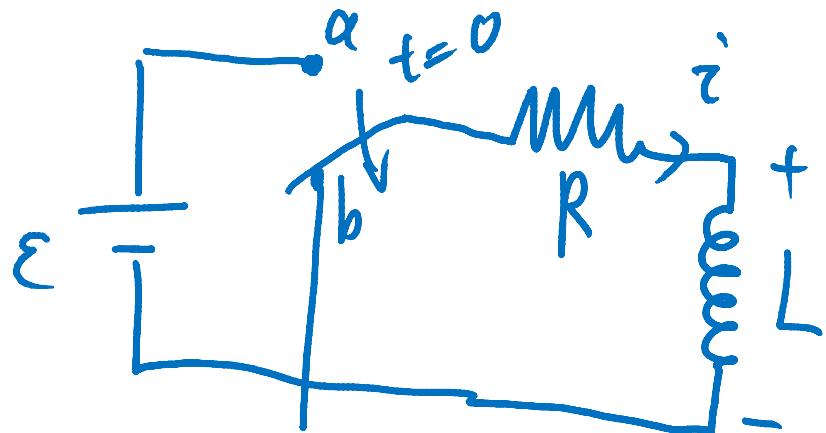

At  $t=0$  switch to  $b$   
discharge inductor

$$t < 0 \quad \dot{i} = \frac{\epsilon}{R}, \quad v_L = 0$$

At  $t=0^+$   $\dot{i} = ?$   $v_L = ?$

no sudden jump of  $i$  on inductor

$$\dot{i}|_{t=0^+} = \dot{i}|_{t<0} = \frac{\epsilon}{R}$$


$$KVL \quad -iR - v_L = 0$$

$$v_L|_{t=0^+} = -\epsilon$$

At  $t=\infty$   $i = 0$   $v_L = 0$

$$\begin{cases} i(t) = \frac{\epsilon}{R} e^{-t/\left(\frac{L}{R}\right)} \\ v_L(t) = -\epsilon e^{-t/\left(\frac{L}{R}\right)} \end{cases}$$

Example

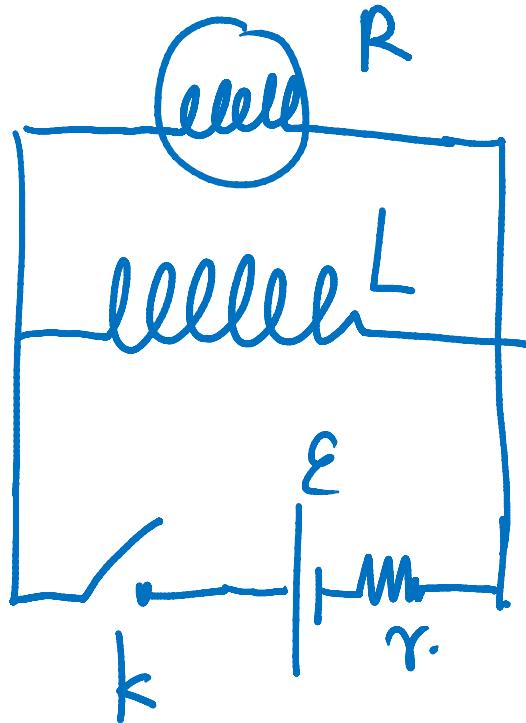


When the switch is closed, light bulb flares up brightly, then dims and goes out.

at  $t = \infty$   $v_L = 0$



$$i = \frac{13}{(4300 + 29000)} = 0.39 \text{ mA}$$
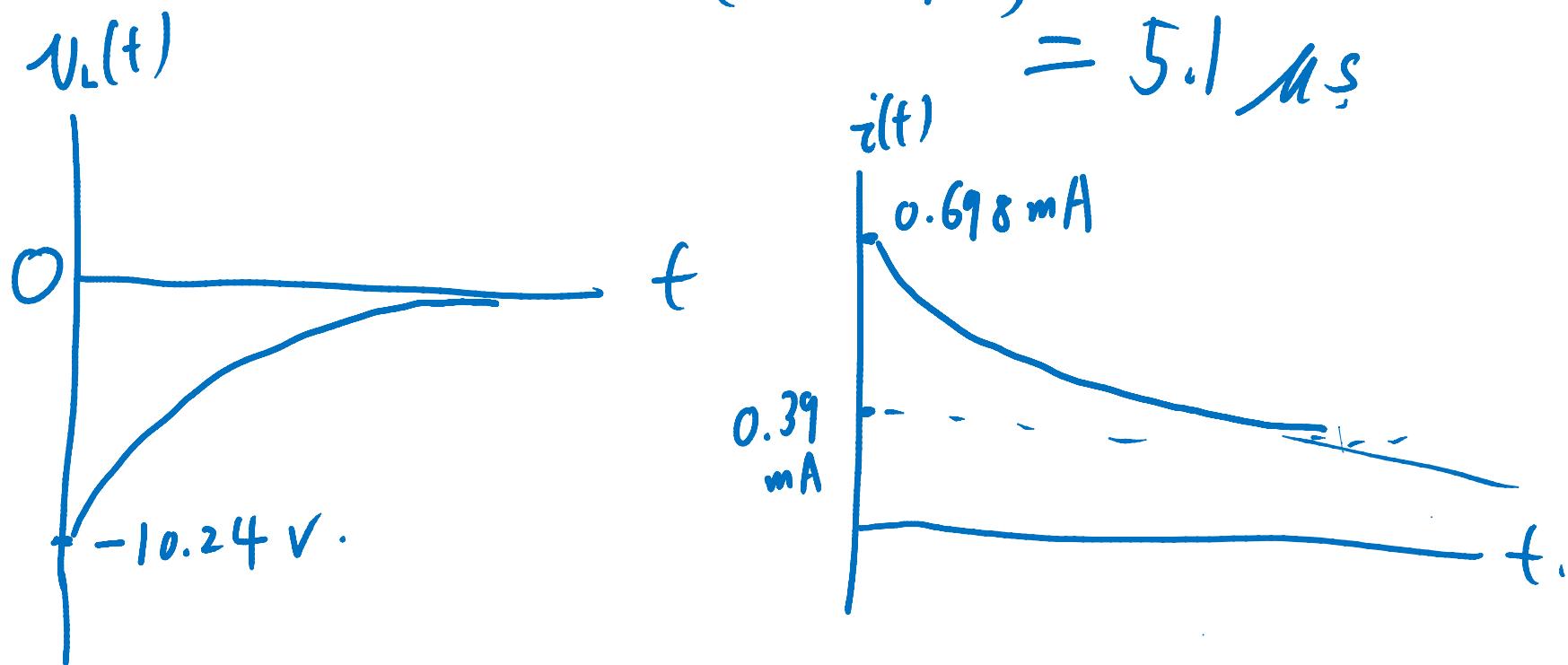
$$T = \frac{L}{R} = \frac{170 \times 10^{-3}}{(4300 + 29000)} = 5.1 \times 10^{-6} \text{ s}$$


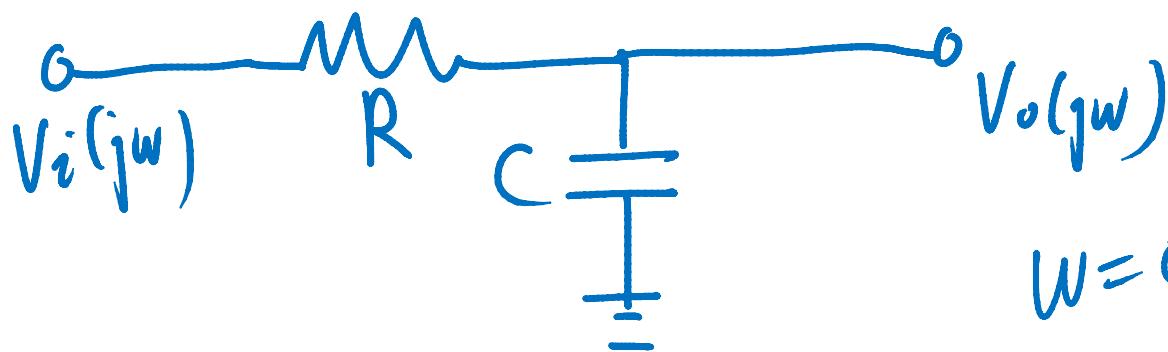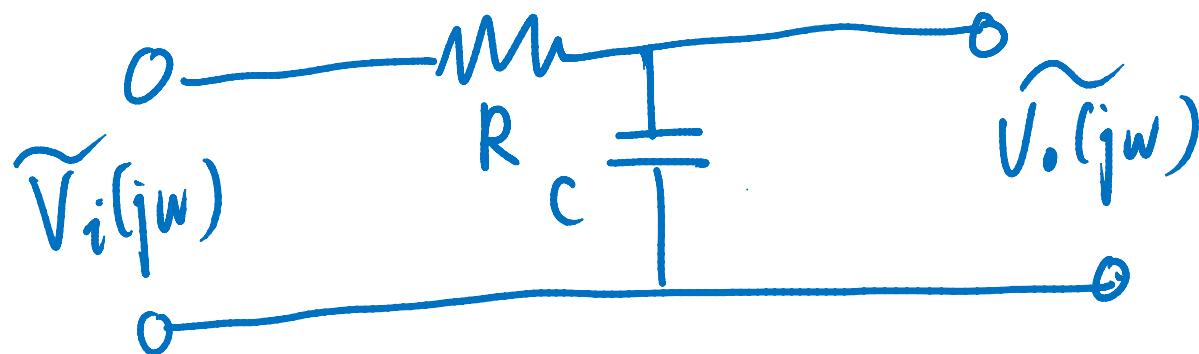
## \* Filter

low pass filter (LPF): a circuit that preserves lower frequencies while attenuating higher frequencies.



$$\tilde{V}_o(j\omega) = \tilde{V}_i(j\omega) \cdot \frac{Z_C}{Z_C + Z_R}$$

$$w=0$$

$$w=\infty$$

$$|V_o| = |V_i|$$

$$|V_o| = 0$$

$$\begin{aligned}
 H_V(j\omega) &= \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_c}{Z_c + Z_R} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = -\frac{-j}{R - \frac{j}{\omega C}} \\
 &= \frac{(-\frac{1}{\omega C}j)(R + \frac{1}{\omega C}j)}{(R - \frac{j}{\omega C})(R + \frac{1}{\omega C}j)} = \frac{\frac{1}{\omega^2 C^2} - \frac{R}{\omega C}j}{R^2 + \frac{1}{\omega^2 C^2}}
 \end{aligned}$$

$$= \frac{1 - R\omega C j}{R^2 \omega^2 C^2 + 1} = \frac{\sqrt{1 + (R\omega C)^2}}{1 + (R\omega C)^2} e^{j[\tan^{-1}(-R\omega C)]}$$

$$\begin{aligned}
 H_V(j\omega) &= \frac{1}{\sqrt{1 + (R\omega C)^2}} e^{-j \tan^{-1}(R\omega C)} \\
 &= \frac{1}{\sqrt{1 + (R\omega C)^2}} \angle[-\tan^{-1}(R\omega C)] \quad |H_V(j\omega)| \leq 1
 \end{aligned}$$

$|H_v(j\omega)| = 1$  means 100% transmission

$|H_v(j\omega)|$  is a measure of signal transmission

$$\theta = -\tan^{-1}(R_w C)$$


phase shift between  $V_o(j\omega)$  and  $V_i(j\omega)$


Define  $\omega_0 = \frac{1}{RC}$

$$H_v(j\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} e^{-j \tan^{-1}\left(\frac{\omega}{\omega_0}\right)}$$

$$\begin{array}{lll} \omega = 0 & |H_v| = 1 & \theta = 0^\circ \\ \omega = \infty & |H_v| = 0 & \theta = -90^\circ \end{array}$$

$$\omega = \omega_0 \quad |H_v| = 1/\sqrt{2} \quad \theta = -45^\circ$$

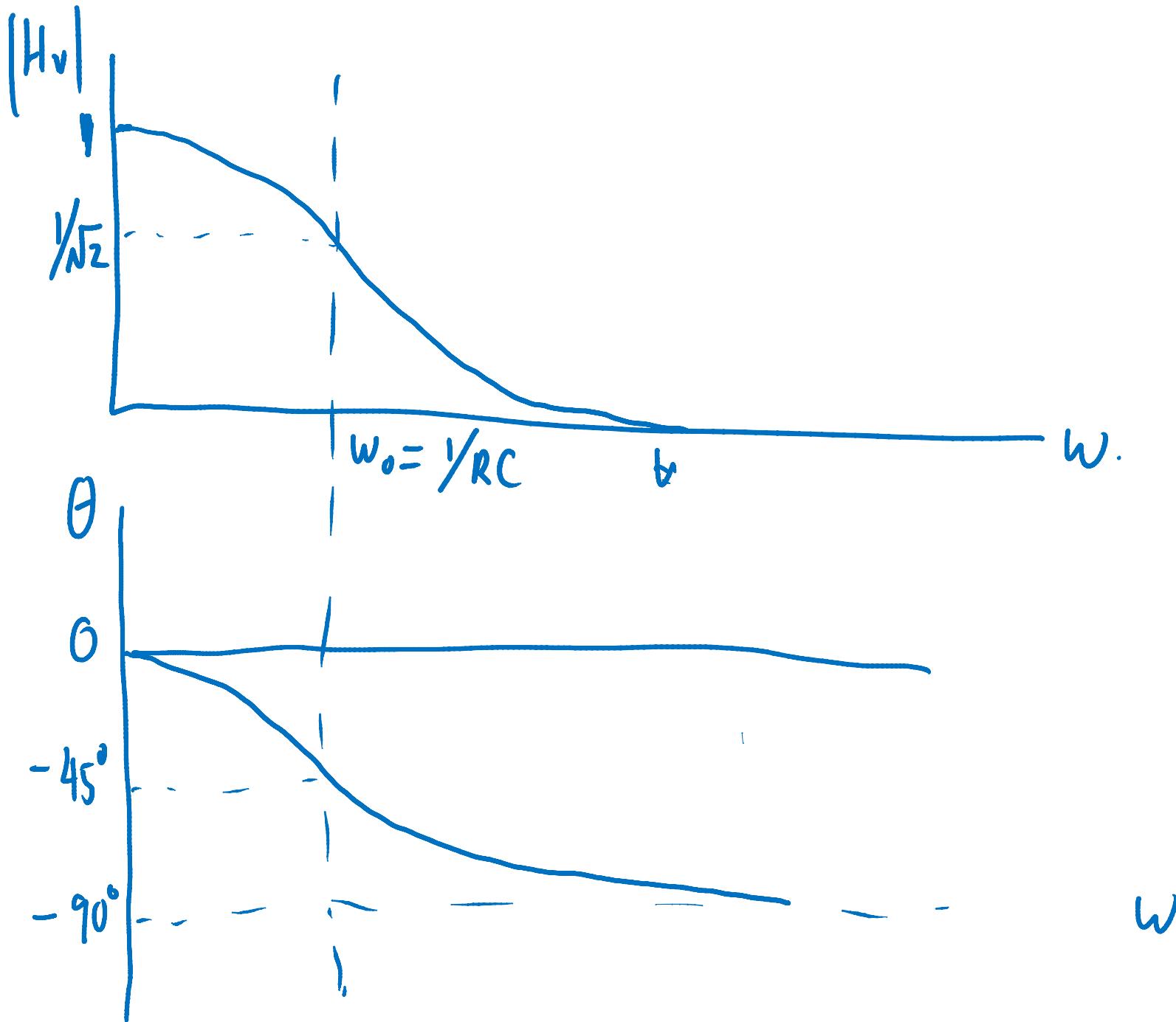


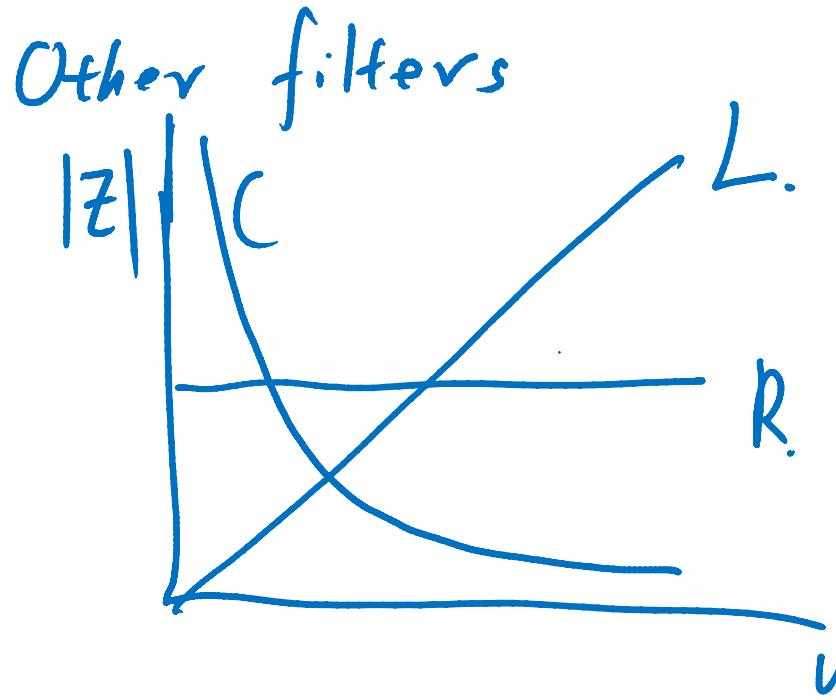

$$Z_C = \frac{1}{jwC}$$

$$Z_L = jwL$$


$$Z_R = R$$

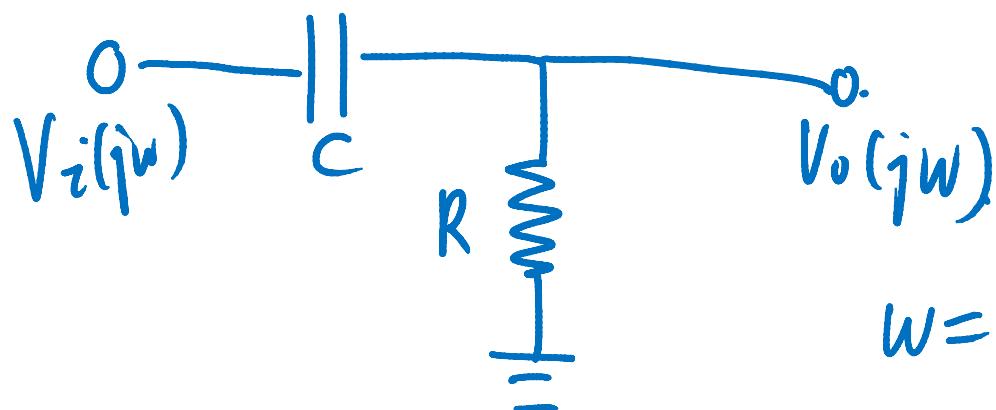

$$w=0 \quad |Z_C|=\infty \quad |V_o|=0$$

$$w=\infty \quad |Z_C|=0 \quad |V_o|=|V_i|$$

high pass filter (HPF)

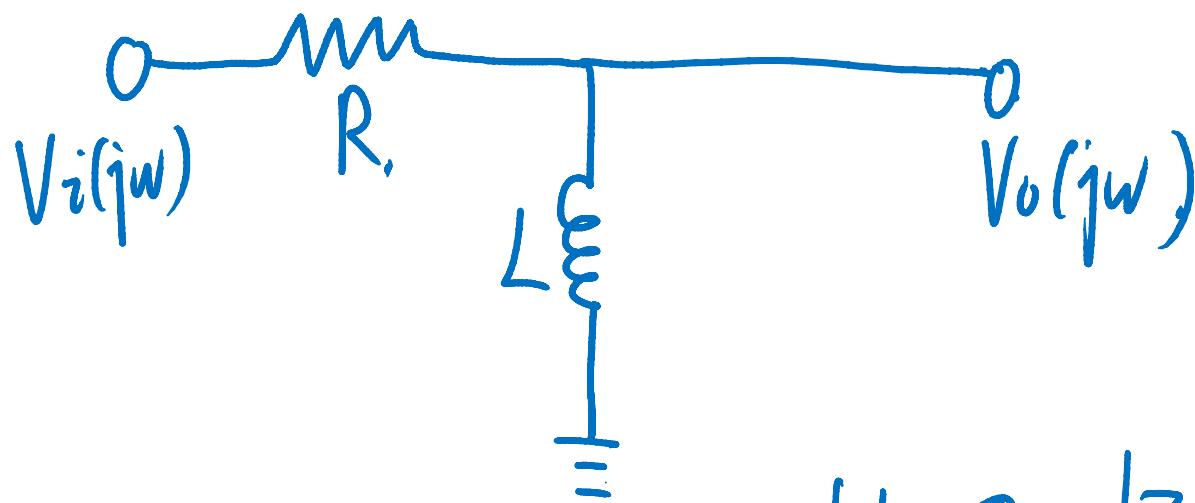


$$\omega = 0 \quad |Z_L| = 0 \quad |V_o| = 0$$

$$\omega = \infty \quad |Z_L| = \infty \quad |V_o| = |V_i|$$

high pass filter (HPF)

$$H_v(j\omega) = \frac{V_o}{V_i} = \frac{Z_L}{Z_L + Z_R}$$

Example

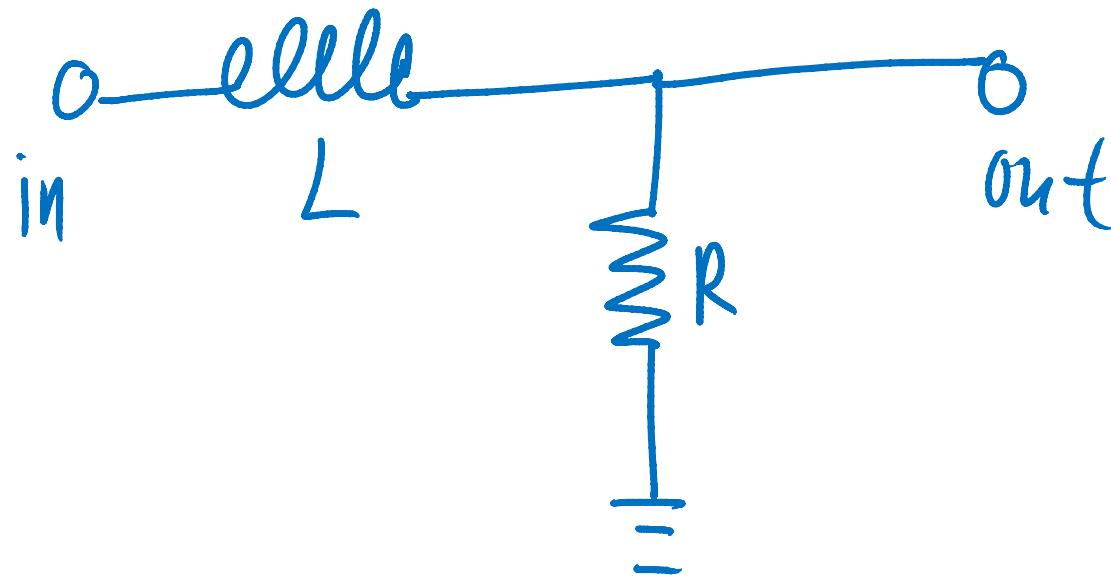


$$\omega = 0 \quad |Z_L| = 0 \quad |V_0| = |V_i|$$

$$\omega = \infty \quad |Z_L| = \infty \quad |V_0| = 0$$

low pass filter (LPF)

# RLC Band-pass filter

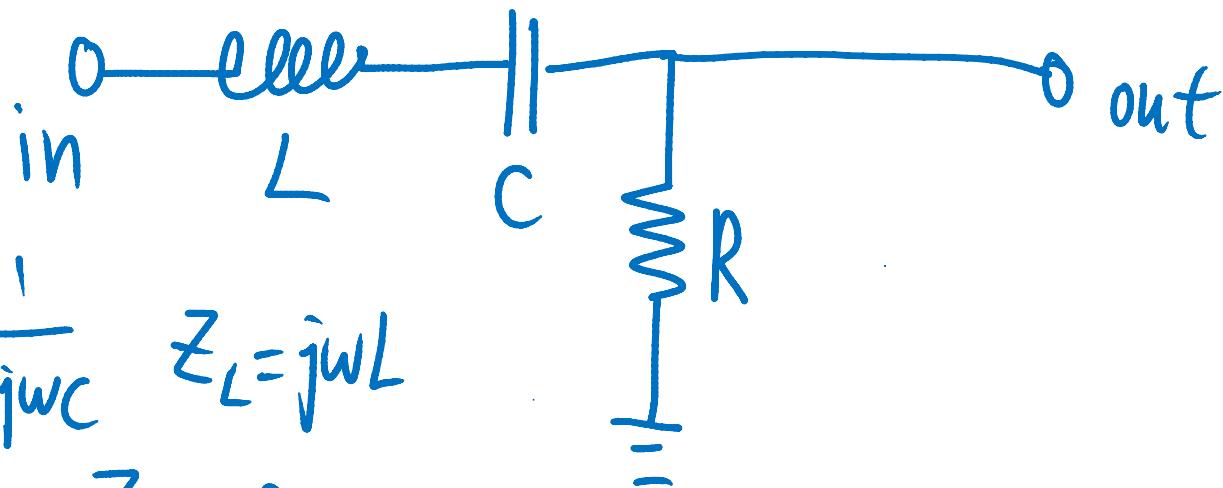


$$Z_C = \frac{1}{j\omega C} \quad Z_L = j\omega L$$

"

$$- \frac{1}{j\omega C} \quad Z_R = R$$

$$\begin{aligned} \omega = 0 & \quad |Z_L| = 0 \quad |Z_C| = \infty \quad |V_o| = 0 \\ \omega = \infty & \quad |Z_L| = \infty \quad |Z_C| = 0 \quad |V_o| = 0 \\ 0 < \omega < \infty & \quad |V_o| > 0 \end{aligned}$$

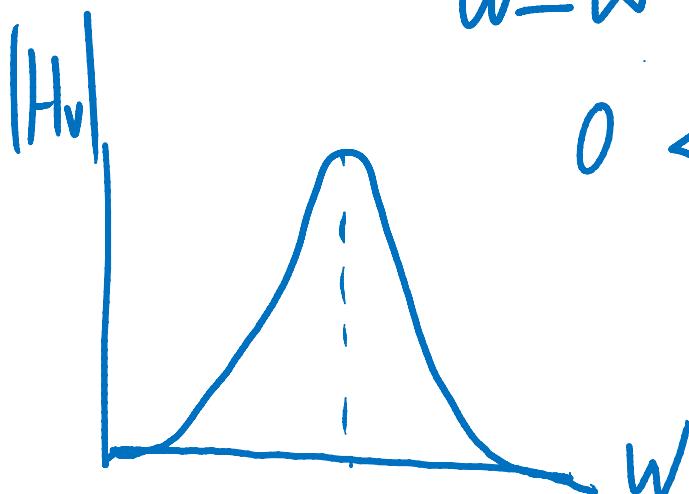


$$V_o = V_i \cdot \frac{Z_R}{Z_C + Z_L + Z_R}$$

$$H_v = \frac{V_o}{V_i} = \frac{Z_R}{Z_C + Z_L + Z_R} = \frac{R}{\frac{1}{j\omega C} + j\omega L + R}$$


$$= \frac{R}{R + \left(\omega L - \frac{1}{\omega C}\right) j}$$

$$H_v \Big|_{\omega = \omega_0} = \Big| H_v \Big|_{\omega_0}$$
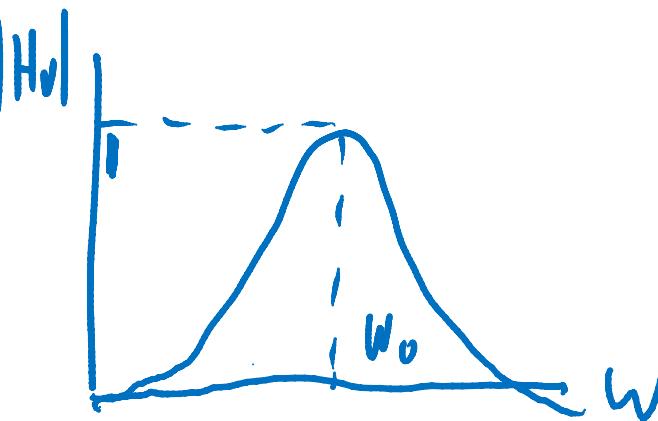
$$\omega L = \frac{1}{\omega C} \quad \omega = \sqrt{\frac{1}{LC}} = \omega_0$$



# Band stop filter

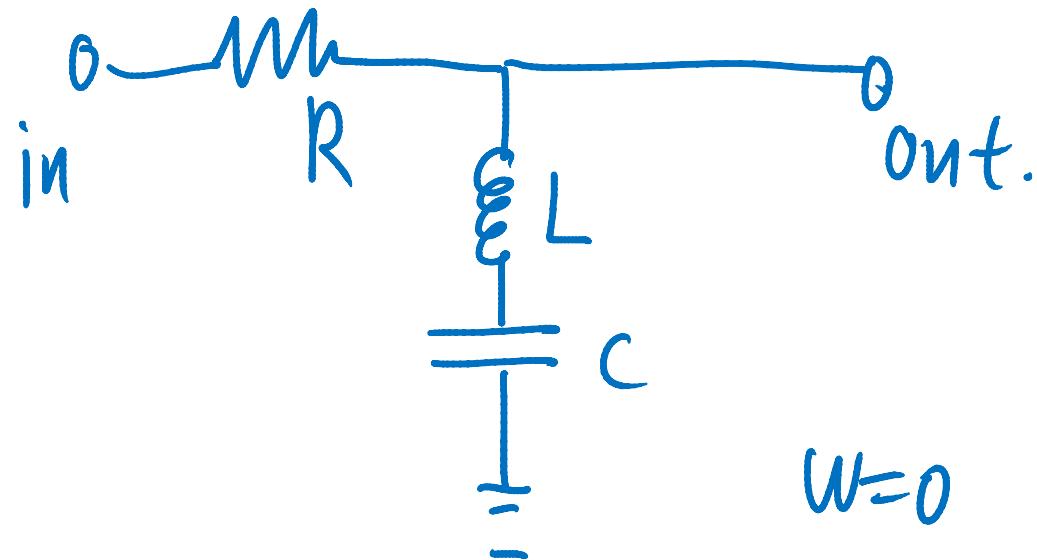

$$w=0 \quad |Z_d|=\infty \quad |Z_L|=0 \quad |V_o|=|V_i|$$

$$w=\infty \quad |Z_d|=0 \quad |Z_L|=\infty \quad |V_o|=|V_i|$$


$$\text{iff } 0 < w < \omega \quad |V_o| < |V_i|$$

$$H_V = \frac{V_o}{V_i} = \frac{Z_L + Z_C}{Z_L + Z_C + R} = \frac{j(\omega L - \frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})}$$


$$\omega L = \frac{1}{\omega C}$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$|H_V|_{\omega=\omega_0} = 0$$

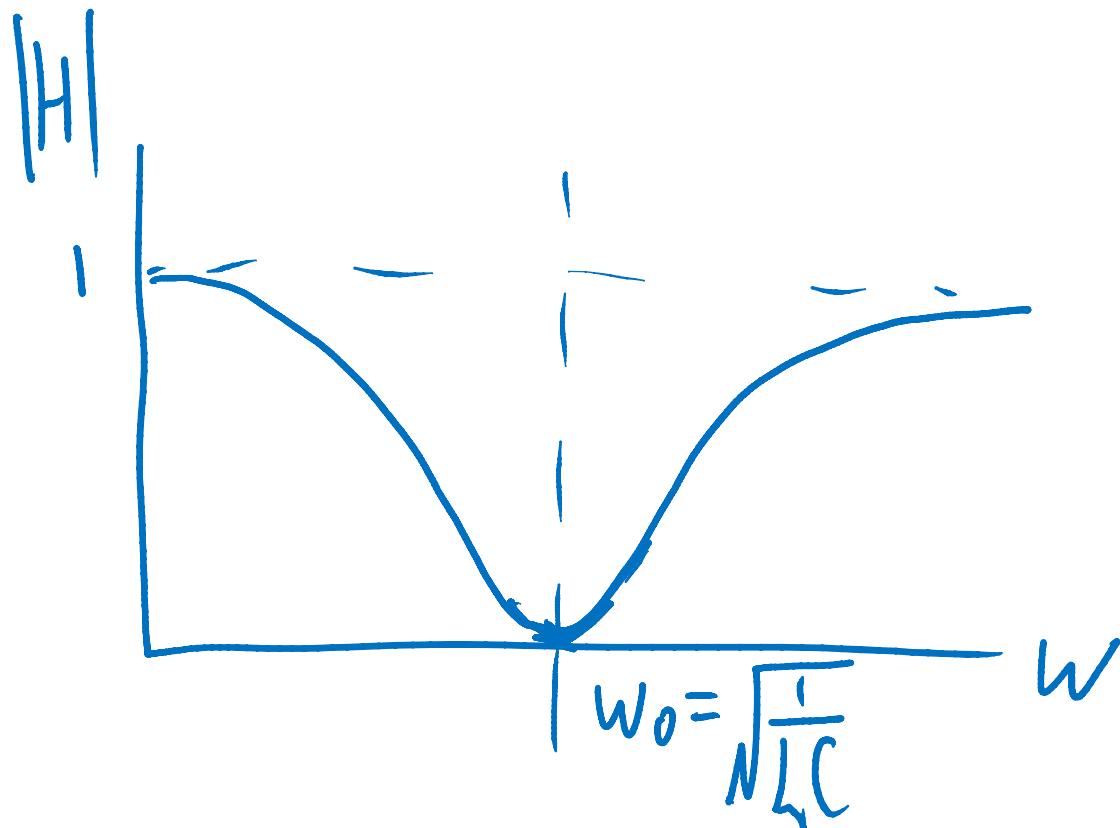

Band stop filter

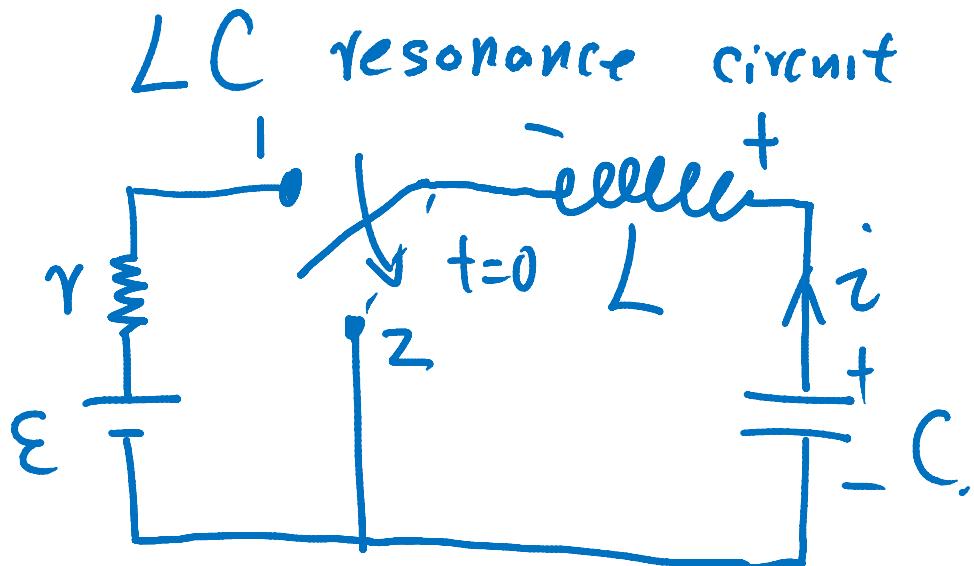

$i = 0 \quad t < 0$   
 $t = 0 \quad$  Switch from 1  
 $\quad \quad \quad$  to 2  
 $t > 0 \quad i \neq 0$

$t > 0$  kVL  $V_C - V_L = 0$

$$\frac{Q}{C} - L \frac{di}{dt} = 0$$

$$i = -\frac{dQ}{Ct}$$

$$\frac{Q}{C} + L \frac{d^2Q}{dt^2} = 0$$

$$\frac{d^2Q}{dt^2} + \frac{1}{LC} Q = 0$$

$$-kx = m \frac{d^2x}{dt^2}$$

$$\frac{d^2x}{dt^2} + \frac{k}{m} x = 0$$

$$\frac{1}{LC} \leftrightarrow \frac{k}{m}$$

$$Q = Q_0 \cos(\omega t + \varphi)$$

$Q_0, \varphi$  determined by initial conditions.

$$-\omega^2 Q_0 \cos(\omega t + \varphi) + \frac{Q_0}{LC} \cos(\omega t + \varphi) = 0$$

$$\left(-\omega^2 + \frac{1}{LC}\right) \cos(\omega t + \varphi) = 0$$


true for any time  $t$

$$-\omega^2 + \frac{1}{LC} = 0$$


$$\omega = \sqrt{\frac{1}{LC}}$$

resonance frequency

$Q$  and  $i$  oscillates sinusoidally.

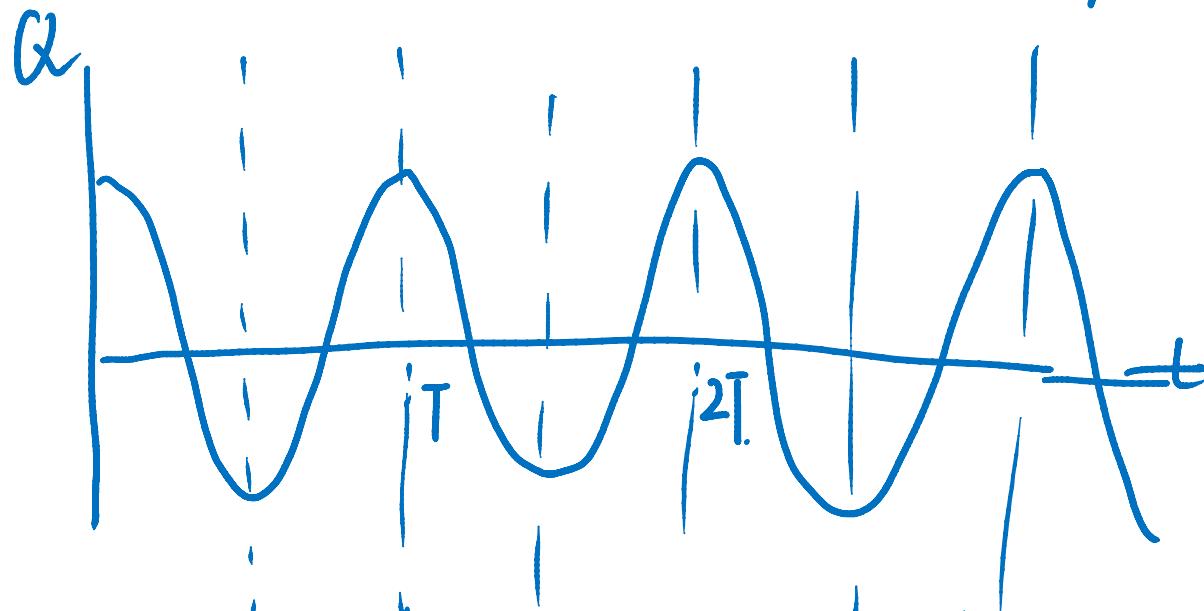

$$E_C = \frac{Q^2}{2C}$$

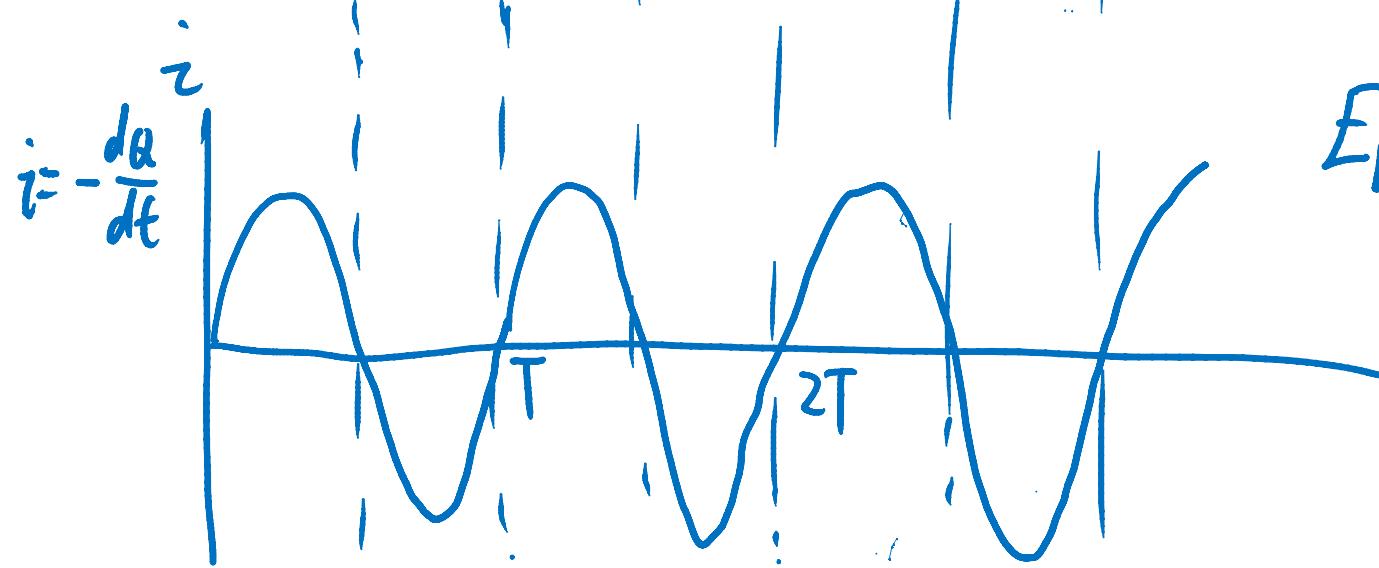

$$E_L = \frac{1}{2} L i^2$$

When  $Q$  is max,  $i = 0$


when  $Q = 0$ ,  $i$  is max

$$E_C = \frac{Q^2}{2C} \quad E_L = \frac{1}{2} L i^2$$

When  $E_C$  is max,  $E_L = 0$

when  $E_C = 0$ ,  $E_L$  is max,

RLC circuit.

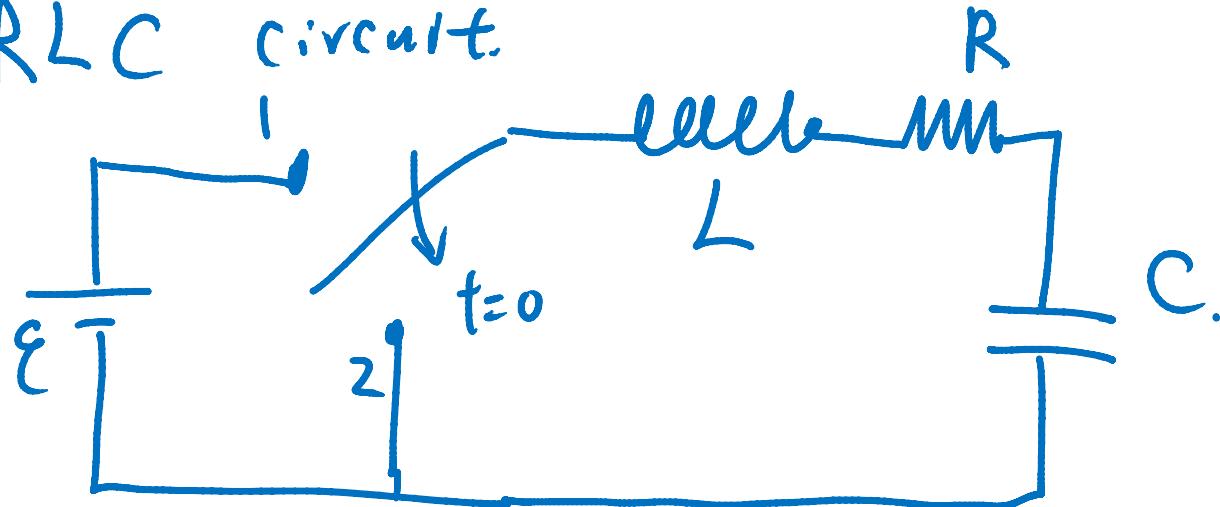

$R$  : energy dissipation.

a damped oscillation.

