



Homework #10

**Problems 5.44, 5.48, 5.55, 5.56,
5.62, and 5.63**



Problem 5.44

Design the circuit of Fig. P5.44 to establish a drain current of 0.1 mA and a drain voltage of +0.3 V. The MOSFET has $V_t = 0.5$ V, $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$, $L = 0.4 \mu\text{m}$, and $W = 5 \mu\text{m}$. Specify the required values for R_S and R_D .

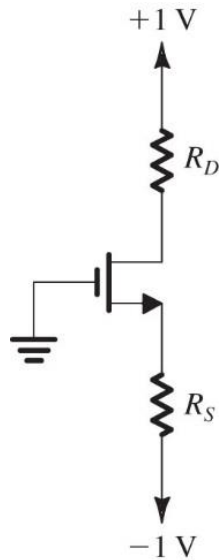


Figure P5.44

$$I_D := 0.1 \text{ mA}$$

$$V_{tn} := 0.5 \text{ V}$$

$$k_n := \frac{400 \mu\text{A}}{\text{V}^2} \cdot \frac{5 \mu\text{m}}{0.4 \mu\text{m}} = 5 \frac{\text{mA}}{\text{V}^2}$$

$$V_{OV} := \sqrt{\frac{2 \cdot I_D}{k_n}} = 0.2 \text{ V}$$

$$V_{GS} := V_{tn} + V_{OV} = 0.7 \text{ V}$$

The gate is grounded so $V_S = 0 \text{ V} - V_{GS} = -0.7 \text{ V}$

$$R_S := \frac{-V_{GS} - (-1 \text{ V})}{I_D} = 3 \text{ k}\Omega$$

The drain voltage is + 0.3 V

$$R_D := \frac{1 \text{ V} - 0.3 \text{ V}}{I_D} = 7 \text{ k}\Omega$$

Problem 5.48

It is required to operate the transistor in the circuit of Fig. P5.47 at the edge of saturation with $I_D = 0.1$ mA. If $V_t = 0.4$ V, find the required value of R_D .

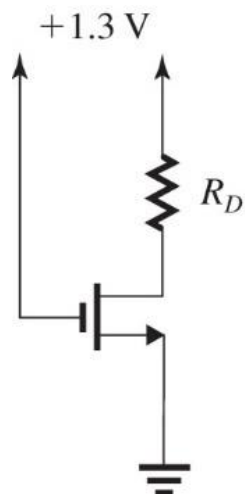


Figure P5.47

$V_{GS} = 1.3\text{V}$ Since gate is tied to V_{DD} (1.3 V) and source is grounded

$$V_{GS} = V_t + V_{OV} = 1.3\text{V}$$

$$V_{OV} = V_{GS} - V_t = 1.3 - 0.4 = 0.9\text{V}$$

Since it is operating at the edge of saturation $V_{DS} = V_{OV} = 0.9\text{V}$


$$R_D = \frac{1.3\text{V} - 0.9\text{V}}{0.1\text{mA}} = 4000\Omega$$



Problem 5.55

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1$ V, $k'(W/L) = 4$ mA/V², and $\lambda = 0$.

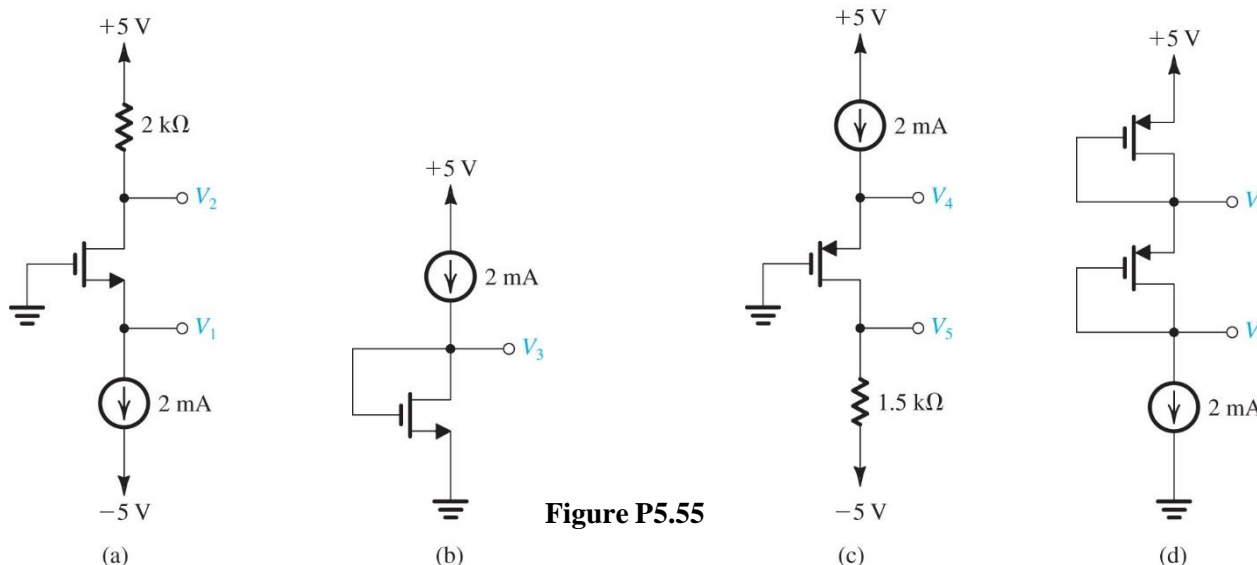- (a) Find the labeled voltages V_1 through V_7 .
- (b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix J. Find the new values of V_1 through V_7 .





Standard Resistor Values

1% Standard Values											
Decade multiples are available from 10.0 Ω through 1.00 M Ω (also 1.10 M Ω , 1.20 M Ω , 1.30 M Ω , 1.50 M Ω , 1.60 M Ω , 1.80 M Ω , 2.00 M Ω and 2.20 M Ω)											
10.0	10.2	10.5	10.7	11.0	11.3	11.5	11.8	12.1	12.4	12.7	13.0
13.3	13.7	14.0	14.3	14.7	15.0	15.4	15.8	16.2	16.5	16.9	17.4
17.8	18.2	18.7	19.1	19.6	20.0	20.5	21.0	21.5	22.1	22.6	23.2
23.7	24.3	24.9	25.5	26.1	26.7	27.4	28.0	28.7	29.4	30.1	30.9
31.6	32.4	33.2	34.0	34.8	35.7	36.5	37.4	38.3	39.2	40.2	41.2
42.2	43.2	44.2	45.3	46.4	47.5	48.7	49.9	51.1	52.3	53.6	54.9
56.2	57.6	59.0	60.4	61.9	63.4	64.9	66.5	68.1	69.8	71.5	73.2
75.0	76.8	78.7	80.6	82.5	84.5	86.6	88.7	90.9	93.1	95.3	97.6

5% Standard Values											
Decade multiples are available from 10 Ω through 22 M Ω											
10	11	12	13	15	16	18	20	22	24	27	30
33	36	39	43	47	51	56	62	68	75	82	91

10% Standard Values											
Decade multiples are available from 10 Ω through 1 M Ω											
10	12	15	18	22	27	33	39	47	56	68	82

<http://www.rfcafe.com/references/electrical/resistor-values.htm>



Problem 5.55a (NMOS)

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1\text{ V}$, $k'(W/L) = 4\text{ mA/V}^2$, and $\lambda = 0$.

$$V_2 = 5 - 2\text{mA} \times 2\text{k}\Omega = 1\text{V}$$


$$v_{OV} = \sqrt{\frac{2i_D}{k'_n \left(\frac{W}{L}\right)}} = 1\text{V}$$

$$v_{GS} = V_t + v_{OV} = 1 + 1 = 2.0\text{V}$$

$$V_1 = -2\text{V} \quad \longrightarrow \quad v_{DS} = 3.0\text{V} > V_{OV} \quad \text{Device is in saturation}$$

$$R_S = \frac{-2\text{V} - (-5\text{V})}{2\text{mA}} = 1.5\text{k}\Omega \quad \text{Closest 1\% value is } 1.50\text{k}\Omega$$

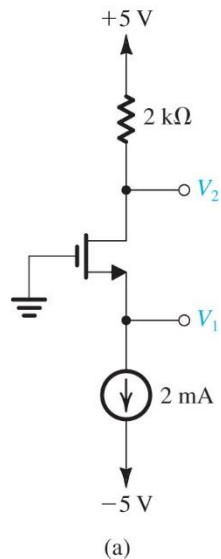- (a) Find the labeled voltages V_1 through V_7 .
 (b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix J. Find the new values of V_1 through V_7 .




Since the resistor is exactly matched the currents and voltages don't change

Figure P5.55



Problem 5.55b (NMOS)

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1\text{ V}$, $k'(W/L) = 4\text{ mA/V}^2$, and $\lambda = 0$.

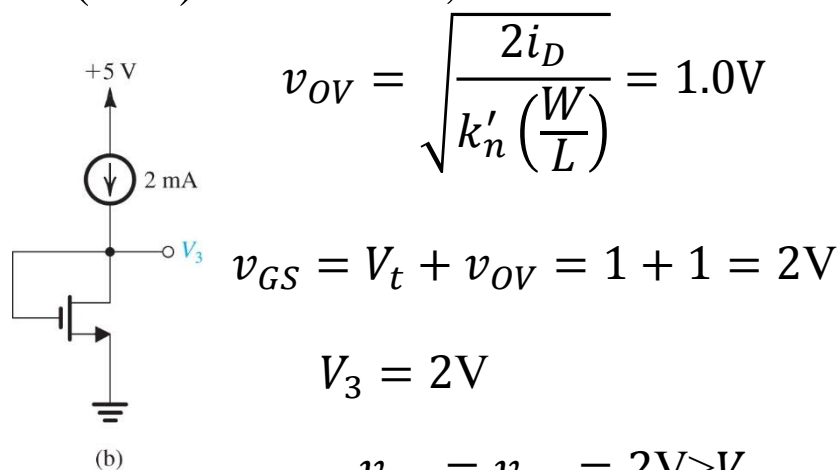

$$v_{OV} = \sqrt{\frac{2i_D}{k'_n \left(\frac{W}{L}\right)}} = 1.0\text{V}$$

$$v_{GS} = V_t + v_{OV} = 1 + 1 = 2\text{V}$$

$$V_3 = 2\text{V}$$

$$v_{DS} = v_{GS} = 2\text{V} > V_{OV}$$

$$R_D = \frac{5\text{V} - 2\text{V}}{3\text{mA}} = 1.5\text{k}\Omega$$

(a) Find the labeled voltages V_1 through V_7 .

(b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix J. Find the new values of V_1 through V_7 .

Device is in saturation


Closest 1% value is $1.5\text{k}\Omega$

Since the resistor is exactly matched the currents and voltages don't change



Problem 5.55c (PMOS)

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1\text{ V}$, $k'(W/L) = 4\text{ mA/V}^2$, and $\lambda = 0$.

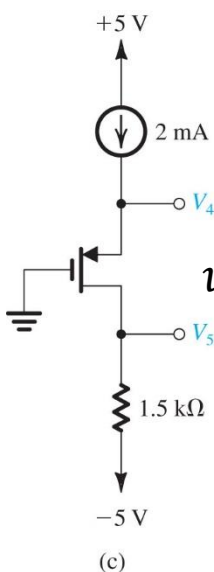

$$v_{OV} = \sqrt{\frac{2i_D}{k'_n \left(\frac{W}{L}\right)}} = 1\text{ V}$$

$$v_{GS} = -V_t - v_{OV} = -1 - 1 = -2\text{ V}$$

$$V_4 = V_S = 2\text{ V}$$

$$V_5 = -5 + 2\text{ mA} \times 1.5\text{ k}\Omega = -2\text{ V}$$

$$R_S = \frac{5\text{ V} - 2\text{ V}}{2\text{ mA}} = 1.5\text{ k}\Omega$$

Closest 1% value is 1.50kΩ


- (a) Find the labeled voltages V_1 through V_7 .
 (b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix J. Find the new values of V_1 through V_7 .

Since the resistor is exactly matched the currents and voltages don't change



Problem 5.55d (PMOS)

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1\text{ V}$, $k'(W/L) = 4\text{ mA/V}^2$, and $\lambda = 0$.

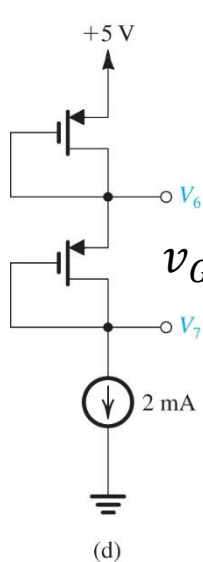

$$v_{OV} = \sqrt{\frac{2i_D}{k'_n \left(\frac{W}{L}\right)}} = 1\text{ V}$$

$$v_{GS} = -V_t - v_{OV} = -1 - 1 = -2\text{ V}$$

$$V_6 = V_{G1} = 5\text{ V} - 2\text{ V} = 3\text{ V}$$

$$V_7 = V_{G2} = V_{G1} - v_{GS2} = 1\text{ V}$$

$$R_D = \frac{1\text{ V}}{2\text{ mA}} = 500\Omega$$


Closest 1% value is 499Ω

- (a) Find the labeled voltages V_1 through V_7 .
- (b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix J. Find the new values of V_1 through V_7 .

Problem 5.55d cont (PMOS)

In the circuits shown in Fig. P5.55, transistors are characterized by $|V_t| = 1\text{ V}$, $k'(W/L) = 4\text{ mA/V}^2$, and $\lambda = 0$.

With $R_D = 499\Omega$

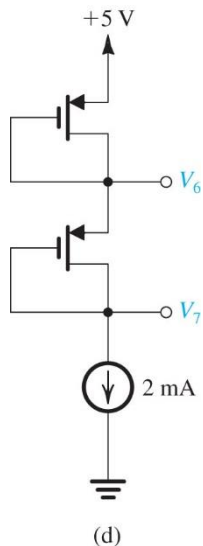

$$I_D = \frac{5\text{V} - 2V_{SG}}{499\Omega}$$

$$I_D = \frac{1}{2}k'_n\left(\frac{W}{L}\right)(V_{SG} - V_t)^2 = \frac{1}{2}\frac{4\text{mA}}{\text{V}^2}(V_{SG} - 1\text{V})^2$$

Solving yields $V_{SG} = 2.003\text{V}$









The new current is then $I_D = 1.992\text{mA}$

- (a) Find the labeled voltages V_1 through V_7 .
- (b) In each of the circuits, replace the current source with a resistor. Select the resistor value to yield a current as close to that of the current source as possible, while using resistors specified in the 1% table provided in Appendix H. Find the new values of V_1 through V_7 .



Problem 5.56


For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors, $k_n'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0$.

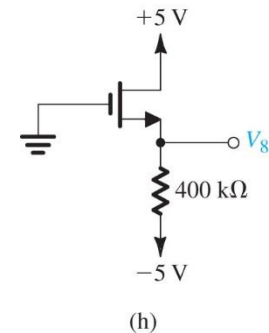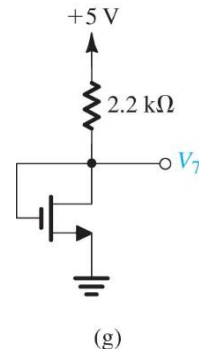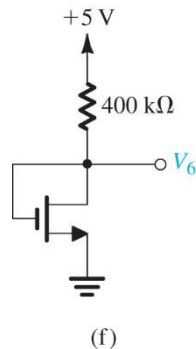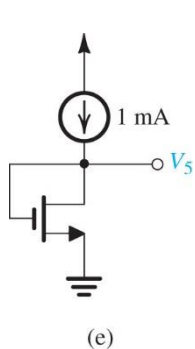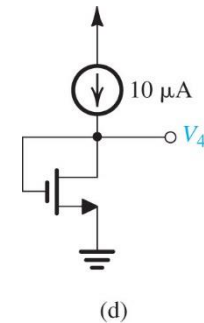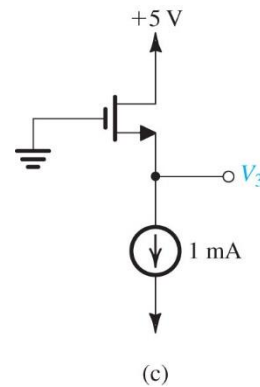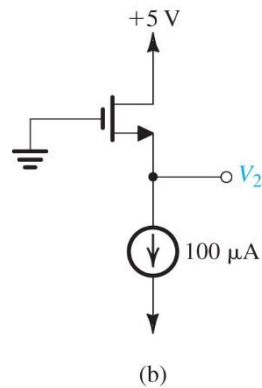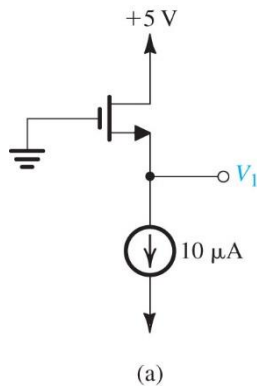



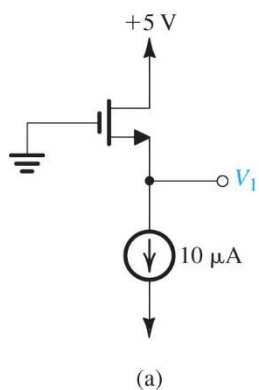Problem 5.56a,b

For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors, $k_n'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0$.




$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{OV}^2$$

$$V_{OV} = \sqrt{\frac{I_D}{\frac{1}{2} k_n' \left(\frac{W}{L} \right)}}$$

$$V_{OV} := \sqrt{\frac{2 \cdot 10 \mu\text{A}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 0.2 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.8 + 0.2 = 1.0 \text{ V}$$

$$V_1 = -1.0 \text{ V}$$

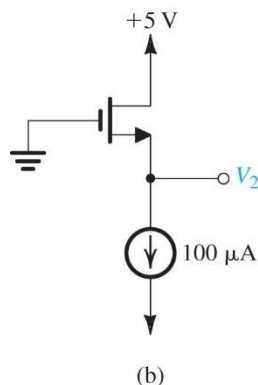


$$V_{OV} := \sqrt{\frac{2 \cdot 100 \mu\text{A}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 0.632 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.8 + 0.632 = 1.432 \text{ V}$$

$$V_2 = -1.432 \text{ V}$$

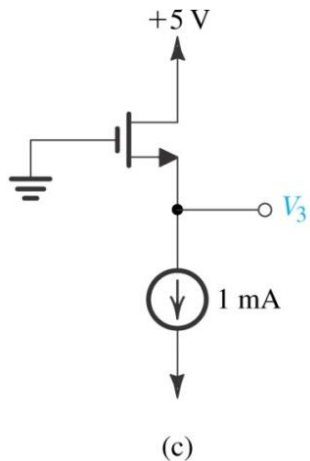Problem 5.56c,d


For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors, $k_n'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0$.



$$V_{OV} := \sqrt{\frac{2 \cdot 1 \text{ mA}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 2 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.8 + 2 = 2.8 \text{ V}$$

$$V_3 = -2.8 \text{ V}$$

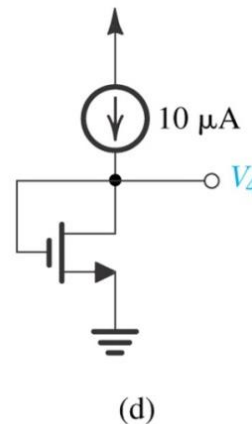

$$V_{OV} := \sqrt{\frac{2 \cdot 10 \mu\text{A}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 0.2 \text{ V}$$


$$V_{GS} = V_t + V_{OV} = 0.8 + 0.2 = 1.0 \text{ V}$$

$$V_4 = 1.0 \text{ V}$$



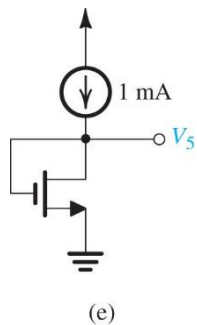Problem 5.56e,f


For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors, $k_n'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0$.



$$V_{OV} := \sqrt{\frac{2 \cdot 1 \text{ mA}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 2 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.8 + 2 = 2.8 \text{ V}$$

$$V_5 = 2.8 \text{ V}$$

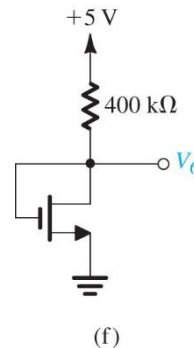

$$V_6 = V_{GS} = 5.0 \text{ V} - I_D 400 \text{ k}\Omega$$

$$V_{OV} = V_{GS} - V_t = 5.0 \text{ V} - I_D 400 \text{ k}\Omega - 0.8 \text{ V}$$

$$V_{OV} = 4.2 \text{ V} - I_D 400 \text{ k}\Omega$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{OV}^2$$

$$I_D = \frac{1}{2} 0.5 \left(\frac{\text{mA}}{\text{V}^2} \right) (4.2 \text{ V} - I_D 400 \text{ k}\Omega)^2$$

From MATHCAD $I_D = 10 \text{ uA}$ or 11.025 uA


$$V_{OV} = 0.2 \text{ V}$$

$$V_6 = V_{GS} = 1 \text{ V}$$



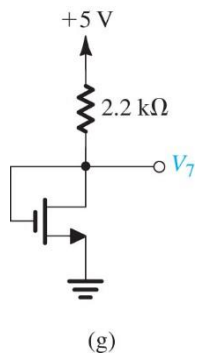Problem 5.56g,h

For each of the circuits in Fig. P5.56, find the labeled node voltages. For all transistors, $k_n'(W/L) = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, and $\lambda = 0$.



$$V_7 = V_{GS} = 5.0\text{V} - I_D 2.2\text{k}\Omega$$

$$V_{OV} = 4.2\text{V} - I_D 2.2\text{k}\Omega$$


$$I_D = \frac{1}{2} 0.5 \left(\frac{\text{mA}}{\text{V}^2} \right) (4.2\text{V} - I_D 2.2\text{k}\Omega)^2$$

(g)

From MATHCAD $I_D = 1 \text{ mA}$

$$V_{OV} := \sqrt{\frac{2 \cdot 1\text{mA}}{0.5 \frac{\text{mA}}{\text{V}^2}}} = 2\text{V}$$

$$V_7 = V_{GS} = 2.8\text{V}$$

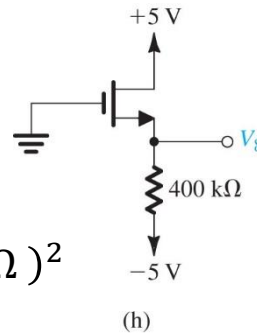

(h)

$$V_8 = -V_{GS} = V_S = -(5.0\text{V} - I_D 400\text{k}\Omega)$$

$$V_{GS} = 5.0\text{V} - I_D 400\text{k}\Omega$$

$$V_{OV} = V_{GS} - V_t = 5.0\text{V} - I_D 400\text{k}\Omega - 0.8\text{V}$$

$$V_{OV} = 4.2\text{V} - I_D 400\text{k}\Omega$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{OV}^2$$

$$I_D = \frac{1}{2} 0.5 \left(\frac{\text{mA}}{\text{V}^2} \right) (4.2\text{V} - I_D 400\text{k}\Omega)^2$$

From MATHCAD $I_D = 10 \text{ uA}$ or 11.025 uA

$$V_{OV} = 0.2\text{V}$$

$$V_8 = -V_{GS} = -1\text{V}$$




Problem 5.62

In a particular application, an n -channel MOSFET operates with V_{SB} in the range 0 V to 4 V. If V_{t0} is normally 1.0 V, find the range of V_t that results if $\gamma = 0.5 \sqrt{V}$ and $2\phi_f = 0.6$ V. If the gate oxide thickness is increased by a factor of 4, what does the threshold voltage become?

$$V_t = V_{t0} + \gamma \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$
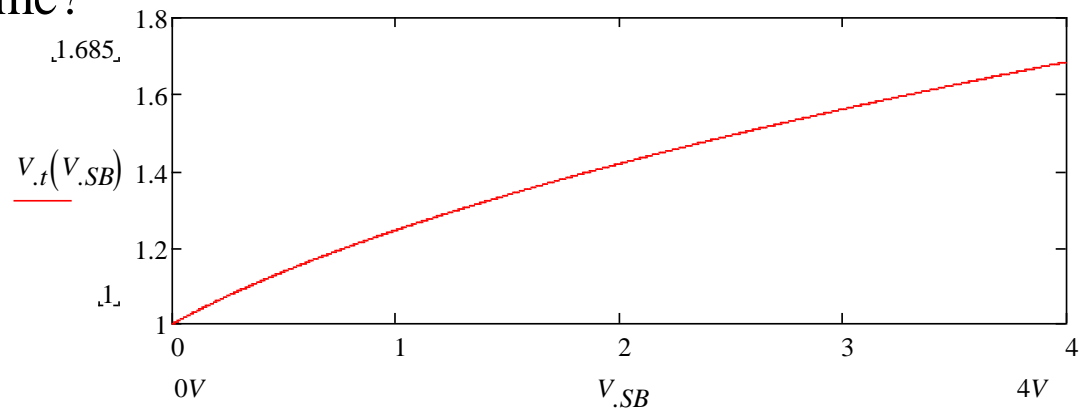
$$\gamma = \frac{\sqrt{2qN_A\epsilon_s}}{C_{ox}}$$



Increasing t_{ox} by 4x reduces C_{ox} by 4x which increases γ by 4x

$$V_t(V_{SB}) := 1V + 2 \cdot \sqrt{V} \cdot (\sqrt{0.6V + V_{SB}} - \sqrt{0.6V})$$

$$V_t(0V) = 1V$$

$$V_t(4V) = 3.74V$$



Problem 5.63

A p-channel transistor operates in saturation with its source voltage 3 V lower than its substrate. For $\gamma = 0.5 \sqrt{V}$, $2\phi_f = 0.75$ V, and $V_{t0} = -0.7$ V, find V_t .

$$V_t = V_{t0} + \gamma \left[\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$V_t := -0.7V - 0.5 \cdot \sqrt{V} \cdot (\sqrt{0.75V + 3V} - \sqrt{0.75V}) = -1.235V$$