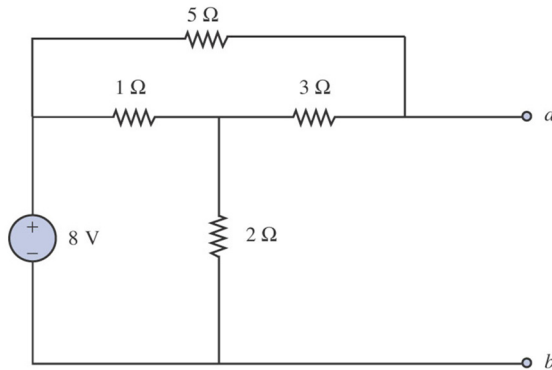
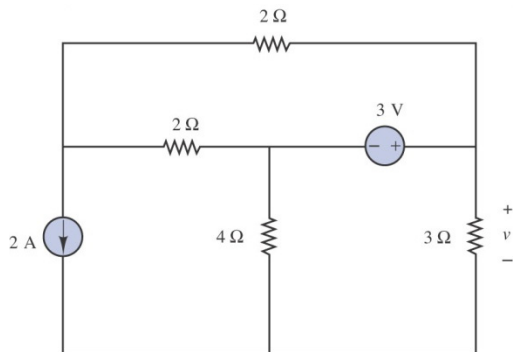


**Problem 1**


Find the Norton equivalent to the left of terminals a and b of the circuit shown in the figure below.

**Problem 2**

Determine the voltage drop on the 3Ω resistor. See the 3Ω resistor as a load resistor. Replace the rest of the network by its Thevenin equivalent. Then calculate the voltage on the 3Ω resistor using the equivalent circuit.


**Problem 3**

Find the Thevenin equivalent circuit and the Norton equivalent circuit that the load sees for the circuit below.

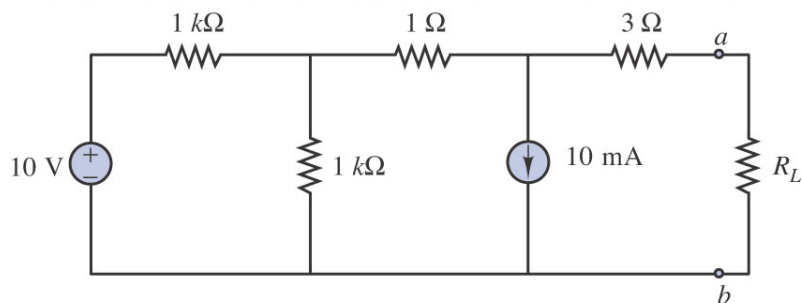


**Problem 4**

Find the Thevenin equivalent and Norton equivalent of the circuit connected to  $R_L$  as shown below.

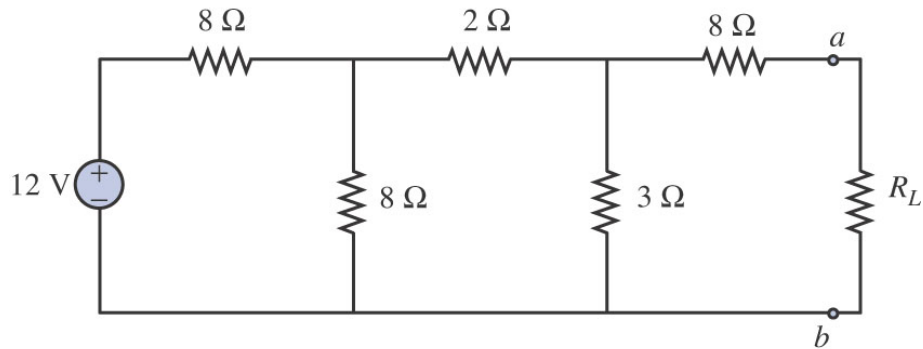**Problem 5**

Find the Thevenin equivalent and the Norton equivalent of the circuit connected to  $R_L$  in the figure below, where  $R_1 = 10\ \Omega$ ,  $R_2 = 20\ \Omega$ ,  $R_g = 0.1\ \Omega$ , and  $R_p = 1\ \Omega$ .

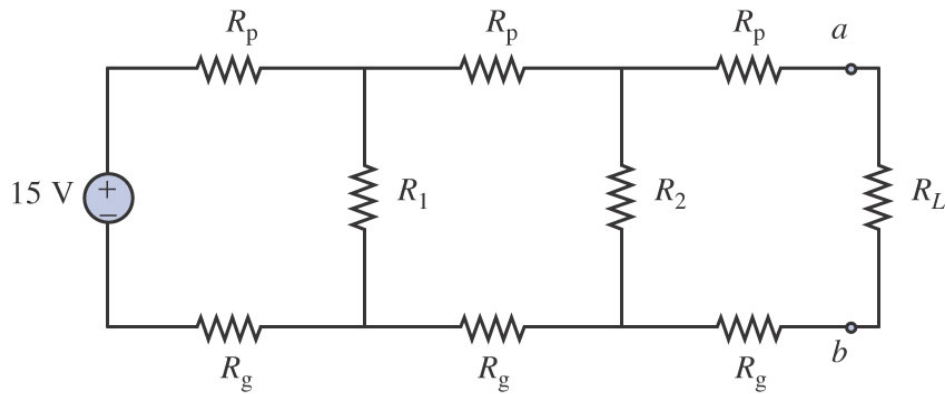

**Problem 6**

Construct the Thevenin equivalent circuit between terminals a and b.  $V_s = 12\text{ V}$ ,  $R = 1\text{ k}\Omega$ ,  $R_x = 996\text{ }\Omega$ .

