ELEG 312 Homework #2 Solutions Problems 8.26, 8.49, 8.66, 8.71, 8.79, 8.81, and 8.83

Homework R. Martin

Problem 8.26a

Consider the CE amplifiers of Fig. 8.13(b) for the case of I = 0.5 mA, $\beta = 100$, and $V_A = 100$ V. Find R_{in} , A_{vo} , and R_o . If it is required to raise R_{in} by a factor of 5 by changing I, what value of I is required, assuming that β remains unchanged? What are the new values of A_{vo} and R_o ? If the amplifier is fed with a signal source having $R_{sig} = 5 \text{ k}\Omega$ and is connected to a load of 100-k Ω resistance, find the overall voltage gain, v_o/v_{sig} .

$$g_{m} = \frac{I_{C}}{V_{T}} = \frac{0.5 \text{mA}}{25 \text{mV}} = 20 \frac{\text{mA}}{\text{V}}$$

$$R_{in} = r_{\pi} = \frac{\beta}{g_{m}} = \frac{100}{20 \text{mA/V}} = 5 \text{k}\Omega$$

$$R_{in} = r_{\sigma} = \frac{\beta}{g_{m}} = \frac{100 \text{V}}{20 \text{mA/V}} = 5 \text{k}\Omega$$

$$R_{in} = r_{\sigma} = \frac{\beta}{g_{m}} = \frac{100 \text{V}}{20 \text{mA/V}} = 5 \text{k}\Omega$$

$$R_{in} = r_{\sigma} = \frac{\beta V_{T}}{R_{in}} = \frac{2.5 \text{V}}{25 \text{k}\Omega} = 0.1 \text{mA}$$

$$R_{o} = r_{o} = \frac{V_{A}}{I_{C}} = \frac{100 \text{V}}{0.5 \text{mA}} = 200 \text{k}\Omega$$

$$R_{o} = r_{o} = \frac{V_{A}}{I_{C}} = \frac{100 \text{V}}{0.1 \text{mA}} = 1 \text{M}\Omega$$

$$A_{vo} = -g_{m}r_{o} = -\left(20\frac{\text{mA}}{\text{V}}\right)(200\text{k}\Omega) = -4000\frac{\text{V}}{\text{V}} \qquad A_{vo_new} = -g_{m}r_{o} = -\left(4\frac{\text{mA}}{\text{V}}\right)(1\text{M}\Omega) = -4000\frac{\text{V}}{\text{V}}$$

$$R_{in_new} = 5R_{in} = 25k\Omega = \frac{\beta}{g_m} = \frac{\beta}{I_C/V_T}$$


$$I_{C_{new}} = \frac{\beta V_T}{R_{in-new}} = \frac{2.5 \text{V}}{25 \text{k}\Omega} = 0.1 \text{mA}$$

$$R_{o_{-new}} = r_o = \frac{V_A}{I_C} = \frac{100 \text{V}}{0.1 \text{mA}} = 1 \text{M}\Omega$$

$$A_{vo_n new} = -g_m r_o = -\left(4\frac{\text{mA}}{\text{V}}\right)(1\text{M}\Omega) = -4000\frac{\text{V}}{\text{V}}$$

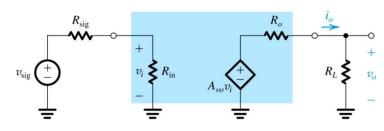Problem 8.26b

Consider the CE amplifiers of Fig. 8.13(b) for the case of I = 0.5 mA, $\beta = 100$, and $V_A = 100$ V. Find R_{in} , A_{vo} , and R_o . If it is required to raise R_{in} by a factor of 5 by changing I, what value of I is required, assuming that β remains unchanged? What are the new values of A_{vo} and R_o ? If the amplifier is fed with a signal source having $R_{sig} = 5$ k Ω and is connected to a load of 100-k Ω resistance, find the overall voltage gain, v_o/v_{sig} .



$$R_{in_new} = 25k\Omega$$

$$R_{o_new} = r_o = 1M\Omega$$

$$A_{vo_new} = -4000 \frac{V}{V}$$

$$G_{v} = \frac{v_{o}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} A_{vo} \frac{R_{L}}{R_{L} + R_{o}}$$

$$= \frac{25k\Omega}{25k\Omega + 5k\Omega} \left(-4000 \frac{V}{V} \right) \frac{0.1M\Omega}{0.1M\Omega + 1M\Omega} = -303.03 \frac{V}{V}$$

Homework R. Martin

Problem 8.49a,b

Transistor Q_1 in the circuit of Fig. P8.49 is operating as a $\acute{\text{CE}}$ amplifier with an active load provided by transistor Q_2 , which is the output transistor in a current mirror formed by Q_2 and Q_3 . (Note that the biasing arrangement for Q_1 is *not* shown.)

(a) Neglecting the finite base currents of Q_2 and Q_3 and assuming that their $V_{BE} = 0.7$ V and that Q_2 has five times the area of Q_3 , find the value of I.

$$I_{REF} = I_{C3} = \frac{V_{CC} - V_{BE3}}{R} = \frac{3V - 0.7V}{46k\Omega} = 0.05\text{mA}$$

 $I = I_{C2} = 5I_{C3} = 5I_{REF} = 0.25\text{mA}$

(b) If Q_1 and Q_2 are specified to have $|V_A| = 30$ V, find r_{01} and r_{02} and hence the total resistance at the collector of Q_1 .

$$r_{o1} = r_{o2} = \frac{V_A}{I_C} = \frac{30\text{V}}{0.25\text{mA}} = 120\text{k}\Omega$$

$$R_o = r_{o1} \parallel r_{o2} = 60\text{k}\Omega$$

Figure P8.49

Problem 8.49c,d


Transistor Q_1 in the circuit of Fig. P8.49 is operating as a CE amplifier with an active load provided by transistor Q_2 , which is the output transistor in a current mirror formed by Q_2 and Q_3 . (Note that the biasing arrangement for Q_1 is *not* shown.)

(c) Find $r_{\pi 1}$ and g_{m1} assuming that $\beta_1 = 50$.

and
$$r_{\pi 1}$$
 and g_{m1} assuming that $\beta_1 = 50$.
$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.25 \text{mA}}{25 \text{mV}} = 10 \frac{\text{mA}}{\text{V}}$$

$$r_{\pi 1} = \frac{\beta_1}{g_m} = \frac{50}{10 \text{mA/V}} = 5 \text{k}\Omega$$
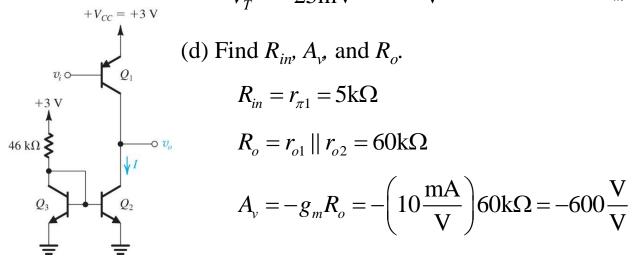
$$r_{\pi 1} = \frac{\beta_1}{g_m} = \frac{50}{10 \,\text{mA/V}} = 5 \text{k}\Omega$$




$$R_{in} = r_{\pi 1} = 5 \mathrm{k}\Omega$$

$$R_o = r_{o1} || r_{o2} = 60 \text{k}\Omega$$

$$A_{v} = -g_{m}R_{o} = -\left(10\frac{\text{mA}}{\text{V}}\right)60\text{k}\Omega = -600\frac{\text{V}}{\text{V}}$$

Figure P8.49

The cascode amplifier of Fig. 8.33 is operated at a current of 0.2 mA with all devices operating at $|V_{OV}| = 0.20$ V. All devices have $|V_A| = 4$ V. Find g_{ml} , the output resistance of the amplifier, R_{on} , the output resistance of the current source, R_{op} , the overall output resistance, R_o , and the voltage gain, A_v .

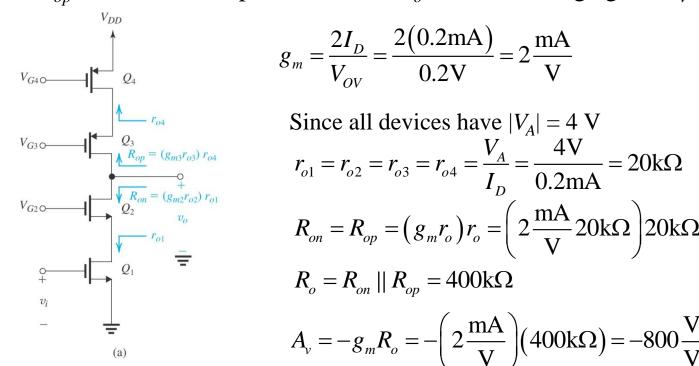

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2(0.2\text{mA})}{0.2\text{V}} = 2\frac{\text{mA}}{\text{V}}$$


$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = \frac{V_A}{I_D} = \frac{4V}{0.2\text{mA}} = 20\text{k}\Omega$$

$$R_{on} = R_{op} = (g_m r_o) r_o = \left(2 \frac{\text{mA}}{\text{V}} 20 \text{k}\Omega\right) 20 \text{k}\Omega = 800 \text{k}\Omega$$

$$R_o = R_{on} \parallel R_{op} = 400 \text{k}\Omega$$

$$A_{v} = -g_{m}R_{o} = -\left(2\frac{\text{mA}}{\text{V}}\right)(400\text{k}\Omega) = -800\frac{\text{V}}{\text{V}}$$

Consider the cascode amplifier of Fig. 8.33 with the dc component at the input V_I = 0.6 V, V_{G2} = 0.9 V, V_{G3} = 0.4 V, V_{G4} = 0.7 V, and V_{DD} = 1.3 V. If all devices are matched, that is $k_{n1} = k_{n2} = k_{p3} = k_{p4}$, and have equal $|V_t|$ of 0.4 V, what is the overdrive voltage at which the four transistors are operating? What is the allowable voltage range at the output?

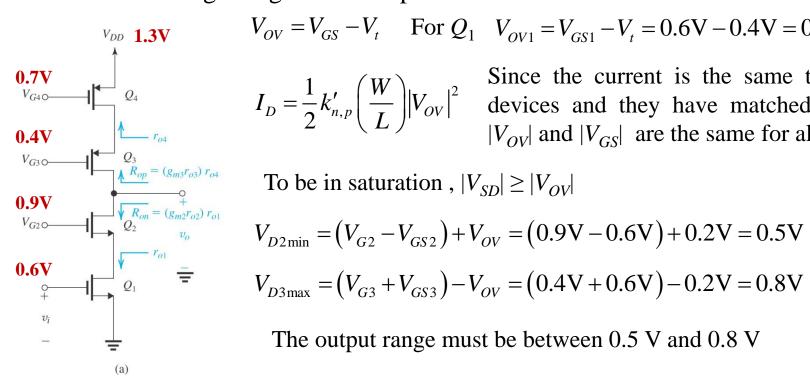

$$V_{OV} = V_{GS} - V_t$$
 For Q_1 $V_{OV1} = V_{GS1} - V_t = 0.6V - 0.4V = 0.2V$

$$I_D = \frac{1}{2} k'_{n,p} \left(\frac{W}{L}\right) \left| V_{OV} \right|^2$$

Since the current is the same through all $I_D = \frac{1}{2} k'_{n,p} \left(\frac{W}{L}\right) |V_{OV}|^2$ Since the current is the same through all devices and they have matched $k'_{n,p}$ then $|V_{OV}|$ and $|V_{GS}|$ are the same for all devices

$$V_{D2 \text{min}} = (V_{G2} - V_{GS2}) + V_{OV} = (0.9 \text{V} - 0.6 \text{V}) + 0.2 \text{V} = 0.5 \text{V}$$

$$V_{D3\text{max}} = (V_{G3} + V_{GS3}) - V_{OV} = (0.4\text{V} + 0.6\text{V}) - 0.2\text{V} = 0.8\text{V}$$


The output range must be between 0.5 V and 0.8 V

A bipolar cascode amplifier has a current-source load with an output resistance βr_o . Let $\beta = 50$, $|V_A| = 100$ V, and I = 0.2 mA. Find the voltage gain A_v .

$$g_{m1} = g_2 = \frac{I_C}{V_T} = \frac{0.2 \text{mA}}{25 \text{mV}} = 8 \frac{\text{mA}}{\text{V}}$$
 $r_{o1} = r_{o2} = \frac{V_A}{I_C} = \frac{100 \text{V}}{0.2 \text{mA}} = 500 \text{k}\Omega$

$$r_{o1} = r_{o2} = \frac{V_A}{I_C} = \frac{100 \text{V}}{0.2 \text{mA}} = 500 \text{k}\Omega$$
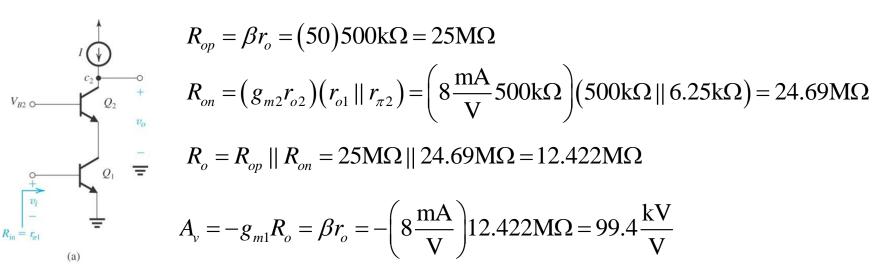
$$r_{\pi} = \frac{\beta}{g_m} = \frac{50}{8 \,\mathrm{mA/V}} = 6.25 \,\mathrm{k}\Omega$$



$$R_{op} = \beta r_o = (50)500 \text{k}\Omega = 25 \text{M}\Omega$$

$$R_{on} = (g_{m2}r_{o2})(r_{o1} || r_{\pi 2}) = \left(8\frac{\text{mA}}{\text{V}}500\text{k}\Omega\right)(500\text{k}\Omega || 6.25\text{k}\Omega) = 24.69\text{M}\Omega$$

$$R_o = R_{op} || R_{on} = 25M\Omega || 24.69M\Omega = 12.422M\Omega$$

$$A_{v} = -g_{m1}R_{o} = \beta r_{o} = -\left(8\frac{\text{mA}}{\text{V}}\right)12.422\text{M}\Omega = 99.4\frac{\text{kV}}{\text{V}}$$

Problem 8.81a

In this problem, we will explore the difference between using a BJT as cascode device and a MOSFET as cascode device. Refer to Fig. P8.81. Given the following data, calculate G_m , R_o , and A_{vo} for the circuits (a) and (b):

$$I = 100 \,\mu\text{A}, \, \beta = 125, \, \mu_n C_{ox} = 400 \,\mu\text{A/V}^2, \, W/L = 25, \, V_A = 1.8 \,\text{V}$$

$$I = 100 \text{ µA}, \beta = 125, \mu_{n}C_{ox} = 400 \text{ µA/V}^{2}, W/L = 25, V_{A} = 1.8 \text{ V}$$

$$\downarrow^{V_{DD}} g_{m1} = \sqrt{2\mu_{n}C_{ox}\left(\frac{W}{L}\right)_{1}}I_{D} = \sqrt{2\left(0.4\frac{\text{mA}}{\text{V}^{2}}\right)25(0.1\text{mA})} = 1.414\frac{\text{mA}}{\text{V}}$$

$$r_{o1} = \frac{V_{A}}{I_{D}} = \frac{1.8\text{V}}{0.1\text{mA}} = 18\text{k}\Omega$$

$$r_{o2} = \frac{V_{A}}{I_{C}} = \frac{1.8\text{V}}{0.1\text{mA}} = 18\text{k}\Omega$$

$$r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{125}{4\text{mA/V}} = 31.25\text{k}\Omega$$

$$R_{o} = (g_{m2}r_{o2})(r_{o1} \parallel r_{\pi 2}) = \left(4\frac{\text{mA}}{\text{V}}\right)18\text{k}\Omega\right)(18\text{k}\Omega \parallel 31.25\text{k}\Omega) = 822.34\text{k}\Omega$$
Figure P8.81

Figure P8.81

$$A_{vo} = -G_m R_o = -\left(1.414 \frac{\text{mA}}{\text{V}}\right) 822.34 \text{k}\Omega = -1163 \frac{\text{V}}{\text{V}}$$

Homework R. Martin

Problem 8.81b

In this problem, we will explore the difference between using a BJT as cascode device and a MOSFET as cascode device. Refer to Fig. P8.81. Given the following data, calculate G_m , R_o , and A_{vo} for the circuits (a) and (b):

$$I = 100 \,\mu\text{A}, \, \beta = 125, \, \mu_n C_{ox} = 400 \,\mu\text{A/V}^2, \, W/L = 25, \, V_A = 1.8 \,\text{V}$$

$$g_{m1} = g_{m2} = \sqrt{2\mu_{n}C_{ox}\left(\frac{W}{L}\right)_{1}I_{D}} = \sqrt{2\left(0.4\frac{\text{mA}}{\text{V}^{2}}\right)25(0.1\text{mA})} = 1.414\frac{\text{mA}}{\text{V}}$$

$$v_{o2} = \frac{V_{A}}{I_{D}} = \frac{1.8\text{V}}{0.1\text{mA}} = 18\text{k}\Omega$$

$$G_{m} = g_{m1} = 1.414\frac{\text{mA}}{\text{V}}$$

$$R_{o} = (g_{m2}r_{o2})r_{o1} = \left(4\frac{\text{mA}}{\text{V}}\right)18\text{k}\Omega = 458\text{k}\Omega$$
Figure P8.81
$$A_{vo} = -G_{m}R_{o} = -\left(1.414\frac{\text{mA}}{\text{V}}\right)458\text{k}\Omega = -648\frac{\text{V}}{\text{V}}$$

Homework R. Martin

Find the output resistance of the double-cascode current mirror of Fig. P8.83.

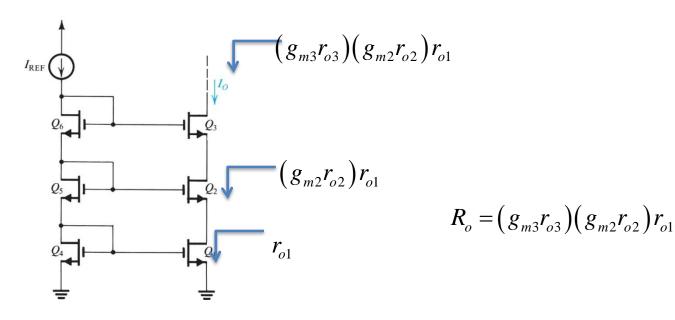


Figure P8.83